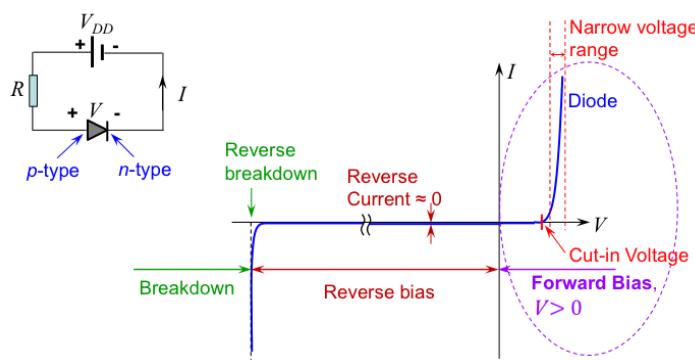




# Diodes

Anode p-type → Cathode n-type





## FORWARD BIAS

$$V > 0$$

Higher voltage @ p-type terminal Wrt n-type terminal  
current flows through the diode from the p-type to n-type side

$$I = I_S e^{\frac{V}{nV_T}} \quad V = nV_T \ln\left(\frac{I}{I_S}\right)$$

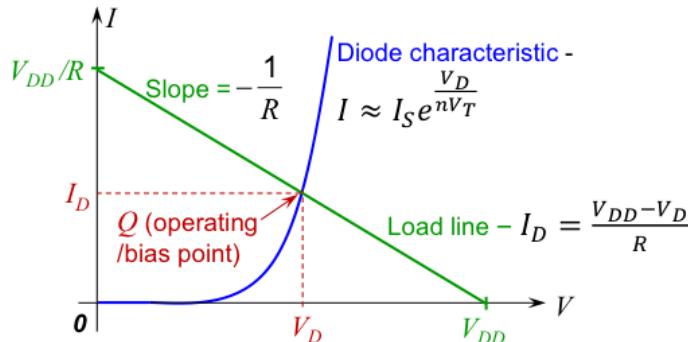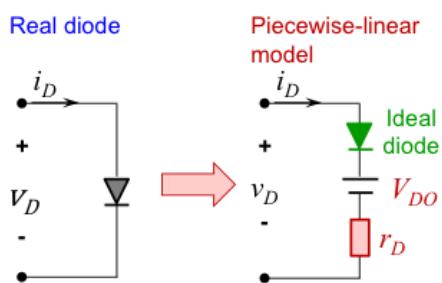$Q$  point : Intersection of Ohm's law & Diode characteristic



## AC Analysis

When adding small AC Source:

$$i_D(t) = I_D + i_d(t)$$

$$i_d(t) = v_a(t) / r_d$$

$$r_d = \frac{nV_T}{I_D}$$

## REVERSE BIAS

$$V < 0, |V| < V_Z$$

Lower voltage @ p-type terminal wrt n-type terminal  
Current flows through the diode from the n-type to p-type side

$$I = -I_S$$

## BREAKDOWN REGION



$$V < 0, V_{DD} > V_Z$$

Voltage across diode stays constant @  $-V_Z$


Polarity & current direction same as Reverse Bias

$$I = \frac{V_{DD} - V_Z}{R}$$

# BJT

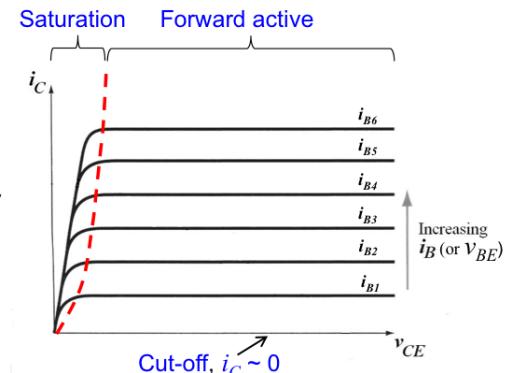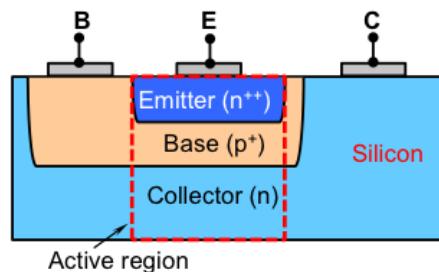

NPN

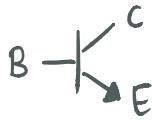

$V_{BE}$

	$V_{BE}$	$V_{BC}$	
Cut-off	-	-	OFF
Forward Active	+	-	Amp
Saturation	+	+	ON
Reverse Active	-	+	X

PNP



$V_{EB}$

	$V_{EB}$	$V_{CB}$	
Cut-off	-	-	OFF
Forward Active	+	-	Amp
Saturation	+	+	ON
Reverse Active	-	+	X

## FORWARD ACTIVE

$$i_C = I_s e^{V_{BE}/V_T} \quad (\text{without Early Effect})$$

$$i_C = I_s e^{V_{BE}/V_T} \left(1 + \frac{V_{CE}}{V_A}\right) \quad (\text{with Early Effect})$$

$$i_C = \beta i_B \rightarrow i_E = (\beta + 1) i_B$$

$$i_E = i_C + i_B \rightarrow = \left(\frac{1}{\beta} + 1\right) i_C$$

$$V_{BE} = 0.7V$$

## FORWARD ACTIVE

$$i_C = I_s e^{V_{EB}/V_T} \quad (\text{without Early Effect})$$


$$i_C = I_s e^{V_{EB}/V_T} \left(1 + \frac{V_{EC}}{V_A}\right) \quad (\text{with Early Effect})$$

$$i_C = \beta i_B \rightarrow i_E = (\beta + 1) i_B$$


$$i_E = i_C + i_B \rightarrow = \left(\frac{1}{\beta} + 1\right) i_C$$

$$V_{EB} = 0.7V$$

## LARGE SIGNAL MODEL

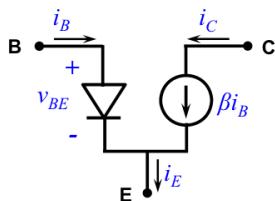

## LARGE SIGNAL MODEL


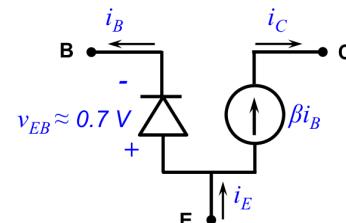


## SMALL SIGNAL MODEL (Same for Both)

$$g_m = \frac{i_c}{v_{be}} = \frac{I_c}{V_T}$$

$$r_\pi = \frac{\beta}{g_m}$$

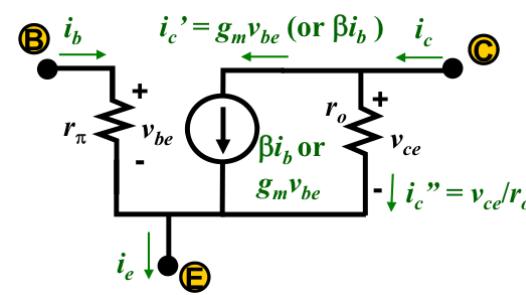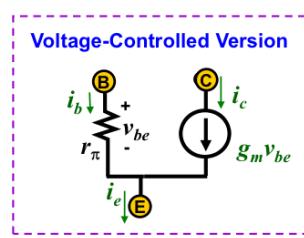
$$r_o = \frac{V_{ce}}{i_c} = \frac{V_A}{I_c} \quad (\text{Hybrid})$$




# MOSFET

## THE MOSFET STORY (using n-channel)

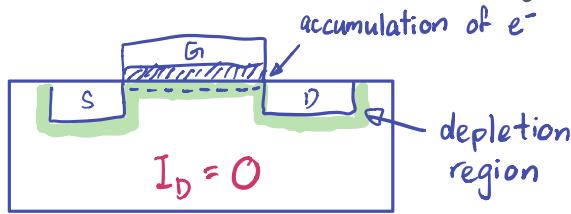
1.  $0 < V_{GS} < V_{Th}$  : Cut-off Region





2.  $V_{GS} \geq V_{Th}$

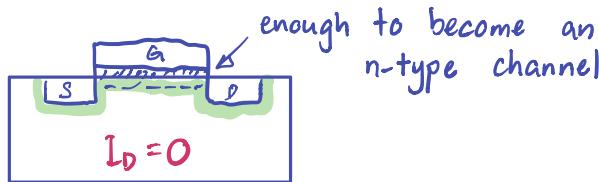


3.  $V_{DS} > 0$  : Linear Region

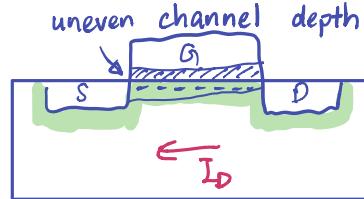

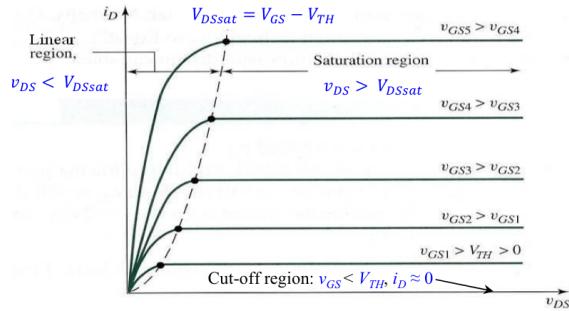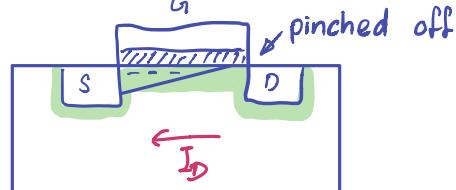4.  $V_{DS} > V_{DSsat}$  : Saturation Region




### N-CHANNEL

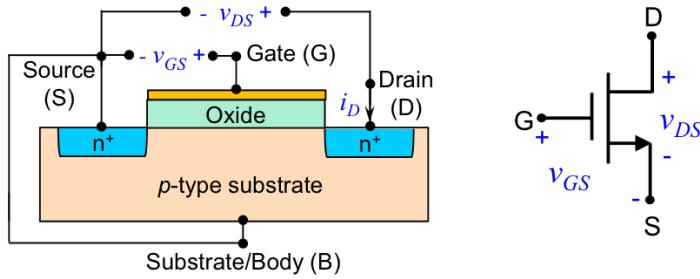

Cut-off	$v_{GS} < V_{Th}$	$i_D \approx 0$	OFF
Linear	$v_{GS} > V_{Th}$	$v_{DS} < v_{GS} - V_{Th}$	ON
Saturation	$v_{GS} > V_{Th}$	$v_{DS} > v_{GS} - V_{Th}$	Amp


### P-CHANNEL

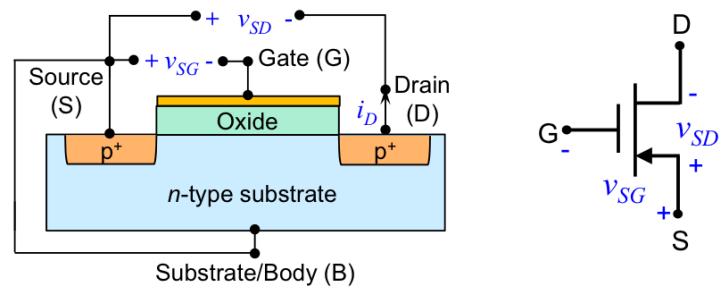

Cut-off	$v_{SG} <  V_{Th} $	$i_D \approx 0$	OFF
Linear	$v_{SG} >  V_{Th} $	$v_{SD} < v_{SG} -  V_{Th} $	ON
Saturation	$v_{SG} >  V_{Th} $	$v_{SD} > v_{SG} -  V_{Th} $	Amp

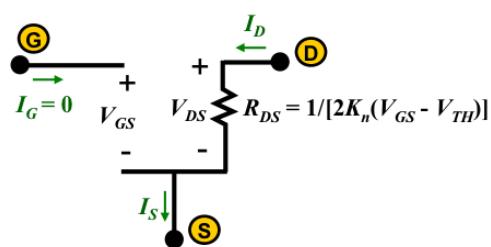
### LINEAR REGION

$$i_D = 2K_n [(V_{GS} - V_{Th}) v_{DS} - 0.5 v_{DS}^2]$$



### LINEAR REGION

Put modulus on all Voltages

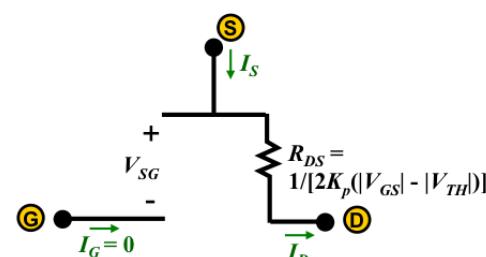


## SATURATION REGION

$$i_D = K_n (V_{GS} - V_{Th})^2 \quad (\text{w/o CLME})$$

$$i_D = K_n (V_{GS} - V_{Th})^2 (1 + \lambda V_{DS}) \quad (\text{w/ CLME})$$


$$\lambda = \frac{1}{V_A}$$

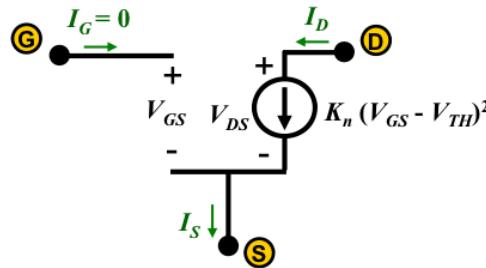

## SMALL SIGNAL MODEL


$$g_m = \frac{i_d}{v_{gs}} = 2K_n (V_{GS} - V_{Th}) = 2\sqrt{K_n I_0}$$
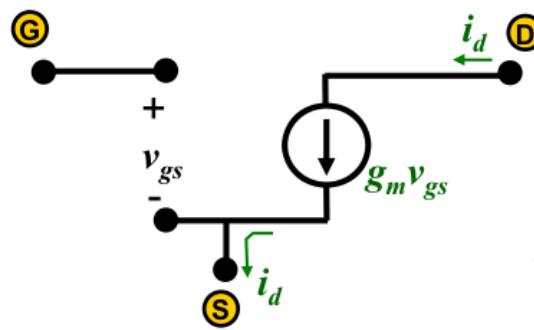
## Hybrid- $\pi$ Model for N-MOSFET or P-MOSFET



## SATURATION REGION

Put modulus on all Voltages

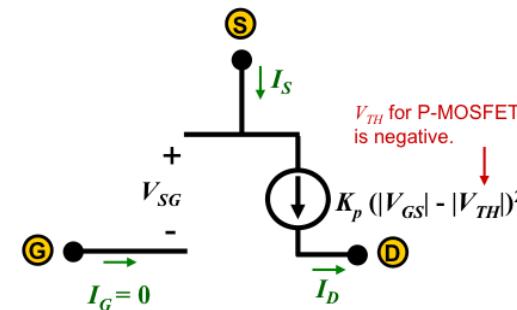


## SMALL SIGNAL MODEL

$$g_m = \frac{i_d}{v_{sg}} = 2K_p (|V_{SG}| - |V_{Th}|) = 2\sqrt{K_p I_0}$$

$$r_o = \frac{v_{ds}}{i_d} = \frac{V_A}{I_0}$$
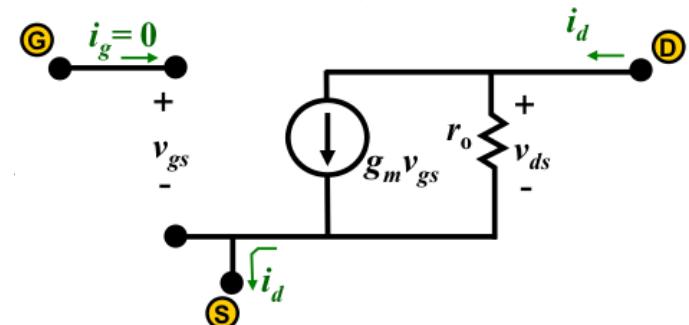
## Hybrid- $\pi$ Model with Output Resistance

(The dependence of  $i_D$  on  $v_{ds}$  is accounted for)




## BODY EFFECT

When Body is not tied to source

$$g_{mb} = \frac{i_d}{v_{sb}}$$

## CMOS INVERTER

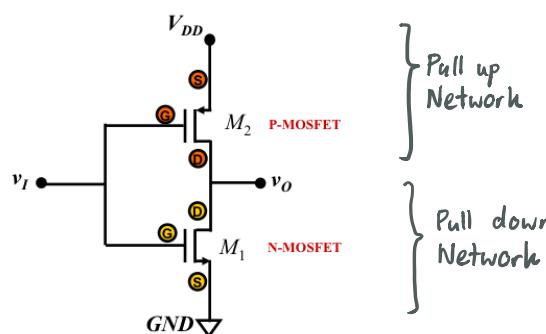

$v_I$  is HIGH



PMOS is cutoff

NMOS is linear or Sat




$v_O$  is LOW

$$\frac{t_{pHL}}{t_{pLH}} = \frac{\frac{1}{\mu_n \left(\frac{W}{L}\right)_N}}{\frac{1}{\mu_p \left(\frac{W}{L}\right)_P}}$$

$$\text{Dynamic Power Dissipation} = f C_L V_{DD}^2$$

# THE ULTIMATE GUIDE TO OP-AMPS

## THE OP AMP

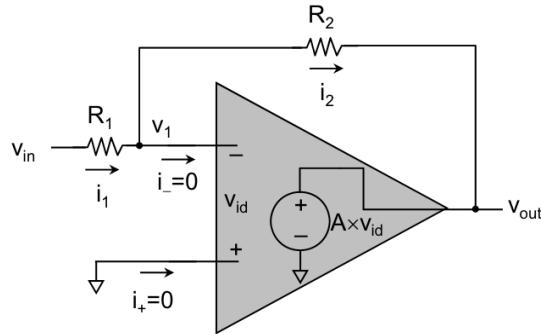

$$R_{in} = \infty$$

$$R_{out} = 0$$

$$A = \infty$$

In Circuit Analysis:

$$i_- = 0$$

$$i_+ = 0$$

$$i_1 = i_2$$

$$v_+ = v_- \text{ (virtual short)}$$

### Open Loop (SSA)


- difficult to control gain
- Simple
- ↓ Power consumption
- Poor Linearity / ↑ Distortion

vs

### Feedback (Op-Amp) Amplifiers


- Accurate gain from Resistors
- Complicated
- ↑ Power Consumption
- High Linearity / ↓ Distortion

### 1. INVERTING AMP

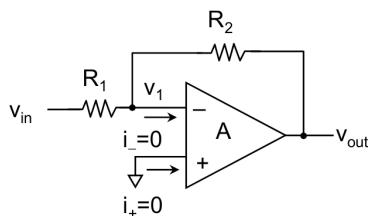


$$v_{out} = -\frac{R_2}{R_1} v_{in}$$

### 3. NON-INVERTING AMP

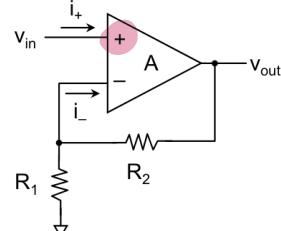

$$v_{out} = \left(1 + \frac{R_1}{R_2}\right) v_{in}$$


### 2. SUMMING AMP

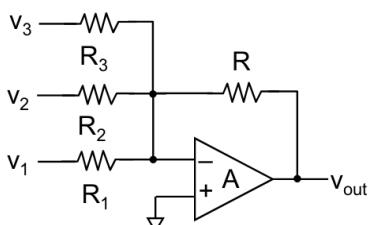

Using Superposition


$$v_{out} = -R \left( \frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} \right)$$

### 4. SOURCE FOLLOWER

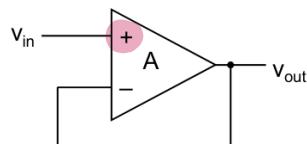

$$v_{out} = v_{in}$$


## 5. LOGARITHMIC AMP

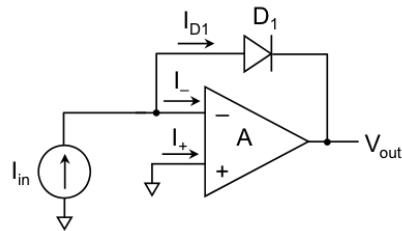

$$V_{out} = -V_T \ln\left(\frac{I_{in}}{I_s}\right)$$

Good for inputs with a wide range


## 6. EXPONENTIAL AMP

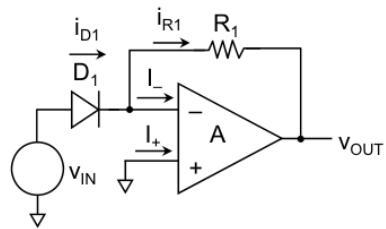

$$V_{out} = -R_1 I_s e^{V_{in}/V_T}$$

Good for inputs with a small range

## 7. INSTRUMENTATION AMP

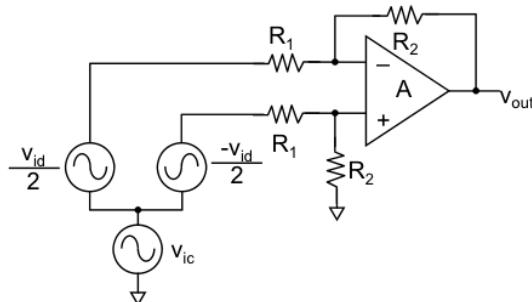


$$V_{out} = -\frac{R_2}{R_1} (V_{id})$$

Rejects Common mode, Amplifies differential

Good for blocking noise

Used in measuring instruments

## 8. INTEGRATOR

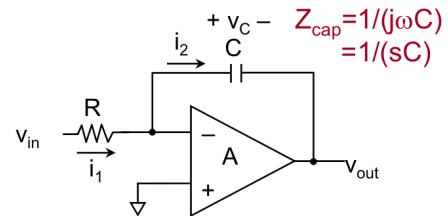


$$v_{out}(t) = -\frac{1}{RC} \int_0^t v_{in}(t) dt$$

$$H(j\omega) = -\frac{Z_{cap}}{R}$$

\* Use on  $\text{V}_U$  to get  $\text{V}_M$ !



Gain  $\downarrow$  as freq  $\uparrow$

## 9. DIFFERENTIATOR


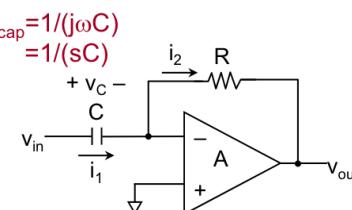


$$v_{out}(t) = -RC \frac{d}{dt} v_{in}(t)$$


## 10. 1<sup>st</sup> ORDER LOWPASS

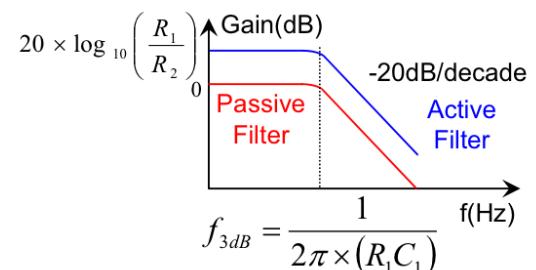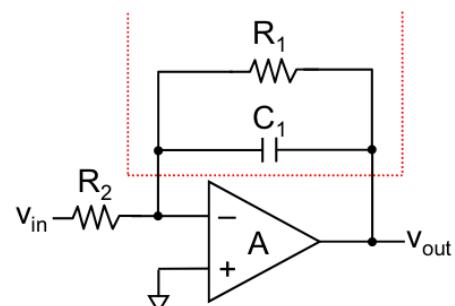


## 11. 1<sup>st</sup> ORDER HIGHPASS

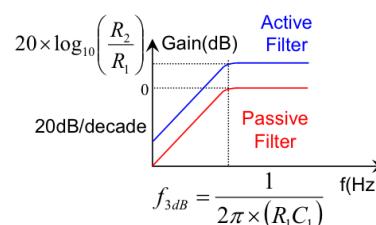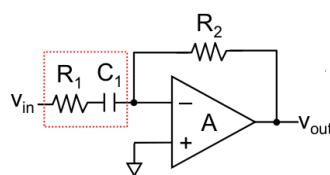

## 14. SUPERDIODE RECTIFIER

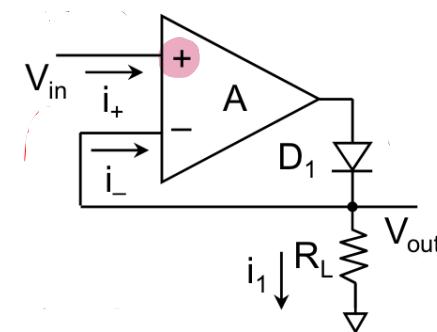


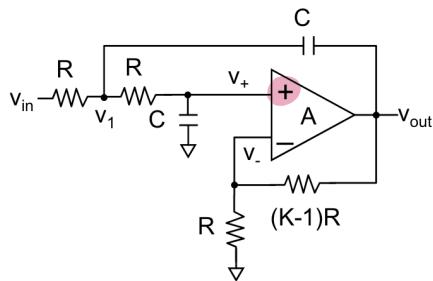
## 12. 2<sup>nd</sup> ORDER SALLEN - KEY LOWPASS FILTER




$$\omega_o = \frac{1}{RC} \quad \frac{1}{Q} = 3 - K \quad H_o = K$$

@ Low freq  $H(j\omega) \approx H_o$

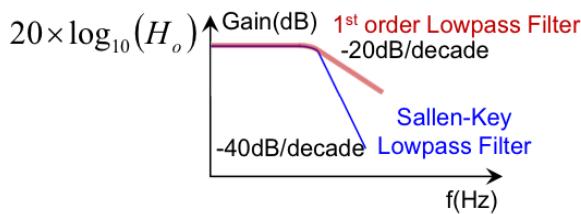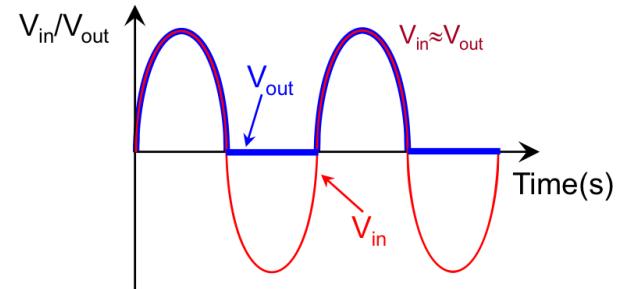@ High freq  $H(j\omega) \approx H_o \omega_o^2 / (\omega)^2$



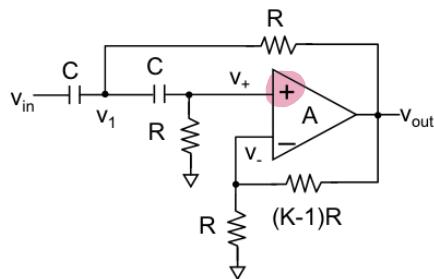
## 13. 2<sup>nd</sup> ORDER SALLEN - KEY HIGHPASS FILTER





@ Low freq,  $H(j\omega) \approx H_o (\omega)^2 / \omega_o^2$

@ High freq,  $H(j\omega) \approx H_o$

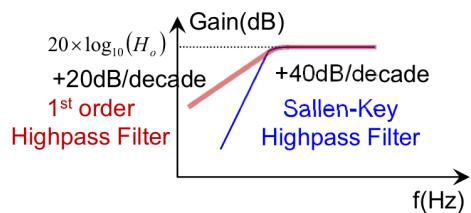


## 15. COMPARATOR

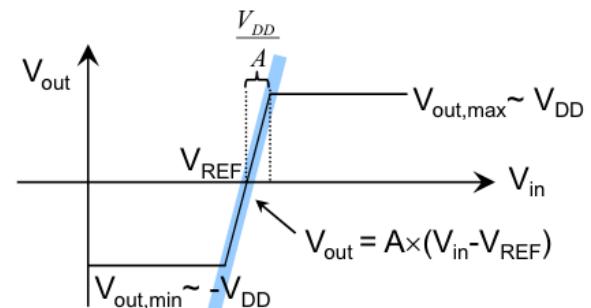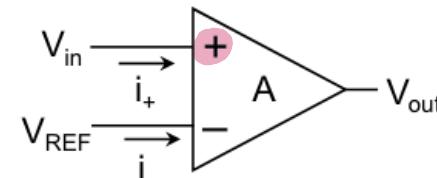

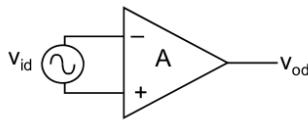
## OP AMP PARAMETERS

Open Loop Voltage Gain ( $A_{OL}$ ): How well the desired signal is amplified



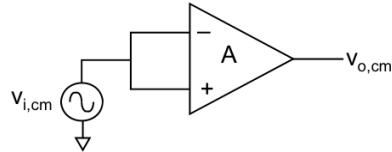
Common Mode Voltage Gain ( $A_{CM}$ ): How much noise is amplified  
Ideal value is 0




Common Mode Rejection Ratio (CMRR): How well noise is rejected  
Ideal is  $\infty$

$$CMRR [dB] = 20 \log \left( \frac{A_{OL}}{A_{CM}} \right)$$

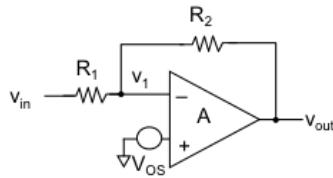Input Offset Voltage ( $V_{OS}$ ): DC output shift  
Use Superposition to find new  $V_{out}$



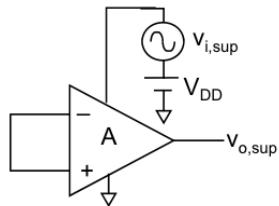Power Supply Rejection Ratio (PSRR): How well supply line ripples are rejected.  
Ideal is  $\infty$



GBW

$$f_{3dB, CL} = 2\pi GBW \times \frac{R_1}{R_1 + R_2}$$

$$f_{3dB, OL} = GBW \div A_{OL}$$

$$A_{SUP} = \frac{V_{o,sup}}{V_{i,sup}}$$

$$PSRR [dB] = 20 \log \left( \frac{A_{OL}}{A_{SUP}} \right)$$


Slew Rate (SR): Maximum slope that can occur @ output  
 $SR = 2\pi f \cdot V_{out,ph} \cdot \sin(2\pi ft)$

... & Many More!

# THE ULTIMATE SINGLE-STAGE amplifiers Guide TO

by Rachelle! v1


## Transconductance Amplifier

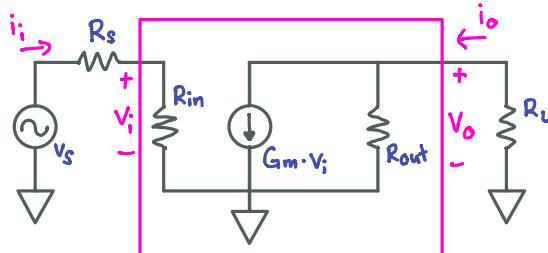

- High  $R_{in}$
- High  $R_{out}$
- Voltage-to-current:  $G_m \cdot V_i$

$$\text{Gain} = \frac{R_{in}}{R_s + R_{in}} \times G_m \times (R_{out} // R_L)$$

## Voltage Amplifier

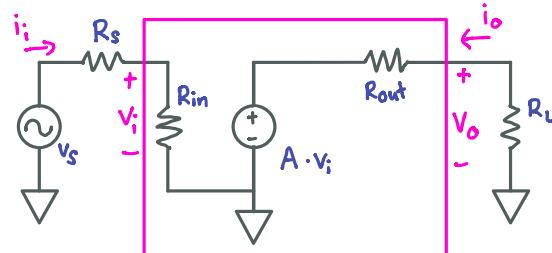

- High  $R_{in}$
- Low  $R_{out}$
- Voltage gain A

## DC ANALYSIS

1. Remove Source & Load
2. ~~+/-~~ Open circuit
3. BJT / MOSFET Analysis

### BJT

$$g_m = \frac{I_c}{V_T}$$

$$r_\pi = \frac{\beta}{g_m}$$

$$r_o = \frac{V_A}{I_c}$$

### MOSFET

$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D}$$


For Body Effect,  $g_{mb} \approx -\frac{g_m}{4}$

$$r_i = \infty$$

$$r_o = \frac{1}{2\lambda_n I_D}$$

## 8 AMPLIFIERS

### Common Emitter (CE)

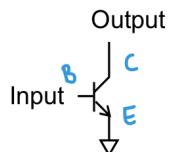


Use Transconductance Amp

$$G_m = g_m$$

$R_{in}$ : Table 1A

$R_{out}$ : Table 1B

### Common Source (CS)

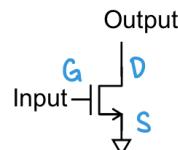

Use Transconductance Amp

$$G_m = g_m$$

$R_{in}$ :  $\infty$


$R_{out}$ :  $r_o$

### CE/CS Characteristics

- High  $R_i$
- High  $R_o$
- Medium Gain

$V_{in}$  &  $V_{out}$  has opp sign  
 $\uparrow G_m$  &  $R_o$  means higher  $A_v$   
 $BJT g_m > MOS g_m$

## Common Base (CB)

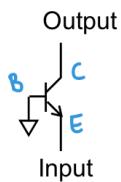


Use Transconductance Amp

$$G_m = -g_m$$

$R_{in}$  : Table 1C

$R_{out}$  : Table 1B

## Common Gate (CG)

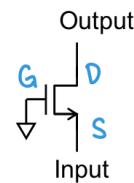

Use Transconductance Amp

$$G_m = g_{mb} - g_m$$

$R_{in}$  : Table 2D

$R_{out}$  : Table 2B

### CB/CG Characteristics

Low  $R_i$

High  $R_o$


Medium Gain

$V_{in}$  &  $V_{out}$  has same sign

$\uparrow G_m$  &  $R_o$  means higher  $A_v$

BJT  $g_m >$  MOS  $g_m - g_{mb}$

## Common Collector (CC)

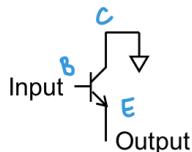

Use Voltage Amplifier


$$A_v = \frac{g_m R_L}{1 + g_m R_L}$$

$\approx 1$  if  $g_m R_L \gg 1$


$R_{in}$  : Table 1A

$R_{out}$  : Table 1C

\* May be able to do:

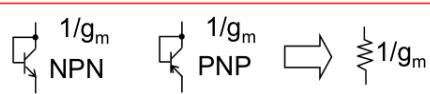

## Common Drain (CD)

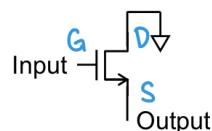

Use Voltage Amplifier


$$A_v = \frac{g_m R_L}{1 + (g_m - g_{mb}) R_L}$$

$\approx \frac{g_m}{g_m - g_{mb}}$  if  $(g_m - g_{mb}) R_L \gg 1$

$R_{in} : \infty$

$R_{out}$  : Table 2C

\* May be able to do:

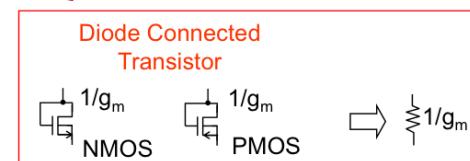

### CC/CD Characteristics

High  $R_i$

Low  $R_o$


$\approx$  Ideal Gain

$V_{in}$  &  $V_{out}$  has same sign

Ideal buffer

BJT  $g_m >$  MOS  $g_m - g_{mb}$

## CE w/ Degeneration

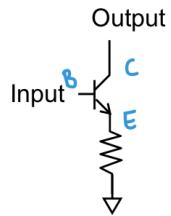


Use Transconductance Amp

$$G_m \approx \frac{g_m}{1 + g_m R_E}$$

$R_{in}$ : Table 1A

$R_{out}$ : Table 1B

## CS w/ Degeneration

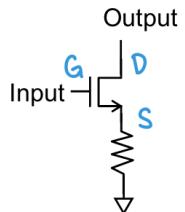

Use Transconductance Amp

$$G_m = \frac{g_m}{1 + (g_m - g_{mb}) R_E}$$

$R_{in} : \infty$

$R_{out}$ : Table 2B

### Degenerates

High  $R_i$

$V_{in}$  &  $V_{out}$  has opp sign

High  $R_o$

Lower gain than w/o Degeneration

## AC Analysis

1.  $\Rightarrow$  Ground
2.  $\Rightarrow$  Open Circuit
3.  $\Rightarrow$  Short Circuit

4. BJT / MOSFET  $\Rightarrow$  small signal AC Model (Personally I don't see how this helps)

5. Find  $R_{in}$ ,  $R_{out}$ ,  $G_m/A_v$



## VI. Single-Stage Amplifier Analysis

### BJT Equivalent Resistance Summary (Table 1)

Blue: look into collector terminal

Red: look into base terminal

Green: look into emitter terminal

Conf	$r_x$	Conf	$r_x$	Conf	$r_x$
	$r_\pi + (1 + \beta)R_E$ $\approx r_\pi (1 + g_m R_E)$ If $R_E = 0$ $r_x = r_\pi$		$r_o \left\{ 1 + g_m [(r_\pi + R_S) // R_E] \left( \frac{r_\pi}{r_\pi + R_S} \right) \right\}$ If $R_S = 0$ and $r_\pi \ll R_E$ $\Rightarrow r_{x,\max} = r_o (\beta + 1)$ If $R_E = 0$ , $r_x = r_o$		$\frac{1}{g_m}$
	$\frac{R_S + r_\pi}{1 + \beta} // r_o$ $\approx \frac{R_S}{1 + \beta} + \frac{1}{g_m}$ If $R_S = 0$ $r_x \approx \frac{1}{g_m}$		$\frac{1}{g_m} \times \frac{r_o + R_C}{r_o + R_C / \beta}$ If $R_C = 0$ , $r_x \approx \frac{1}{g_m}$		

### MOS Equivalent Resistance Summary (Table 2)

Blue: look into drain terminal

Red: look into gate terminal

Green: look into source terminal

Conf	$r_x$	Conf	$r_x$	Conf	$r_x$
	$\infty$		$r_o [1 + (g_m - g_{mb}) R_E]$ If $R_E = 0$ , $r_x = r_o$		$\frac{1}{g_m}$
	$\frac{1}{g_m - g_{mb}}$		$\frac{1}{g_m - g_{mb}} \times \frac{r_o + R_C}{r_o}$ If $R_C = 0$ , $r_x \approx \frac{1}{g_m - g_{mb}}$		