


EE2027 Electronic Circuits

Single-Stage Amplifier

Lecture Outline

- **2-Port Network (Voltage Amplifier and Transconductance Amplifier)**
2-port network parameters: R_{in} , R_{out} , voltage gain (A_v) or transconductance (G_m)
- **Single-Stage Amplifiers**
CE/CS, CB/CG.

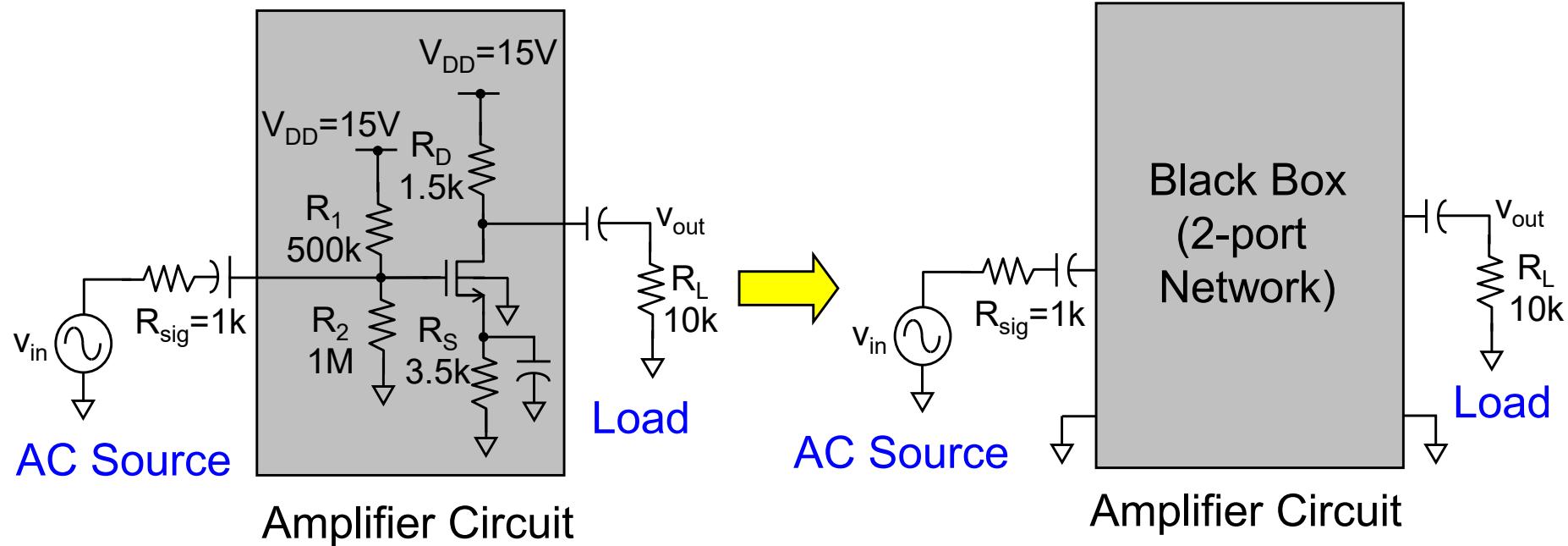Modeling Amplifier Circuit using 2-Port Network (in small-signal ac operation)



Can we fully characterize the complicated amplifier circuit using a **simple black box (2-port network)** with limited set of parameters?


Concept is similar to replacing a single-port complex linear network by Thevenin Equivalent with only one Thevenin voltage source (V_{THV}) in series with one Thevenin equivalent resistor (R_{THV}), i.e., only 2 parameters.

Analogy of 2-Port Network to Investment Scheme



- We are only interested in the **relationship between output and input**
- We don't care about what happens in between

Why Use 2-port Network?


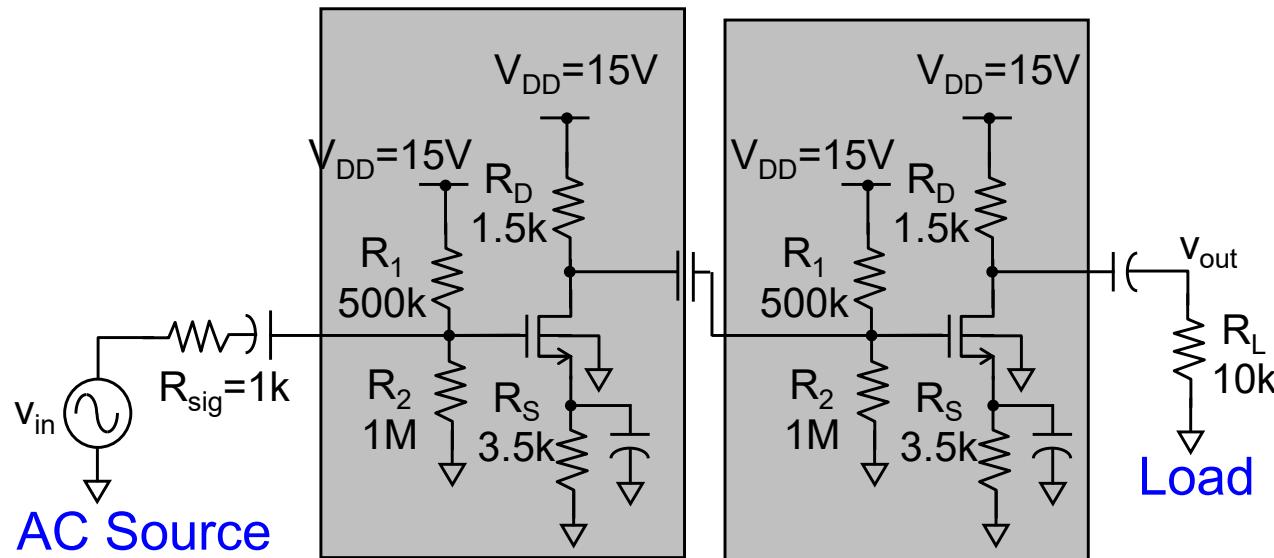


Amplifier Circuit


Amplifier Circuit

Easier to analyze complicated circuit (e.g., multi-stage amplifier) as each amplifier stage is simplified to its equivalent 2-port network.


Cascaded 2-port networks can be combined into a 'bigger' 2-port network.

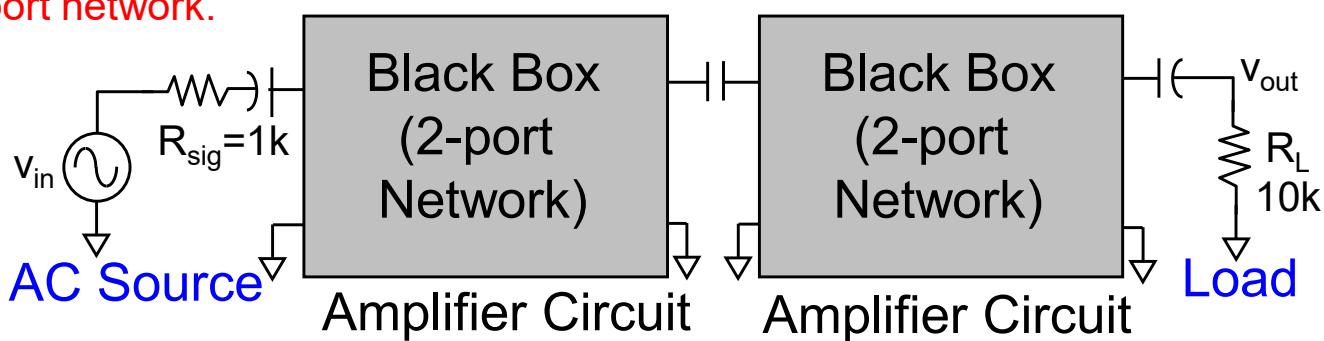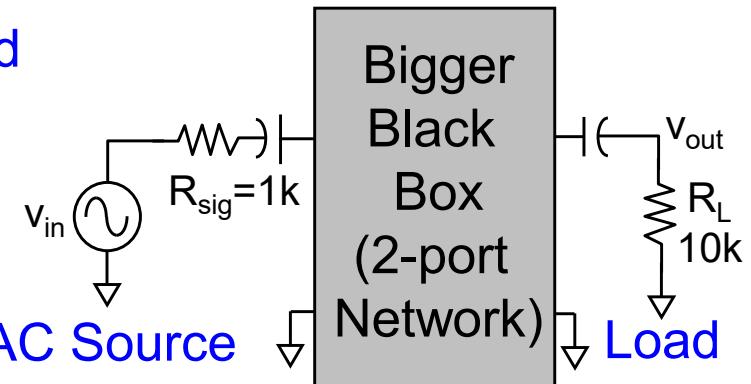


Different 2-Port Amplifier Models

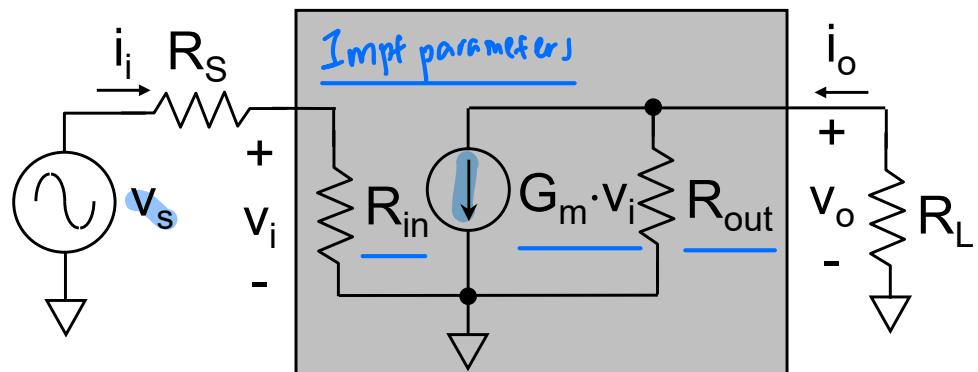


*** 2-Port Transconductance Amplifier

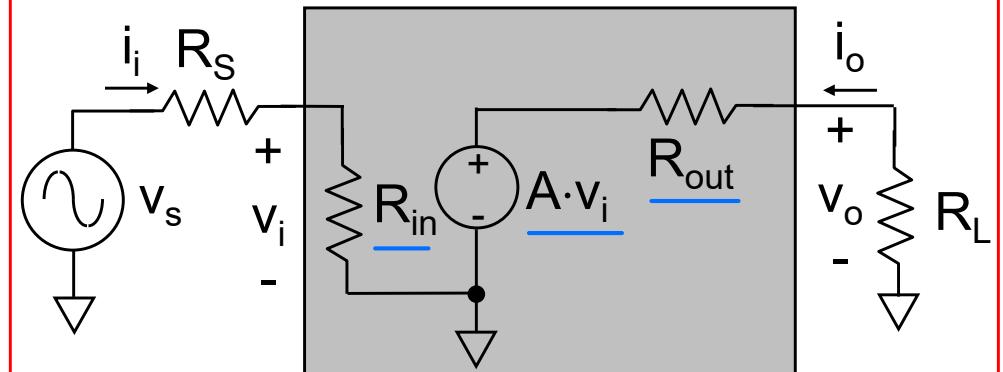

*** 2-Port Voltage Amplifier

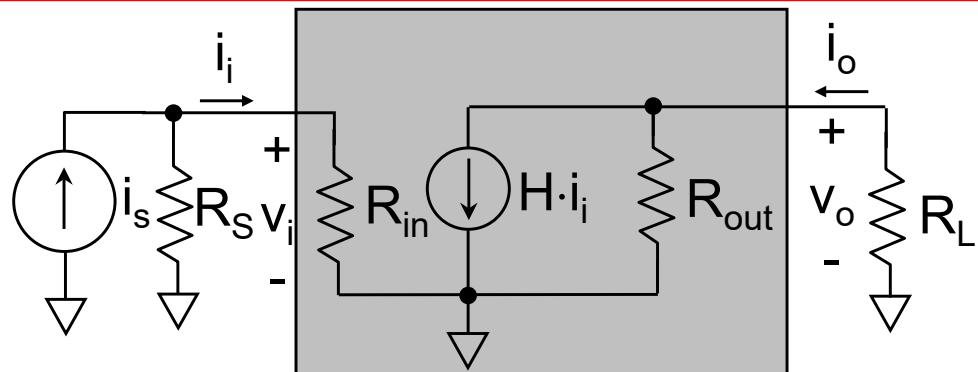


2-Port Current Amplifier *(Not tested)*

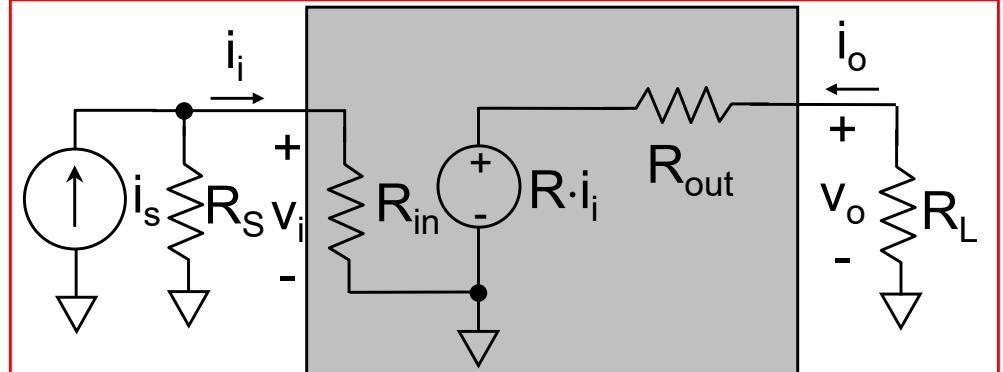

(Not tested) 2-Port Trans-resistance Amplifier

- All four can be used to represent the same amplifier circuit.
 - Same concept as Thevenin equivalent versus Norton equivalent (for a single-port linear network).
- In some scenarios, it is easier to represent the amplifier circuit as 2-Port Transconductance Amplifier to simplify the analysis. In others, it is easier to represent the amplifier circuit as 2-Port Voltage Amplifier to simplify the analysis. Same reasoning applies to 2-Port Current and Trans-resistance amplifier.
- In this module, only 2-Port Transconductance Amplifier and 2-Port Voltage Amplifier are considered as they simplify the analysis (based on experience of circuit designers).

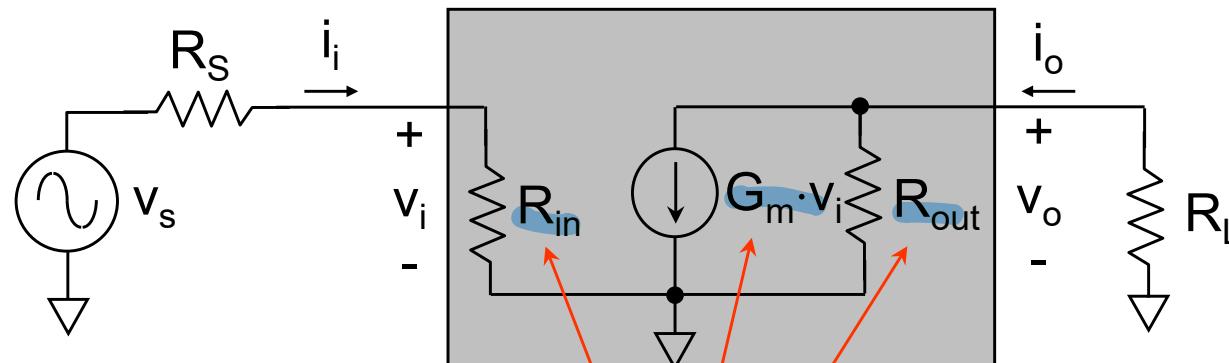Two-Port Network – Transconductance Amplifier






R_{in} , G_m and R_{out} characterize the whole two-port network used to represent the transconductance amplifier

- After converting amplifier circuit to 2-port network, it is easier to cascade multiple of them together and analyze (Refer to slide SSA1-4)


Characteristics:

- High input resistance (R_{in})
- High output resistance (R_{out})
- Transconductance amplifier (Voltage-to-current conversion: $G_m v_i$)

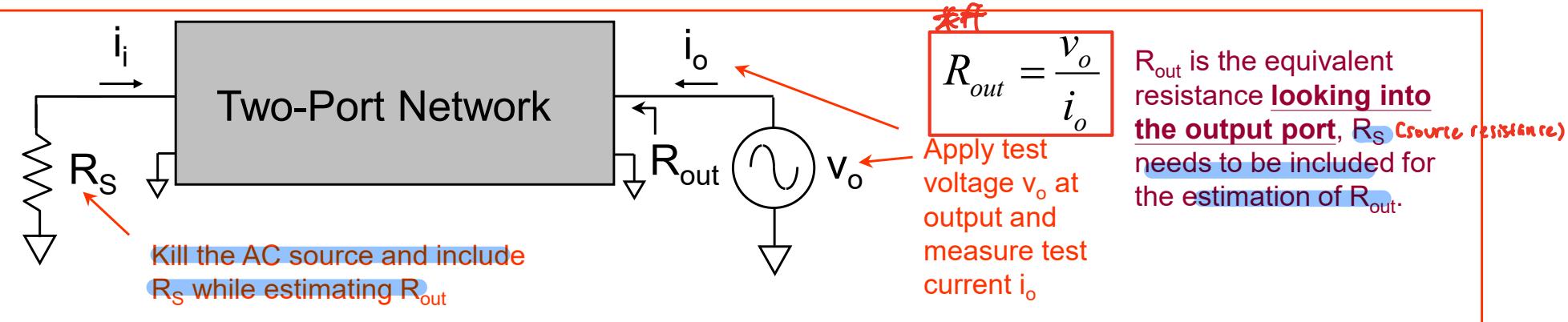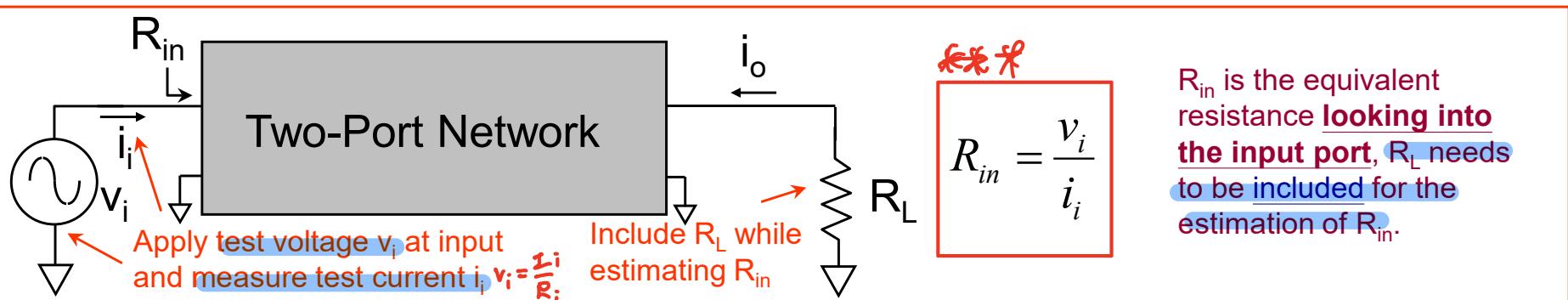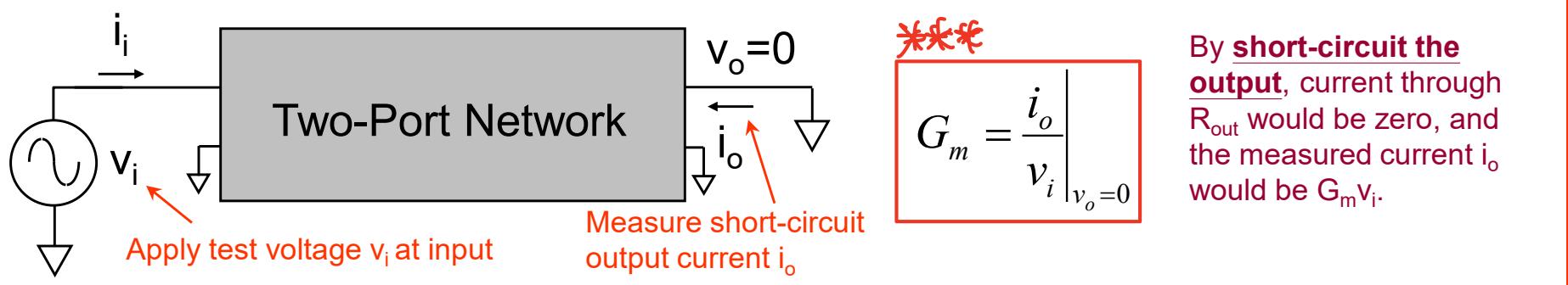Transconductance Amplifier – Parameter Characterizations




Equivalent Resistance

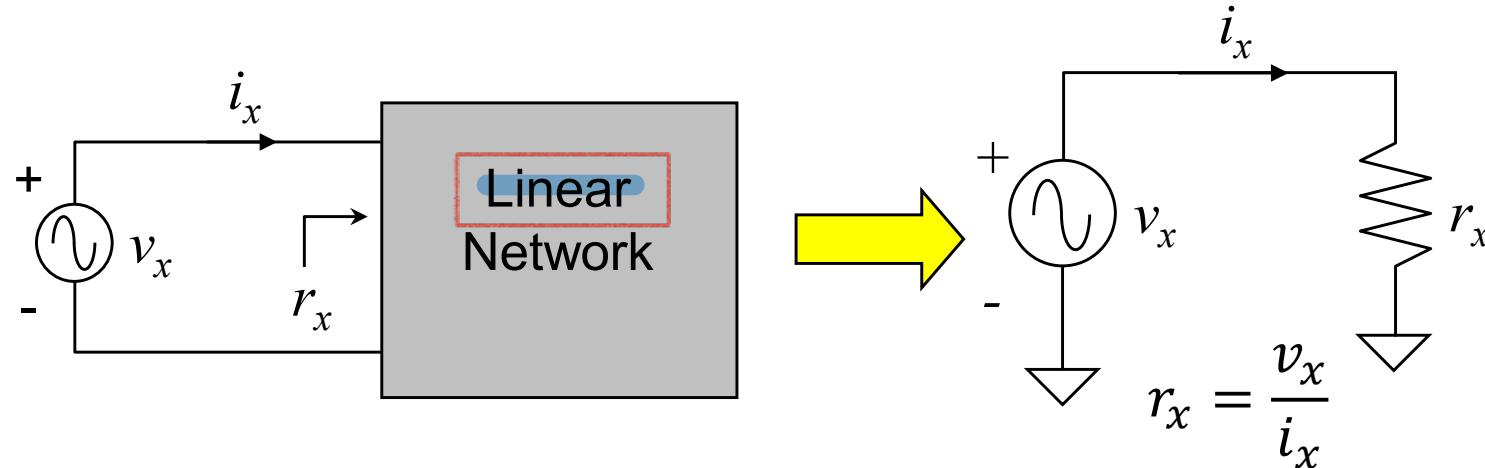

If the single-port **linear** network draws a current of i_x under an applied test voltage of v_x , the relation between i_x and v_x is **linear**. The linear network therefore behaves similarly to a simple resistor r_x , obeying Ohm's law

- Similar concept as Thevenin equivalent
- For a ~~complicated~~ **single-port LINEAR** network without any dependent voltage/current source, the current-voltage relationship can be modeled as a simple equivalent resistor

Two-Port Network – Voltage Amplifier



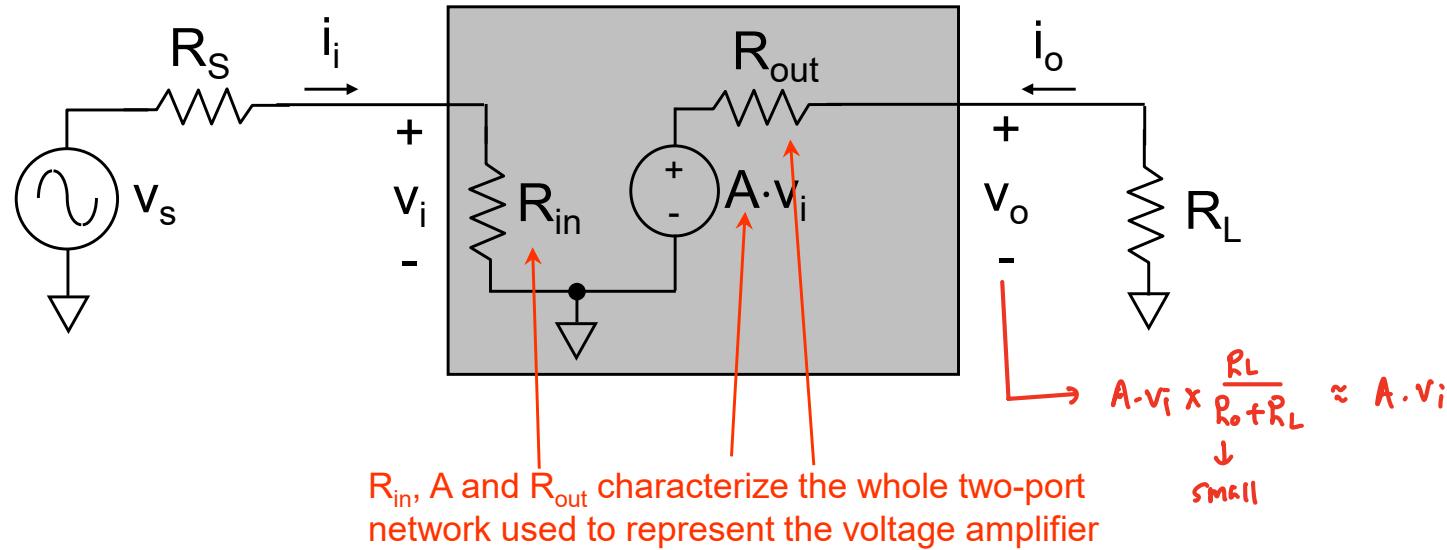


- After converting amplifier circuit to 2-port network, it is easier to cascade multiple of them together and analyze (Refer to slide SSA1-4)


Characteristics:

- High input resistance (R_{in})
- Low output resistance (R_{out})
- Voltage amplifier (Voltage gain: A)

Two-Port Network – Voltage Amplifier

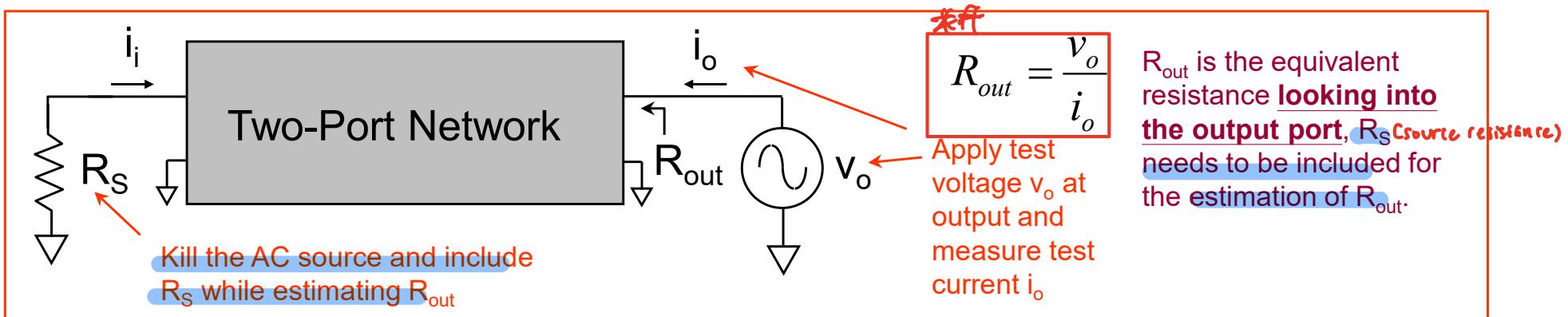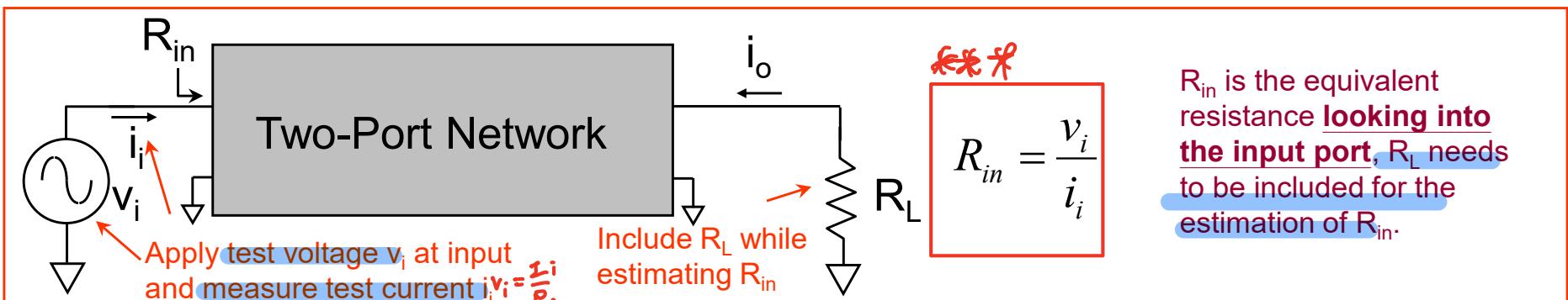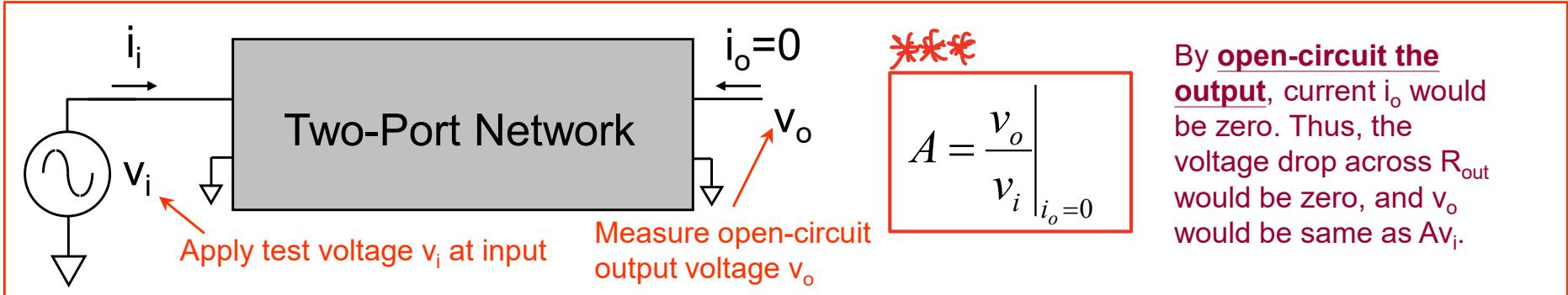

Example on Cascade Two-Port

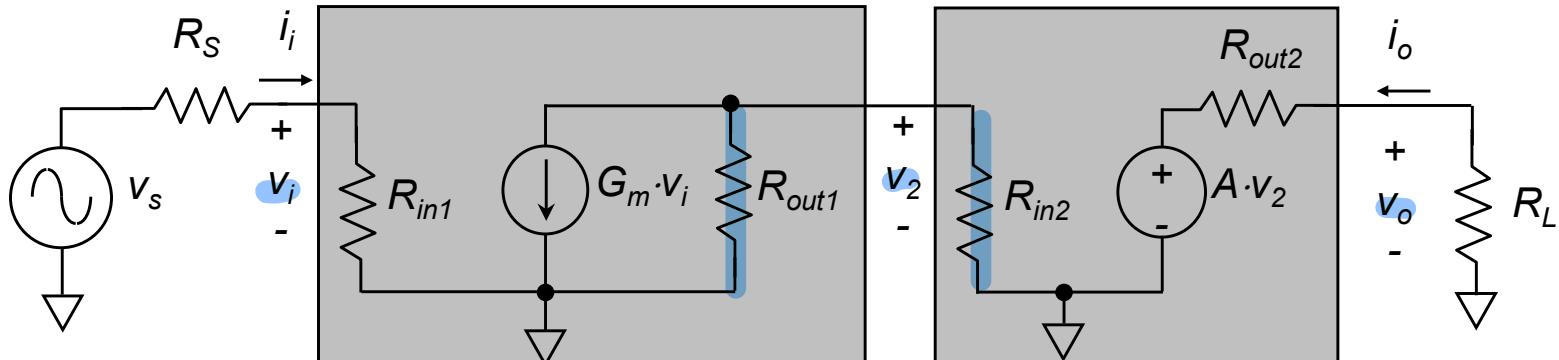

$$v_i = \frac{R_{in1}}{R_{in1} + R_s} \times v_s$$

~~$$v_2 = -G_m v_i \times (R_{out1} // R_{in2})$$~~

~~$$= -G_m \times \frac{R_{in1}}{R_{in1} + R_s} \times v_s \times (R_{out1} // R_{in2})$$~~

$$v_o = A v_2 \times \frac{R_L}{R_{out2} + R_L}$$

$$= \frac{A R_L}{R_{out2} + R_L} \left[-G_m \times \frac{R_{in1}}{R_{in1} + R_s} \times v_s \times (R_{out1} // R_{in2}) \right]$$



$$Gain = \frac{v_o}{v_s} = \underbrace{\frac{R_{in1}}{R_{in1} + R_s}}_{1^{st}} \times \underbrace{\left[-G_m \times (R_{out1} // R_{in2}) \right]}_{2^{nd}} \times \underbrace{A \times \frac{R_L}{R_{out2} + R_L}}_{3^{rd}} = \frac{v_i}{v_s} \times \frac{v_2}{v_i} \times \frac{v_o}{v_2}$$

Amplifier Circuit 2


In amplifier design,

- How should you choose R_{in1} with respect to R_s ?
- How should you choose R_{out2} with respect to R_L ?
- Why?
- What if the source and load are antenna or equipment with long coaxial cable?

How to Treat Capacitors?







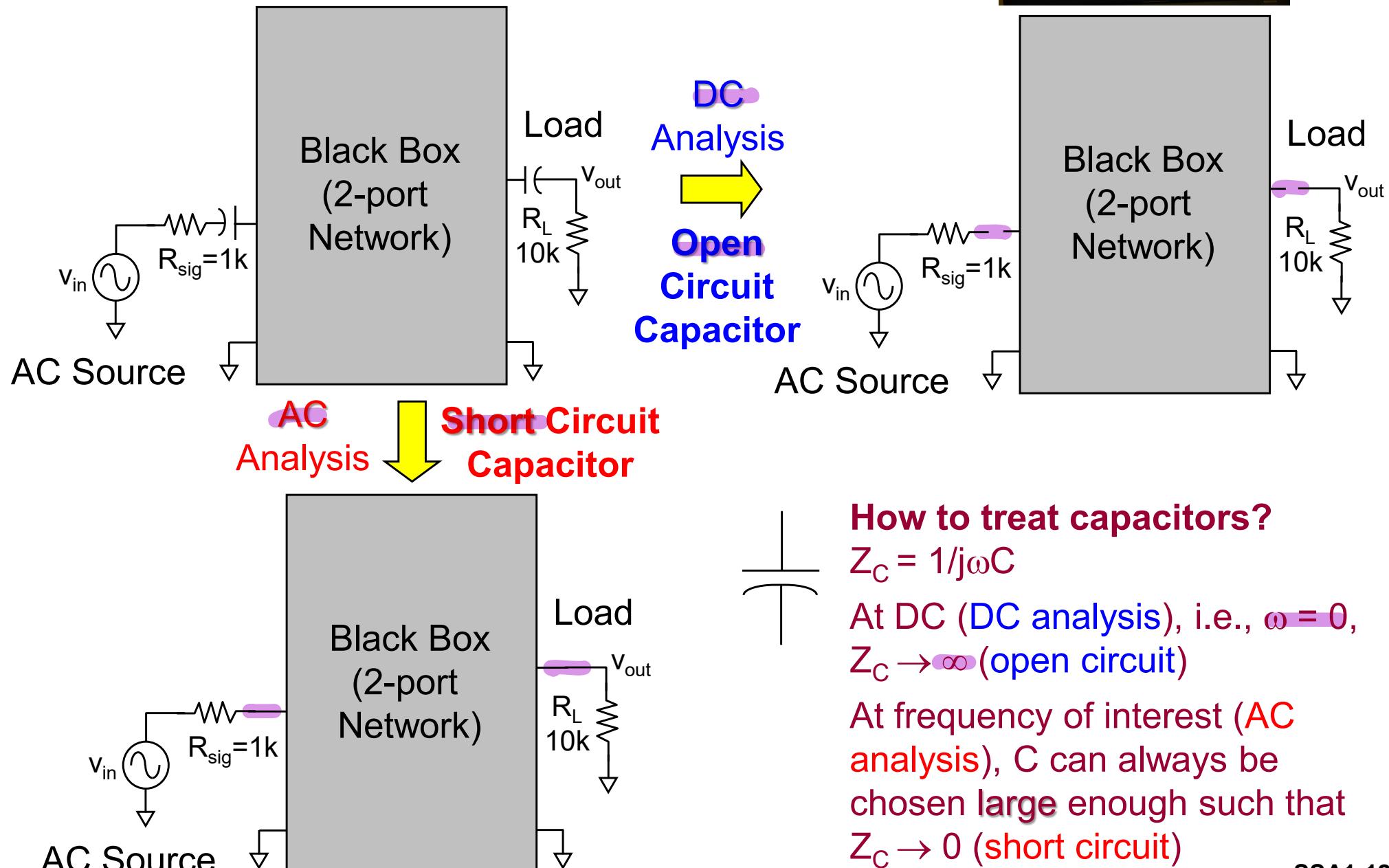
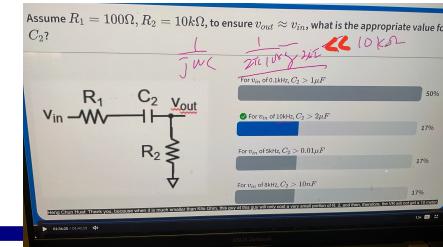


Steps for Circuit Analysis

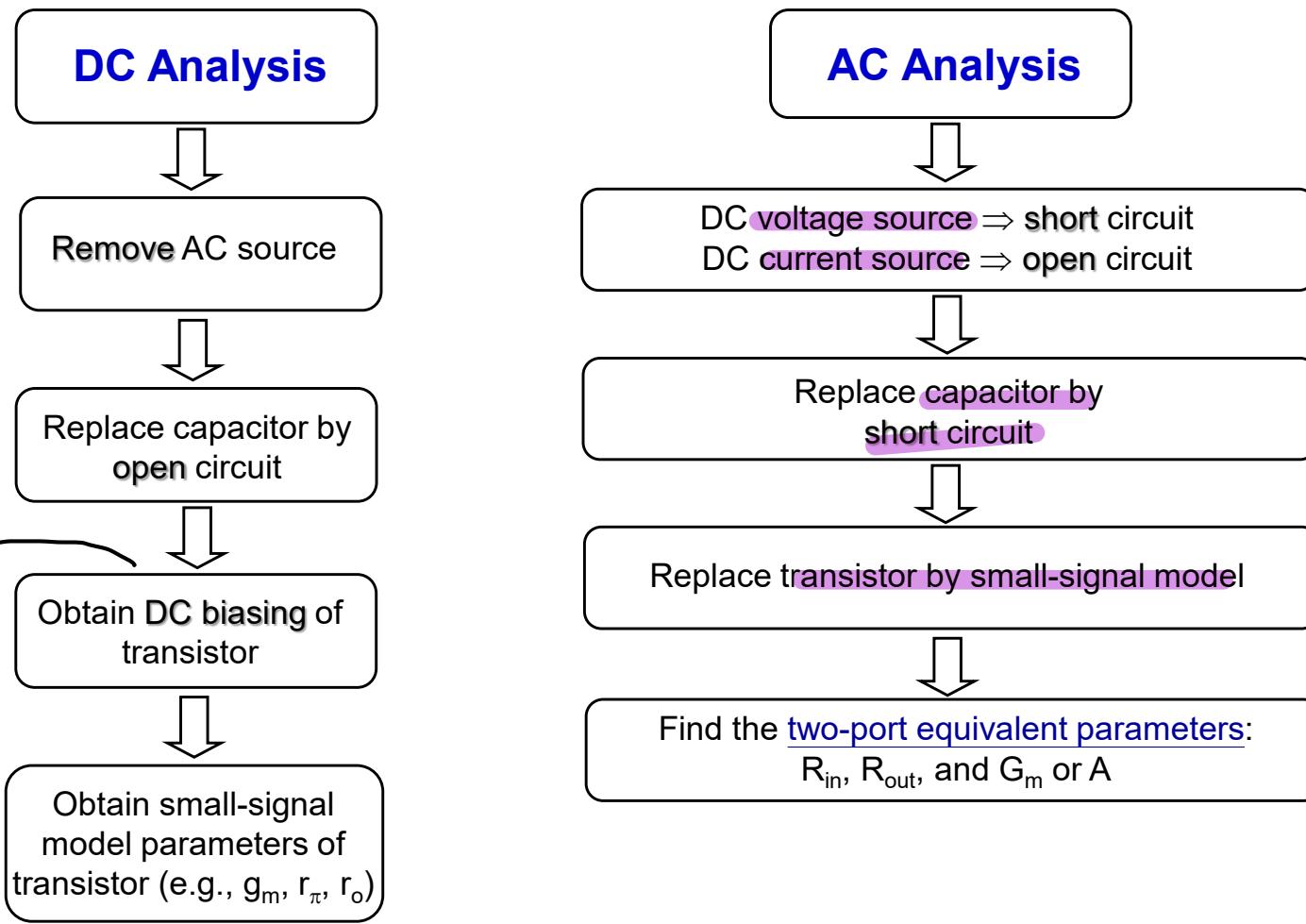



8 Amplifier Configurations

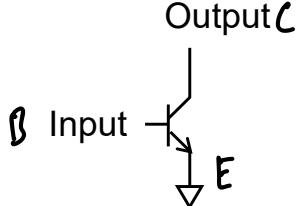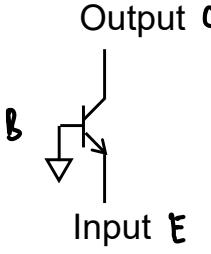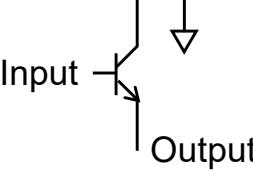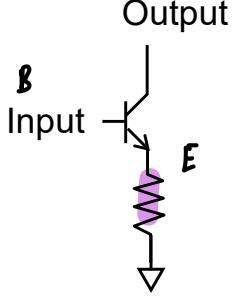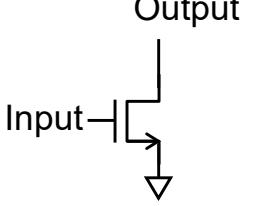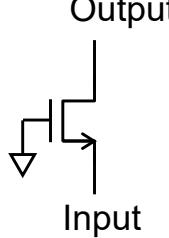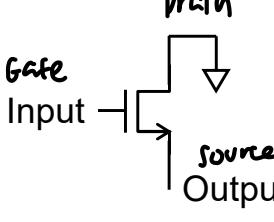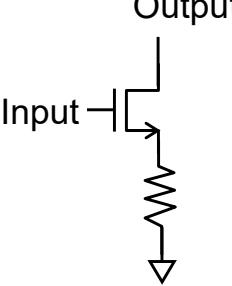
 <p>Input – Base Output – Collector Neither – Emitter \Rightarrow CE</p>	 <p>Input – Emitter Output – Collector Neither – Base \Rightarrow CB</p>	 <p>Input – Base Output – Emitter Neither – Collector \Rightarrow CC</p>	 <p>Input – Base Output – Collector Neither – Emitter (with resistor) \Rightarrow CE with degeneration</p>
 <p>Input – Gate Output – Drain Neither – Source \Rightarrow CS</p>	 <p>Input – Source Output – Drain Neither – Gate \Rightarrow CG</p>	 <p>Input – Gate Output – Source Neither – Drain \Rightarrow CD</p>	 <p>Input – Gate Output – Drain Neither – Source (with resistor) \Rightarrow CS with degeneration</p>

Common Emitter (CE) Amplifier


$$I_S = 10^{-15} \text{ A}$$

$$\beta = 100$$

$$V_A = 100 \text{ V}$$

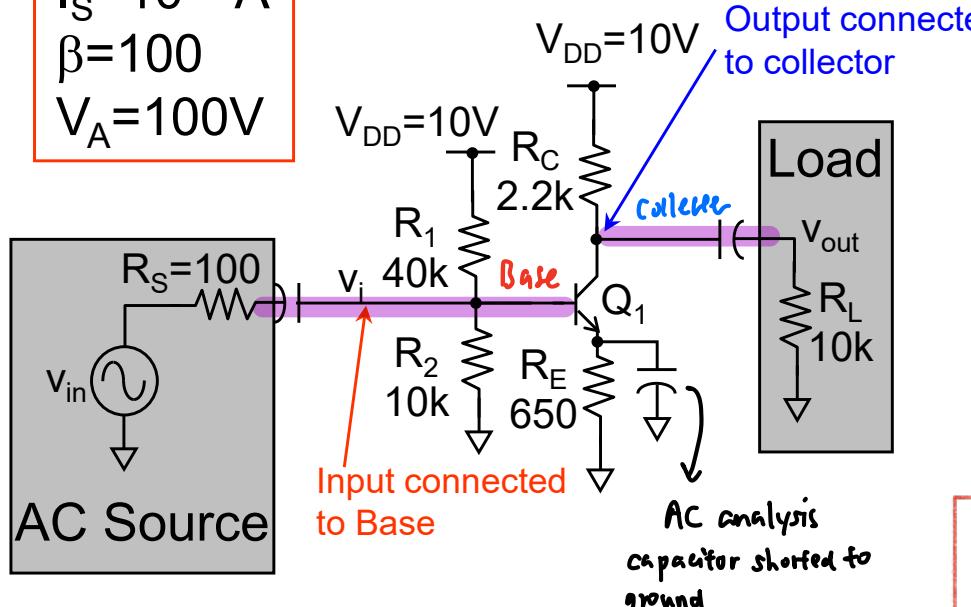

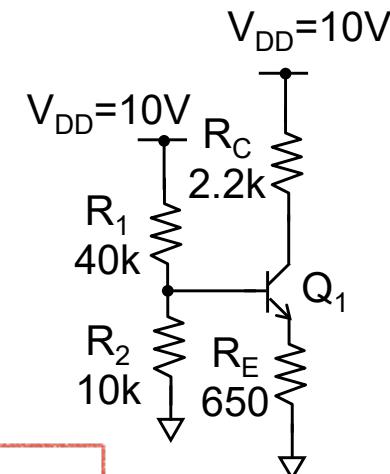For DC analysis, remove AC source and open circuit capacitors



Notations:


$V_{B,Q1}$: Base voltage of Q_1

$V_{E,Q1}$: Emitter voltage of Q_1

$V_{C,Q1}$: Collector voltage of Q_1

- Identify AC Source and Load
- To identify amplifier configuration, we need to consider AC equivalent circuit, i.e., short circuit capacitors
 - Input connected to **Base**, output connected to **Collector**, Emitter connected to neither input nor output \Rightarrow Common Emitter (CE)
- DC Analysis – refer to “BJT Lecture Notes” slides **BJT-21 to BJT-28**

DC Analysis for CE Amplifier

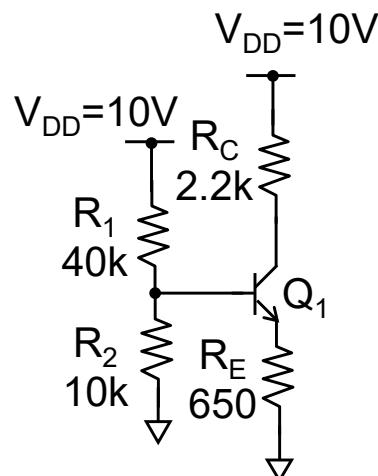

$$I_S = 10^{-15} \text{ A}$$

$$\beta = 100$$

$$V_A = 100 \text{ V}$$

Determine DC biasing

Assume $V_{BE,Q1} = 0.7 \text{ V}$ and

$$I_{B,Q1} \ll I_{R1}, I_{R2}$$

\Rightarrow voltage divider method

$$V_{B,Q1} = \frac{10\text{k}}{40\text{k} + 10\text{k}} \times 10 = 2 \text{ V}$$

$$V_{E,Q1} = 2 - 0.7 = 1.3 \text{ V}$$

$$I_{C,Q1} \approx I_{E,Q1} = \frac{1.3}{650} = 2 \text{ mA}$$

$$I_{B,Q1} = \frac{I_{C,Q1}}{100} \approx 20 \mu\text{A} \quad I_C = \beta I_B$$

$$I_{R1} \approx I_{R2} \approx 200 \mu\text{A} \gg I_{B,Q1}$$

\Rightarrow voltage divider valid

$$V_{BC,Q1} = V_{B,Q1} - V_{C,Q1}$$

$$= 2 - (V_{DD} - I_{C,Q1} \times R_C) = -3.6 \text{ V}$$

Assume forward active operation.
Need to verify.

Determine AC small-signal parameters

$$g_m = \frac{I_C}{V_T} \approx 25 \text{ mS}$$

$$r_\pi = \frac{\beta}{g_m} = 1.25 \text{ k}\Omega$$


$$r_o = \frac{V_A}{I_C} = 50 \text{ k}\Omega$$

BJT operates in forward active region.

$$V_{BE} > 0$$

$$V_{BC} < 0$$

AC Analysis for CE

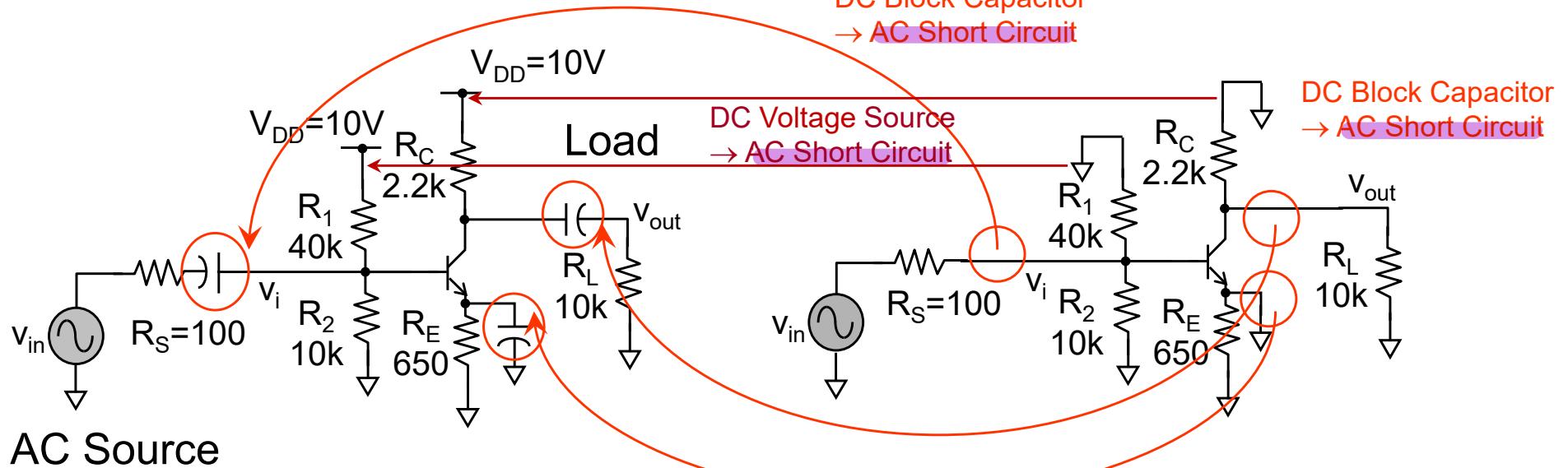

For AC analysis, need to consider the AC equivalent circuit -

Continue the analysis with AC equivalent circuit on the right.

$$g_m = 80 \text{ mA/V}$$


$$r_\pi = 1.25 \text{ k}\Omega$$

$$r_o = 50 \text{ k}\Omega$$


- Step 1 : Replace capacitor with AC short circuit
- Step 2 : Replace DC voltage source with AC short circuit
- Step 3 : Replace DC current source with AC open circuit

AC Analysis for CE
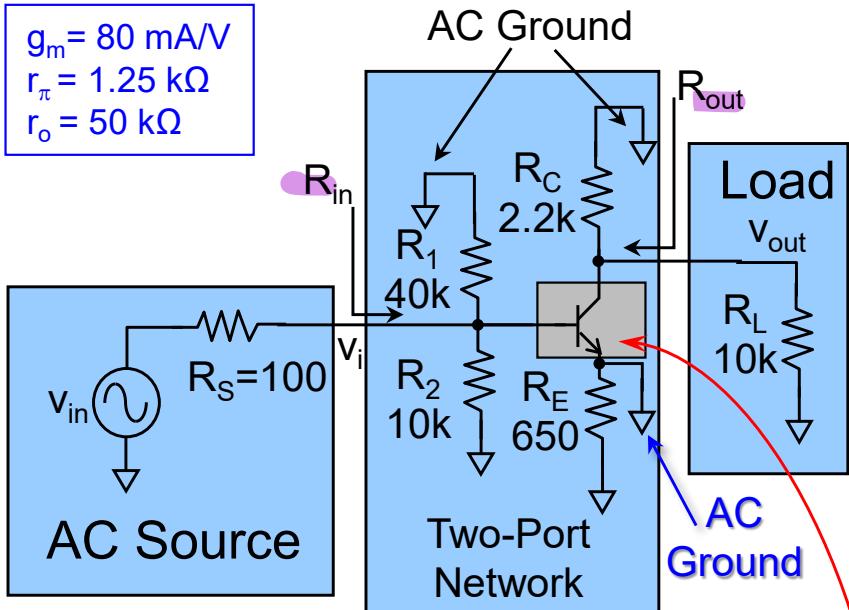
$$\begin{aligned} g_m &= 80 \text{ mA/V} \\ r_\pi &= 1.25 \text{ k}\Omega \\ r_o &= 50 \text{ k}\Omega \end{aligned}$$



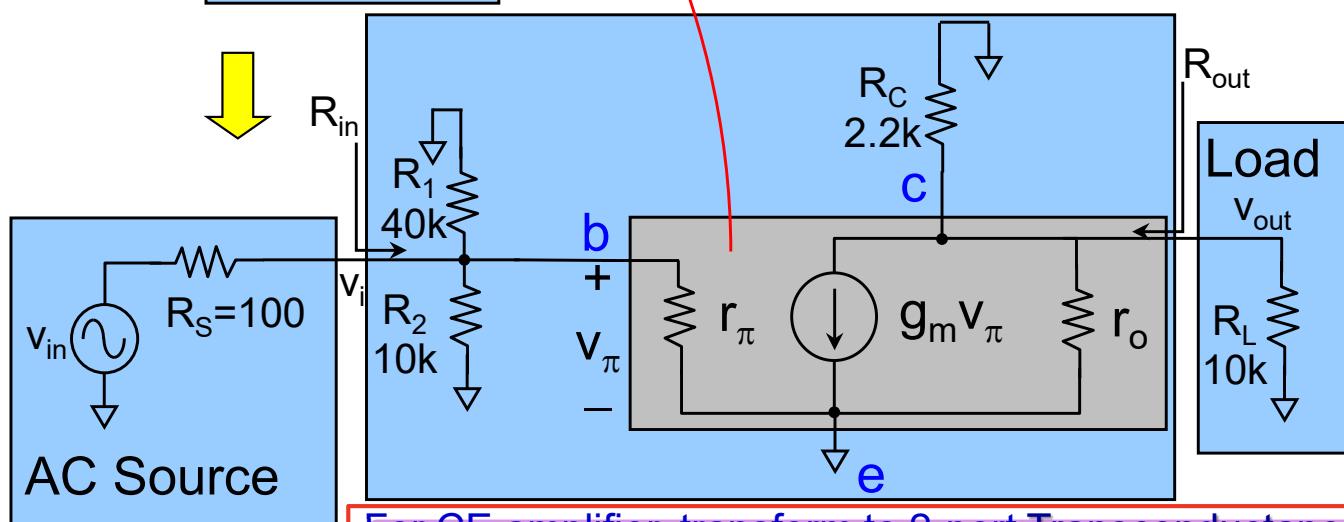
- Step 1 : Identify AC source and load
- Step 2 : Group the remaining components (the amplifier circuit) into two-port network
- Step 3 : Replace transistor with small-signal AC model



For CE amplifier, transform to 2-port Transconductance Amplifier (based on experience of circuit designers). Need to evaluate G_m , R_{in} and R_{out} .

Two-Port Network (G_m) CE
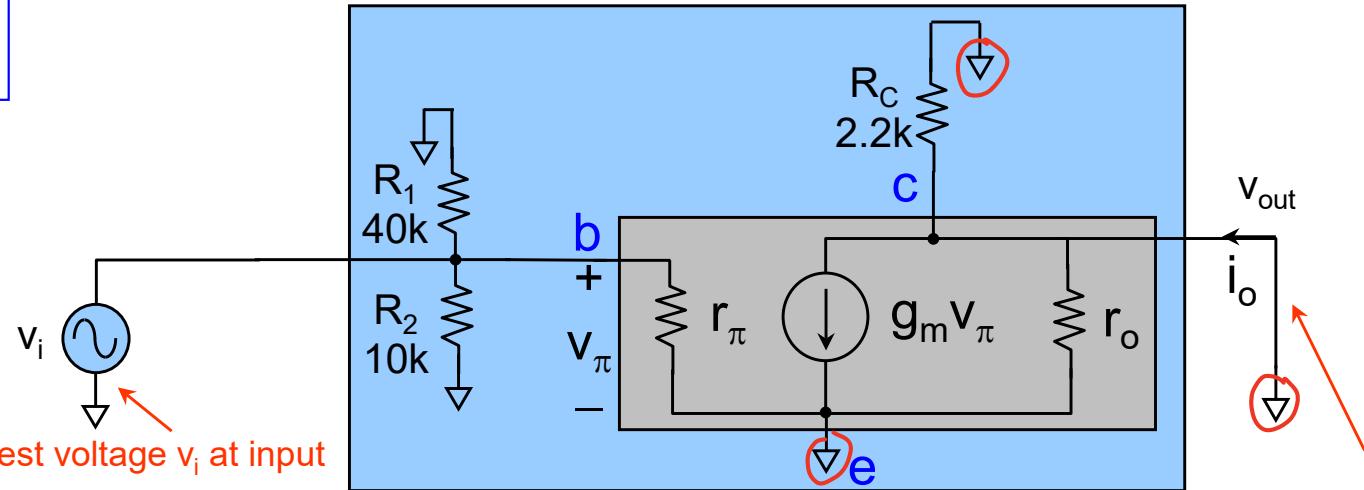
$$\begin{aligned} g_m &= 80 \text{ mA/V} \\ r_\pi &= 1.25 \text{ k}\Omega \\ r_o &= 50 \text{ k}\Omega \end{aligned}$$



Refer to slide SSA1-7 for the evaluation of G_m .

There is no current through r_o and R_c .

$$\therefore i_o = g_m v_\pi = g_m v_i \rightarrow v_\pi = v_i \text{ (parallel)}$$


$$\therefore G_m = \left. \frac{i_o}{v_i} \right|_{v_{out}=0} = g_m$$



Important Result:
For CE, G_m is directly given by g_m . **No need to rederive.**

Two-Port Network (R_{in}) CE
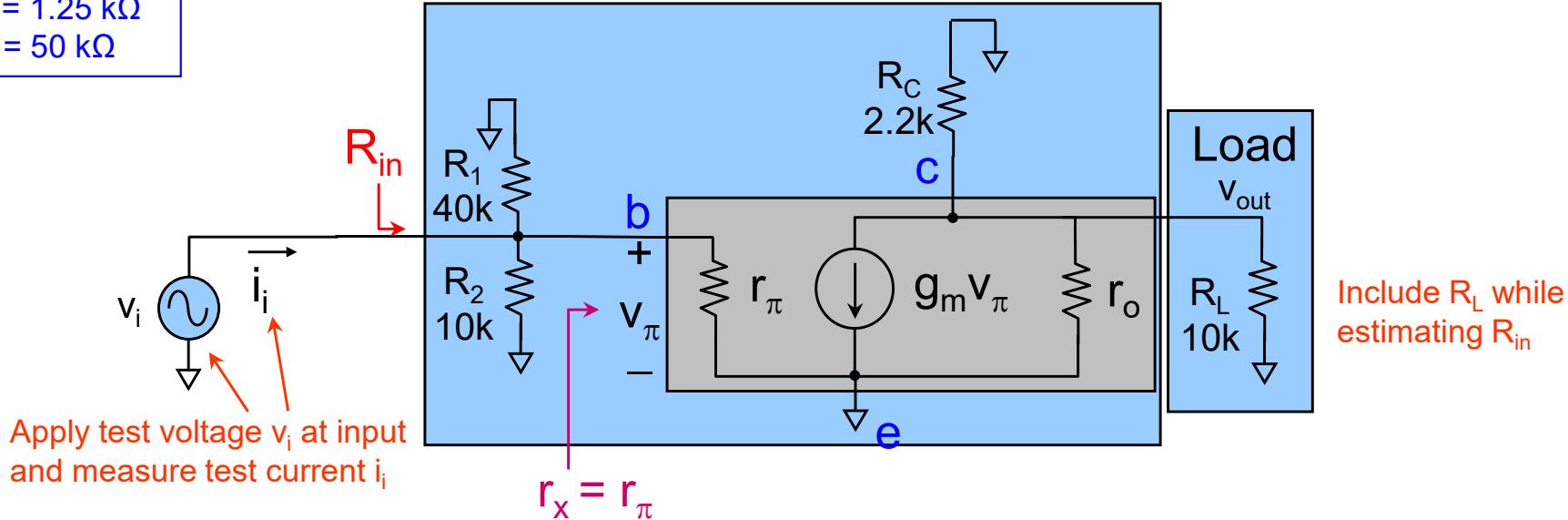
$$\begin{aligned} g_m &= 80 \text{ mA/V} \\ r_\pi &= 1.25 \text{ k}\Omega \\ r_o &= 50 \text{ k}\Omega \end{aligned}$$



Refer to slide SSA1-7 for evaluation of R_{in} .


No part of i_i flows to the output circuit.

$$\text{Hence } i_i = \frac{v_i}{R_1 // R_2 // r_\pi}.$$

Two slanted parallel lines mean resistors in parallel

$$\text{Hence } R_{in} = \frac{v_i}{i_i} = R_1 // R_2 // r_\pi.$$

Two-Port Network (R_{in}) CE

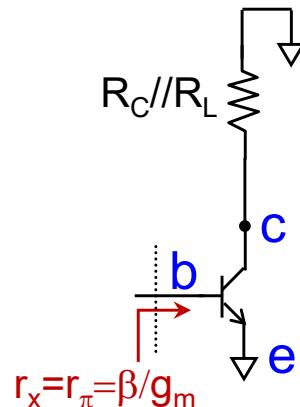


Important Result:

If you see a BJT connected in similar fashion, the **equivalent resistance looking into the base (r_x)** is directly given by r_π . **No need to rederive.** The resistance in the collector branch has no effect on r_x .

Two-Port Network (R_{out}) CE
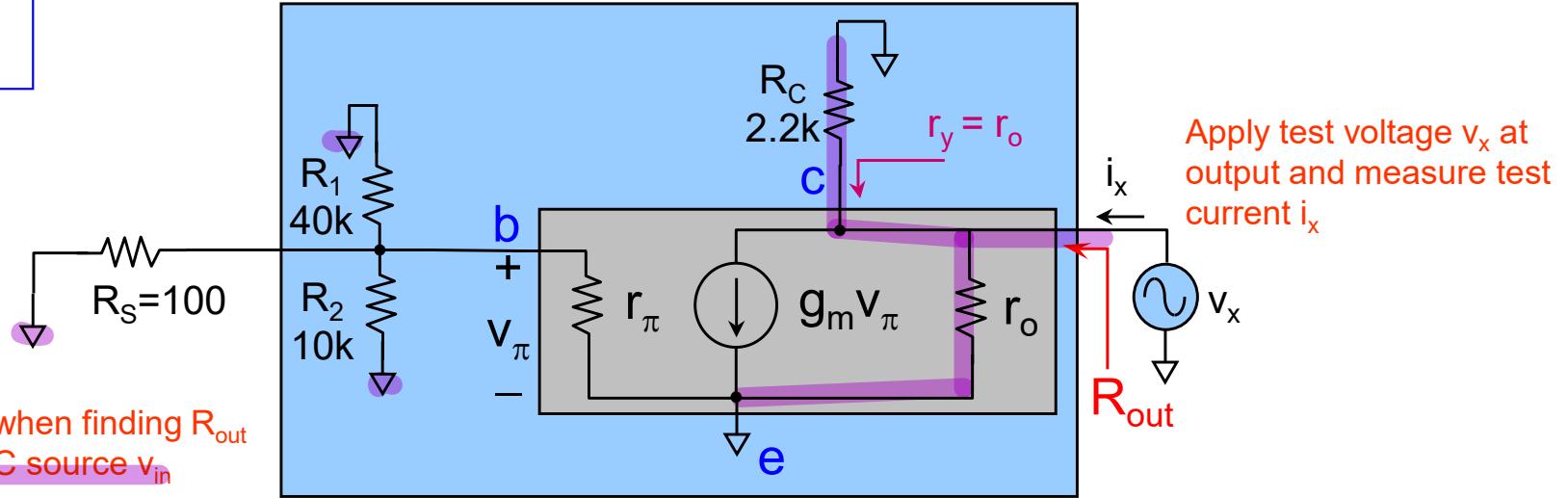
$$\begin{aligned} g_m &= 80 \text{ mA/V} \\ r_\pi &= 1.25 \text{ k}\Omega \\ r_o &= 50 \text{ k}\Omega \end{aligned}$$




Refer to slide SSA1-7 for evaluation of R_{out} .

As there is no base current, $v_\pi = 0 \Rightarrow g_m v_\pi = 0$. \rightarrow (This means that $g_m V_\pi$ is open circuit)

$$\text{Hence, } i_x = \frac{v_x}{R_c // r_o}.$$

$$\text{Hence } R_{out} = \frac{v_x}{i_x} = R_c // r_o.$$

Two-Port Network (R_{out}) CE

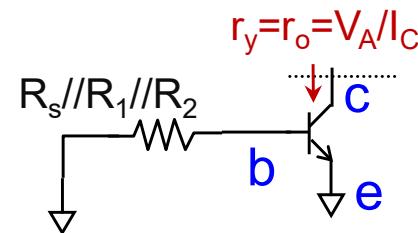


Important Result:

If you see a BJT connected in similar fashion, the equivalent resistance looking into the collector (r_y) is directly given by r_o . No need to rederive. The resistance in the base branch has no effect on r_y .

AC Analysis for CE



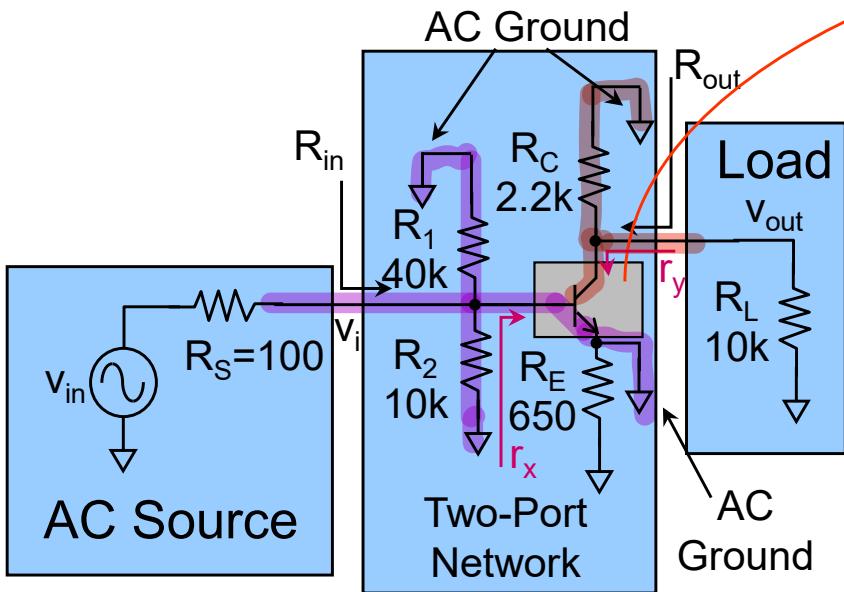**Short cut AC treatment
for quicker analysis.**




$$\begin{aligned} g_m &= 80 \text{ mA/V} \\ r_\pi &= 1.25 \text{ k}\Omega \\ r_o &= 50 \text{ k}\Omega \end{aligned}$$

Important Result:

If you see a BJT connected in similar fashion, the equivalent resistance looking into the Base (r_x) is directly given by r_π .
No need to rederive. The resistance in the Collector branch has no effect on r_x .

$$R_{in} = R_1 // R_2 // r_\pi.$$

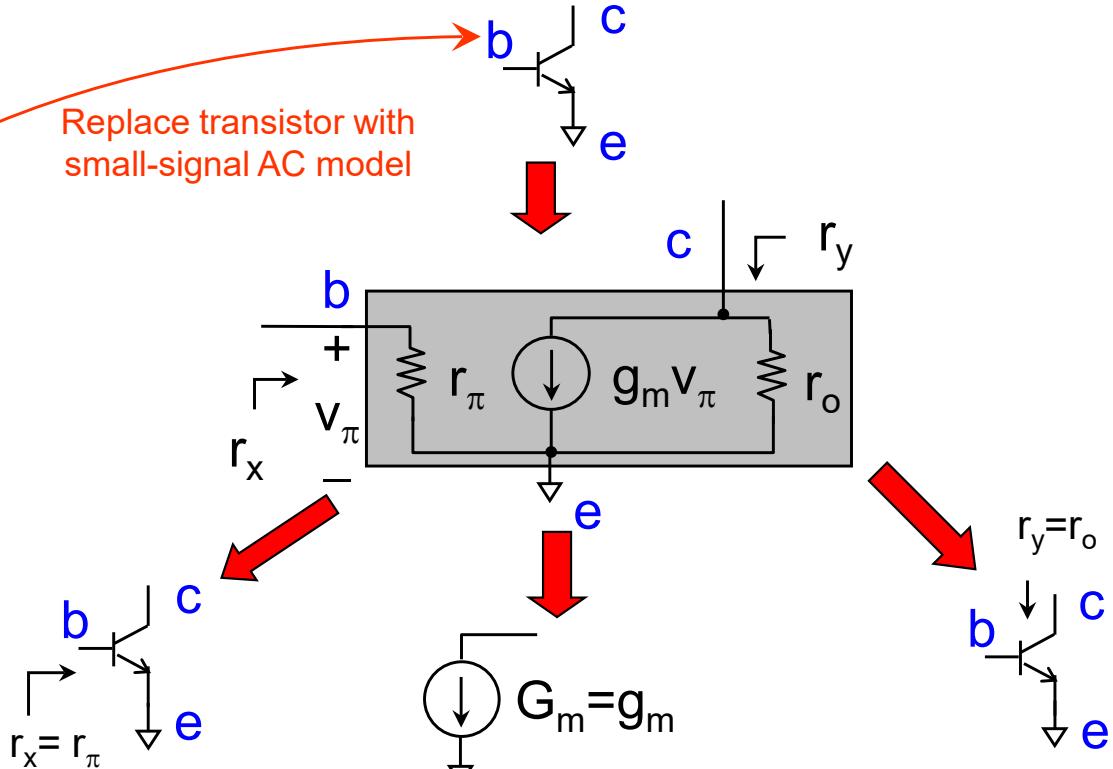Replace transistor with
small-signal AC model



Important Result:

For CE, G_m is directly given by g_m . No need to rederive.

CE

$$G_m = \frac{g_m}{r_\pi}$$

↓
BJT g_m


$$R_{out} = R_c // r_o.$$

Important Result:


If you see a BJT connected in similar fashion, the equivalent resistance looking into the Collector (r_y) is directly given by r_o . No need to rederive. The resistance in the Base branch has no effect on r_y .

Two-Port Network (A_V) CE
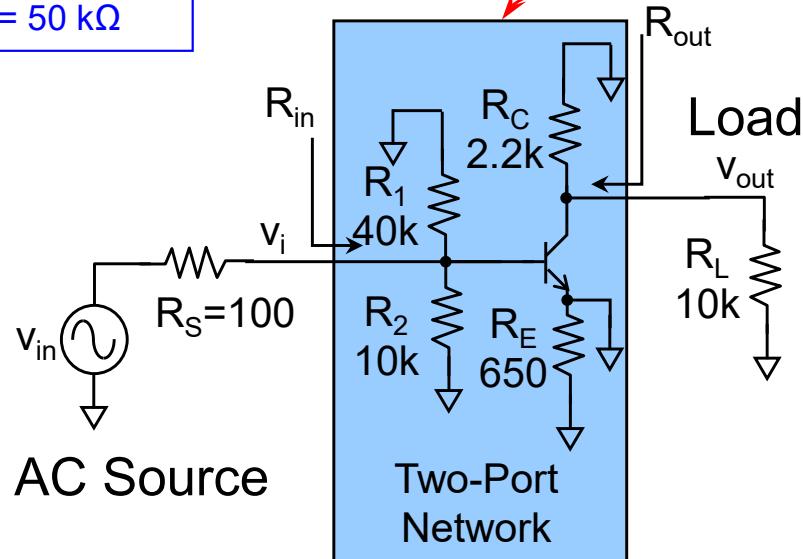
$$\begin{aligned} g_m &= 80 \text{ mA/V} \\ r_\pi &= 1.25 \text{ k}\Omega \\ r_o &= 50 \text{ k}\Omega \end{aligned}$$



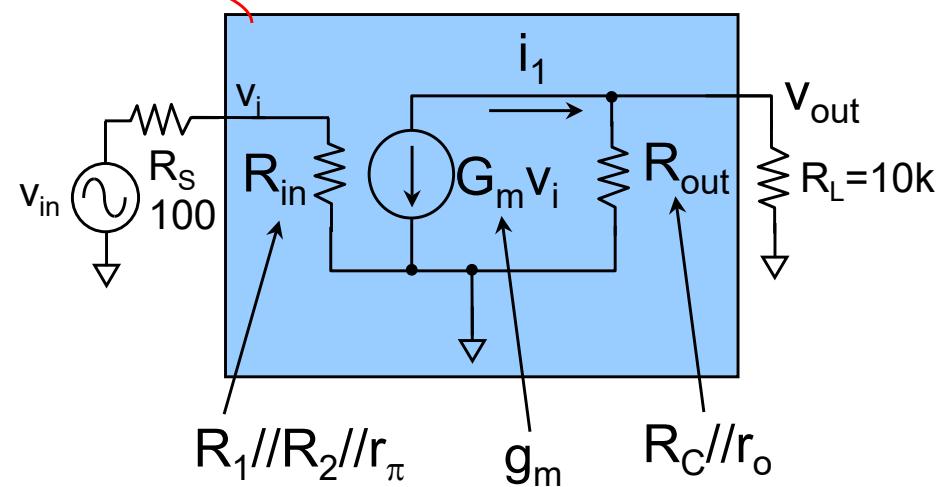Transform CE amplifier to its equivalent 2-port Transconductance Amplifier



$$v_i = \frac{R_{in}}{R_s + R_{in}} v_{in} = \frac{R_1 // R_2 // r_\pi}{R_s + R_1 // R_2 // r_\pi} v_{in} \approx v_{in}, \text{ as } R_s \ll R_1 // R_2 // r_\pi$$

* * * (Don't Assume This unless
Rs given)

$$i_1 = -g_m v_i \approx -g_m v_{in}$$

$$v_{out} = i_1 \times [R_{out} // R_L] = i_1 \times [(R_C // r_o) // R_L] = -g_m (R_C // r_o // R_L) v_{in}$$



$$\Rightarrow A_V = \frac{v_{out}}{v_{in}} = -g_m (R_C // r_o // R_L) = -144.3$$

Common Source (CS) Amplifier


$$K_n = 500 \mu\text{A/V}^2$$

$$V_{TH} = 1 \text{ V}$$

No body effect (Body and source shorted)

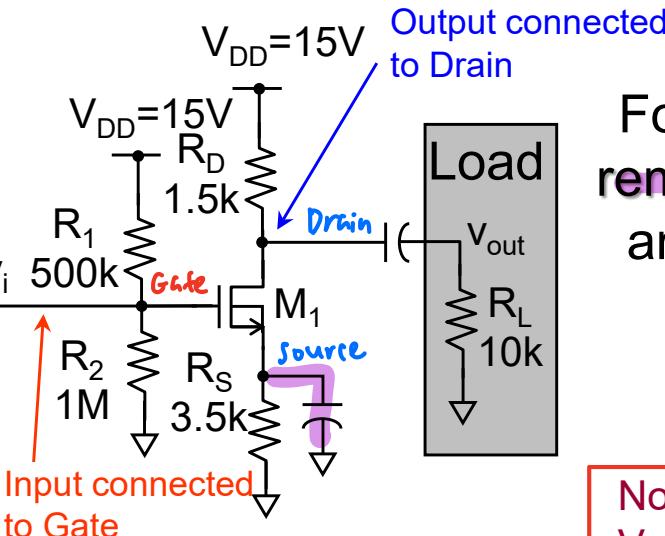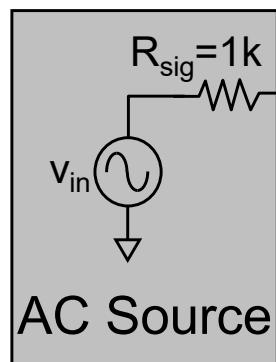

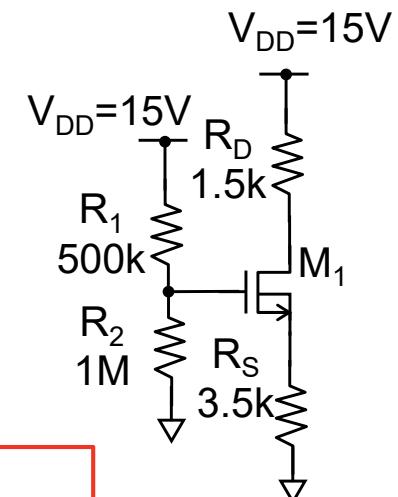For DC analysis, remove AC source and open circuit capacitors



Notations:

$V_{G,M1}$: Drain voltage of M_1


$V_{S,M1}$: Source voltage of M_1

$V_{D,M1}$: Drain voltage of M_1

$V_{B,M1}$: Body voltage of M_1

- Identify AC Source and Load
- To identify amplifier configuration, we need to consider AC equivalent circuit, i.e., short circuit capacitors
 - Input connected to Gate, output connected to Drain, Source connected to neither input nor output \Rightarrow Common Source (CS)
- DC Analysis - refer to "MOSFET Lecture Notes" slides **MOSFET-30 to MOSFET-33.**

DC Analysis for CS Amplifier

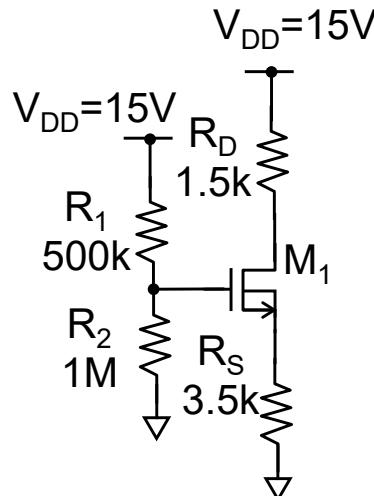

$K_n = 500 \mu\text{A/V}^2$
 $V_{TH} = 1 \text{ V}$
 No body effect (Body and source shorted)

Determine DC biasing

$$V_{G,M1} = \frac{1\text{M}}{500\text{k} + 1\text{M}} \times 15 = 10 \text{ V}$$

Square Law :

$$\begin{aligned} I_{D,M1} &= K_n (V_{GS} - V_{TH})^2 \\ &= K_n (V_{G,M1} - V_{S,M1} - V_{TH})^2 \\ &= 500\mu(9 - V_{S,M1})^2 \end{aligned}$$

✖✖
 Square Law is applicable for saturation region operation of MOSFET. Need to verify.

Ohm's Law :

$$I_{D,M1} = I_{S,M1} = \frac{V_{S,M1}}{R_S} = \frac{V_{S,M1}}{3.5\text{k}}$$

$$\Rightarrow \frac{V_{S,M1}}{3.5\text{k}} = 500\mu(9 - V_{S,M1})^2$$

$$1.75V_{S,M1}^2 - 32.5V_{S,M1} + 141.75 = 0$$

$$\Rightarrow V_{S,M1} = 6.94 \text{ or } 11.63 \text{ V}$$

$11.63 \text{ V} > V_{G,M1} \Rightarrow$ invalid

$$I_{D,M1} = 2 \text{ mA}$$

$$V_{DS} = V_{DD} - I_{D,M1} R_D - V_{S,M1} = 5.06 \text{ V}$$

$$V_{GS} - V_{TH} = 2.06 \text{ V}$$

$$\Rightarrow V_{DS} > V_{GS} - V_{TH}$$

Device operates in saturation region

Determine AC small-signal parameters


$$g_m = 2\sqrt{K_n I_{D,M1}} = 2 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_{D,M1}} = \infty$$

AC Analysis for CS (Self Reading)

For AC analysis, need to consider the AC equivalent circuit -
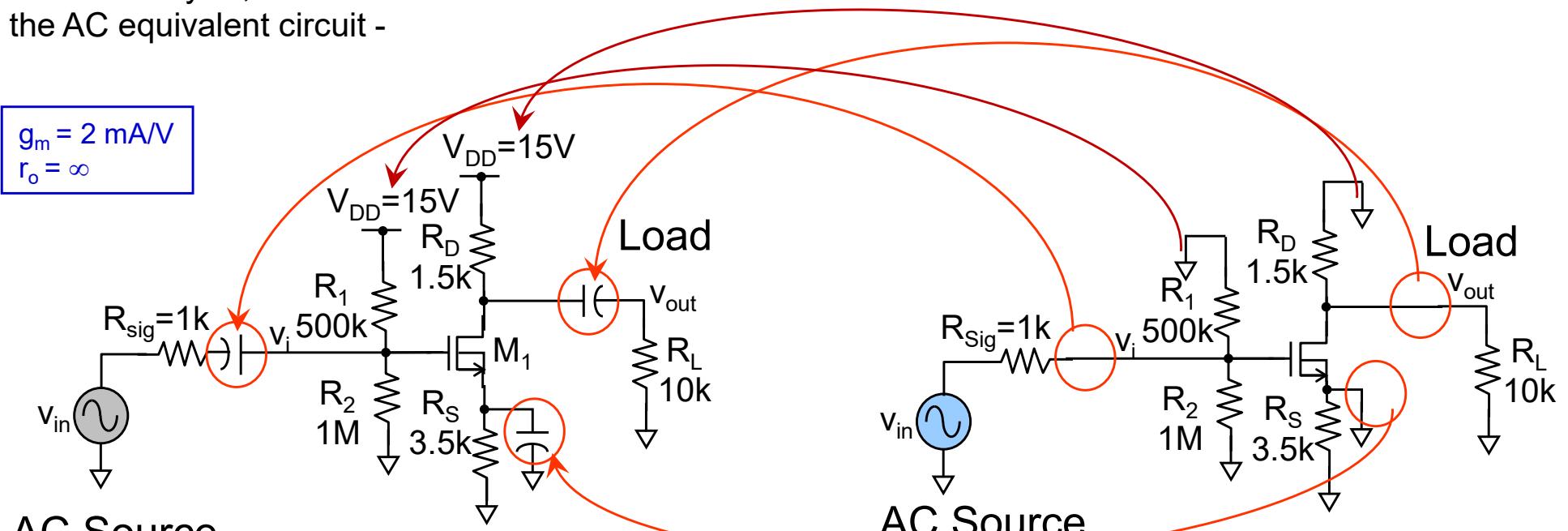
$$\begin{aligned} g_m &= 2 \text{ mA/V} \\ r_o &= \infty \end{aligned}$$



AC Source


Continue the analysis with AC equivalent circuit on the right.

Step 1 :
Replace capacitor with AC short circuit

Step 2 :
Replace DC voltage source with AC short circuit

Step 3 :
Replace DC current source with AC open circuit


AC Analysis for CS (Self Reading)

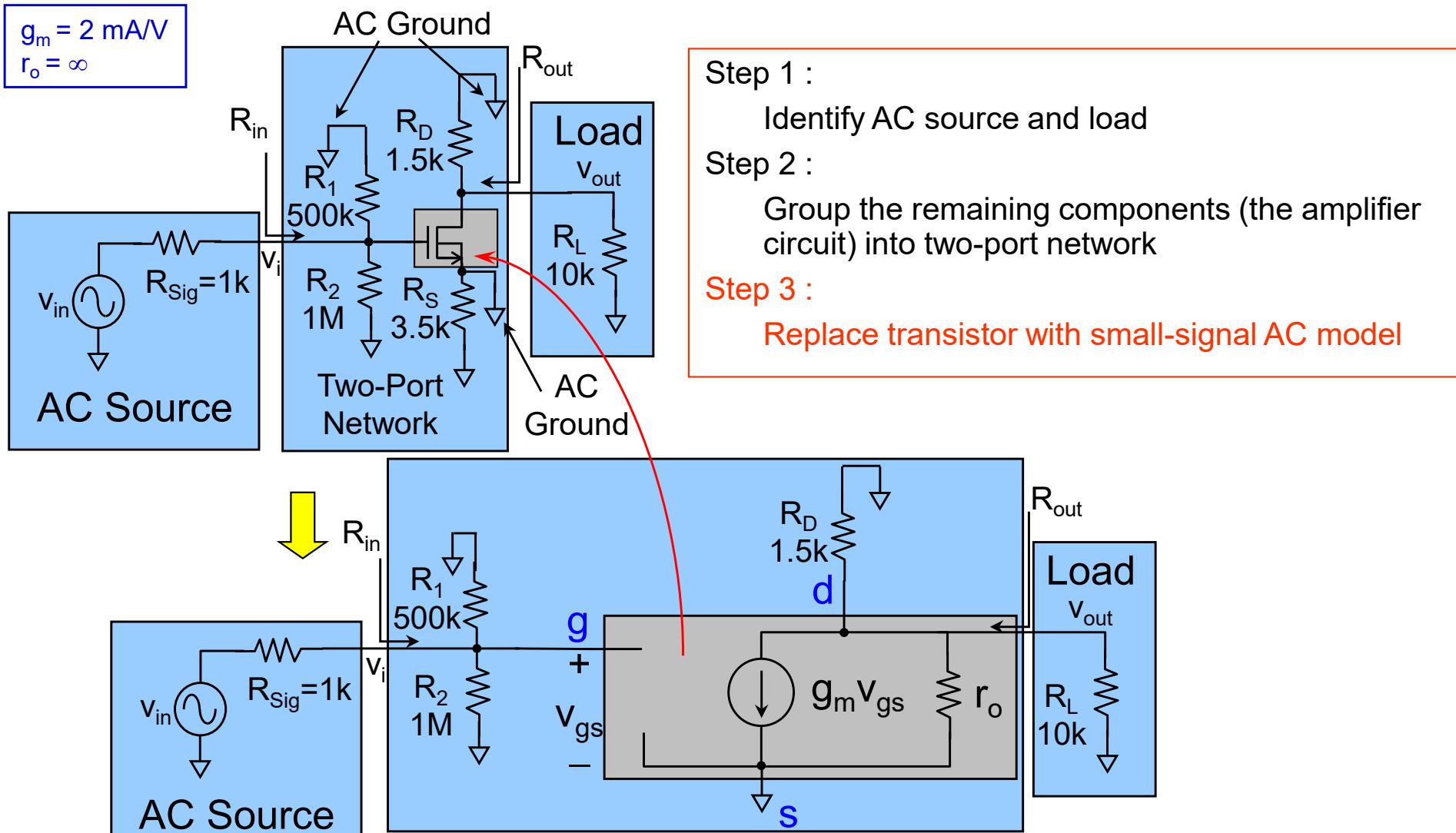

For CS amplifier, transform to 2-port Transconductance Amplifier (based on experience of circuit designers). Need to evaluate G_m , R_{in} and R_{out} .

Two-Port Network(G_m)CS (Self Reading)
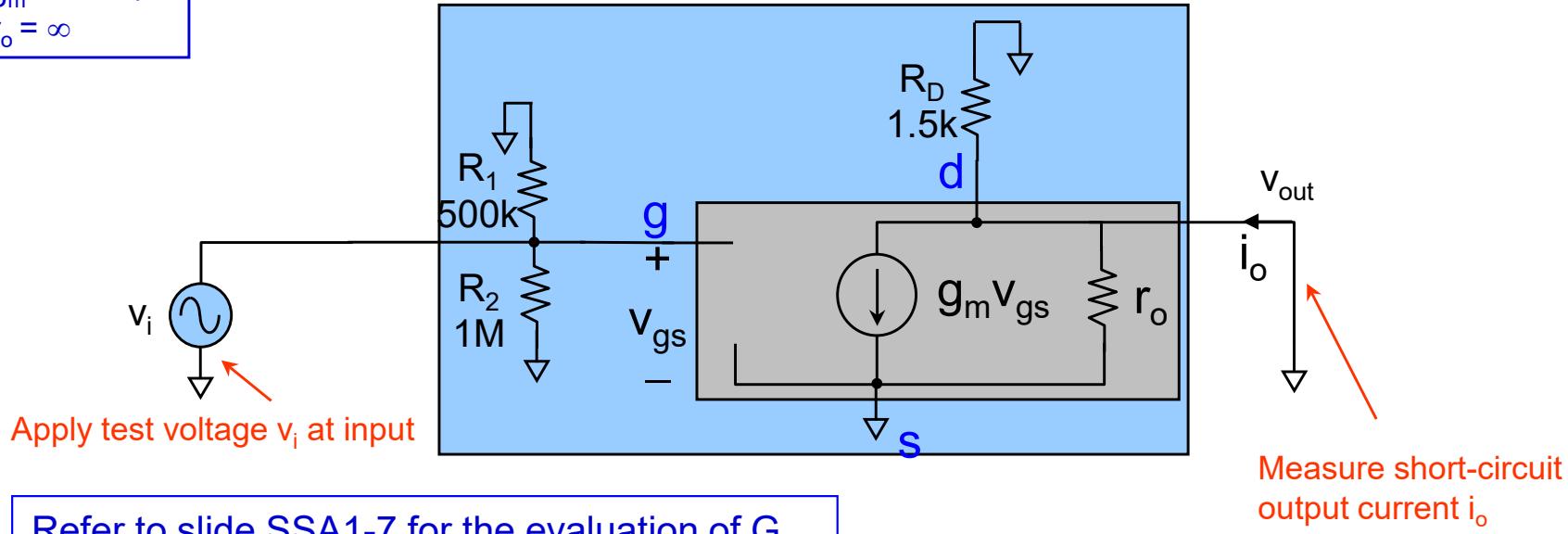
$$g_m = 2 \text{ mA/V}$$
$$r_o = \infty$$



There is no current through r_o and R_D .

$$\therefore i_o = g_m v_{gs} = g_m v_i.$$


$$\therefore G_m = \frac{i_o}{v_i} \Big|_{v_{out}=0} = g_m$$

Important Result:
For CS, G_m is directly given by g_m . No need to rederive.

Two-Port Network(R_{in})CS (Self Reading)

$$g_m = 2 \text{ mA/V}$$

$$r_o = \infty$$

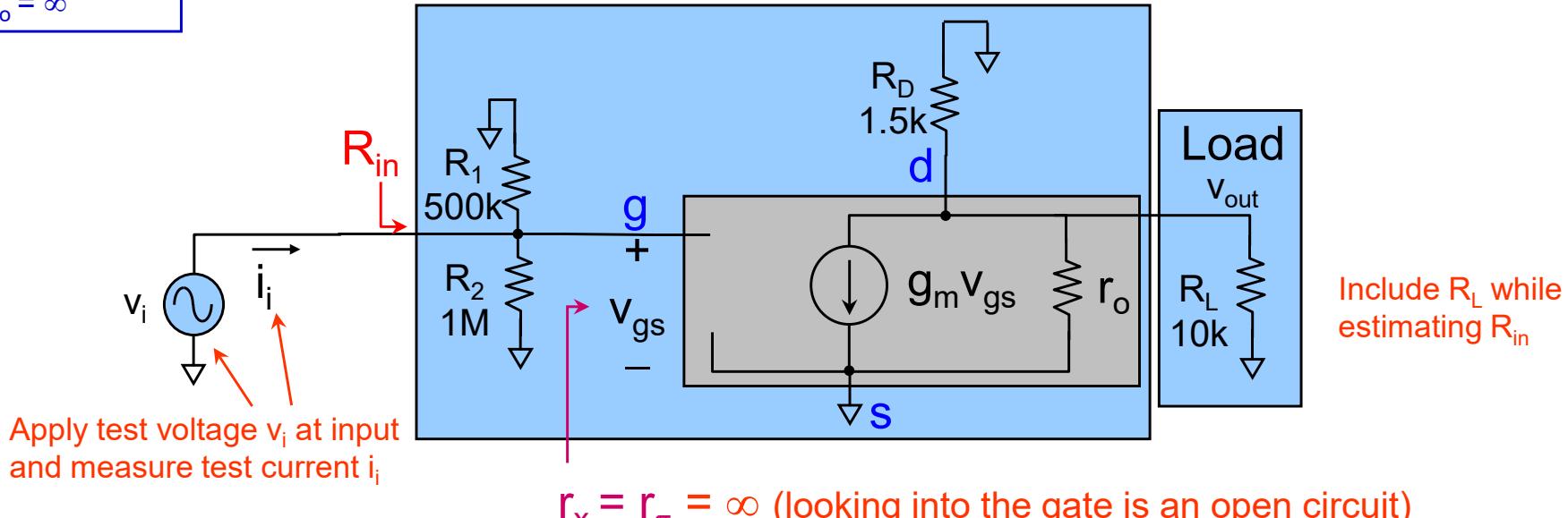

Refer to slide SSA1-7 for the evaluation of R_{in} .


No part of i_i flows to the output circuit.

Hence $i_i = \frac{v_i}{R_1 // R_2}$.

Two slanted parallel lines mean resistors in parallel

Hence $R_{in} = \frac{v_i}{i_i} = R_1 // R_2$.

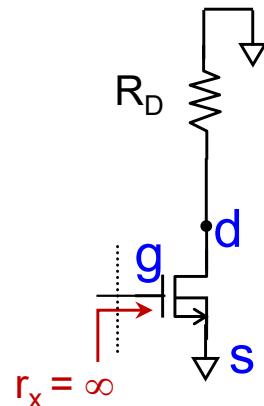Two-Port Network(R_{in})CS (Self Reading)




Important Result:

If you see a MOSFET connected in similar fashion, the **equivalent resistance** looking into the **gate** (r_x) is ∞ . **No need to rederive**. The resistance in the drain branch has no effect on r_x .

Two-Port Network(R_{out})CS (Self Reading)

$$g_m = 2 \text{ mA/V}$$

$$r_o = \infty$$

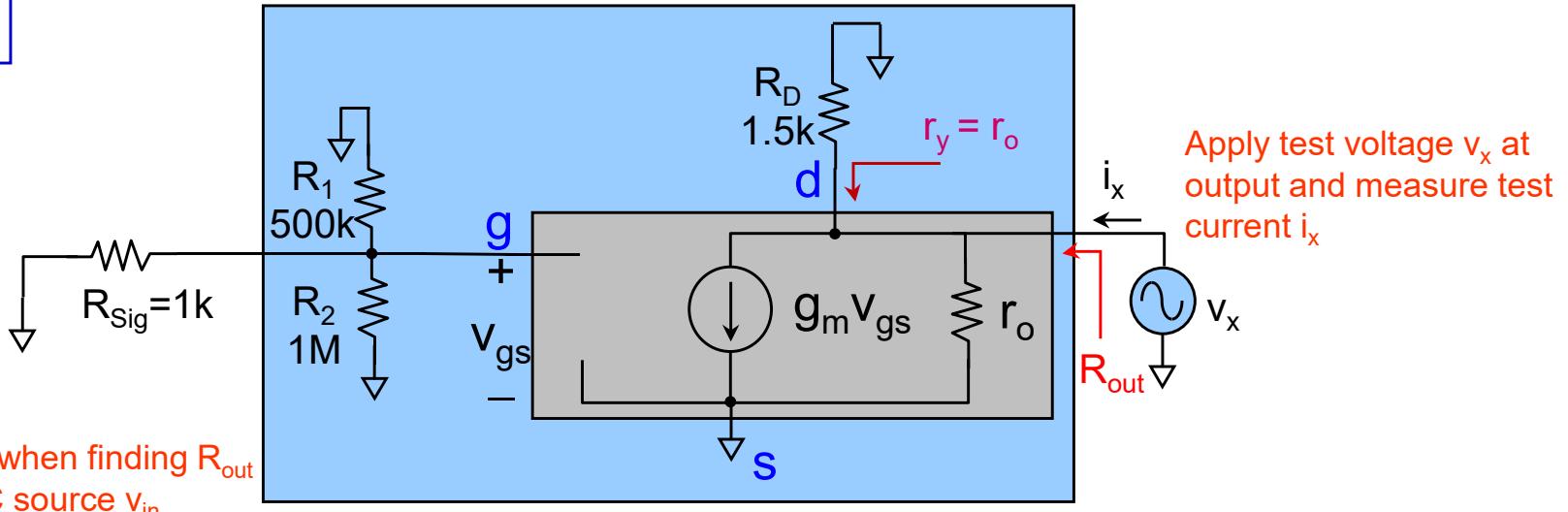


Refer to slide SSA1-7 for the evaluation of R_{out} .

As there is no gate current, $v_{gs} = 0 \Rightarrow g_m v_{gs} = 0$.

Hence, $i_x = \frac{v_x}{R_D // r_o}$.

Hence $R_{out} = \frac{v_x}{i_x} = R_D // r_o$.

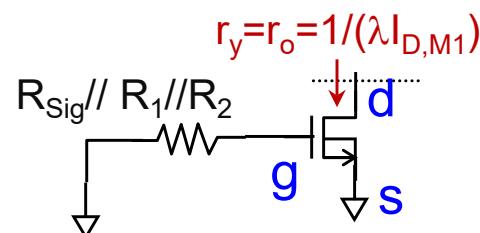Two-Port Network(R_{out})CS (Self Reading)




Important Result:

If you see a MOSFET connected in the similar fashion, the **equivalent resistance** looking into the drain (r_y) is directly given by r_o . **No need to rederive**. The resistance in the gate branch has no effect on r_y .


AC Analysis for CS

* * * * *

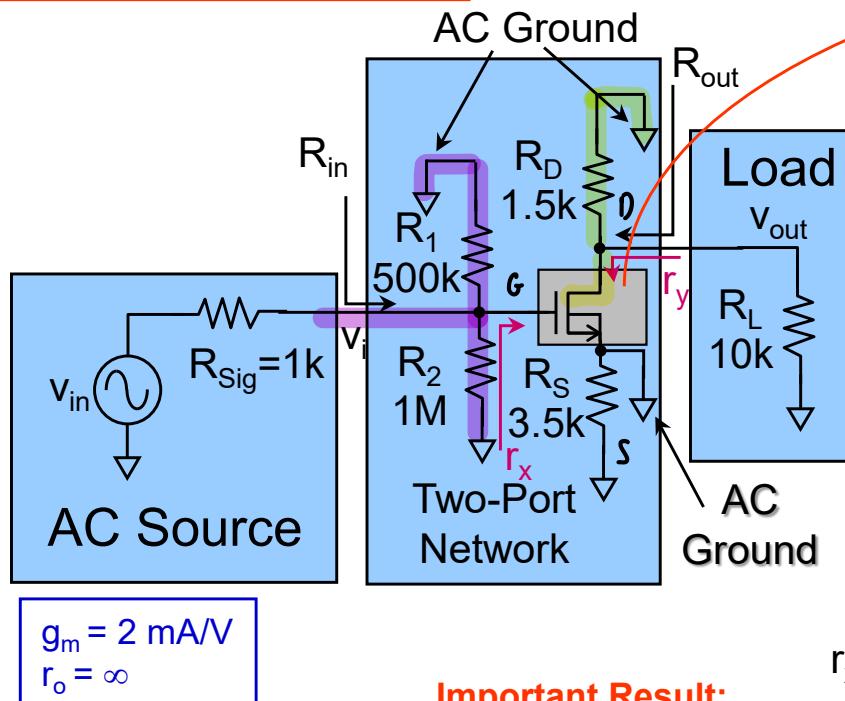Short cut AC treatment
for quicker analysis.



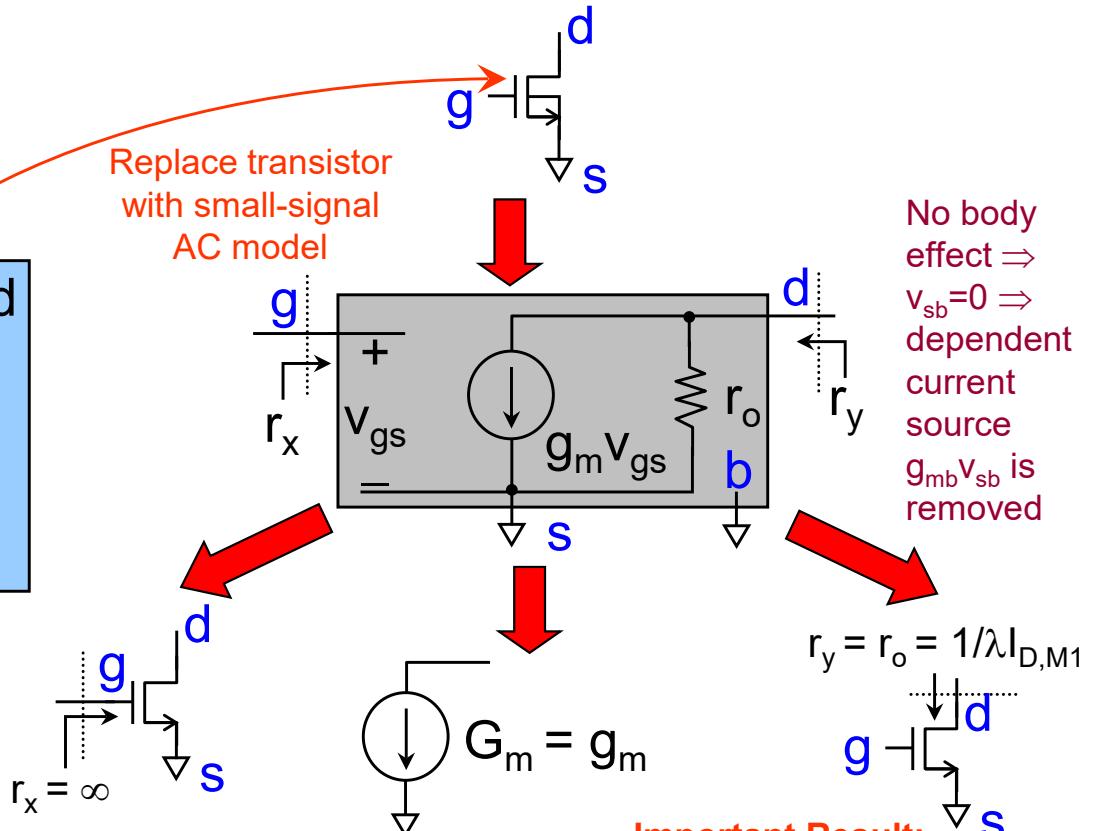Replace transistor
with small-signal
AC model



Important Result:
If you see a MOSFET connected in similar fashion, the equivalent resistance looking into the gate (r_x) is open circuit. No need to rederive. The resistance in the drain branch has no effect on r_x .

$$R_{in} = R_1 // R_2$$

CS

$$G_m = g_m$$

MOSFET g_m


Important Result:
If you see a MOSFET connected in similar fashion, the equivalent resistance looking into the drain (r_y) is directly given by r_o . No need to rederive. The resistance in the gate branch has no effect on r_y .

$$R_{out} = R_D // r_o$$

Two-Port Network (A_V) CS

$$g_m = 2 \text{ mA/V}$$

$$r_o = \infty$$

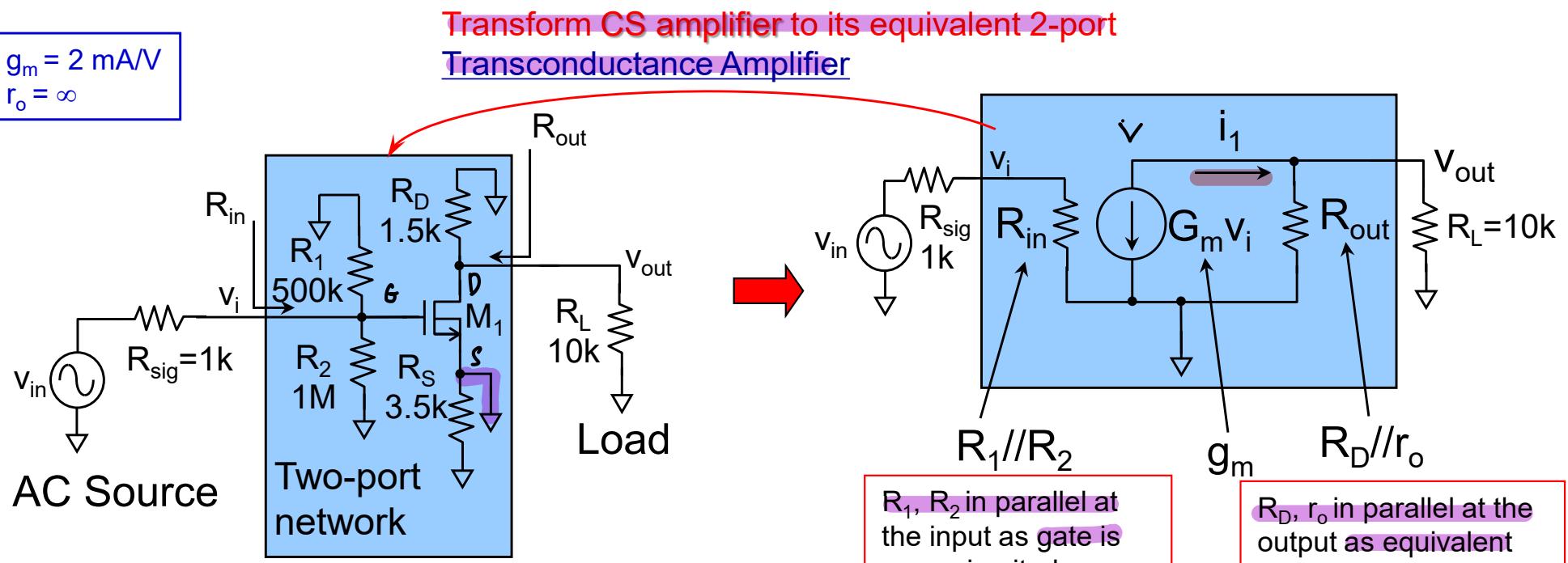

$$v_i = \frac{R_{in}}{R_{sig} + R_{in}} v_{in} = \frac{R_1 // R_2}{R_{sig} + R_1 // R_2} v_{in} \approx v_{in} \quad \therefore R_{sig} \ll R_1, R_2$$

$$i_1 = -g_m v_i \approx -g_m v_{in}$$

$$v_{out} = i_1 \times [R_{out} // R_L] = i_1 \times [(R_D // r_o) // R_L] = -g_m (R_D // r_o // R_L) v_{in}$$

$$\Rightarrow A_V = \frac{v_{out}}{v_{in}} = -g_m (R_D // r_o // R_L) = -2.61$$


Characteristics of CE/CS

- High input resistance
- High output resistance
- Medium gain
- Polarity inversion, i.e., v_{out} and v_{in} has opposite sign
if input +ve , output -ve and vice versa
- The higher the G_m and the total output resistance, the higher the gain (A_v)
- BJT provides larger g_m than MOS


$$g_m = \frac{I_C}{V_T} \quad g_m = 2 \sqrt{k_n I_D}$$

Common Gate (CG)
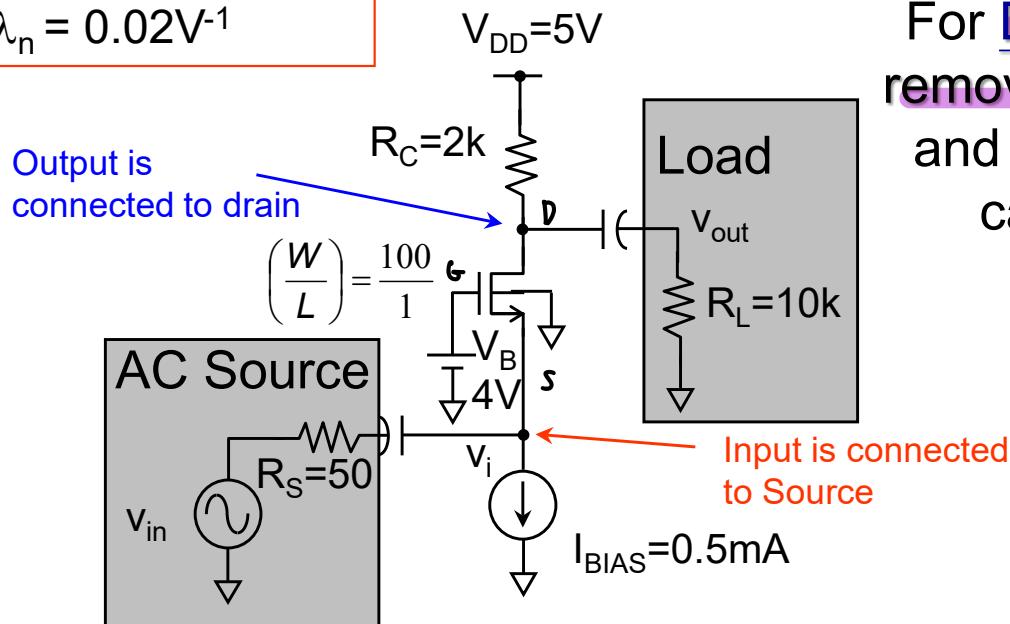
$$\begin{aligned}\mu_n C_{ox} &= 80 \mu\text{A/V}^2 \\ V_{THN} &= 0.7\text{V} \\ \lambda_n &= 0.02\text{V}^{-1}\end{aligned}$$



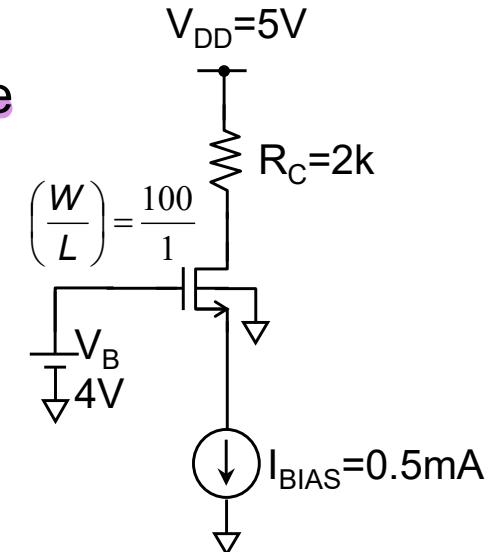
For DC analysis, remove AC source and open circuit capacitors



- Identify AC Source and Load
- To identify amplifier configuration, we need to consider AC equivalent circuit, i.e., short circuit capacitors
 - Input connected to Source, output connected to Drain, Gate connected to neither input nor output \Rightarrow Common Gate (CG)

DC Analysis for CG

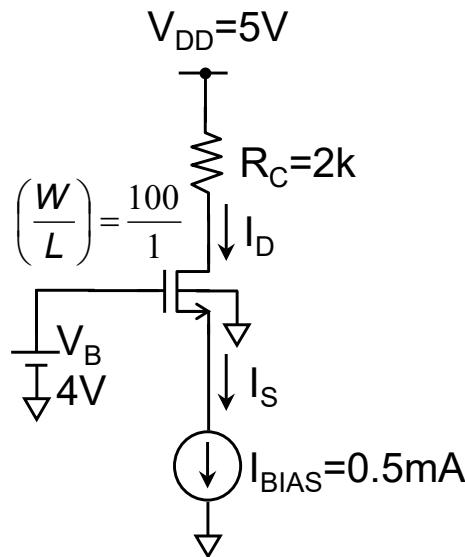- Remove AC source and open circuit capacitors when doing DC analysis



$$\begin{aligned}\mu_n C_{ox} &= 80 \mu\text{A}/\text{V}^2 \\ V_{THN} &= 0.7\text{V} \\ \lambda_n &= 0.02\text{V}^{-1}\end{aligned}$$

Determine DC biasing

$$I_D = I_S = I_{BIAS} = 0.5 \text{ mA}$$

$$\left(\frac{W}{L}\right) = \frac{100}{1}$$

Good approximation, no need to go through detailed calculations

Determine AC small-signal parameters

$$\begin{aligned}g_m &= \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D} \\ &= 2.83 \text{ mA/V}\end{aligned}$$

$$\begin{aligned}g_m &= \frac{2\sqrt{k_n I_D}}{\lambda_n} \\ &= \frac{2\sqrt{4 \times \frac{1}{2} \dots I_D}}{\lambda_n} \\ &= \sqrt{2\mu_n \dots I_D}\end{aligned}$$

MOSFET has body effect
(body not shorted to source)


$$g_{mb} \approx -\frac{g_m}{4} = -0.71 \text{ mA/V}$$

$$r_i = \infty$$

$$r_o = \frac{1}{\lambda_n I_D} = 100 \text{ k}\Omega$$


AC Analysis for CG

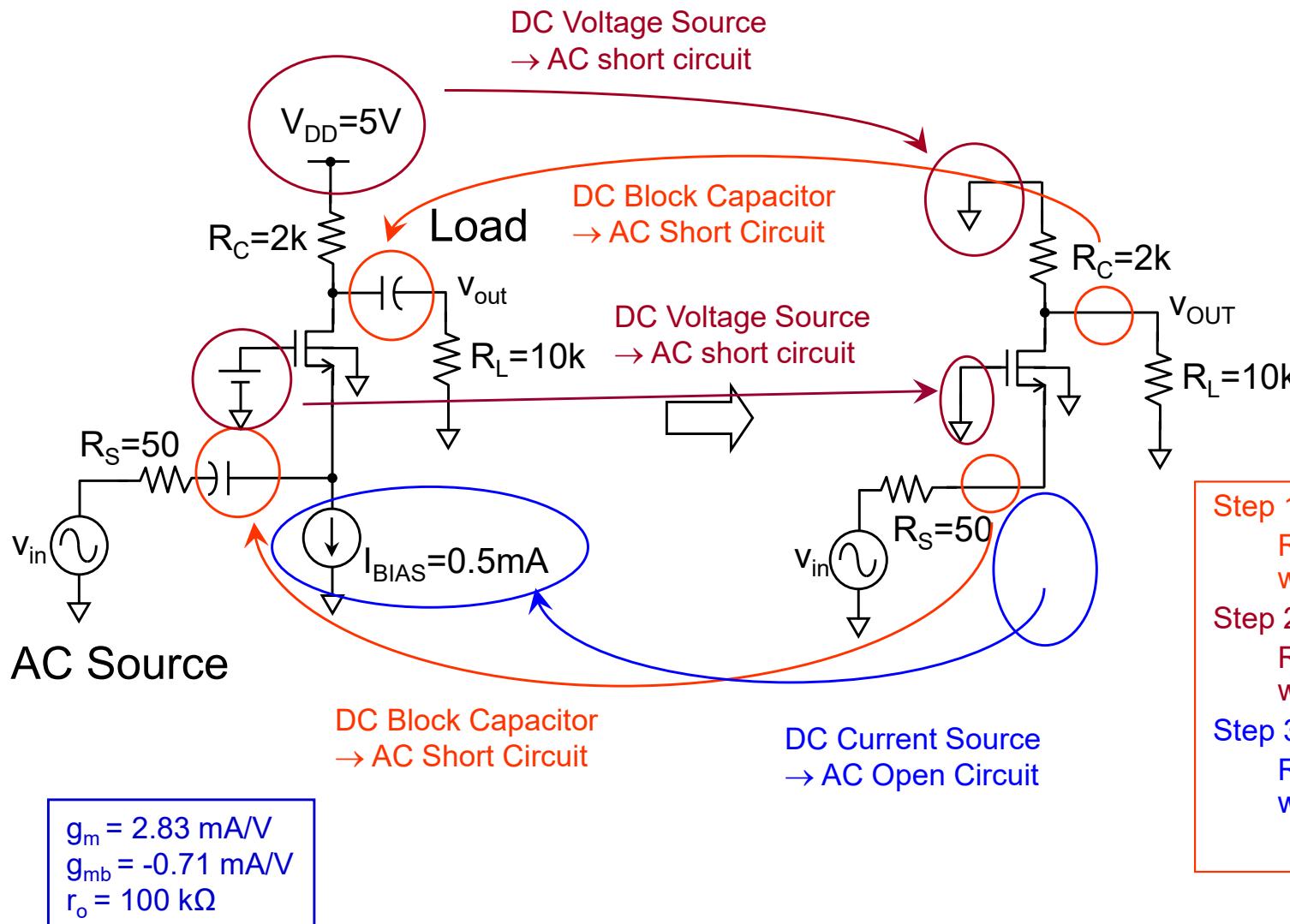For AC analysis, need to consider the AC equivalent circuit -



- Step 1 :
Replace DC block capacitor
with AC short circuit
- Step 2 :
Replace DC voltage source
with AC short circuit
- Step 3 :
Replace DC current source
with AC open circuit

AC Analysis for CG

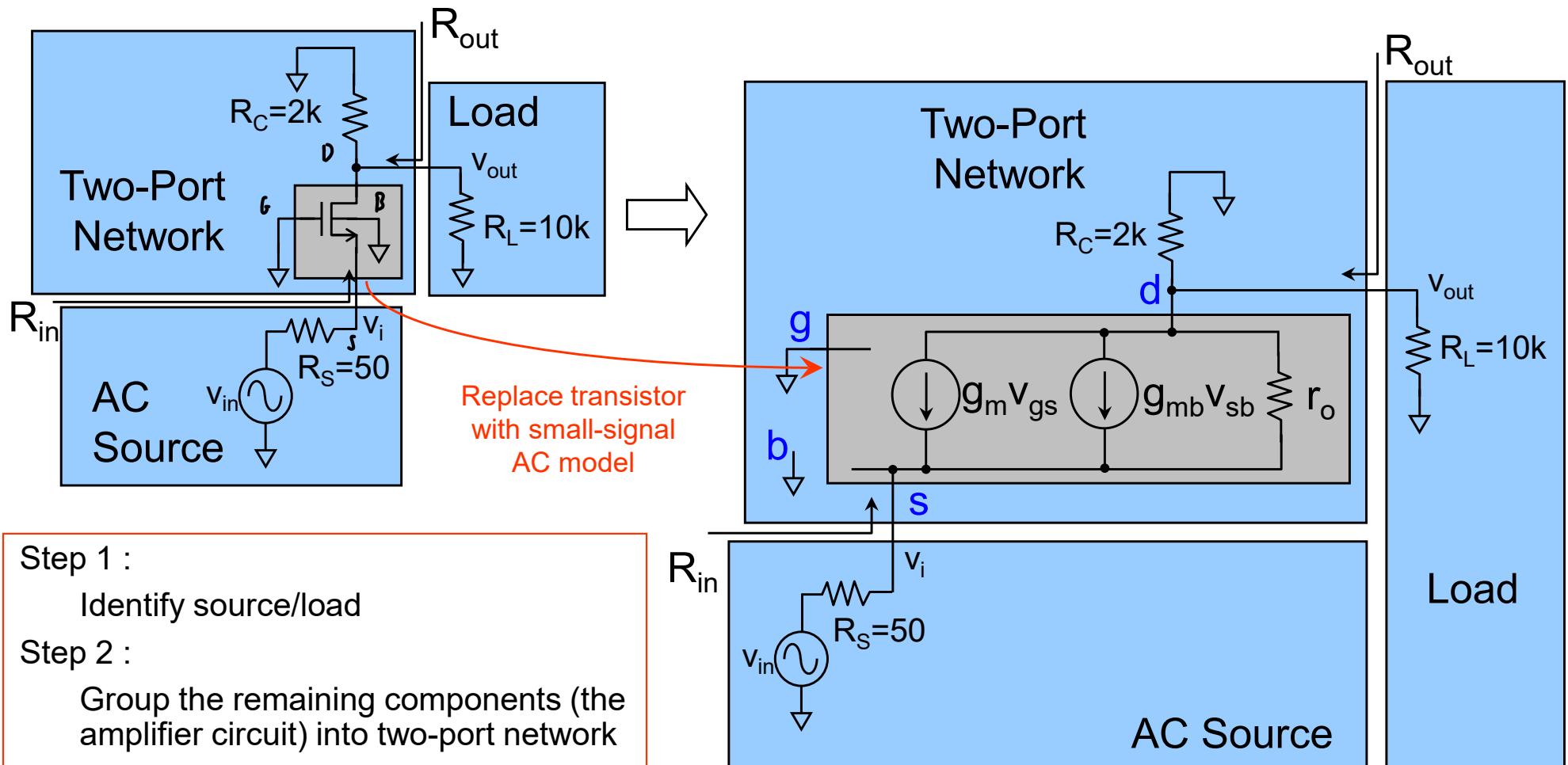

Step 1 :

Identify source/load

Step 2 :


Group the remaining components (the amplifier circuit) into two-port network

Step 3 :

Replace transistor with small-signal AC model

For CG amplifier, transform to 2-port Transconductance Amplifier (based on experience of circuit designers). Need to evaluate G_m , R_{in} and R_{out} .

CG – Two-Port Network (G_m)

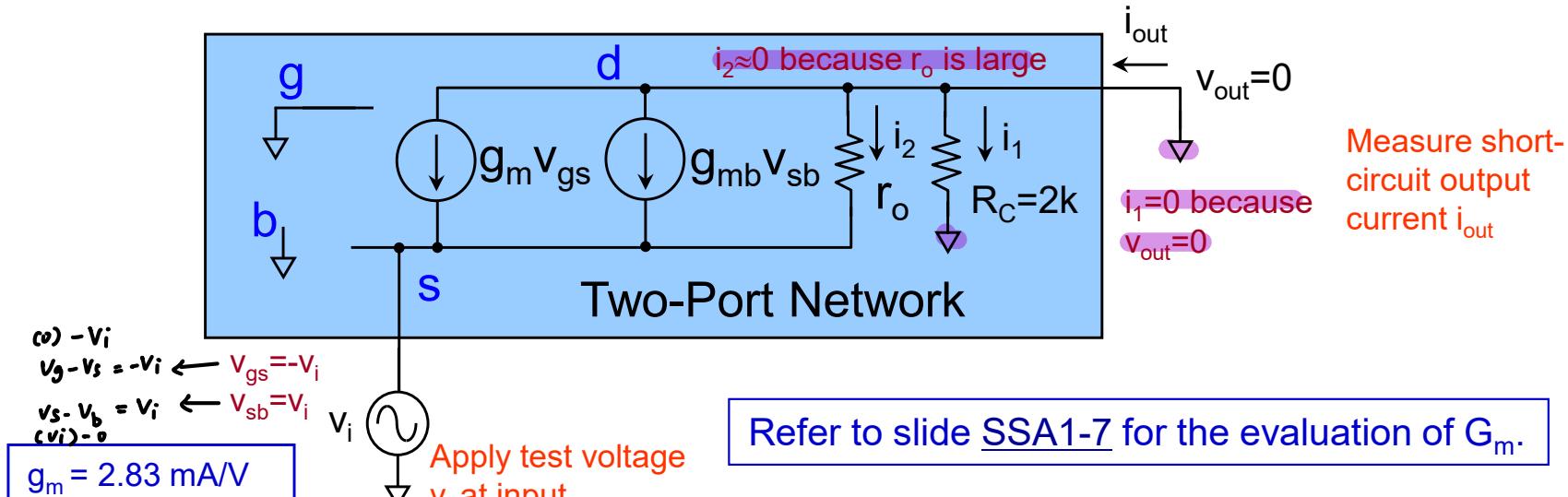

Refer to slide SSA1-7 for the evaluation of G_m .

$$i_{out} \Big|_{v_{out}=0} = g_m V_{gs} + g_{mb} V_{sb} + i_2 \approx -(g_m - g_{mb}) V_i$$

$$G_m = \frac{i_{out}}{V_i} \Big|_{v_{out}=0} \approx -(g_m - g_{mb})$$


Important Result :

Transconductance (G_m)
for CG is just $-(g_m - g_{mb})$

→ if there is no body
effect, (body shorted to source)
result is just $-g_m$.

CG – Two-Port Network (R_{in})

KCL

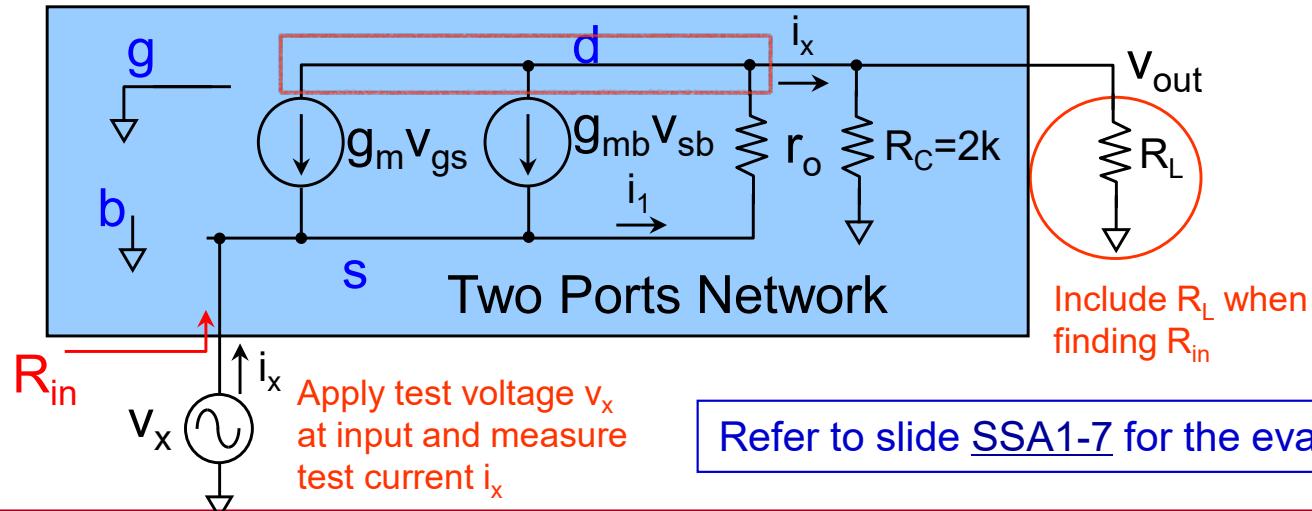

$R_{in} = \frac{v_x}{i_x}$ By KCL

$$\left\{ \begin{array}{l} i_x = -g_m v_{gs} - g_{mb} v_{sb} + i_1 \\ \qquad \qquad \qquad \text{Eliminate } v_{out} \text{ and keep } v_x \text{ and } i_x \\ = (g_m - g_{mb}) v_x + \frac{v_x - v_{out}}{r_o} \\ v_{out} = i_x (R_C // R_L) \end{array} \right.$$


$$\Rightarrow i_x = (g_m - g_{mb}) v_x + \frac{v_x}{r_o} - i_x \frac{(R_C // R_L)}{r_o}$$

$$\Rightarrow R_{in} = \frac{1 + \frac{(R_C // R_L)}{r_o}}{(g_m - g_{mb}) + \frac{1}{r_o}}$$

$$\approx \frac{1}{g_m - g_{mb}} \cdot \frac{r_o + (R_C // R_L)}{r_o}$$

$g_m - g_{mb} > 1/r_o$

CG – Two-Port Network (R_{in})

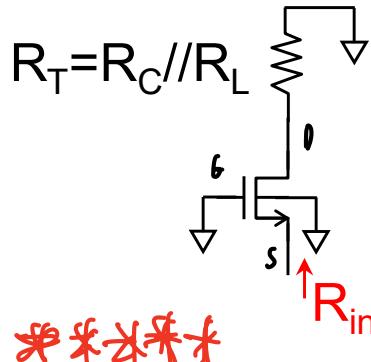

* * * *

$$R_T = R_C // R_L$$
$$R_{in} \approx \frac{1}{g_m - g_{mb}} \cdot \frac{r_o + R_T}{r_o}$$
$$\approx \frac{1}{g_m - g_{mb}} \quad [If \quad R_T \ll r_o]$$

Important Result:

If you see a MOSFET connected in similar fashion, the equivalent resistance looking into the source (R_{in}) is directly given by the formula. No need to rederive.


Example :

$$R_C = 2k \quad R_L = 10k \quad r_o = 100k$$
$$\Rightarrow R_T = (R_C // R_L) \ll r_o$$
$$\Rightarrow R_{in} = \frac{1}{g_m - g_{mb}} = 282$$

- If $R_C//R_L$ is negligible compared to r_o , the input resistance (R_{in}) is reduced to the inverse of the transconductance $[1/(g_m - g_{mb})]$

CG – Two-Port Network (R_{out})

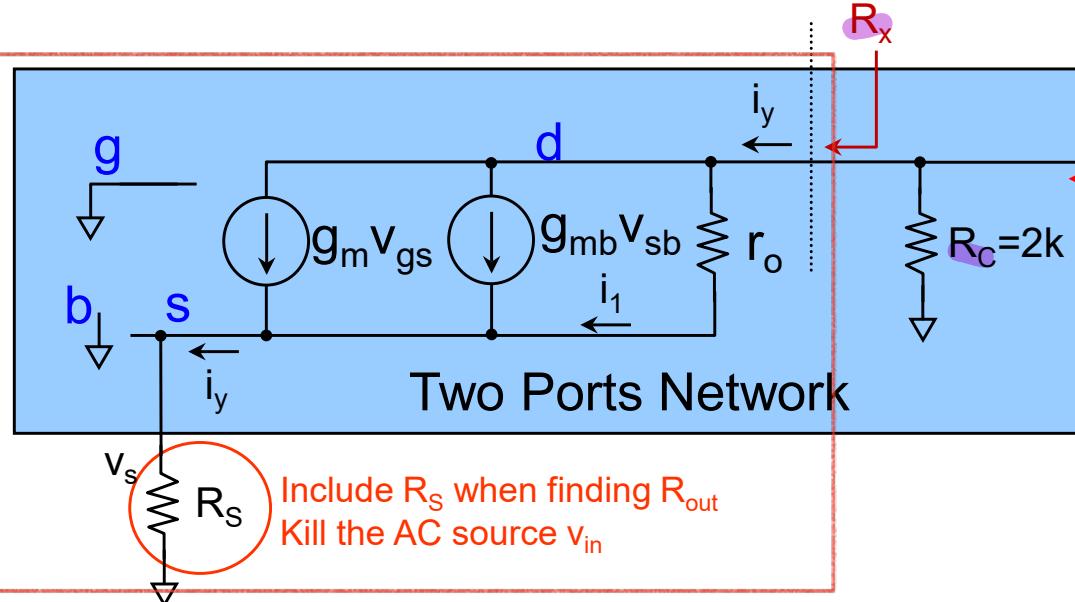Refer to slide SSA1-7 for the evaluation of R_{out} .



Apply test voltage v_x at output
and measure test current i_x

$$\begin{aligned}v_{gs} &= -v_s \quad v_{sb} = v_s \\i_1 &= i_y - g_m v_{gs} - g_{mb} v_{sb} \\&= i_y + (g_m - g_{mb}) v_s\end{aligned}$$

R_{out} is just parallel combination of R_C and R_x

$$R_S \ll r_o [1 + (g_m - g_{mb}) R_S]$$

$$R_{out} = R_C // R_x$$

Eliminate v_s and keep v_x and i_y


$$\Rightarrow v_x = i_y R_S + i_y r_o + i_y (g_m - g_{mb}) R_S r_o$$

$$\Rightarrow R_x = \frac{v_x}{i_y} = R_S + r_o [1 + (g_m - g_{mb}) R_S]$$

Here only can bcos $R_C \ll R_x$
($r_o \approx 100k$)

$$\begin{aligned}R_{out} &= R_C // R_x \\&\approx R_C // \{r_o [1 + (g_m - g_{mb}) R_S]\} \approx R_C\end{aligned}$$

CG – Two-Port Network (R_{out})

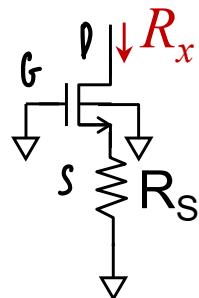

$$R_x \approx r_o [1 + (g_m - g_{mb}) R_S]$$

Important Result: * * * * *

If you see a MOSFET connected in similar fashion, the equivalent resistance looking into the drain (R_x) is directly given by the formula. No need to rederive.

Example :

$$R_S = 50 \quad r_o = 100k$$

$$g_m = 2.83m \quad g_{mb} = -0.71m$$

$$\Rightarrow R_x \approx 118k \gg R_C$$

$$\Rightarrow R_{out} \approx R_C = 2k$$

- Source side resistor helps boost up the output resistance of the transistor (R_x)

CG – Important Results




1

Important Result :


Transconductance (G_m)
for CG is just $-(g_m - g_{mb})$

2

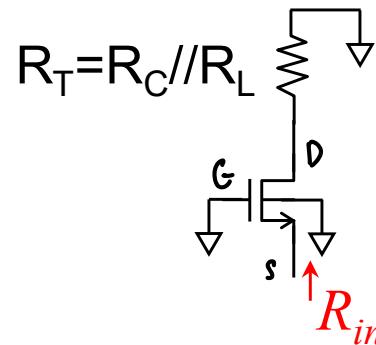


$$R_{in} \approx \frac{1}{g_m - g_{mb}} \cdot \frac{r_o + R_T}{r_o}$$
$$\approx \frac{1}{g_m - g_{mb}} \quad [If \quad R_T \ll r_o]$$

3

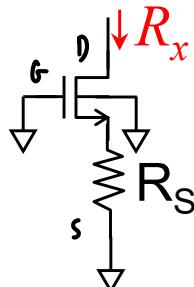


$$R_x \approx r_o [1 + (g_m - g_{mb}) R_S]$$

CG – Two-Port Network

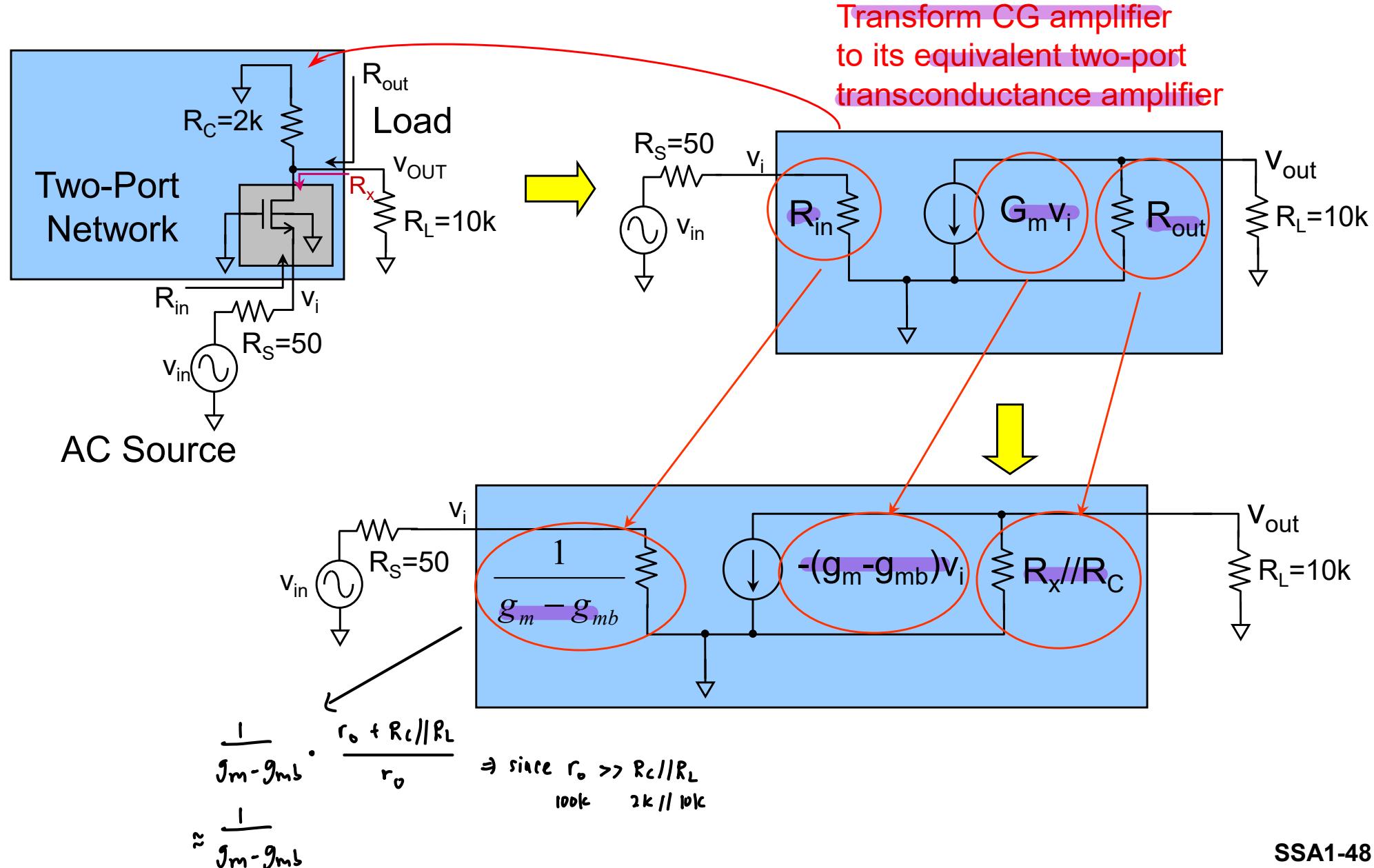

CG - Two-Port Network (A_V)
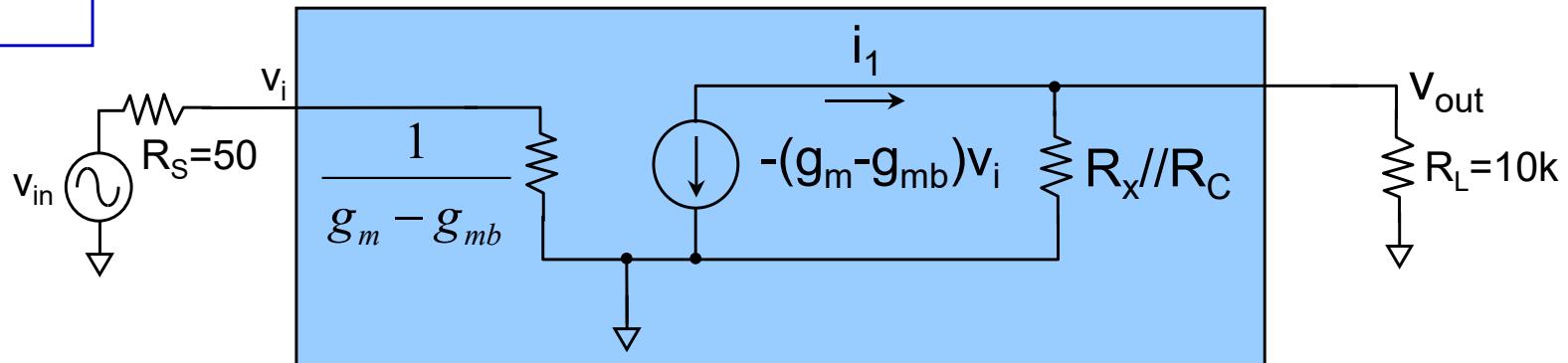
$$\begin{aligned} g_m &= 2.83 \text{ mA/V} \\ g_{mb} &= -0.71 \text{ mA/V} \\ r_o &= 100 \text{ k}\Omega \end{aligned}$$




$$v_i = v_{in} \times \frac{R_{in}}{R_S + R_{in}}$$

$$R_{in} = \frac{1}{g_m - g_{mb}}$$



$$\begin{aligned} i_1 &= -[-(g_m - g_{mb})v_i] \\ &= (g_m - g_{mb})v_i \end{aligned}$$

$$\begin{aligned} v_{out} &= i_1 \times \left[\left(\cancel{R_x} // R_C \right) // R_L \right] \\ &\approx (g_m - g_{mb}) \times v_i \times (R_C // R_L) \\ &\approx (g_m - g_{mb}) \times \left(v_{in} \times \frac{R_{in}}{R_S + R_{in}} \right) \times (R_C // R_L) \\ \Rightarrow A_V &= \frac{v_{out}}{v_{in}} = \frac{R_{in}}{R_S + R_{in}} (g_m - g_{mb})(R_C // R_L) \\ &= 5.01 \end{aligned}$$

Common Base (CB) Amplifier

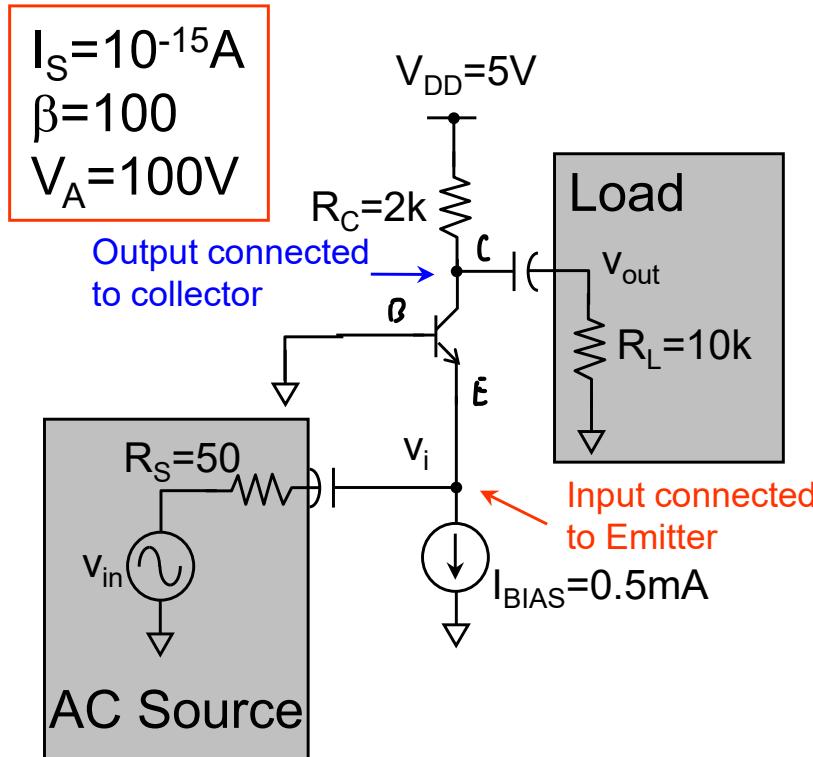

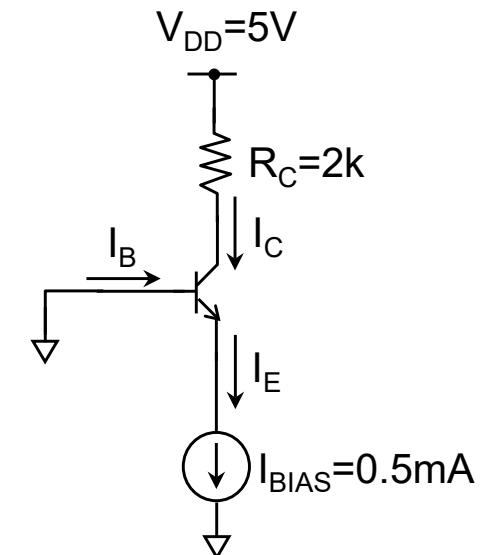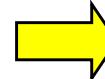
For DC analysis,
remove AC source
and open circuit
capacitors



- Identify AC Source and Load
- To identify amplifier configuration, we need to consider AC equivalent circuit, i.e., short circuit capacitors
 - Input connected to Emitter, output connected to Collector, Base connected to neither input nor output \Rightarrow Common Base (CB)

DC Analysis for CB

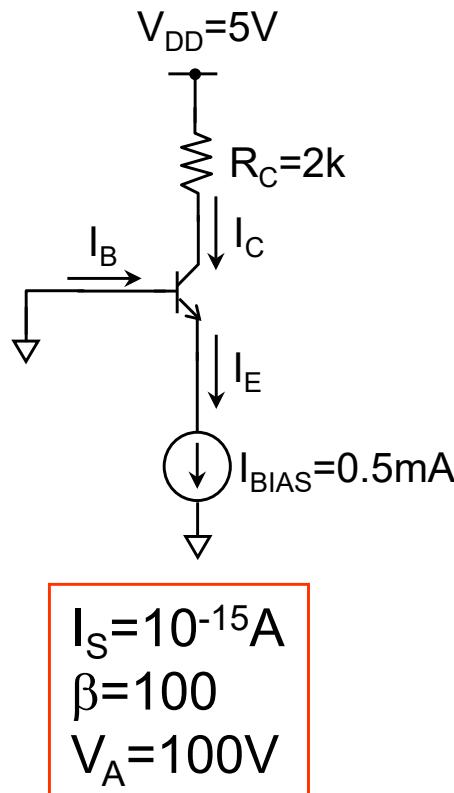- Remove AC source and open circuit capacitors when doing DC analysis



Determine DC biasing


$$V_T = \frac{kT}{q} = 26\text{ mV}$$
$$I_E = I_{BIAS} = 0.5\text{ mA}$$
$$I_C = \frac{\beta}{\beta+1} I_E = 0.495\text{ mA}$$
$$I_B = \frac{I_C}{\beta} = 4.95\text{ }\mu\text{A}$$

Determine AC small-signal parameters

$$g_m = \frac{I_C}{V_T} = 19\text{ mA/V}$$
$$r_\pi = \frac{\beta}{g_m} = 5.26\text{ k}\Omega$$
$$r_o = \frac{V_A}{I_C} = 202\text{ k}\Omega$$

AC Analysis for CB (Self Reading)

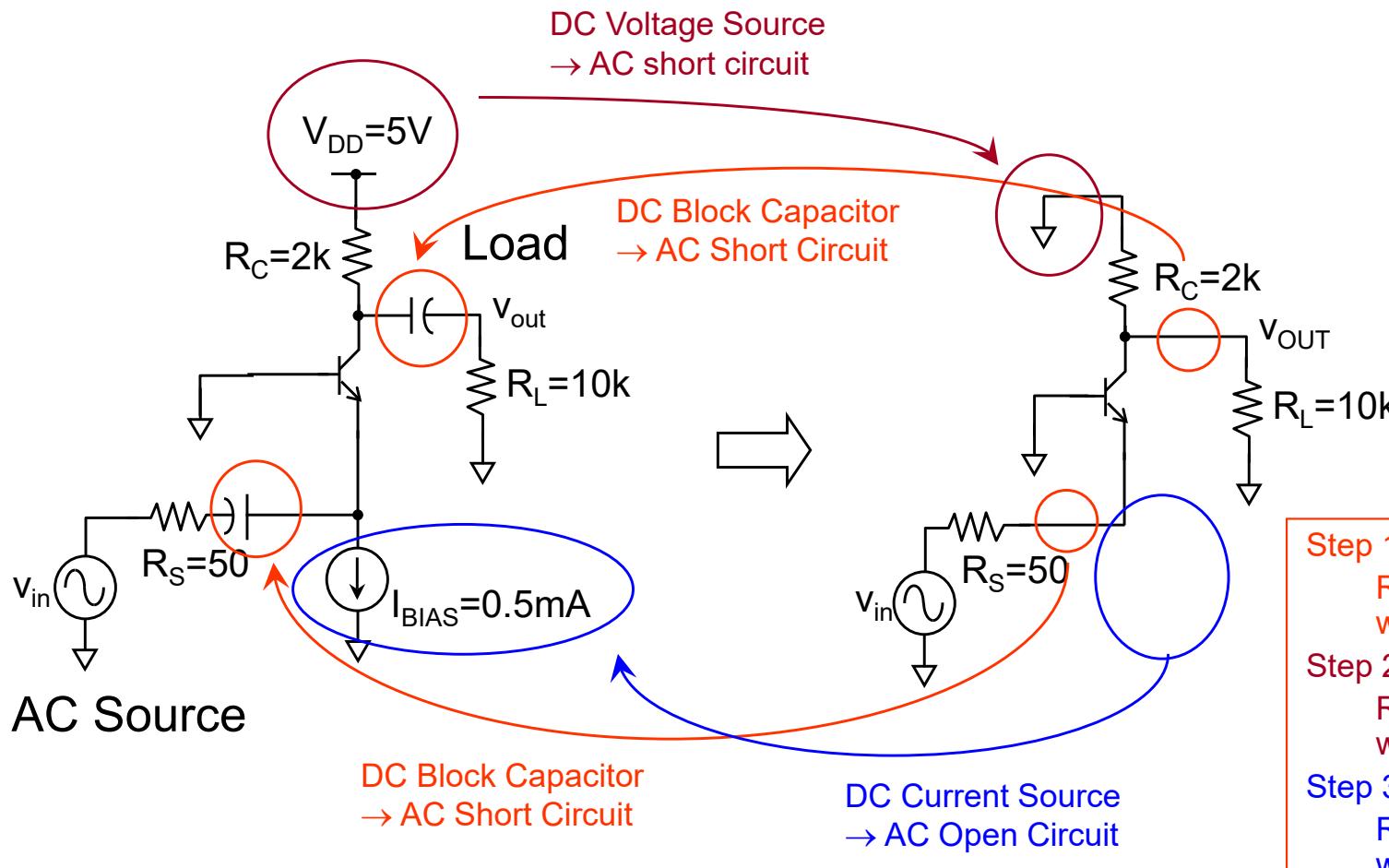
For AC analysis, need to consider the AC equivalent circuit -



- Step 1 : Replace DC block capacitor with AC short circuit
- Step 2 : Replace DC voltage source with AC short circuit
- Step 3 : Replace DC current source with AC open circuit


Continue the analysis with AC equivalent circuit on the right.

AC Analysis for CB (Self Reading)

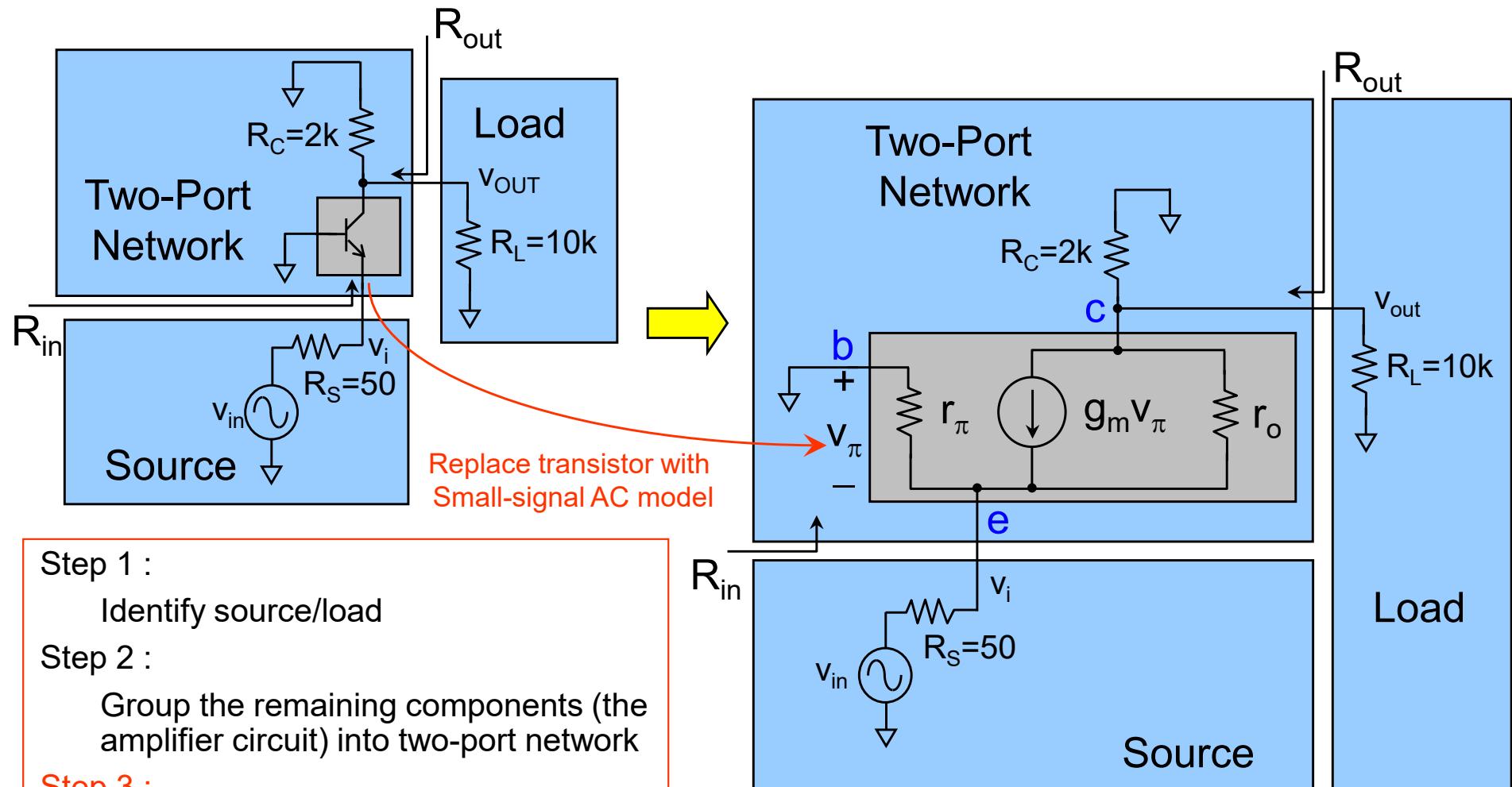

For CB amplifier, transform to 2-port Transconductance Amplifier (based on experience of circuit designers). Need to evaluate G_m , R_{in} and R_{out} .

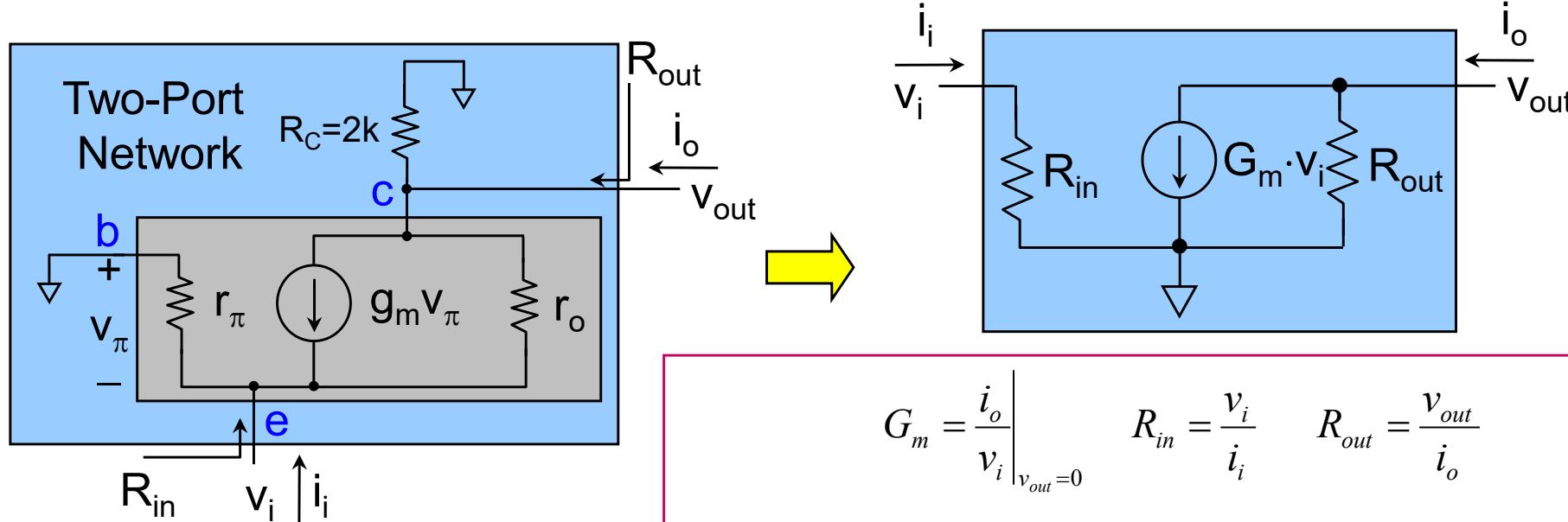Mapping Two-Port Network for CB (Self Reading)




$$G_m = \left. \frac{i_o}{v_i} \right|_{v_{out}=0} \quad R_{in} = \frac{v_i}{i_i} \quad R_{out} = \frac{v_{out}}{i_o}$$

Refer to slide SSA1-7 for evaluation of 2-port parameters: G_m , R_{in} , R_{out} .


- Similar concept as Thevenin equivalent.
- Complicated two-port network can be represented by a two-port network characterized by only 3 parameters: R_{in} , R_{out} and G_m .

CB – Finding G_m (Self Reading)

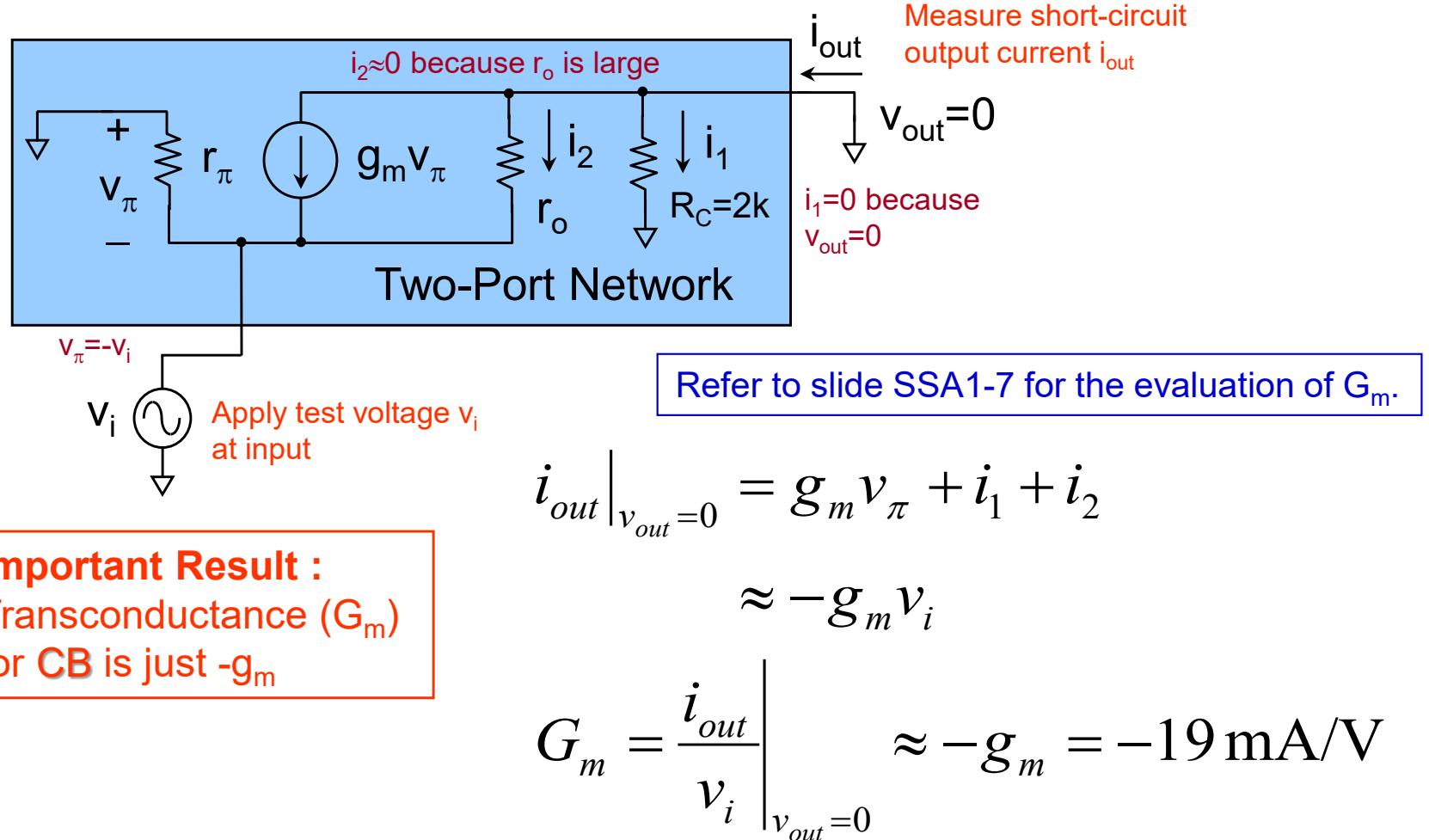

CB – Finding R_{in} (Self Reading)

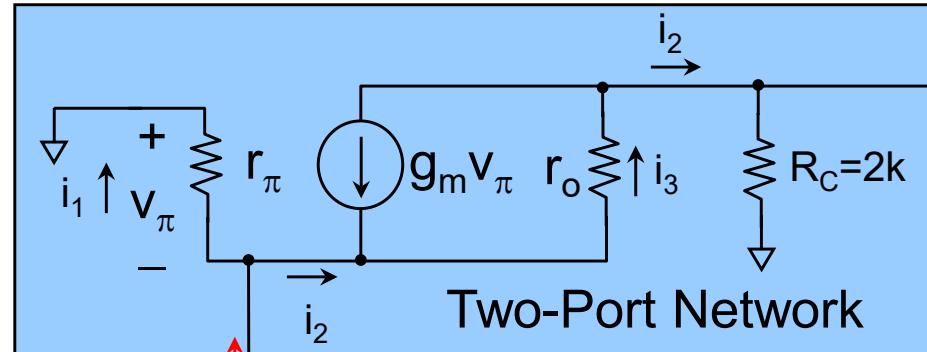Refer to slide SSA1-7 for the evaluation of R_{in} .



R_{in}

Apply test voltage v_x at input and measure test current i_x

v_{π}

i_1

i_2

i_3

R_L

Include R_L when finding R_{in}

$$v_{\pi} = -v_x \quad i_1 = \frac{v_x}{r_{\pi}} \quad i_3 = \frac{v_x - v_{out}}{r_o}$$

$$i_2 = i_x - i_1 = i_x - \frac{v_x}{r_{\pi}}$$

KCL

$$R_{in} = \frac{v_x}{i_x} \quad \left\{ \begin{array}{l} i_x = i_1 - g_m v_{\pi} + i_3 = \frac{v_x}{r_{\pi}} + g_m v_x + \frac{v_x - v_{out}}{r_o} \\ v_{out} = i_2 (R_C // R_L) = \left(i_x - \frac{v_x}{r_{\pi}} \right) (R_C // R_L) \end{array} \right.$$

$$\Rightarrow i_x = \frac{v_x}{r_{\pi}} + g_m v_x + \frac{v_x}{r_o} - i_x \frac{(R_C // R_L)}{r_o} + \frac{v_x (R_C // R_L)}{r_{\pi} r_o}$$


Eliminate v_{out} and keep v_x and i_x

$g_m >> 1/r_{\pi}$ and $1/r_o$

$$\Rightarrow R_{in} = \frac{1 + \frac{(R_C // R_L)}{r_o}}{g_m + \frac{1}{r_{\pi}} + \frac{1}{r_o} + \frac{(R_C // R_L)}{r_{\pi} r_o}}$$

$$\approx \frac{1}{g_m} \cdot \frac{r_o + (R_C // R_L)}{r_o + \frac{(R_C // R_L)}{\beta}}$$

CB – Finding R_{in} (Self Reading)
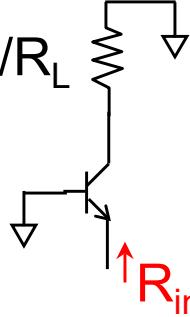
$$R_T = R_C // R_L$$

$$R_{in} \approx \frac{1}{g_m} \cdot \frac{r_o + R_T}{r_o + \frac{R_T}{\beta}}$$
$$\approx \frac{1}{g_m} \quad [If \quad R_T \ll r_o]$$

Example :

$$R_C = 2k \quad R_L = 10k \quad r_o = 202k$$

$$\Rightarrow R_T = (R_C // R_L) \ll r_o$$

$$\Rightarrow R_{in} = \frac{1}{g_m} = 53$$


Important Result:

If you see a BJT connected in similar fashion, the **equivalent resistance** looking into the **emitter** (R_{in}) is directly given by the formula. **No need to rederive.**

- If $R_C//R_L$ is negligible compared to r_o , the input resistance (R_{in}) reduced to the inverse of the transconductance ($1/g_m$)

CB – Finding R_{out} (Self Reading)

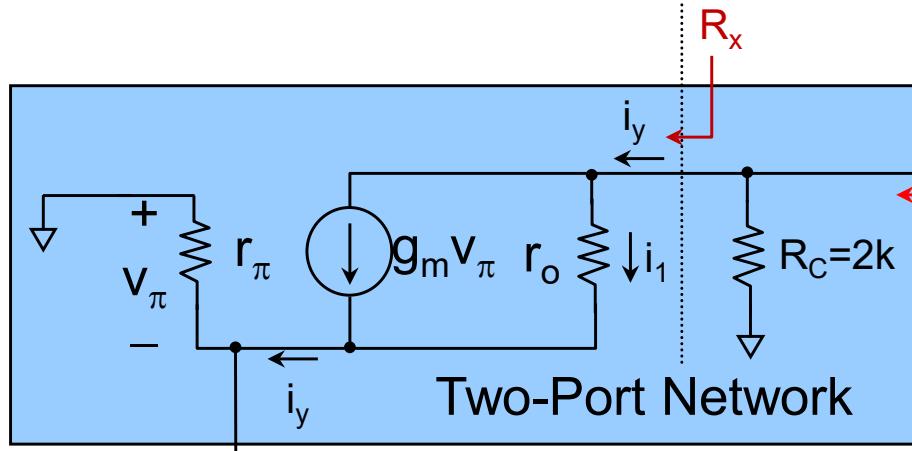Refer to slide SSA1-7 for the evaluation of R_{out} .



Apply test voltage v_x at output and measure test current i_x

$$v_\pi = -v_s$$

$$i_1 = i_y - g_m v_\pi = i_y + g_m v_s$$

R_{out} is just parallel combination of R_C and R_x

Include R_S when finding R_{out}
Kill the AC source v_{in}

$$R_{out} = R_C // R_x$$

$$R_x = \frac{v_x}{i_y}$$

Eliminate v_s and keep v_x and i_y

$$\begin{cases} v_s = i_y (r_\pi // R_S) \\ v_x = v_s + i_1 r_o = v_s + (i_y + g_m v_s) r_o \end{cases}$$

$$r_\pi // R_S \ll r_o [1 + g_m (r_\pi // R_S)]$$


$$\Rightarrow v_x = i_y (r_\pi // R_S) + i_y r_o + i_y g_m (r_\pi // R_S) r_o$$

$$\Rightarrow R_x = \frac{v_x}{i_y} = (r_\pi // R_S) + r_o [1 + g_m (r_\pi // R_S)]$$

$$R_{out} = R_C // R_x$$


$$\approx R_C // \{r_o [1 + g_m (r_\pi // R_S)]\} \approx R_C$$

Equivalent Resistance (Self Reading)

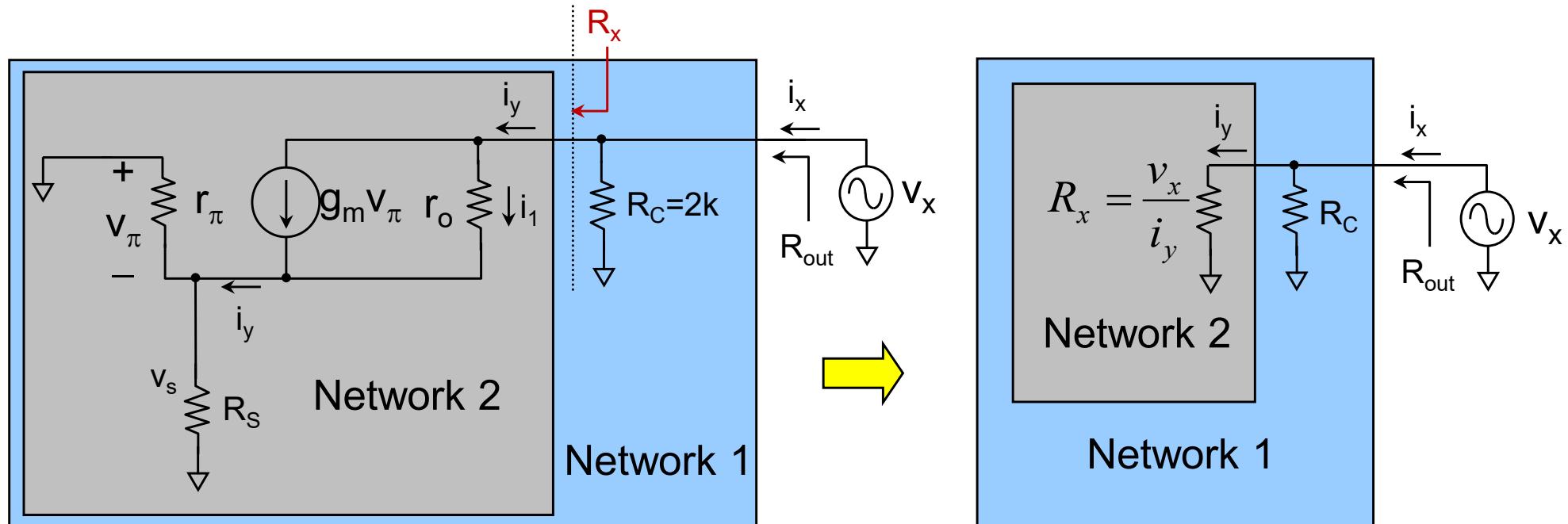

- A complicated linear network (gray box) can be replaced by an equivalent resistance, R_x

CB – Finding R_{out} (Self Reading)

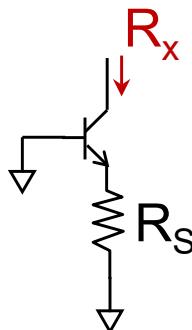

$$R_x \approx r_o [1 + g_m (r_\pi // R_S)]$$

$$\text{If } R_S \ll r_\pi \Rightarrow R_x = r_o (1 + g_m R_S)$$

$$\begin{aligned} \text{If } R_S \gg r_\pi \Rightarrow R_x &= r_o (1 + g_m r_\pi) \\ &= r_o (1 + \beta) \end{aligned}$$

Important Result:

If you see a BJT connected in similar fashion, the **equivalent resistance** looking into the **collector** (R_x) is directly given by the formula. **No need to rederive.**

Example :

$$R_S = 50 \quad r_\pi = 5.26k$$

$$r_o = 202k \quad g_m = 19m$$

$$\Rightarrow R_x \approx 394k \gg R_C$$

$$\Rightarrow R_{out} \approx R_C = 2k$$

- Emitter side resistor helps boost up the output resistance of the transistor (R_x)
- For BJT, the maximum achievable boost up is $(1+\beta)r_o$


CB - Important Results



1

Important Result :
Transconductance (G_m)
for CB is just $-g_m$


2

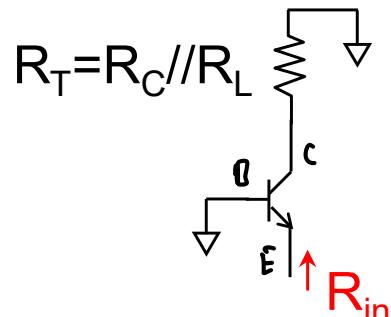

$$R_{in} \approx \frac{1}{g_m} \cdot \frac{r_o + R_T}{r_o + \frac{R_T}{\beta}}$$

$$\approx \frac{1}{g_m} \quad [If \quad R_T \ll r_o]$$

3

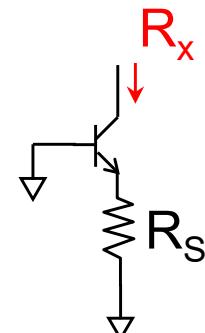


$$R_x \approx r_o [1 + g_m (r_\pi // R_S)] \quad \text{use this}$$

$$If \quad R_S \ll r_\pi \Rightarrow R_x = r_o (1 + g_m R_S)$$


$$If \quad R_S \gg r_\pi \Rightarrow R_x = r_o (1 + g_m r_\pi) \\ = r_o (1 + \beta)$$

CB - Two-Port Network

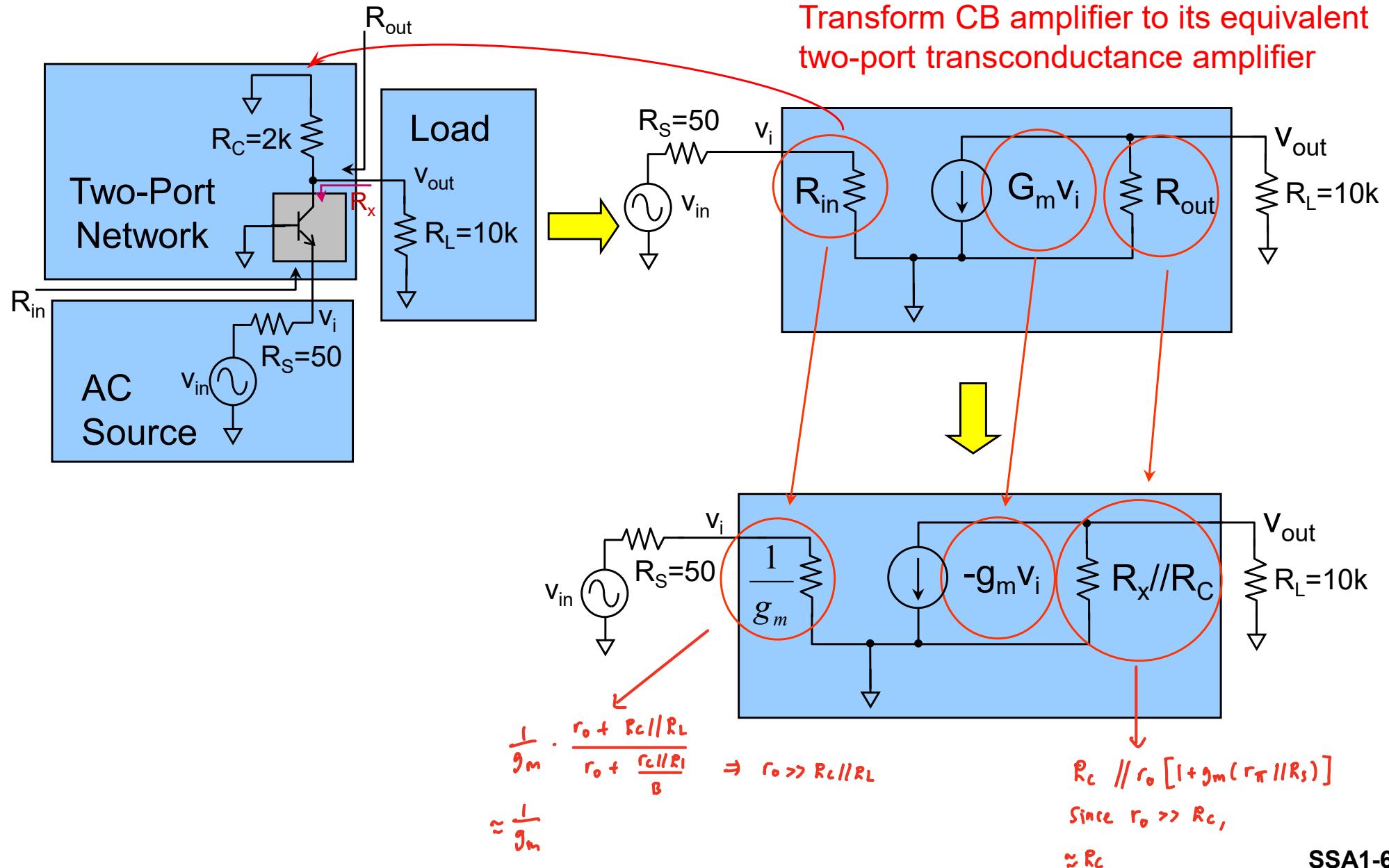

CB – Two-Port Network (A_V)
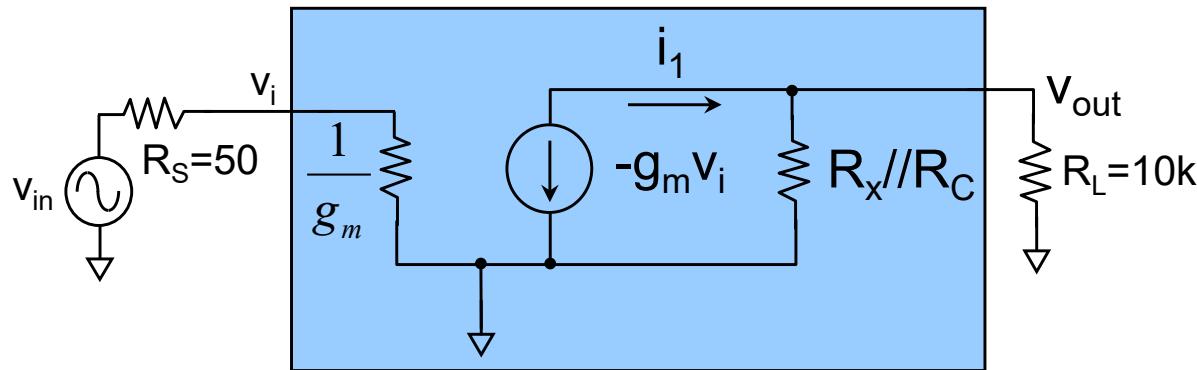
$$\begin{aligned} g_m &= 19 \text{ mA/V} \\ r_\pi &= 5.26 \text{ k}\Omega \\ r_o &= 202 \text{ k}\Omega \end{aligned}$$



$$v_i = v_{in} \times \frac{R_{in}}{R_S + R_{in}}$$

$$R_{in} = \frac{1}{g_m}$$

$$i_1 = -(-g_m v_i) = g_m v_i$$

$$\begin{aligned} v_{out} &= i_1 \times [(R_x // R_C) // R_L] \\ &= g_m \times v_i \times [(R_x // R_C) // R_L] \\ &\approx g_m \times \left(v_{in} \times \frac{R_{in}}{R_S + R_{in}} \right) \times (R_C // R_L) \\ \Rightarrow A_V &= \frac{v_{out}}{v_{in}} \approx \frac{R_{in}}{R_S + R_{in}} g_m (R_C // R_L) = 16.3 \end{aligned}$$

R_x is too big

Characteristics of CB/CG

- Low input resistance
- High output resistance
- Medium gain
- No polarity inversion
- The higher the G_m and the total output resistance, the higher the gain (A_v)
- BJT provides larger g_m than MOS ($g_m - g_{mb}$)