

EE2027 Electronic Circuits


Single-Stage Amplifier

Lecture Outline


- **Single-Stage Amplifiers**
CC/CD, CE/CS with degeneration
- **Effect of Capacitors**
Frequency response
- **Current Source**
Current mirror
- **Multi-Stage Amplifier Analysis Concept**

Common Drain (CD)
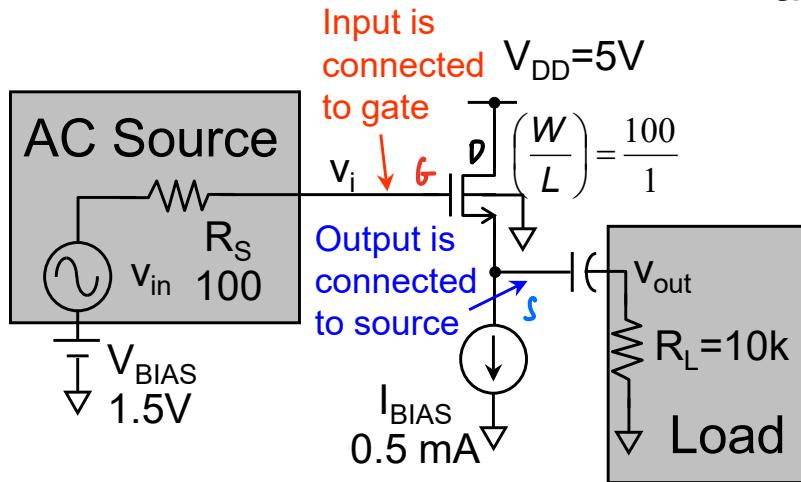
$$\begin{aligned}\mu_n C_{ox} &= 80 \mu\text{A/V}^2 \\ V_{THN} &= 0.7\text{V} \\ \lambda_n &= 0.02\text{V}^{-1}\end{aligned}$$



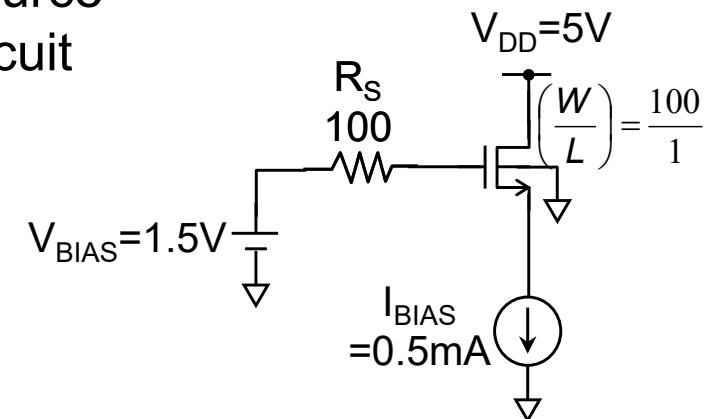
For DC analysis,
remove AC source
and open circuit
capacitor



- Identify AC Source and Load
- To identify amplifier configuration, we need to consider AC equivalent circuit, i.e., short circuit capacitors
 - Input connected to Gate, output connected to Source, Drain connected to neither input nor output \Rightarrow Common Drain (CD)

DC Analysis - CD

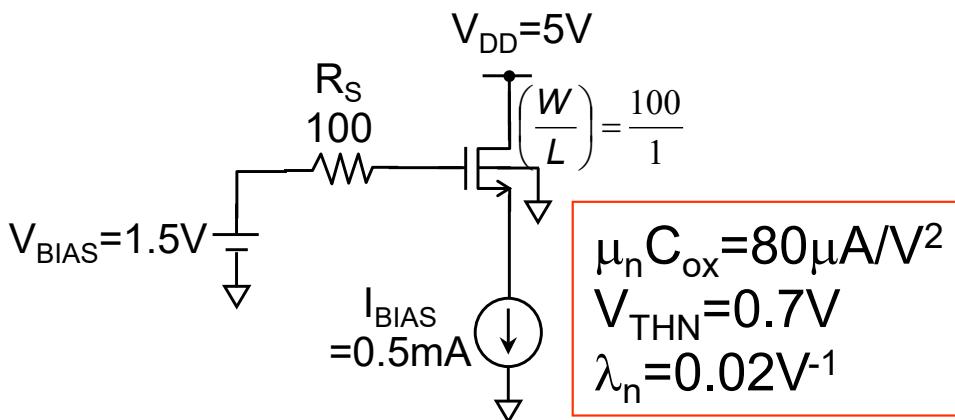- Remove AC source and open circuit capacitor when doing DC analysis



Determine DC biasing

$$I_D = I_S = I_{BIAS} = 0.5 \text{ mA}$$

Good approximation, no need to go through detailed calculations

Determine AC small-signal parameters

$$\left(\frac{W}{L}\right) = \frac{100}{1}$$

$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D} = 2.83 \text{ mA/V}$$

MOSFET has body effect

(body not shorted to source)



$$g_{mb} \approx -\frac{g_m}{4} = -0.71 \text{ mA/V}$$

$$r_i = \infty$$

$$r_o = \frac{1}{\lambda_n I_D} = 100 \text{ k}\Omega$$

AC Analysis - CD

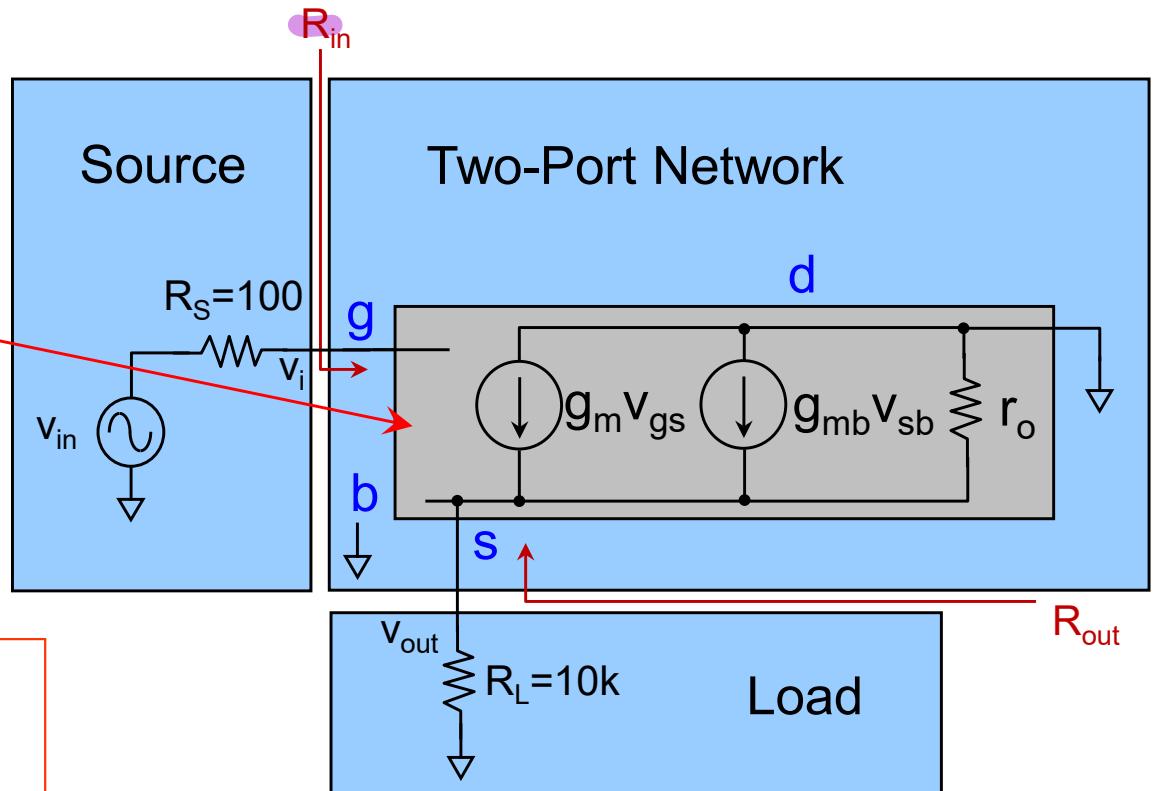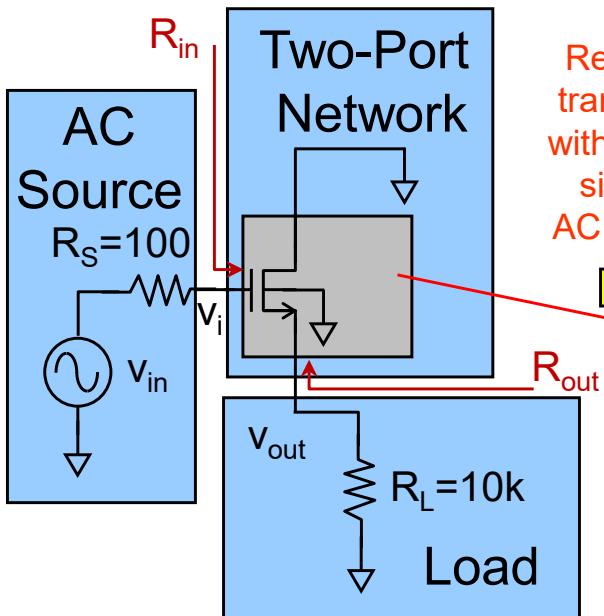For AC analysis, need to consider the AC equivalent circuit (i.e., short circuit capacitor, replace DC voltage source by short circuit and replace DC current source by open circuit).



Step 1 :

Identify AC source and load

Step 2 :

Group the remaining components (the amplifier circuit) into two-port network

Step 3 :

Replace transistor with small-signal model

For CD amplifier, transform to 2-port Voltage Amplifier (based on experience of circuit designers). Need to evaluate R_{in} , R_{out} and A .


$$R_{in} = \infty$$

CD – Two-Port Network (R_{out})

$$\begin{aligned} g_m &= 2.8 \text{ mA/V} \\ g_{mb} &= -0.71 \text{ mA/V} \\ r_o &= 100 \text{ k}\Omega \end{aligned}$$

Include R_s when finding R_{out}
Kill the AC source v_{in}

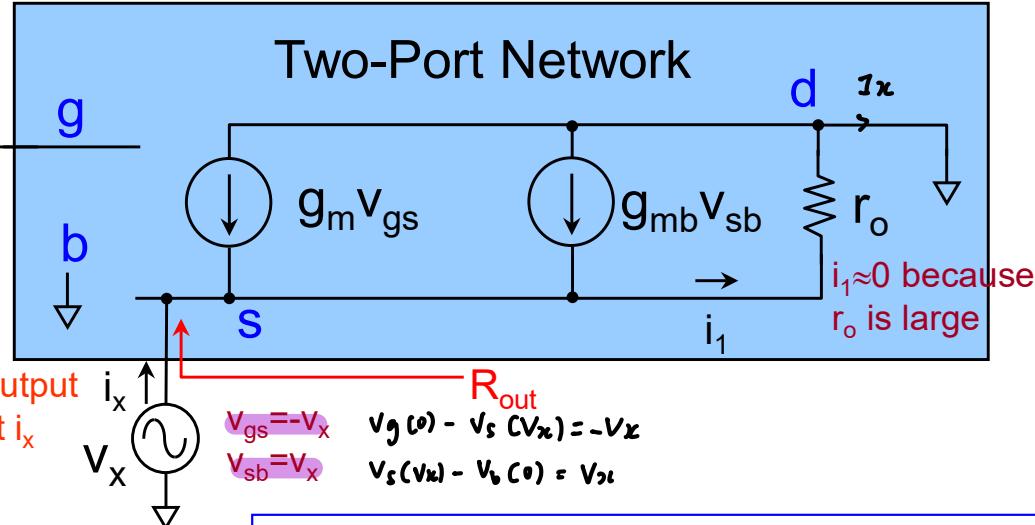Apply test voltage v_x at output
and measure test current i_x




Refer to slide SSA1-10 for the evaluation of R_{out} .

$$R_{out} = \frac{v_x}{i_x} \quad \left\{ \begin{array}{l} i_x \approx -g_m v_{gs} - g_{mb} v_{sb} = (g_m - g_{mb}) v_x \\ \Rightarrow R_{out} \approx \frac{1}{g_m - g_{mb}} \end{array} \right.$$

CD – Two-Port Network (R_{out})

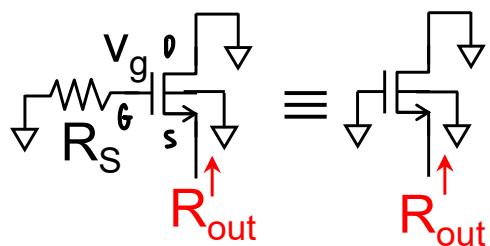Since no current flow through R_s , v_g is same as AC ground



$$R_{out} \approx \frac{1}{g_m - g_{mb}}$$

Important Result: * * * * *

If you see a MOSFET connected in similar fashion, the equivalent resistance looking into the source (R_{out}) is directly given by the formula. No need to rederive.

Example :


$$R_s = 100 \quad r_o = 100k$$

$$g_m = 2.83m \quad g_{mb} = -0.71m$$



$$\Rightarrow R_{out} \approx 283$$

- The output resistance does not depend on R_s




MOS – Equivalent Resistance

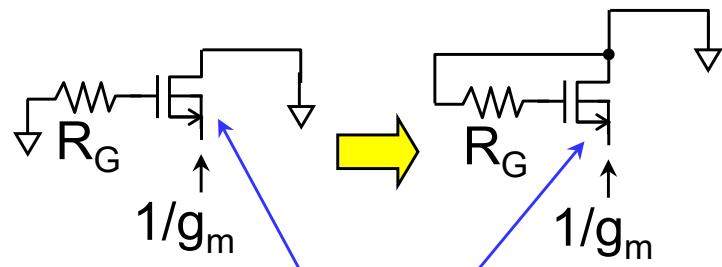

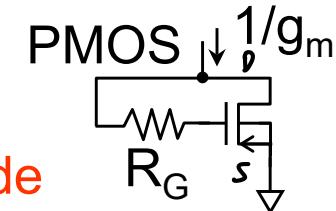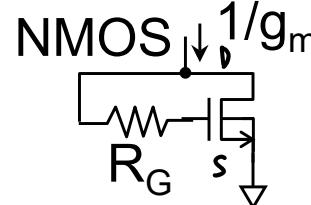
When body and source connected together, i.e., $v_{sb}=0$
→ there is no body effect
→ $g_{mb}v_{sb}=0$, eliminate g_{mb}



Diode Connected Transistor

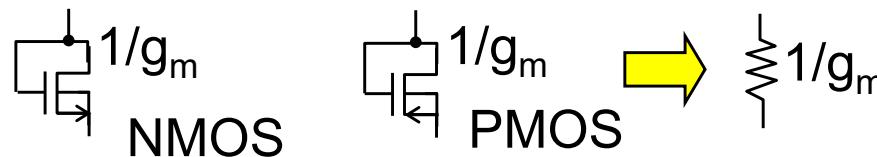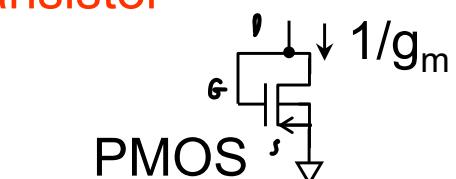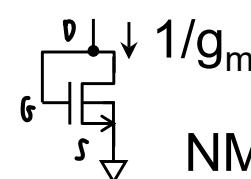

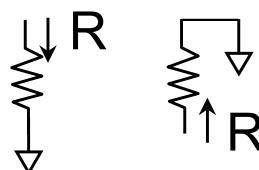Since no current flows through R_G , there is no voltage drop across R_G , R_G is effectively short circuited




A resistor, whether you look from top or bottom, is always a resistor with resistance R

Only APPLICABLE for AC analysis

- When the drain and gate are connected together, the transistor is called diode connected transistor
- Diode connected transistor has an equivalent resistance of $1/g_m$

CD – Two-Port Network (A_V)

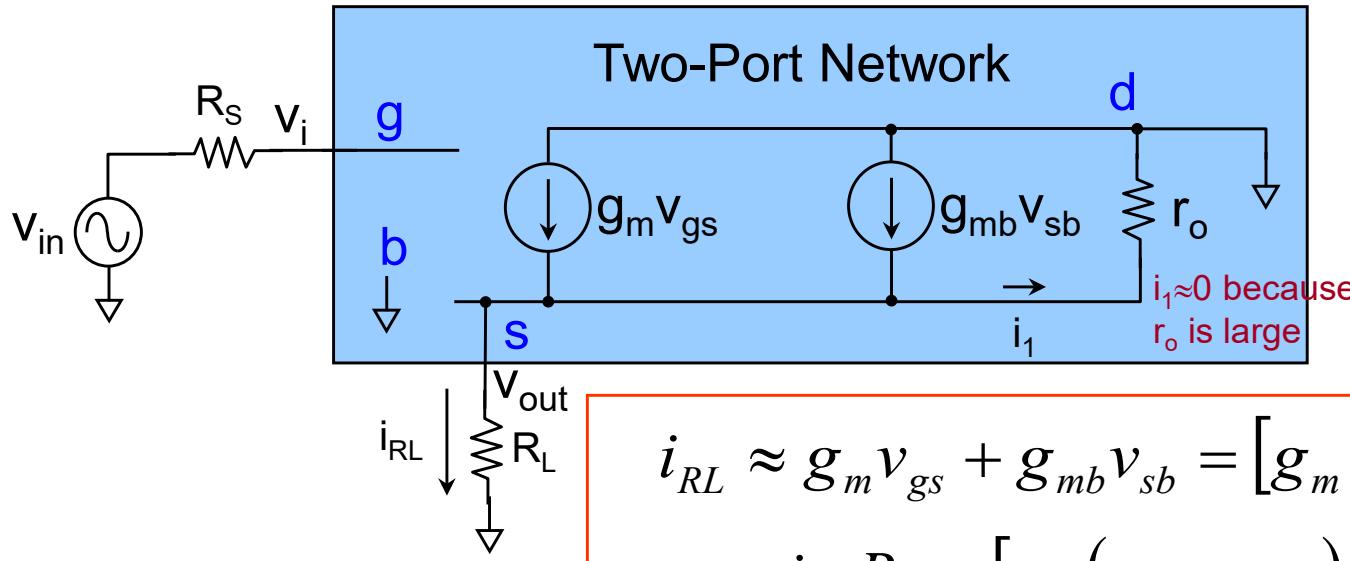

No body effect means source and body are connected together
 $\Rightarrow g_{mb}$ can be eliminated in the equation

$$v_{gs} = v_{in} - v_{out}$$

$$v_{sb} = v_{out}$$

$$i_{RL} \approx g_m v_{gs} + g_{mb} v_{sb} = [g_m(v_{in} - v_{out}) + g_{mb} v_{out}]$$

$$v_{out} = i_{RL} R_L \approx [g_m(v_{in} - v_{out}) + g_{mb} v_{out}] R_L$$

$$\Rightarrow [1 + (g_m - g_{mb}) R_L] v_{out} = g_m R_L v_{in}$$

$$\Rightarrow A_V = \frac{v_{out}}{v_{in}} = \frac{g_m R_L}{1 + (g_m - g_{mb}) R_L} \approx \frac{g_m}{g_m - g_{mb}} \approx 0.8$$

If $(g_m - g_{mb}) R_L \gg 1$


- Without body effect, $g_{mb} v_{sb} = 0 \Rightarrow A_V \approx 1$
- For CD amplifier, we calculate v_{out}/v_{in} directly.

CD – Important Results




1

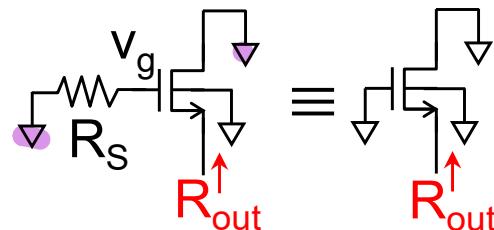Since no current flows through R_s , v_g is same as AC ground



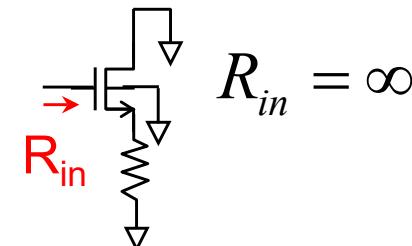
$$R_{out} \approx \frac{1}{g_m - g_{mb}}$$



2

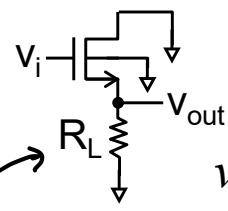Relationship between v_i and v_{out} is defined as follows:






one
resistor
only


$$v_{out} = \frac{g_m R_L}{1 + (g_m - g_{mb}) R_L} v_i$$

3

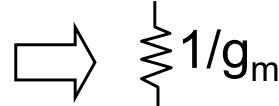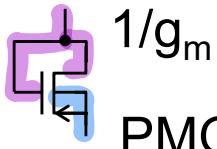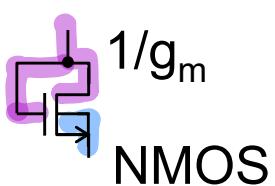
Diode Connected Transistor
(Gate and drain shorted)
(No body effect)



CD - Two-Port Network

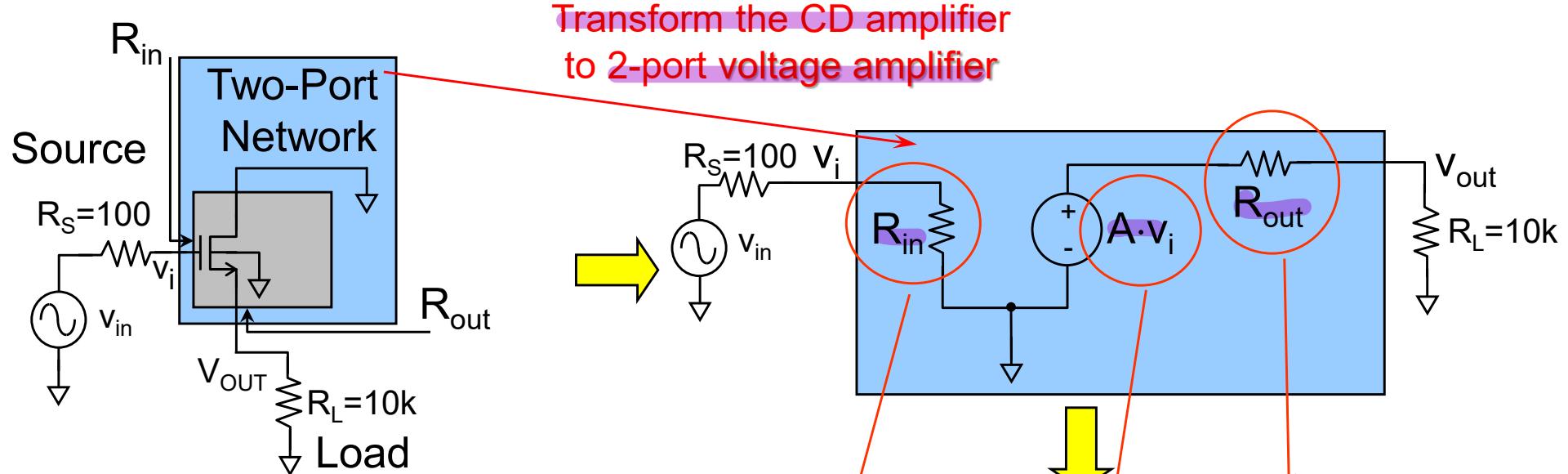

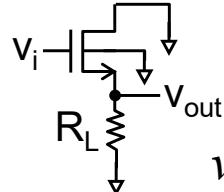Relationship between v_i and v_{out} is defined as follows:



$$v_{out} = \frac{g_m R_L}{1 + (g_m - g_{mb}) R_L} v_i$$

It is simpler to remember $A_v (=v_{out}/v_i)$ rather than A

A can be found based on the A_v .

$$\frac{v_{out}}{v_{in}} = \frac{v_i}{v_{in}} \times \frac{v_{out}}{v_i} = \frac{g_m R_L}{1 + (g_m - g_{mb}) R_L}$$


\Rightarrow

$$v_i = \frac{R_{in}}{R_{in} + R_s} v_{in}$$


$$\frac{v_i}{v_{in}} \times \frac{v_{out}}{v_i} = \frac{\frac{R_{in}}{R_{in} + R_s} v_{in}}{\frac{R_{in}}{R_{in} + R_s} v_{in}} \times \frac{\frac{g_m R_L}{1 + (g_m - g_{mb}) R_L}}{1 + (g_m - g_{mb}) R_L} \approx$$

$$\frac{R_{in}}{R_{in} + R_s} \times \frac{g_m R_L}{1 + (g_m - g_{mb}) R_L}$$

Common Collector (CC)

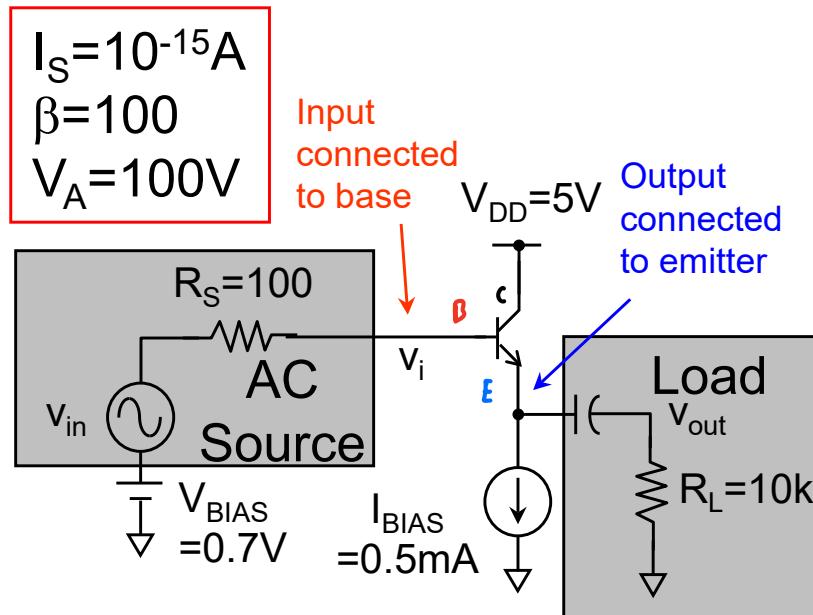

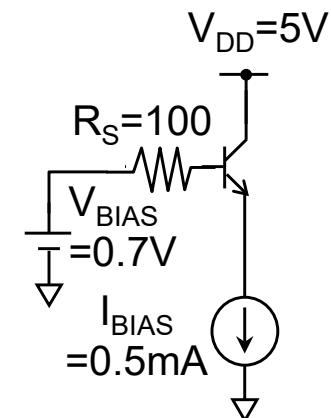
For DC analysis,
remove AC source
and open circuit
capacitor



- Identify AC Source and Load
- To identify amplifier configuration, we need to consider AC equivalent circuit, i.e., short circuit capacitors
 - Input connected to Base, output connected to Emitter, Collector connected to neither input nor output \Rightarrow Common Collector (CC)

DC Analysis - CC

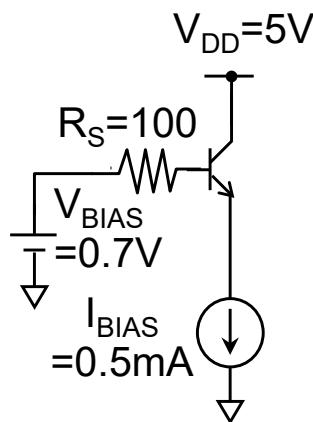- Remove AC source and open circuit capacitors when doing DC analysis



$$\begin{aligned}I_S &= 10^{-15}A \\ \beta &= 100 \\ V_A &= 100V\end{aligned}$$

Determine DC biasing

$$V_T = 26\text{ mV}$$

$$I_E = I_{BIAS} = 0.5\text{ mA}$$

$$I_C = \frac{\beta}{\beta+1} I_E = 0.495\text{ mA}$$

$$I_B = 4.95\text{ }\mu\text{A}$$

$$I_B = \frac{I_C}{\beta}$$

$$I_C \approx I_E$$

Determine AC small-signal parameters

$$g_m = \frac{I_C}{V_T} = 19\text{ mA/V}$$



$$r_\pi = \frac{\beta}{g_m} = 5.26\text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = 202\text{ k}\Omega$$

Finding the
current I_C is key

CC - AC Analysis (Self Reading)

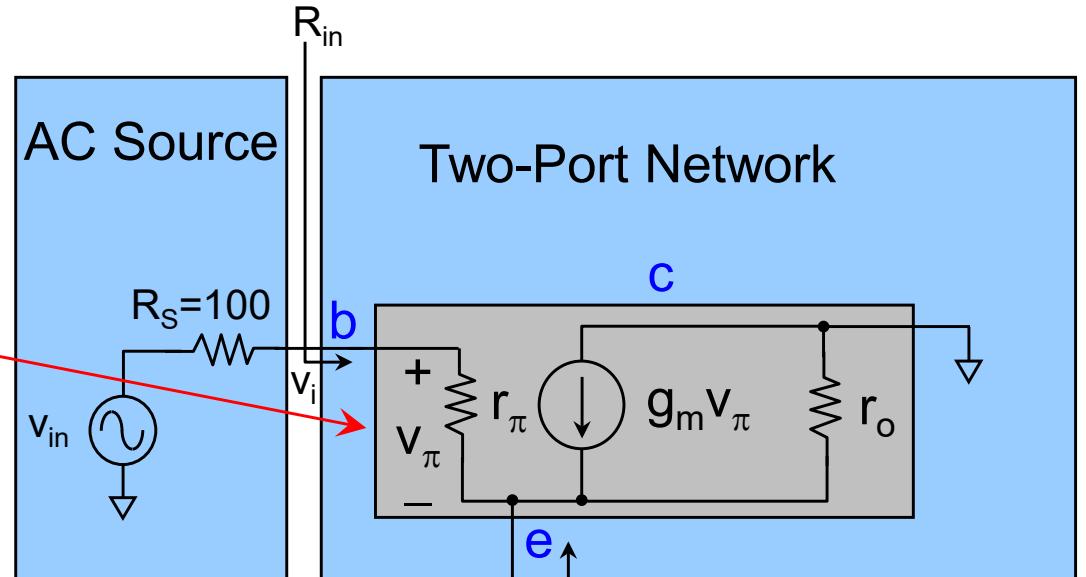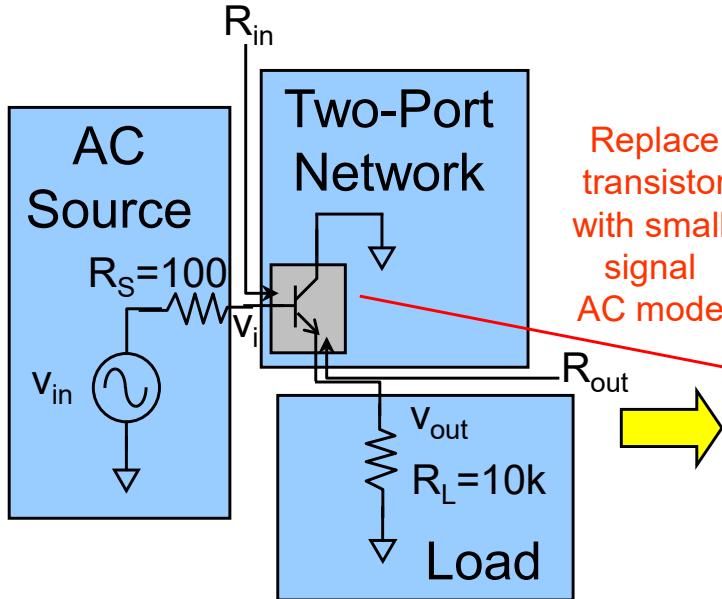For AC analysis, need to consider the AC equivalent circuit (i.e., short circuit capacitor, replace DC voltage source by AC short circuit and replace DC current source with AC open circuit).



Step 1 :


Identify AC source and load

Step 2 :

Group the remaining components into two-port network

Step 3 :

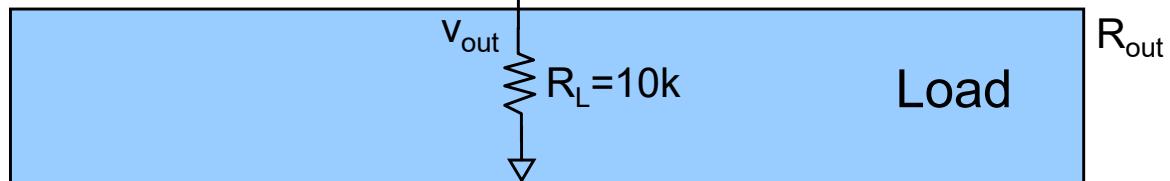
Replace transistor with small-signal model



For CC amplifier, transform to 2-port Voltage Amplifier (based on experience of circuit designers). Need to evaluate R_{in} , R_{out} and A .


CC – Two-Port Network (R_{in}) (Self Reading)

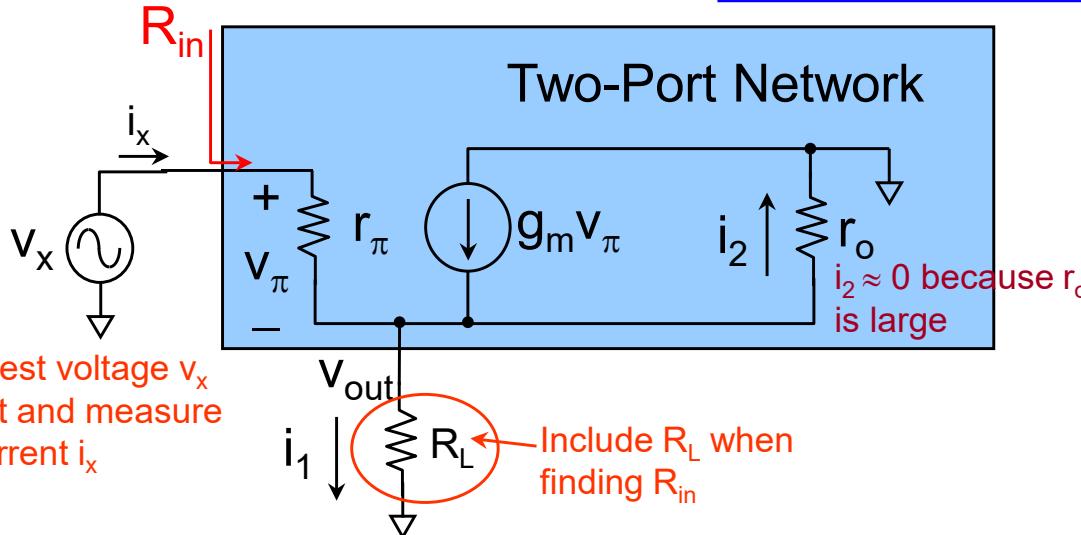Refer to slide SSA1-10 for the evaluation of R_{in} .



$$R_{in} = \frac{v_x}{i_x} = \left[\begin{array}{l} v_x = v_\pi + v_{out} = i_x r_\pi + v_{out} \quad \text{Eliminate } v_{out} \text{ and keep } v_x \text{ and } i_x \\ \bullet \quad v_{out} = i_1 R_L \\ \bullet \quad i_1 = i_x + g_m v_\pi - i_2 \approx i_x + g_m v_\pi = i_x + i_x g_m r_\pi \\ \therefore v_x = i_x r_\pi + v_{out} \approx i_x r_\pi + (i_x + i_x g_m r_\pi) R_L \\ \Rightarrow R_{in} = \frac{v_x}{i_x} \approx r_\pi + (1 + g_m r_\pi) R_L = r_\pi + (1 + \beta) R_L \approx r_\pi (1 + g_m R_L) \end{array} \right] \quad (\text{N.B. } g_m r_\pi = \beta \gg 1)$$

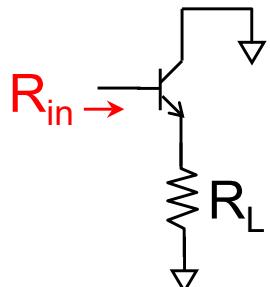CC – Two-Port Network (R_{in}) (Self Reading)



$$\begin{aligned}R_{in} &\approx r_\pi + (1 + \beta)R_L \\&\approx r_\pi + \beta R_L \\&\approx r_\pi(1 + g_m R_L)\end{aligned}$$

Important Result:

If you see a BJT connected in similar fashion, the **equivalent resistance** looking into the **base** (R_{in}) is directly given by the formula. **No need to rederive.**


Example :

$$\begin{aligned}R_L &= 10k \quad r_o = 202k \\ \Rightarrow R_{in} &= r_\pi + (\beta + 1)R_L \\ &= 1.01M\end{aligned}$$

- Emitter side resistor helps boost up the input resistance looking into the base

CC – Two-Port Network (R_{out}) (Self Reading)

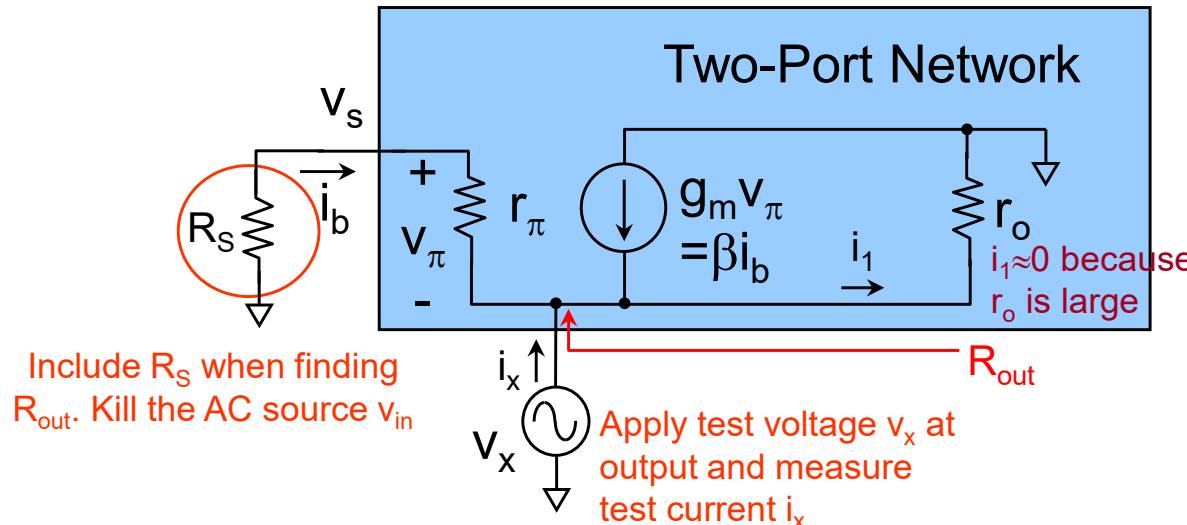
Refer to slide SSA1-10 for the evaluation of R_{out} .



Eliminate i_b and keep v_x and i_x

$$R_{out} = \frac{v_x}{i_x} \Rightarrow \begin{cases} i_x \approx -(\beta + 1)i_b \\ i_b = -\frac{v_x}{R_s + r_\pi} \end{cases} \Rightarrow R_{out} = \frac{R_s + r_\pi}{\beta + 1} \approx \frac{R_s}{\beta + 1} + \frac{1}{g_m}$$

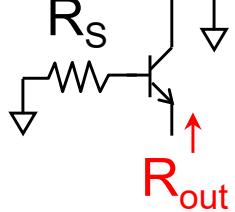CC – Two-Port Network (R_{out}) (Self Reading)



$$R_{out} \approx \frac{R_S}{\beta + 1} + \frac{1}{g_m}$$
$$\approx \frac{1}{g_m} \quad [\text{if } R_S \text{ is small}]$$

Important Result:

If you see a BJT connected in similar fashion, the equivalent resistance looking into the emitter (R_{out}) is directly given by the formula. **No need to rederive.**

Example :

$$R_S = 100 \quad r_\pi = 5.26 \text{ k}$$

$$r_o = 202 \text{ k} \quad g_m = 19 \text{ m}$$

$$\Rightarrow R_{out} \approx 54$$



- If R_S is small, the output impedance is just the inverse of the transconductance of BJT

BJT – Diode Connected Transistor Equivalent Resistance (Self Reading)

For

$$R_s = 0$$
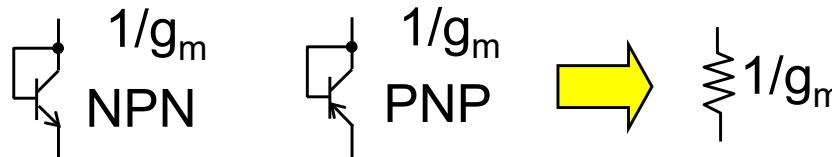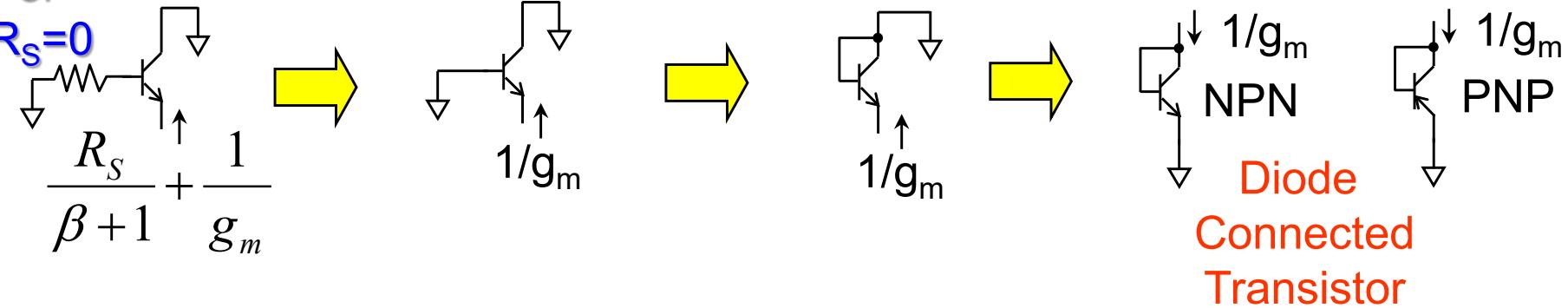
$$\frac{R_s}{\beta + 1} + \frac{1}{g_m}$$





A resistor, whether you look from top or bottom, always is a resistor with resistance R

Only APPLICABLE for AC analysis

- When the **collector** and **base** are connected together, the transistor is called **diode connected transistor**
- Diode connected transistor has an equivalent resistance of $1/g_m$

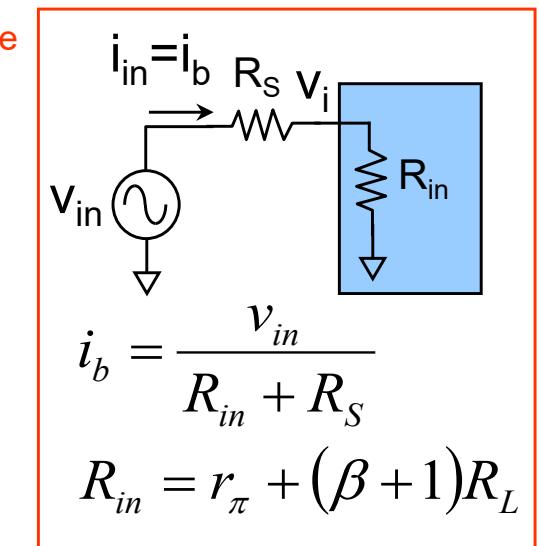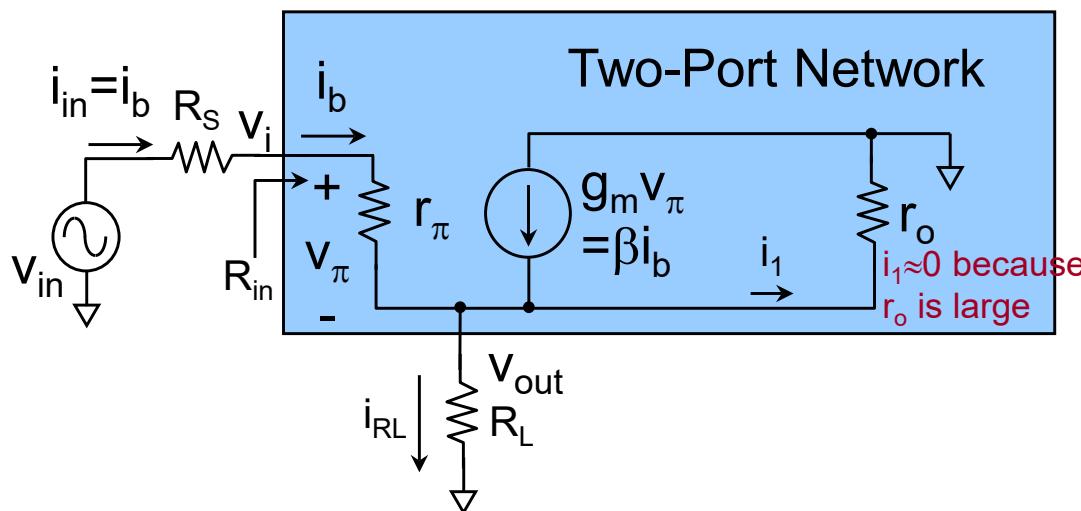CC – Two-Port Network (A_V) (Self Reading)



$$i_{RL} = (\beta + 1)i_b - i_1$$

$$v_{out} = i_{RL} \times R_L$$

$$= (\beta + 1)i_b \times R_L$$

$$\Rightarrow A_V = \frac{v_{out}}{v_{in}} = \frac{(\beta + 1)i_b \times R_L}{[R_s + r_\pi + (\beta + 1)R_L]i_b}$$

$$= \frac{(\beta + 1)R_L}{R_s + r_\pi + (\beta + 1)R_L}$$


$$= \frac{g_m R_L}{1 + g_m R_L} \approx 1 \quad [\text{If } g_m R_L \gg 1]$$

Eliminate i_b and keep v_{out} and v_{in}

- For CC amplifier, we calculate v_{out}/v_{in} directly.
- $v_{out}/v_{in} \approx v_{out}/v_i$ as both i_b and R_s are small.


CC - Important Results

1

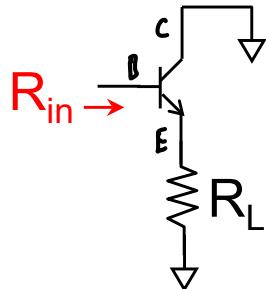


$$\begin{aligned} R_{in} &\approx r_\pi + (1 + \beta)R_L \\ &\approx r_\pi + \beta R_L \\ &\approx r_\pi(1 + g_m R_L) \text{ ***} \end{aligned}$$

2

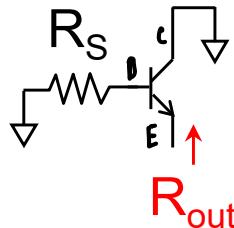

$$\begin{aligned} R_{out} &\approx \frac{R_S}{\beta + 1} + \frac{1}{g_m} \text{ ***} \\ &\approx \frac{1}{g_m} \quad [\text{if } R_S \text{ is small}] \end{aligned}$$

3

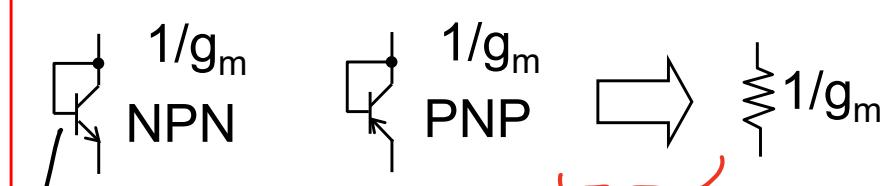


During AC * analysis
only

base and collector
shorted

4

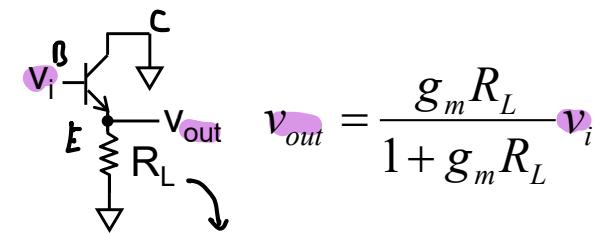
Relationship between v_i and v_{out} is defined as follows:




$$v_{out} = \frac{g_m R_L}{1 + g_m R_L} v_i$$

only 1 resistor, if more then one need to simplify to 1

CC - Two-Port Network

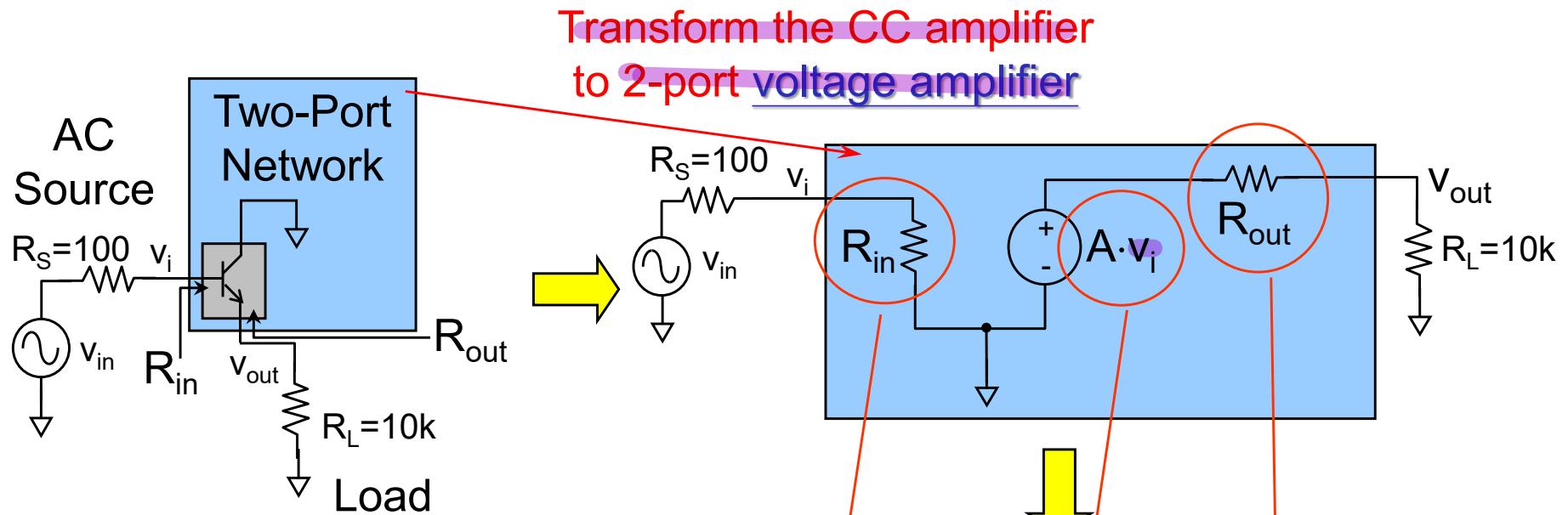

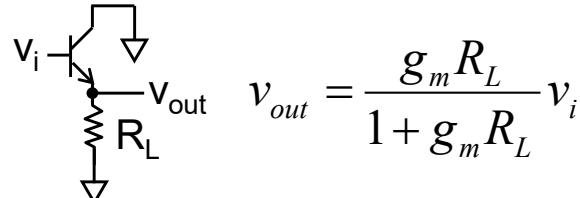Relationship between v_i and v_{out} is defined as follows:



$$\frac{v_{out}}{v_{in}} = \frac{v_i}{v_{in}} \times \frac{v_{out}}{v_i} = \frac{R_{in}}{R_S + R_{in}} \times \frac{g_m R_L}{1 + g_m R_L}$$

It is simpler to remember $A_v (=v_{out}/v_i)$ rather than A

A can be found based on A_v

Characteristics of CC/CD

- High input resistance
- Low output resistance ***
- Close to unity gain
- No polarity inversion
- Ideal buffer (Emitter/Source follower)
- BJT provides larger g_m than MOS ($g_m - g_{mb}$)

⇒ Lower output resistance





$$\frac{g_m R_L}{1 + g_m R_L}$$

⇒ Better buffer

CE with Emitter Degeneration

Emitter connected to some resistor

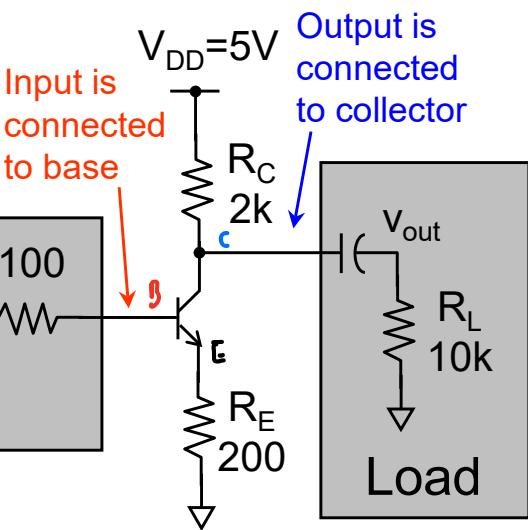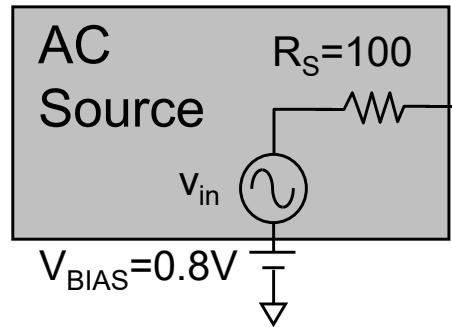
$$\begin{aligned} I_S &= 10^{-15} \text{ A} \\ \beta &= 100 \\ V_A &= 100 \text{ V} \end{aligned}$$



For DC analysis, remove AC source and open circuit capacitor



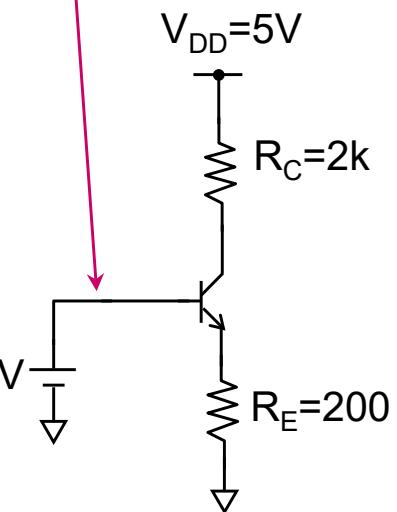
$I_B R_S$ voltage drop is negligible due to small I_B and R_S



- Identify AC Source and Load
- To identify amplifier configuration, we need to consider AC equivalent circuit, i.e., short circuit capacitors
 - Input connected to Base, output connected to Collector, Emitter connected to neither input nor output and is connected to a resistor \Rightarrow CE with Emitter Degeneration

DC Analysis

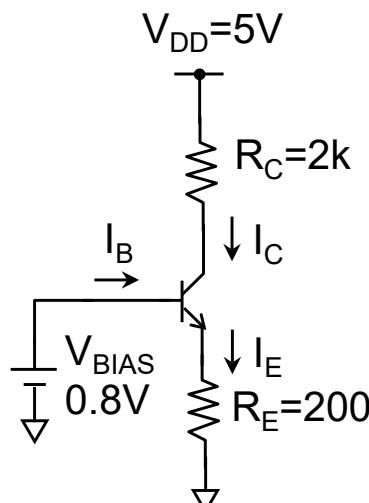- Remove AC source and open circuit capacitor when doing DC analysis



$$\begin{aligned}I_S &= 10^{-15} \text{ A} \\ \beta &= 100 \\ V_A &= 100 \text{ V}\end{aligned}$$

Determine DC biasing

$$V_T = 26 \text{ mV}$$

Assume $V_{BE} \approx 0.7 \text{ V}$

$$I_E = \frac{V_{BIAS} - V_{BE}}{R_E} = 0.5 \text{ mA}$$

$$I_C = \frac{\beta}{\beta + 1} I_E = 0.495 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) \approx 0.7001$$

∴ Valid Assumption

$$I_B = 4.95 \mu\text{A}$$

V_B is small so need to check

Determine AC Small-signal parameters

$$g_m = \frac{I_C}{V_T} = 19 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = 5.26 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = 202 \text{ k}\Omega$$


If the assumption is invalid, use the updated V_{BE} , re-estimate I_C , a few iterations might be needed.

* Never estimate I_C using the exponential transistor equation using $V_{BE} \approx 0.7 \text{ V}$.

$$i_C = I_S e^{v_{BE}/V_T},$$

AC Analysis

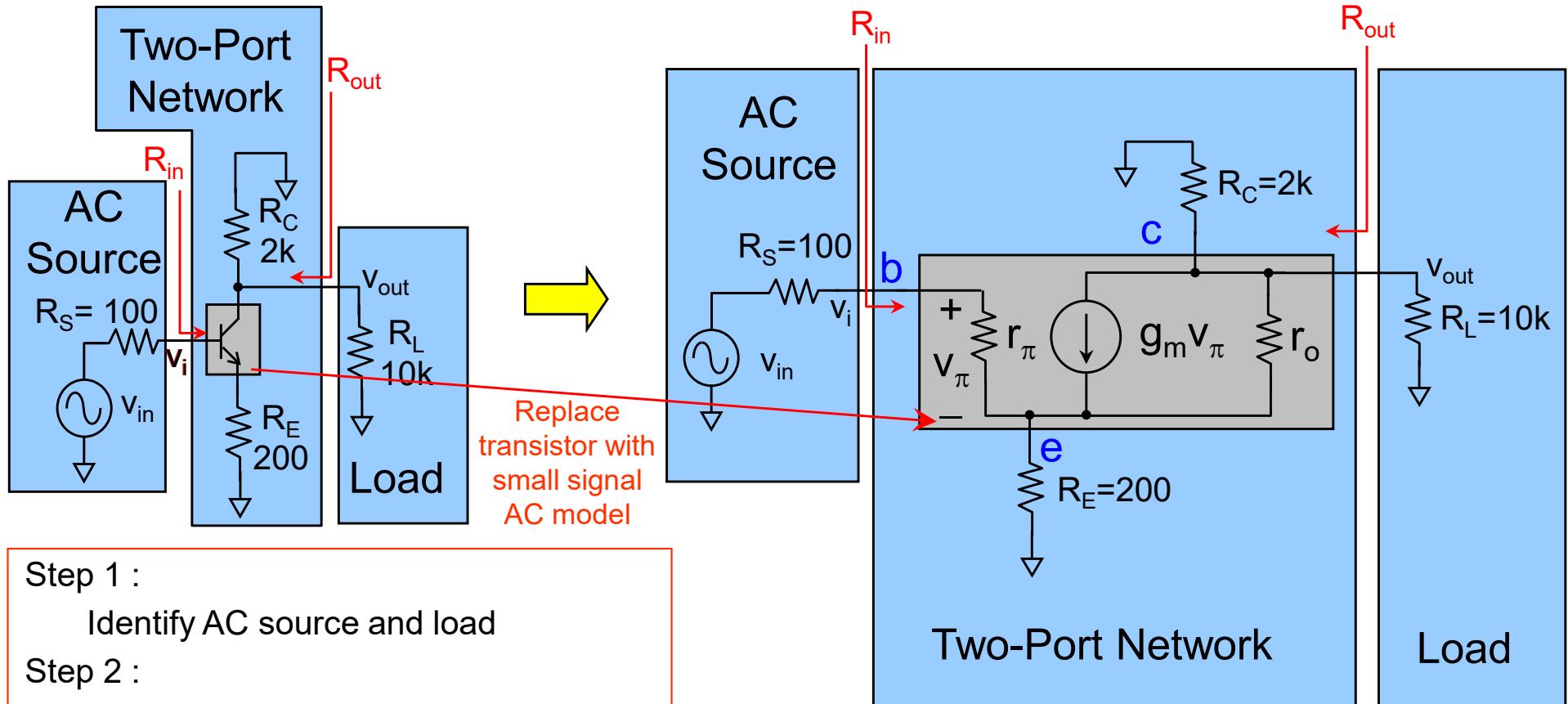For AC analysis, need to consider the AC equivalent circuit (i.e., short circuit capacitor, replace DC voltage source by AC short circuit and replace DC current source with AC open circuit).



Step 1 :

Identify AC source and load

Step 2 :

Group the remaining components (the amplifier circuit) into two-port network

Step 3 :

Replace transistor with small signal AC model


Two-Port Network

Load

For CE with emitter degeneration amplifier, transform to 2-port Transconductance Amplifier (based on experience of circuit designers). Need to evaluate G_m , R_{in} and R_{out} .

CE with Emitter Degeneration – Two-Port Network (G_m)

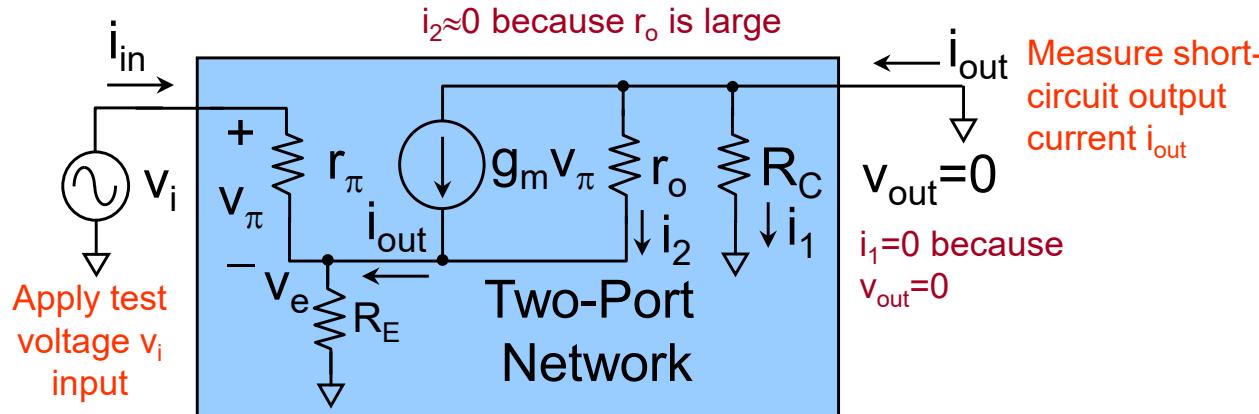Refer to slide SSA1-7 for the evaluation of G_m .



Important Result :
Transconductance (G_m) is just $g_m / (1 + g_m R_E)$


In normal CE, (G_m) is g_m ,
hence CE with degen $\rightarrow g_m$ smaller

$$G_m = \frac{i_{out}}{v_i} \Big|_{v_{out}=0}$$

$$\left\{ \begin{array}{l} v_i = v_\pi + v_e = i_{in}r_\pi + (i_{in} + i_{out})R_E = i_{in}(r_\pi + R_E) + i_{out}R_E \\ \text{Eliminate } i_{in} \text{ and keep } v_i \text{ and } i_{out} \\ i_{out} = g_m v_\pi + i_2 \approx g_m v_\pi = g_m i_{in} r_\pi \Rightarrow i_{in} = \frac{i_{out}}{g_m r_\pi} \\ \Rightarrow v_i = \left[\frac{i_{out}}{g_m r_\pi} \right] \times (r_\pi + R_E) + i_{out} R_E = i_{out} \times \frac{r_\pi + R_E(1 + g_m r_\pi)}{g_m r_\pi} \\ \Rightarrow G_m = \frac{i_{out}}{v_i} = \frac{g_m r_\pi}{r_\pi + R_E(1 + g_m r_\pi)} \approx \frac{g_m}{1 + g_m R_E} = 4 \text{ mA/V } (\text{N.B. } g_m r_\pi = \beta \gg 1) \end{array} \right.$$

CE with Emitter Degeneration – Two-Port Network (R_{in})

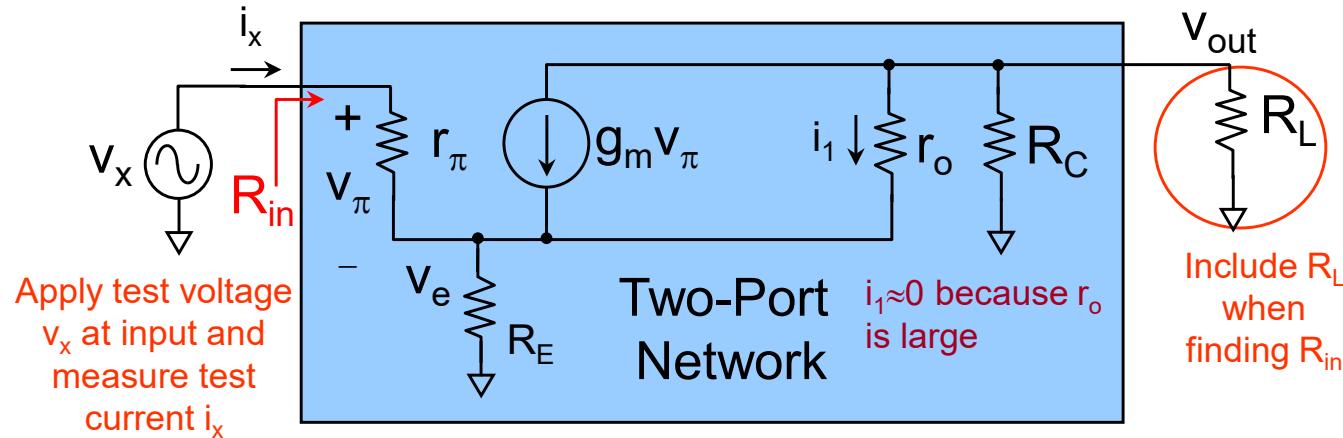Refer to slide SSA1-7 for the evaluation of R_{in} .




$$R_{in} = \frac{v_x}{i_x} - \left[\begin{array}{l} i_x \approx \frac{v_e}{R_E} - g_m v_{\pi} = \frac{v_e}{R_E} - g_m i_x r_{\pi} \\ v_e = v_x - v_{\pi} = v_x - i_x r_{\pi} \\ \text{Eliminate } v_e \text{ and keep } v_x \text{ and } i_x \\ \Rightarrow i_x \approx \frac{(v_x - i_x r_{\pi})}{R_E} - g_m i_x r_{\pi} \end{array} \right]$$

$$\Rightarrow R_{in} = \frac{v_x}{i_x} = r_{\pi} + g_m r_{\pi} R_E + R_E$$

$$= r_{\pi} + (\beta + 1)R_E$$

$$\approx r_{\pi}[1 + g_m R_E]$$

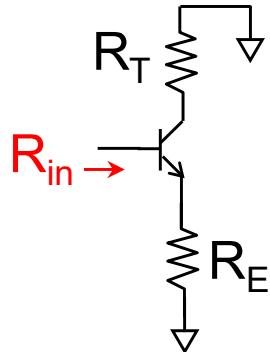CE with Emitter Degeneration – Two-Port Network (R_{in})



$$R_{in} = r_\pi + (\beta + 1)R_E$$
$$\approx r_\pi[1 + g_m R_E]$$

Important Result:


If you see a BJT connected in similar fashion, the **equivalent resistance looking into the base (R_{in})** is directly given by the formula. **No need to rederive.** The **resistance in the collector branch has no effect on R_{in} .**

Example :

$$R_E = 200 \quad r_o = 202k$$
$$\Rightarrow R_{in} = r_\pi + (\beta + 1)R_E$$
$$= 25.5k$$

- Emitter side resistor helps boost up the input resistance looking into the base, **same formula as CC**

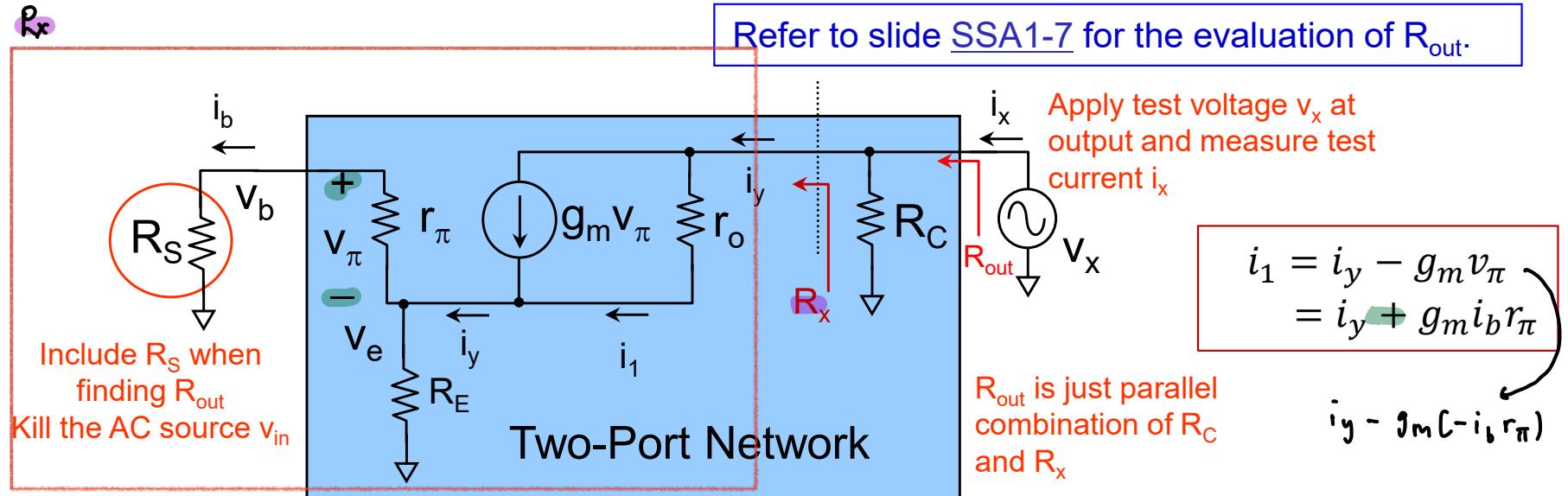CE with Emitter Degeneration – Two-Port Network (R_{out})



$$R_{out} = R_x // R_C$$

$$R_x = \frac{v_x}{i_y}$$

$$v_x = v_e + i_1 r_o = v_e + (i_y - g_m v_\pi) r_o = v_e + (i_y + g_m i_b r_\pi) r_o$$

$$v_e = i_y [(R_S + r_\pi) // R_E]$$

$$i_b = \frac{v_e}{R_S + r_\pi} = \frac{i_y}{R_S + r_\pi} [(R_S + r_\pi) // R_E]$$


Eliminate v_e , i_b and keep v_x and i_y

$$\Rightarrow v_x = i_y [(R_S + r_\pi) // R_E] + i_y r_o + i_y g_m \left(\frac{r_\pi}{R_S + r_\pi} \right) [(R_S + r_\pi) // R_E] r_o$$

$$\Rightarrow R_x = \frac{v_x}{i_y} = r_o \left\{ 1 + g_m [(R_S + r_\pi) // R_E] \left(\frac{r_\pi}{R_S + r_\pi} \right) \right\}$$

$$\Rightarrow R_{out} = R_x // R_C \approx R_C$$

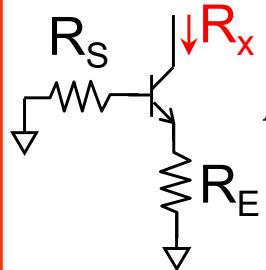CE with Emitter Degeneration – Two-Port Network (R_{out})



$$R_x = r_o \left\{ 1 + g_m [(R_S + r_\pi) // R_E] \left(\frac{r_\pi}{R_S + r_\pi} \right) \right\}$$

Important Result:

If you see a BJT connected in similar fashion, the equivalent resistance looking into the collector (R_x) is directly given by the formula.

No need to rederive.

Example :

$$R_S = 100 \quad r_\pi = 5.26k$$

$$R_E = 200 \quad r_o = 202k$$

$$g_m = 19m$$

$$\Rightarrow R_x \approx 928k$$

$$\Rightarrow R_{out} \approx R_C = 2k$$

- Emitter side resistor helps boost up the transistor output resistance (R_x)
- Very similar to CB configuration. Same formula as CB if $R_S = 0$.

CE with Degeneration – Important Results




1

Important Result :


Transconductance
(G_m) is just
 $g_m/(1+g_mR_E)$

2

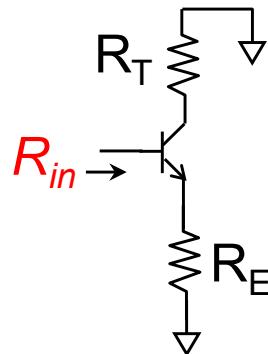


$$R_{in} = r_\pi + (\beta + 1)R_E \\ \approx r_\pi[1 + g_m R_E]$$

3

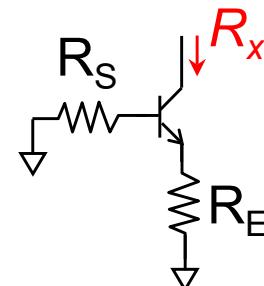


$$R_x = r_o \left\{ 1 + g_m [(R_S + r_\pi) // R_E] \left(\frac{r_\pi}{R_S + r_\pi} \right) \right\}$$

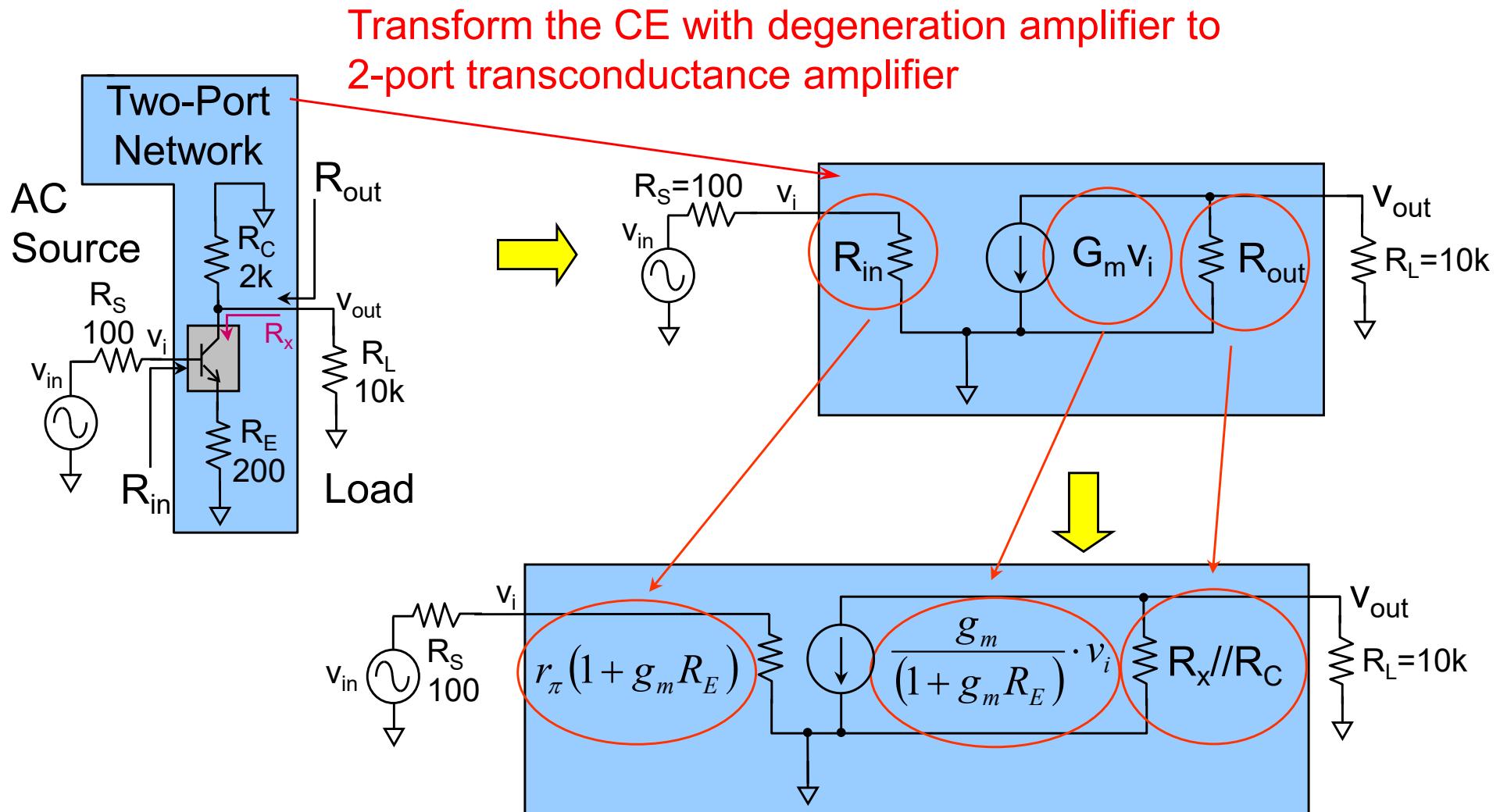CE with Emitter Degeneration – Two-Port Network



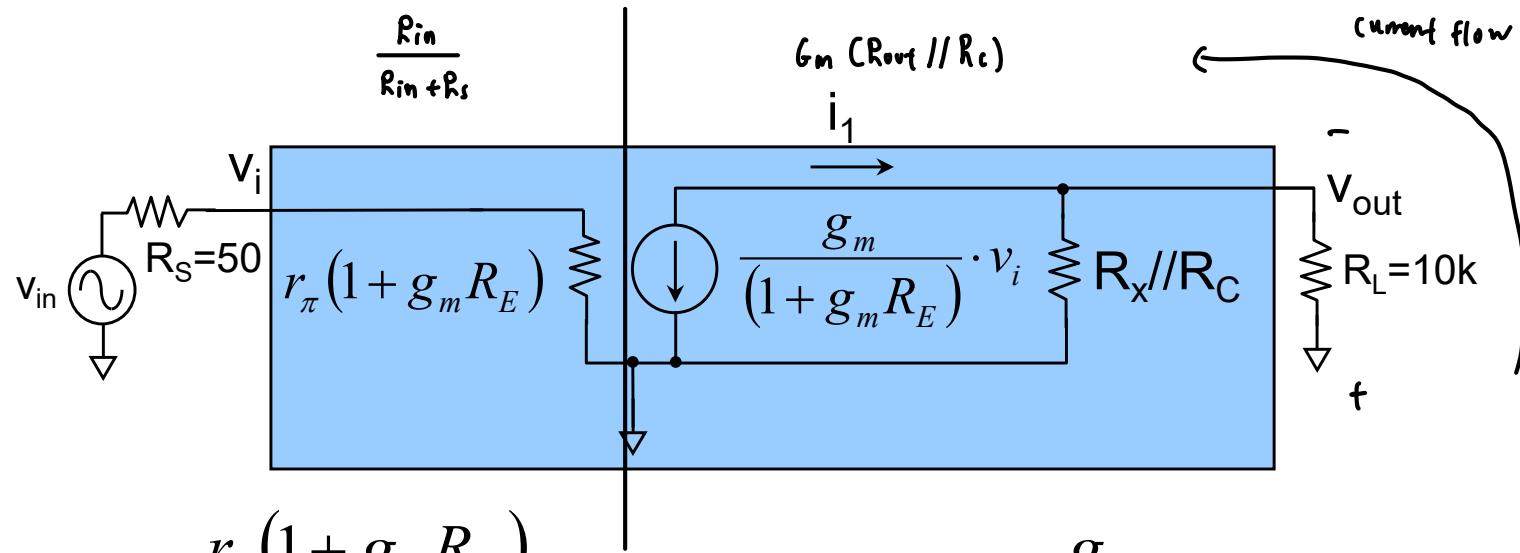CE with Emitter Degeneration – Two-Port Network (A_V)



$$v_i = \frac{r_\pi(1 + g_m R_E)}{R_S + r_\pi(1 + g_m R_E)} v_{in}$$

$$i_1 = -\frac{g_m}{1 + g_m R_E} v_i$$

$$v_{out} = i_1 \times [(R_x // R_C) // R_L]$$


$$= -\frac{g_m}{1 + g_m R_E} v_i \times [(R_x // R_C) // R_L]$$

$$A_V = \frac{v_{out}}{v_{in}} = -\frac{r_\pi(1 + g_m R_E)}{R_S + r_\pi(1 + g_m R_E)} \times \frac{g_m}{1 + g_m R_E} \times [(R_x // R_C) // R_L]$$


CS with Source Degeneration

$$\begin{aligned}\mu_n C_{ox} &= 80 \mu\text{A/V}^2 \\ V_{THN} &= 0.7 \text{ V} \\ \mu_n &= 0.02 \text{ V}^{-1}\end{aligned}$$
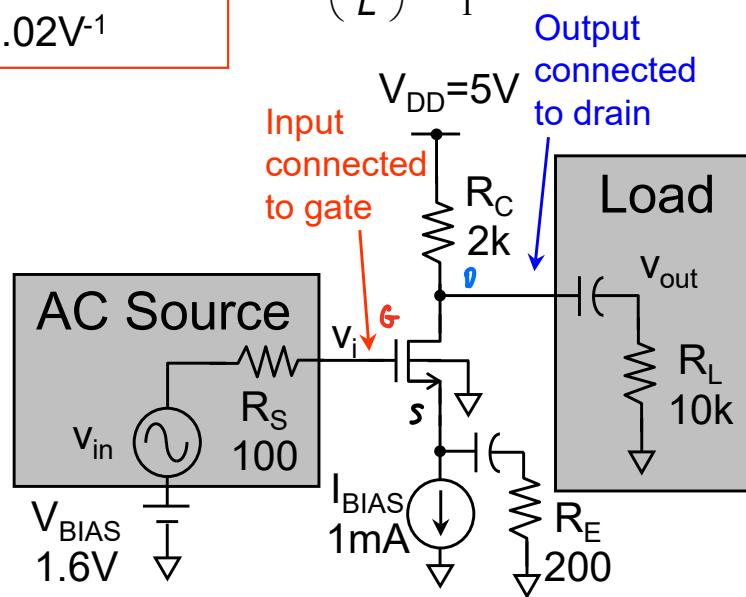
$$\left(\frac{W}{L}\right) = \frac{100}{1}$$



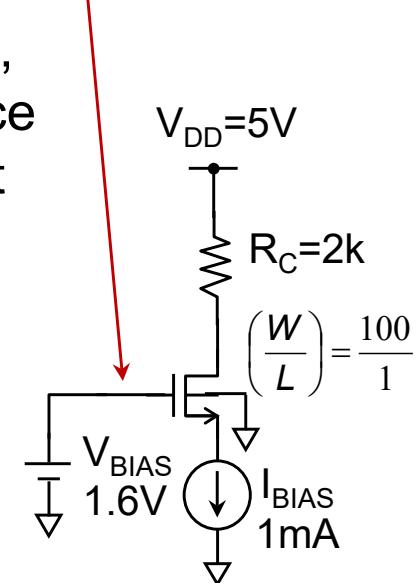
For DC analysis, remove AC source and open circuit capacitors



- Identify Source and Load
- To identify amplifier configuration, we need to consider AC equivalent circuit, i.e., short circuit capacitors
 - Input connected to **Gate**, output connected to **Drain**, Source connected to neither input nor output and is connected to a resistor \Rightarrow CS with Source Degeneration

DC Analysis

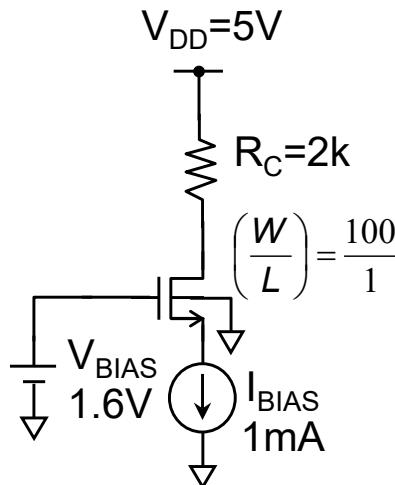- Remove AC source and open circuit capacitors when doing DC analysis



$$\begin{aligned}\mu_n C_{ox} &= 80 \mu\text{A/V}^2 \\ V_{THN} &= 0.7 \text{ V} \\ \mu_n &= 0.02 \text{ V}^{-1}\end{aligned}$$

Determine DC biasing

$$I_D = I_S = I_{BIAS} = 1 \text{ mA}$$

$$\left(\frac{W}{L}\right) = \frac{100}{1}$$

Good approximation, no need to go through detailed calculations

Determine AC small-signal parameters

$$\begin{aligned}g_m &= \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)} I_D \\ &= 4 \text{ mA/V}\end{aligned}$$


MOSFET has body effect
(body not shorted to source)

$$g_{mb} \approx -\frac{g_m}{4} = -1 \text{ mA/V}$$


$$r_i = \infty$$

$$r_o = \frac{1}{\lambda_n I_D} = 50 \text{ k}\Omega$$

AC Analysis (Self Reading)

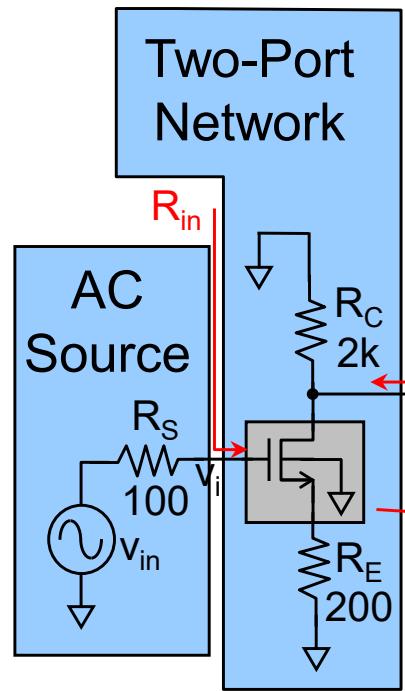

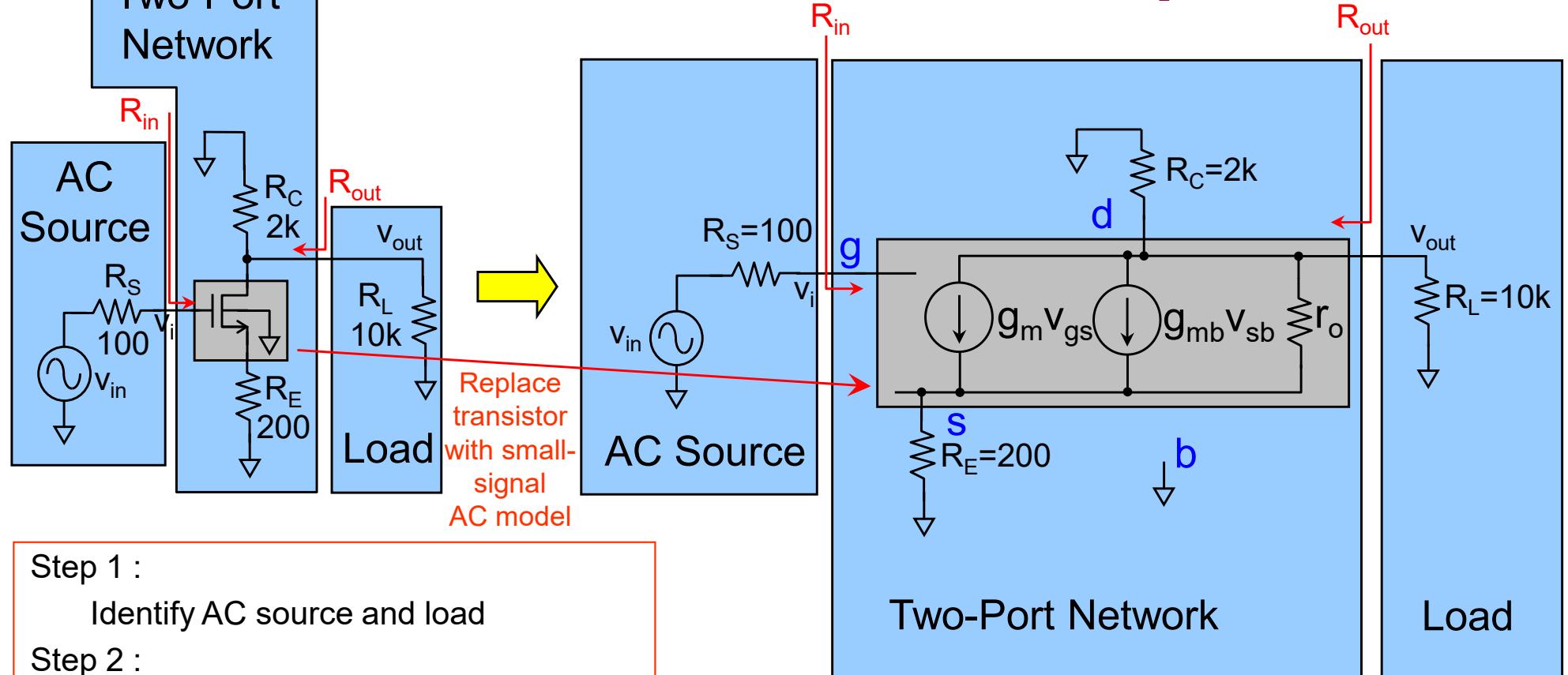Short circuit DC voltage source, open circuit DC current source, short circuit capacitor \Rightarrow Source terminal of transistor is connected directly to R_E



Step 1 :

Identify AC source and load

Step 2 :

Group the remaining component into two-port network


Step 3 :

Replace transistor with small-signal AC model

For CS with emitter degeneration amplifier, transform to 2-port Transconductance Amplifier (based on experience of circuit designers). Need to evaluate G_m , R_{in} and R_{out} .

$$R_{in} = \infty$$

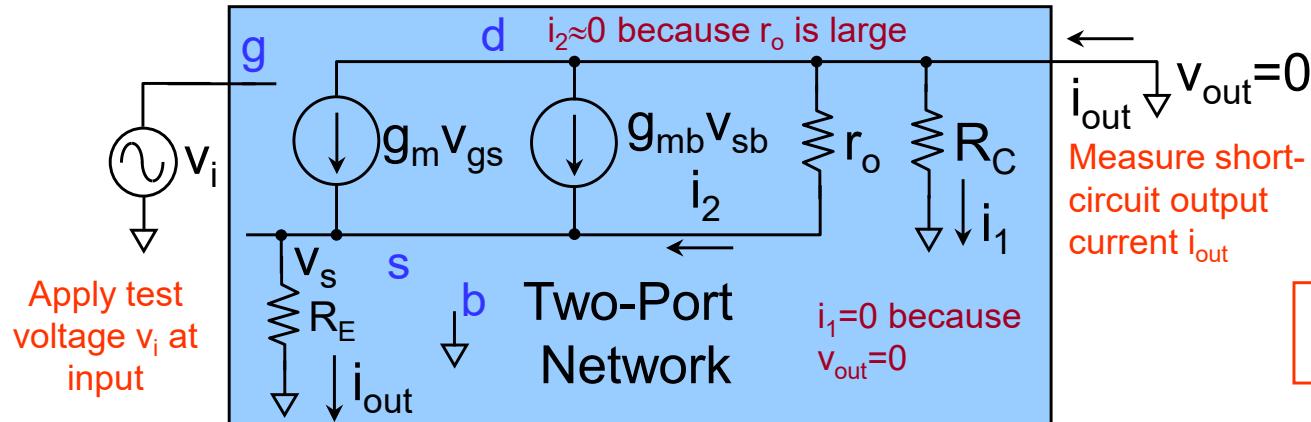CS with Source Degeneration – Two-Port Network (G_m) (Self Reading)



Eliminate v_s and keep v_i and i_{out}

$$G_m = \frac{i_{out}}{v_i} \Big|_{v_{out}=0}$$


$$\left\{ \begin{array}{l} v_s \approx i_{out} \Big|_{v_{out}=0} \times R_E \\ i_{out} \Big|_{v_{out}=0} \approx g_m v_{gs} + g_{mb} v_{sb} \\ \approx g_m (v_i - v_s) + g_{mb} v_s \end{array} \right.$$

$$\Rightarrow i_{out} \Big|_{v_{out}=0} \approx g_m v_i - (g_m - g_{mb}) i_{out} \Big|_{v_{out}=0} \times R_E$$

$$G_m = \frac{g_m}{1 + (g_m - g_{mb})R_E}$$

$$= 2 \text{ mA/V}$$

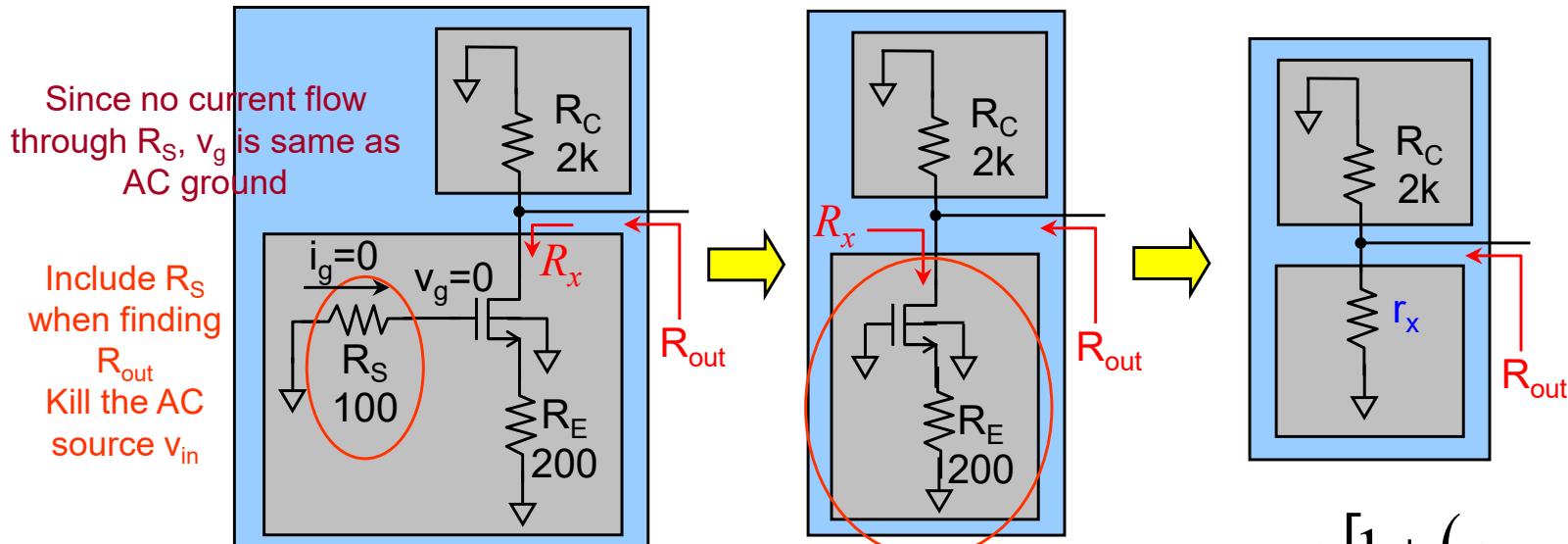CS with Source Degeneration – Two-Port Network (R_{out}) (Self Reading)



Any complicated network can be reduced to an equivalent resistance (AC analysis only)

Slide SSA1-47
CG

$$R_x = r_o [1 + (g_m - g_{mb}) R_E] \approx 100k$$

$$R_{out} = R_C / R_x \approx R_C = 2k$$

- Source side resistance helps boost up the transistor output resistance (R_x)
- Same as CG (slide SSA1-47)


CS with Degeneration – Important

1

Important Result :
Transconductance
 (G_m) is just
 $g_m/[1+(g_m-g_{mb})R_E]$


In normal CS,
 $G_m = g_m$

2

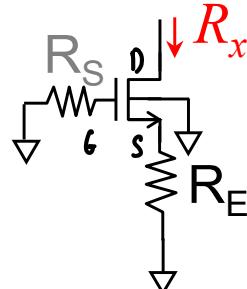


$$R_x \approx r_o [1 + (g_m - g_{mb}) R_E]$$

3

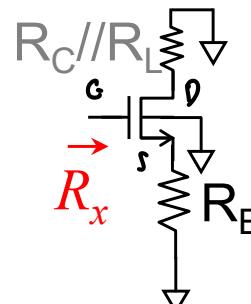


$$R_x = \infty$$

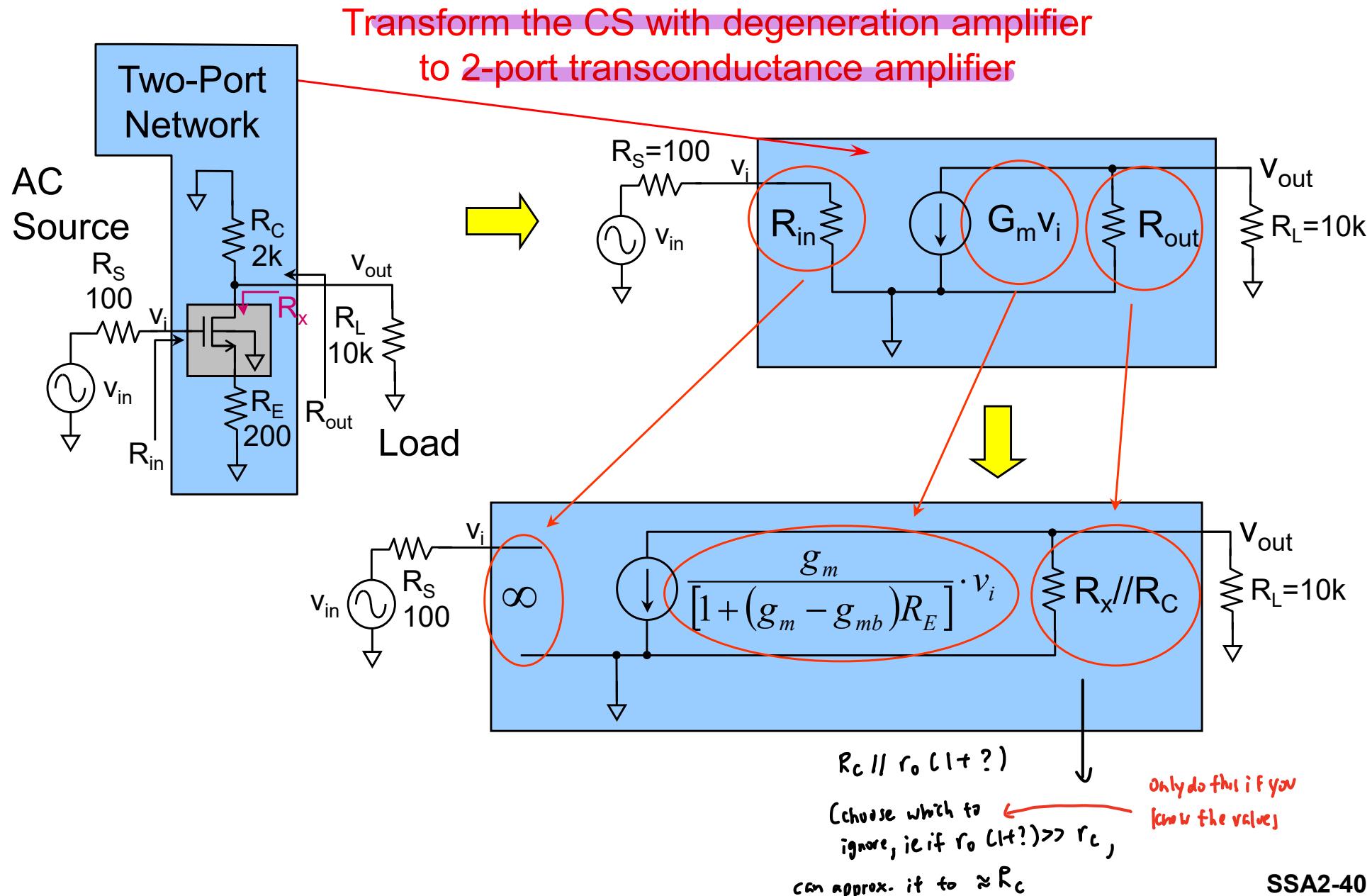CS with Source Degeneration – Two-Port Network



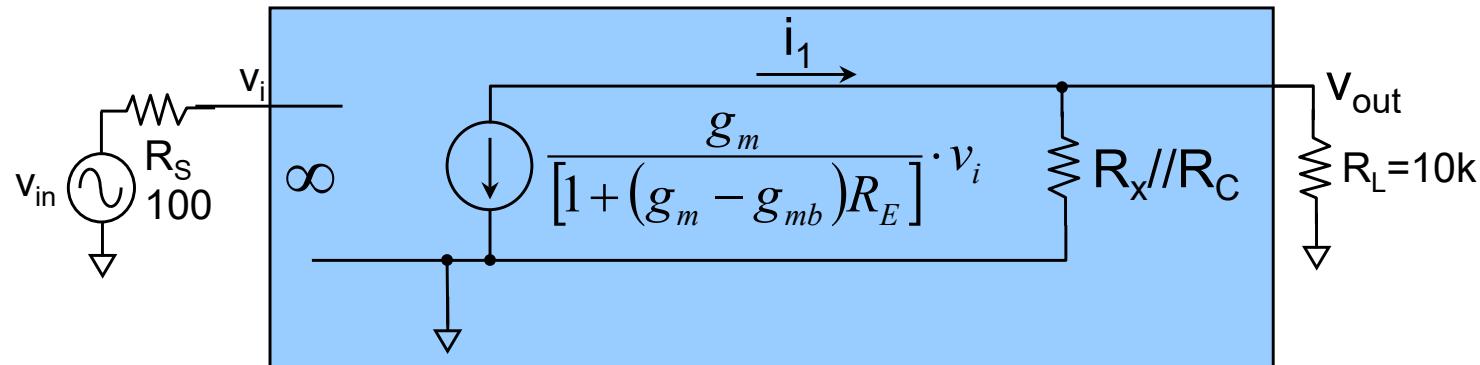CS with Source Degeneration – Two-Port Network (A_V)



$$v_i = v_{in} \quad i_1 = -\frac{g_m}{1 + (g_m - g_{mb})R_E} \times v_i$$

$$v_{out} = i_1 \times (R_{out} // R_L) = -\frac{g_m}{1 + (g_m - g_{mb})R_E} \times v_i \times (R_{out} // R_L)$$

$$\approx -v_{in} \times \frac{g_m}{1 + (g_m - g_{mb})R_E} \times [(R_C // R_x) // R_L]$$

$$\Rightarrow A_V \approx -\frac{g_m}{1 + (g_m - g_{mb})R_E} \times (R_C // R_L)$$

Characteristic of CE/CS with Emitter/Source Degeneration

- High input resistance
- High output resistance
- Lower Gain than CE/CS → to get better linearity
- Polarity inversion

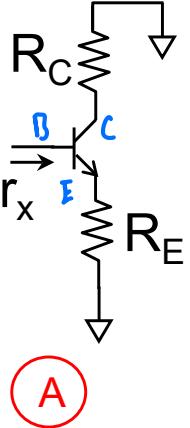
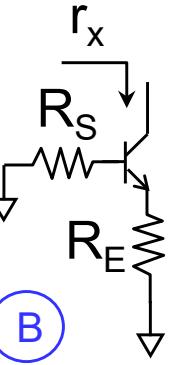
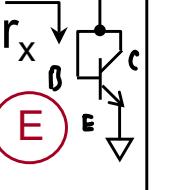
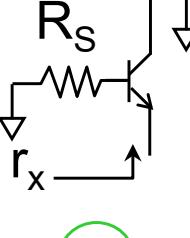
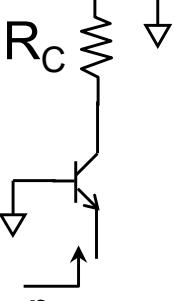
BJT Equivalent Resistance Summary

(Table 1)

Blue: look into collector terminal

Red: look into base terminal

Green: look into emitter terminal

Conf	r_x	Conf	r_x	Conf	r_x
 A	$r_\pi + (1 + \beta)R_E$ $\approx r_\pi (1 + g_m R_E)$ <p>If $R_E = 0$ $r_x = r_\pi$</p>	 B	$r_o \left\{ 1 + g_m [(r_\pi + R_S) // R_E] \left(\frac{r_\pi}{r_\pi + R_S} \right) \right\}$ <p>If $R_S = 0$ and $r_\pi \ll R_E$ $\Rightarrow r_{x,\max} = r_o (\beta + 1)$</p> <p>If $R_E = 0$, $r_x = r_o$</p>	 E	$\frac{1}{g_m}$
 C	$\frac{R_S + r_\pi}{1 + \beta} // r_o$ $\approx \frac{R_S}{1 + \beta} + \frac{1}{g_m}$ <p>If $R_S = 0$ $r_x \approx \frac{1}{g_m}$</p>	 D	$\frac{1}{g_m} \times \frac{r_o + R_C}{r_o + R_C // \beta}$ <p>If $R_C = 0$, $r_x \approx \frac{1}{g_m}$</p>		

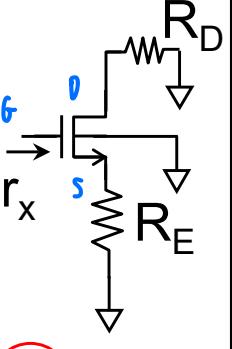
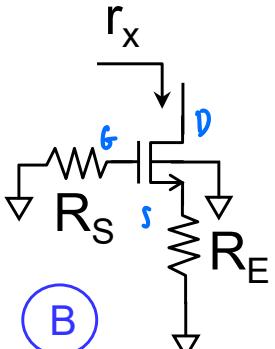
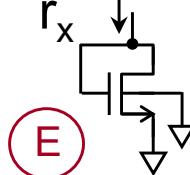
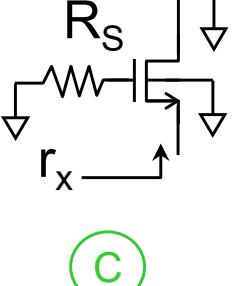
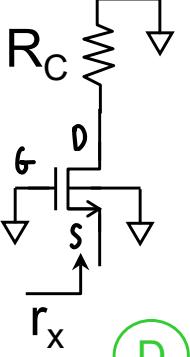
MOS Equivalent Resistance Summary

(Table 2) *

Blue: look into drain terminal

Red: look into gate terminal

Green: look into source terminal

Conf	r_x	Conf	r_x	Conf	r_x
 A	∞	 B	$r_o [1 + (g_m - g_{mb}) R_E]$ <i>If source and body shorted, $g_{mb} = 0$, no body effect</i> $If R_E = 0, r_x = r_0$	 E	$\frac{1}{g_m}$
 C	$\frac{1}{g_m - g_{mb}}$	 D	$\frac{1}{g_m - g_{mb}} \times \frac{r_o + R_C}{r_o}$ $If R_C = 0, r_x \approx \frac{1}{g_m - g_{mb}}$		

BJT Amplifier Configurations

(Table 3) * * * * *

BJT	G_m	A_v (gain)
CE Ⓐ	g_m	Derive Based on 2-port Network <i>transconductance</i> -ve
CB Ⓑ	$-g_m$	Derive Based on 2-port Network <i>transconductance</i> +ve
CC Ⓒ	Too Complex To Be Useful <i>Two port voltage</i>	$\frac{g_m R_L}{1 + g_m R_L}$ <i>voltage amplifier</i> +ve
CE with Degeneration (R_E) Ⓓ	$\frac{g_m}{1 + g_m R_E}$	Derive Based on 2-port Network <i>transconductance</i> -ve



MOS Amplifier Configurations (Table 4)

MOS	G_m	A_v
CS Ⓐ	g_m	Derive Based on 2-port Network <i>transconductance</i>
CG Ⓑ	$-(g_m - g_{mb})$ <i>Drop g_{mb} if no body effect</i>	Derive Based on 2-port Network <i>transconductance</i>
CD Ⓒ	Too Complex To Be Useful	$\frac{g_m R_L}{1 + (g_m - g_{mb}) R_L} \approx \frac{g_m}{g_m - g_{mb}}$ <i>Drop g_{mb} if no body effect</i> <i>voltage amplifier</i>
CS with degeneration (R_E) Ⓓ	$\frac{g_m}{1 + (g_m - g_{mb}) R_E}$ <i>Drop g_{mb} if no body effect</i>	Derive Based on 2-port Network <i>transconductance</i>

Effect of Capacitors

Consider CB amplifier example ([Slide SSA1-50](#)):

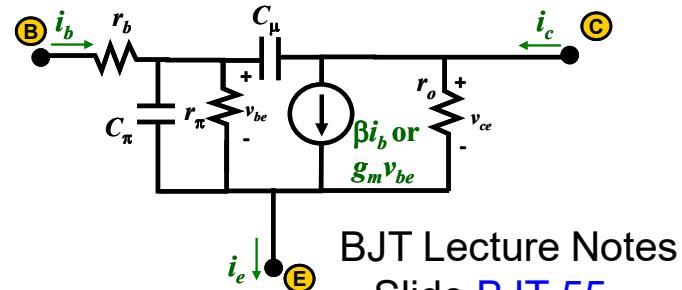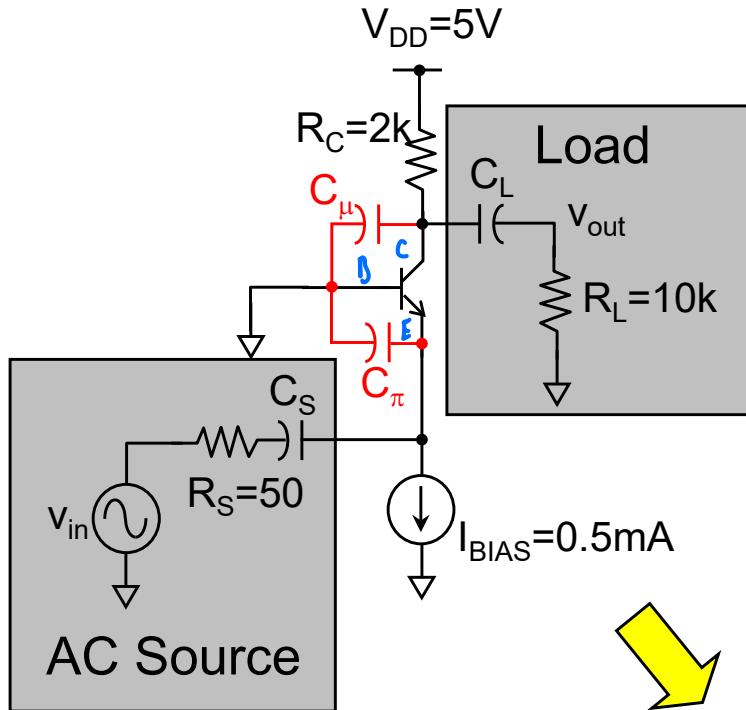- C_L and C_S are external capacitors added to the circuit, they are usually large ($\sim \mu\text{F}$ range)
- C_μ and C_π are **parasitic** capacitors inherent to BJT, they are usually small ($\sim \text{pF}$ range)




	Low freq ($\rightarrow \text{DC}$)	Mid freq	High freq
C_S, C_L	Open	Short	Short
C_μ, C_π	Open	Open	Short

Audio : $<20\text{kHz}$


Video : $<6\text{MHz}$

RF : $\sim \text{GHz}$

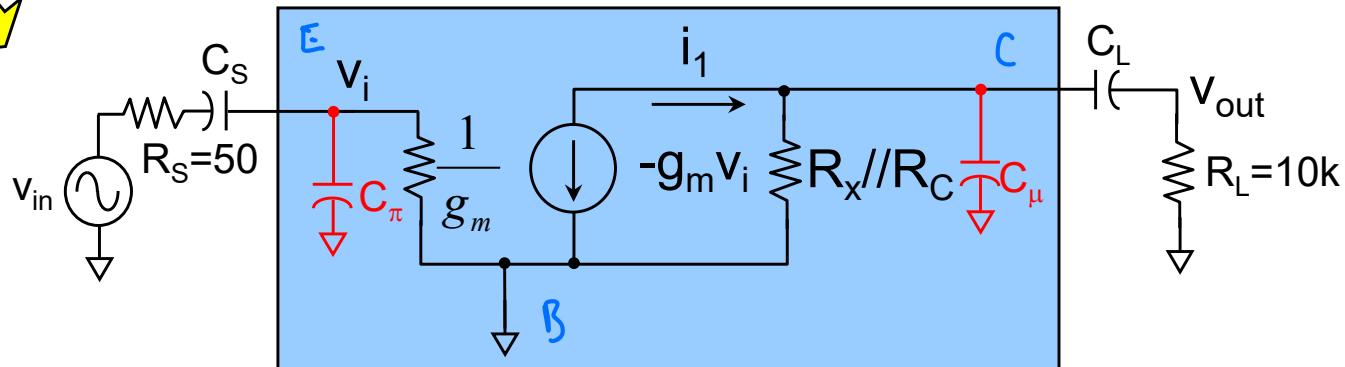


Effect of Capacitors

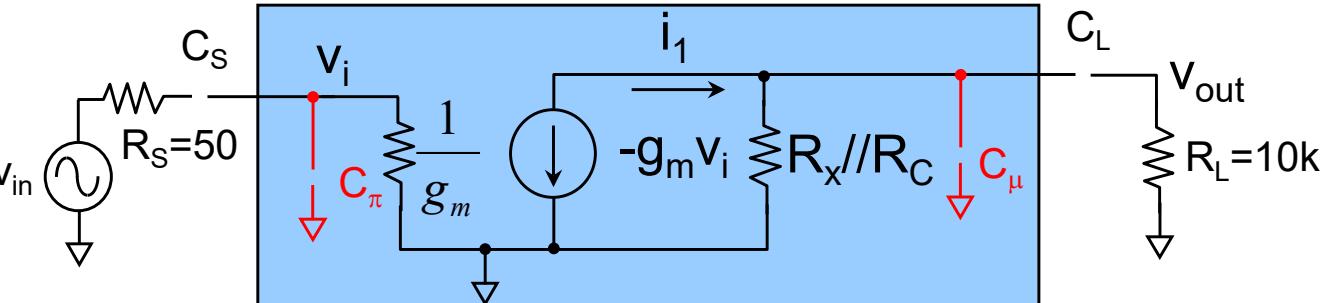
At low frequency,
 $C_S, C_L, C_\mu, C_\pi \rightarrow$ open circuit
 v_{out} isolated from $v_{in} \Rightarrow v_{out} = 0$



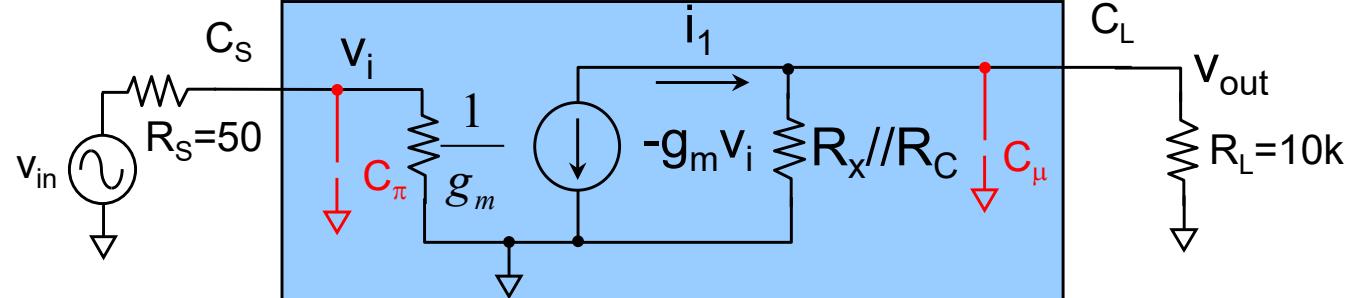
At mid frequency,
 $C_S, C_L \rightarrow$ short circuit
 $C_\mu, C_\pi \rightarrow$ open circuit
 $2\text{-port network} \Rightarrow v_{out} = A_V \times v_{in}$



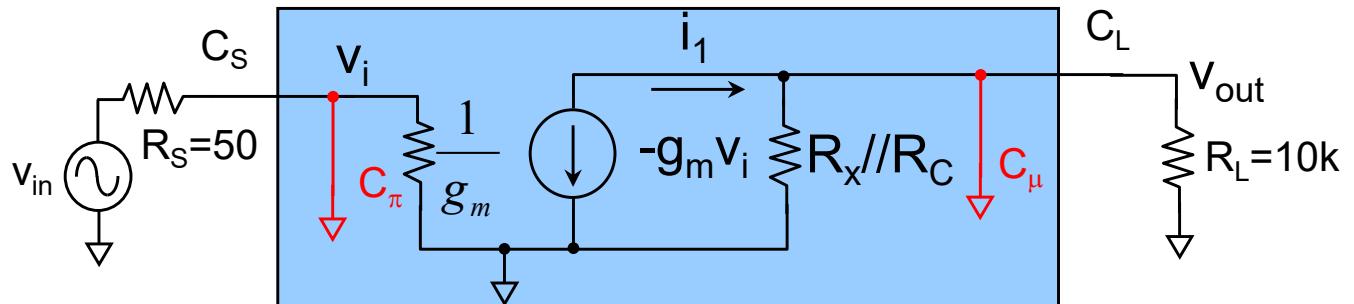At high frequency,
 $C_S, C_L \rightarrow$ short circuit
 $C_\mu, C_\pi \rightarrow$ short circuit
 v_{in} and v_{out} short to ground
 $\Rightarrow v_{out} = 0$



Frequency Response

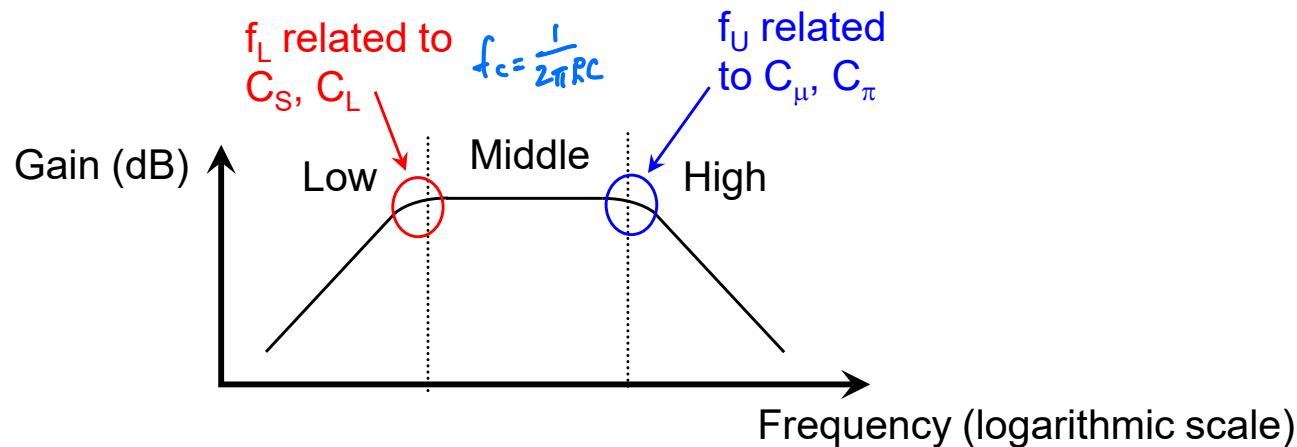

- C_S and C_L cause the gain to drop at low frequency due to open circuit at low frequency.
- C_μ and C_π cause the gain to drop at high frequency due to short circuit at high frequency.
- At the mid frequency, C_S and C_L are short circuit whereas C_μ and C_π are open circuit. The amplifier behaves like 2-port network with gain.
- The lower cut-off point (f_L), i.e., the frequency below which the gain starts to drop is related to RC time constant related to C_S and C_L .
- The upper cut-off point (f_U), i.e. the frequency above which the gain starts to drop is related to RC time constant related to C_μ and C_π .

Definition of Decibel


Decibel (dB)[Power Ratio]

$$Y(dB) = 10 \times \log\left(\frac{P_{out}}{P_{in}}\right) = 10 \times \log(|\text{Power Gain}|)$$

Decibel (dB)[Voltage Ratio]


$$Y(dB) = 20 \times \log\left(\frac{V_{out}}{V_{in}}\right) = 20 \times \log(|\text{Gain}|)$$

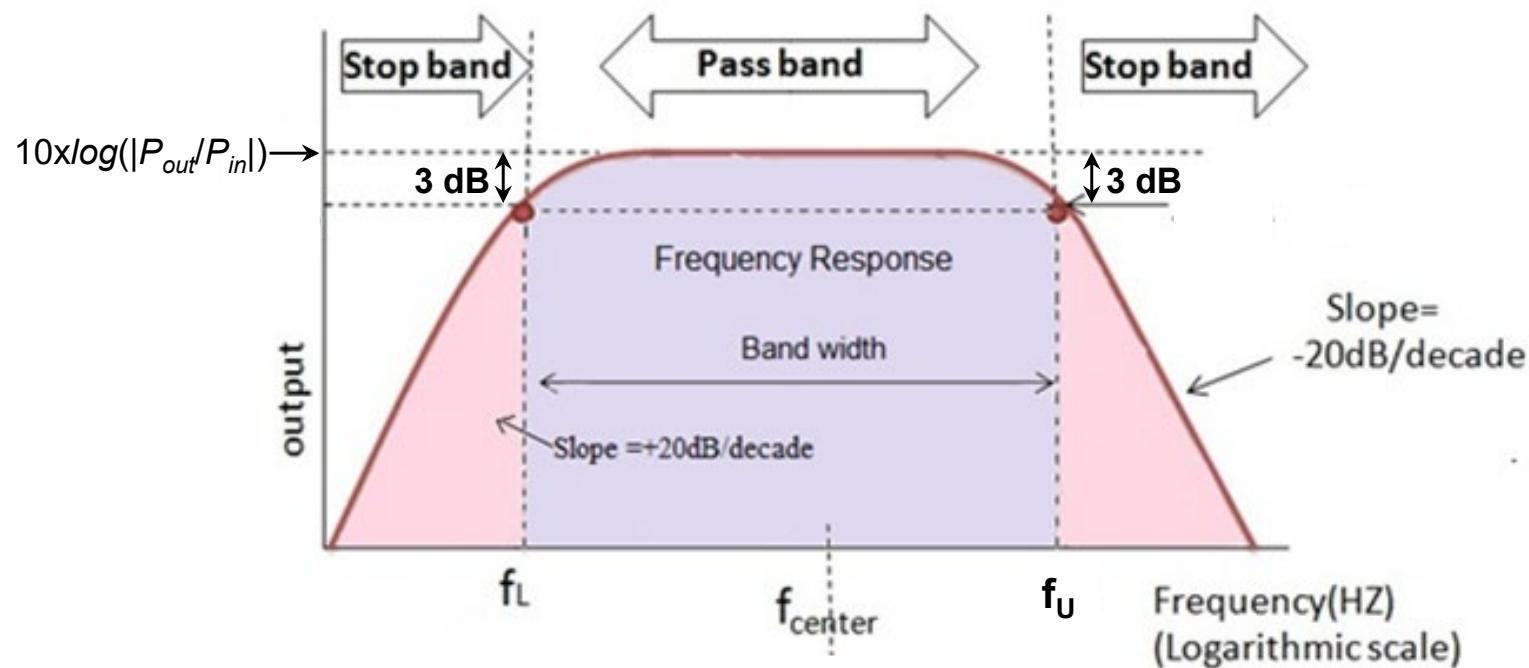Half-power point of an electronic amplifier is the frequency at which the output power has dropped to half of its mid-band value (equivalent to a drop of 3 dB). The half-power point is a commonly used definition of cut-off frequency (see slides 1-30 & 1-31)




Ideal versus Non-ideal Current Source


Ideal Current Source

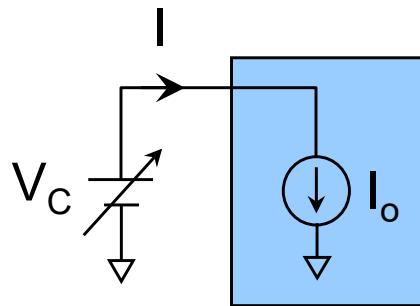

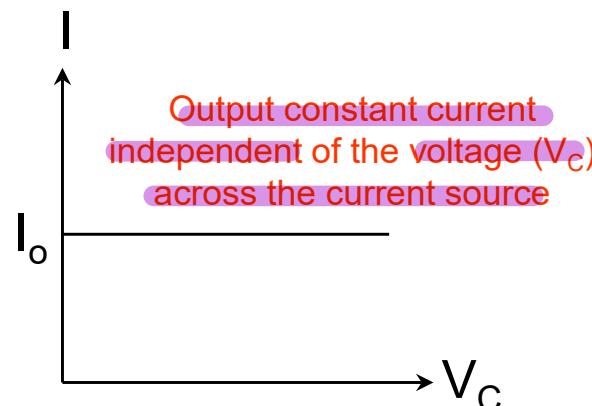
Ideal current source is simply a parallel combination of ideal current source (I_o) with infinite output resistance (∞)





Non-ideal Current Source

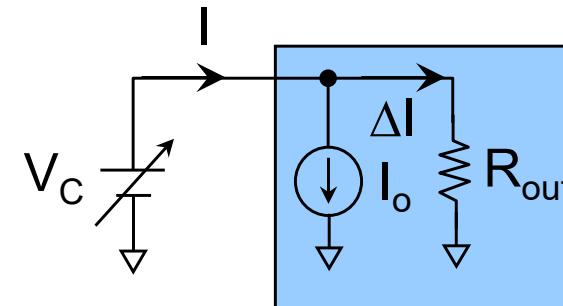

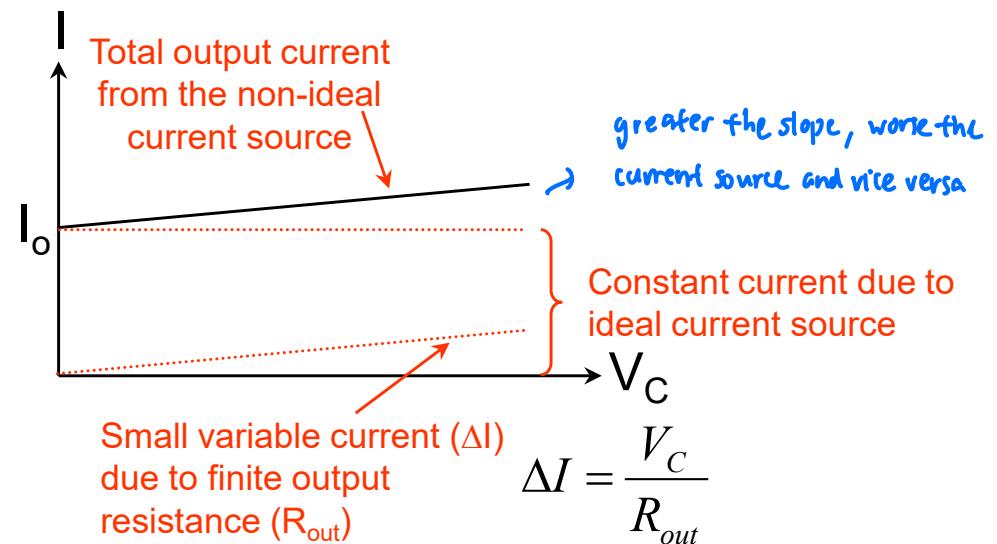Non-ideal current source is simply a parallel combination of ideal current source (I_o) with finite output resistance (R_{out})




Transistor as Current Source

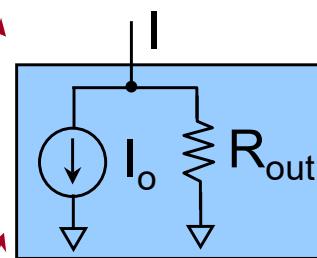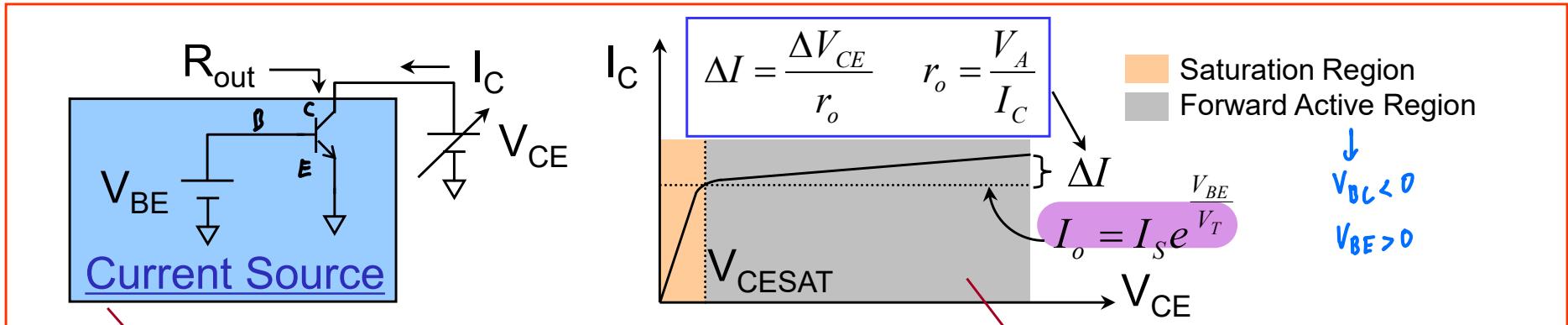


$R_{out} = r_o = V_A / I_C$ for BJT
 transistor current source
 $R_{out} = r_o = 1 / (\lambda I_D)$ for MOS
 transistor current source

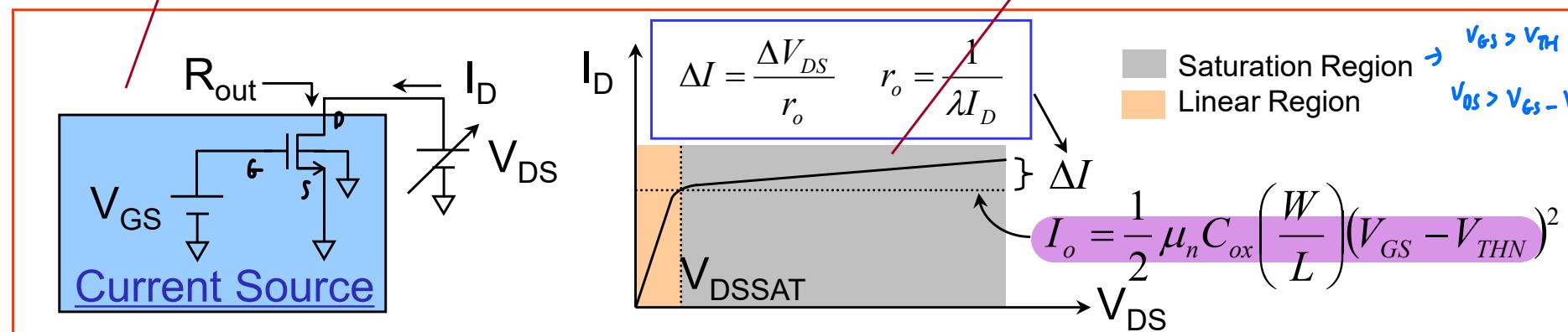Transistor with voltage bias behaves very similarly to non-ideal current source as long as it operates in GRAY region




BJT Current Mirror

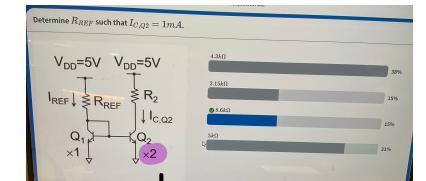


$I_{C_2,Q_2} = I_m A$, since 2 times of α_1 , $I_{C_1,Q_1} = 0.5mA$
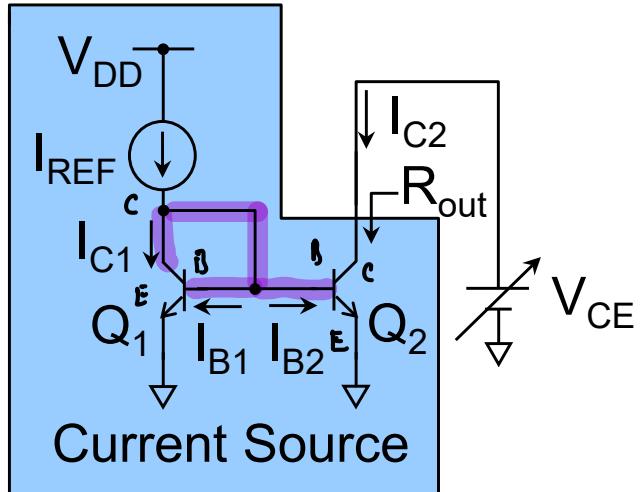
$$I_{ref}(1.5m) = \frac{5 - V_{BE}}{R_{ref}} = \frac{5 - 0.7}{0.5k} = 8.6k$$



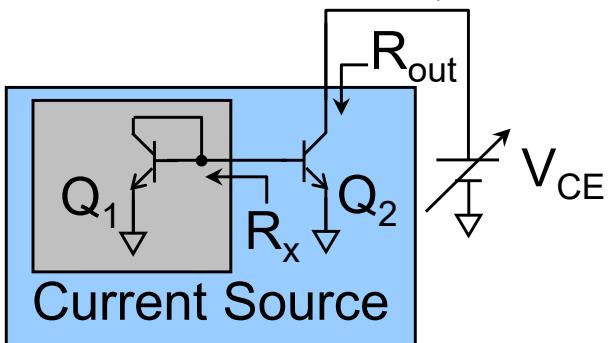AC Analysis
(Current source open circuit)



Determine DC Biasing

$$I_{REF} = I_{C1} + I_{B1} + I_{B2}$$

$$\because V_{BE1} = V_{BE2} \rightarrow I_C = I_s e^{\frac{V_{BE}}{V_T}}$$

$$\Rightarrow I_{B1} = I_{B2} = \frac{I_{C1}}{\beta}$$

$$\Rightarrow I_{C2} \approx I_{C1} \approx \frac{\beta}{\beta + 2} I_{REF}$$


Determine AC small signal parameters

$$g_{m1} = g_{m2} = \frac{I_C}{V_T}$$


$$R_{out} = r_o = \frac{V_A}{I_C}$$

I_{C2} not exactly equal to I_{REF} due to finite current gain β


Look-up Table 1

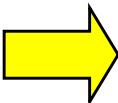

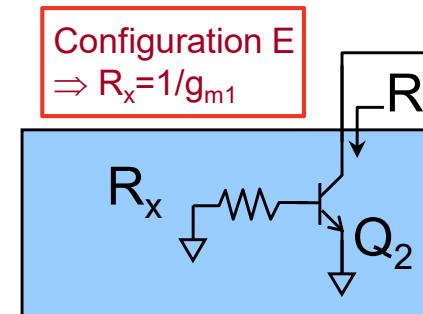
Configuration E
 $\Rightarrow R_x = 1/g_{m1}$



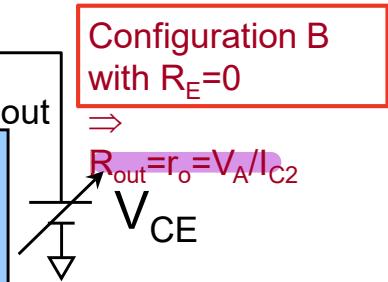Configuration B with $R_E=0$
 $\Rightarrow R_{out} = r_o = V_A/I_{C2}$



BJT Current Mirror

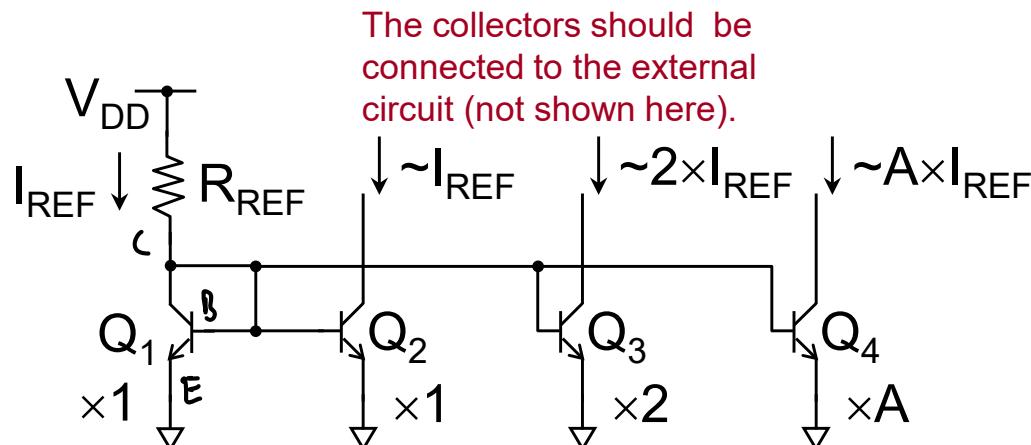

Because all BJTs share the same V_{BE} , the transistor currents are proportional to their corresponding area ratio

$$I_{REF} = \frac{V_{DD} - V_{BE}}{R_{REF}}$$

I_{REF} can be obtained easily through a resistor

$$I_{C1} \approx I_{REF} = J_S e^{\frac{V_{BE}}{V_T}} \times \text{Area}^*$$

$$I_{C2} \approx I_{C1} \quad I_{C3} \approx 2 \times I_{C1}$$


$$I_{C4} \approx A \times I_{C1}$$

- Using same V_{BE} created from the reference branch, different current sources can be created by laying out different area of BJT
- The current source current is not identical to I_{REF} due to:
 - Finite current gain β
 - Finite output resistance r_o and different V_{CE} from the reference branch


*Area refers to the cross-sectional area of the BJT active region (i.e., base-emitter junction), see BJT notes, slide BJT-2.

* J_S is the Saturation current density of BJT = I_S / Area

MOS Current Mirror

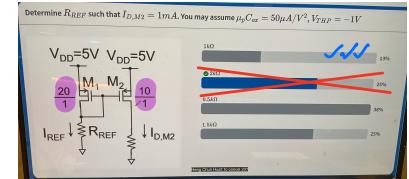

$I_{D, M1}$ have to be 2times bigger,
 $2mA = \frac{1}{2} \mu_p C_{ox} \left(|V_{GS}| - |V_{TH}| \right)^2$
 $\Rightarrow \left(|V_{GS}| - |V_{TH}| \right)^2 = 2 \cdot |V_{GS}| - |V_{TH}|$
 $|V_{GS}| = J$

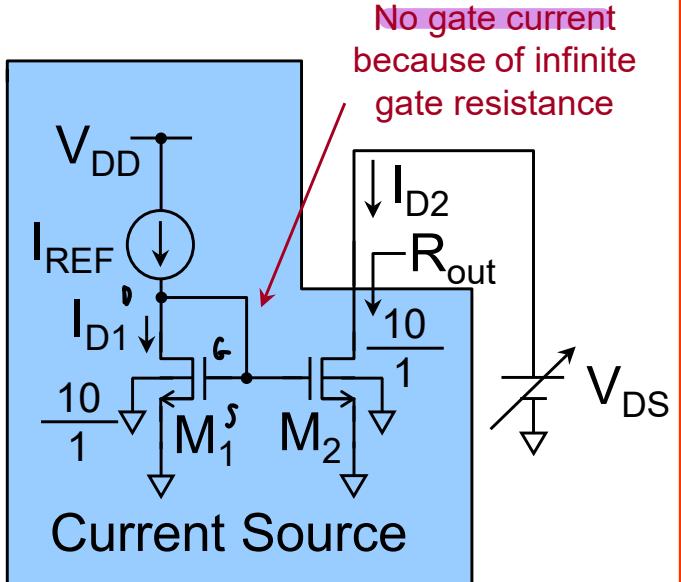

Determine DC Biasing

$$I_{REF} = I_{D1}$$

$$\because V_{GS1} = V_{GS2}$$

$$\Rightarrow I_{D1} = I_{D2} = I_{REF}$$



Determine AC small signal parameters

$$g_{m1} = g_{m2}$$

$$= \sqrt{2\mu_n C_{ox} \left(\frac{10}{1} \right) I_{D1}}$$


$$R_{out} = r_o = \frac{1}{\lambda I_{D2}}$$

AC Analysis

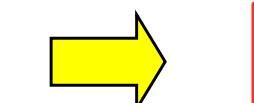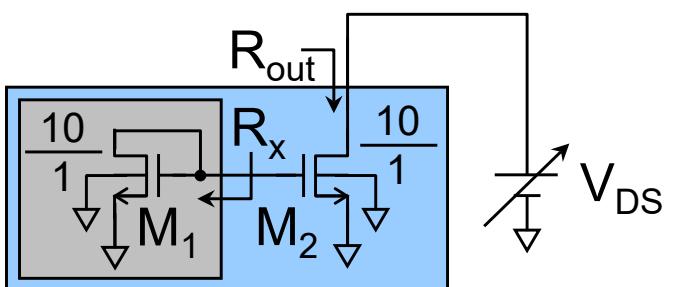


Configuration E
 $\Rightarrow R_x = 1/g_{m1}$

Look-up Table 2

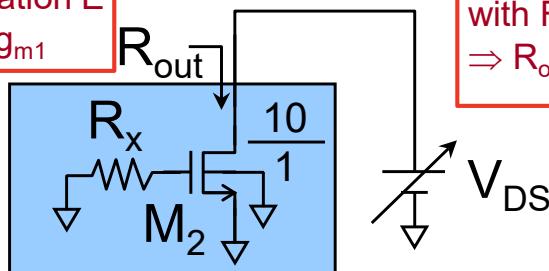

Configuration B with $R_E=0$
 $\Rightarrow R_{out} = r_o = 1/\lambda I_{D2}$

MOS Current Mirror

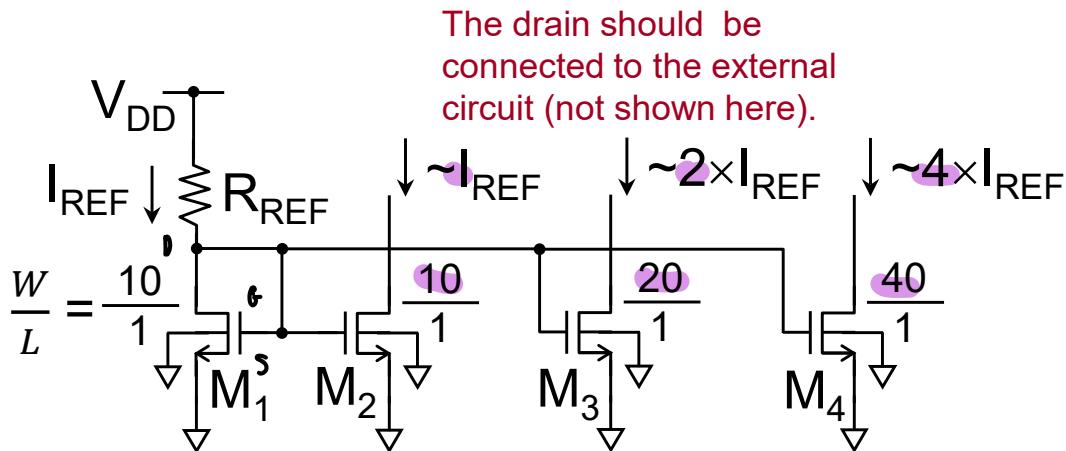

Because all MOSFETs share the same V_{GS} , the transistor currents are proportional to their corresponding sizing ratio

$$I_{REF} = \frac{V_{DD} - V_{GS}}{R_{REF}}$$

I_{REF} can be obtained easily through a resistor

$$I_{D1} = I_{REF}$$
$$= \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_{M1} (V_{GS} - V_{THN})^2$$

$$I_{D2} = I_{D1} \quad I_{D3} = 2 \times I_{D1} \quad I_{D4} = 4 \times I_{D1}$$

- Using same V_{GS} created from the reference branch, different current sources can be created by laying out different sizing (e.g., w/L) of MOS transistors
- The current source current is not identical to I_{REF} due to finite output resistance r_o and different V_{DS} from the reference branch


EE2027 Electronic Circuits

Multi-Stage Amplifier

Lecture Outline

- Multi-Stage Amplifier Analysis Concept**

Old Ways of Analyzing Circuits


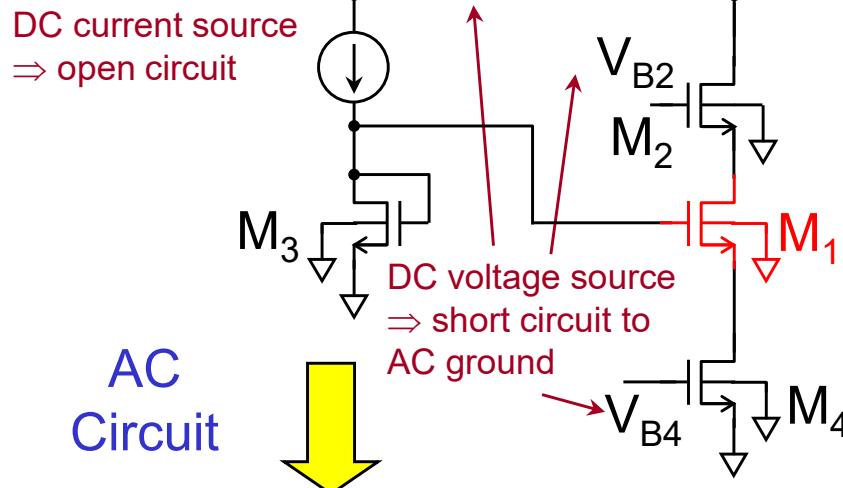


$$v_{g,M1} = v_{gs,M3} = -g_{m,M3} v_{gs,M3} \times r_{o,M3} \dots (1)$$

$$v_{s,M1} = v_{ds,M4} = (i_{d,M1} - g_{m,M4} v_{gs,M4}) \times r_{o,M4} \dots (2)$$

⋮

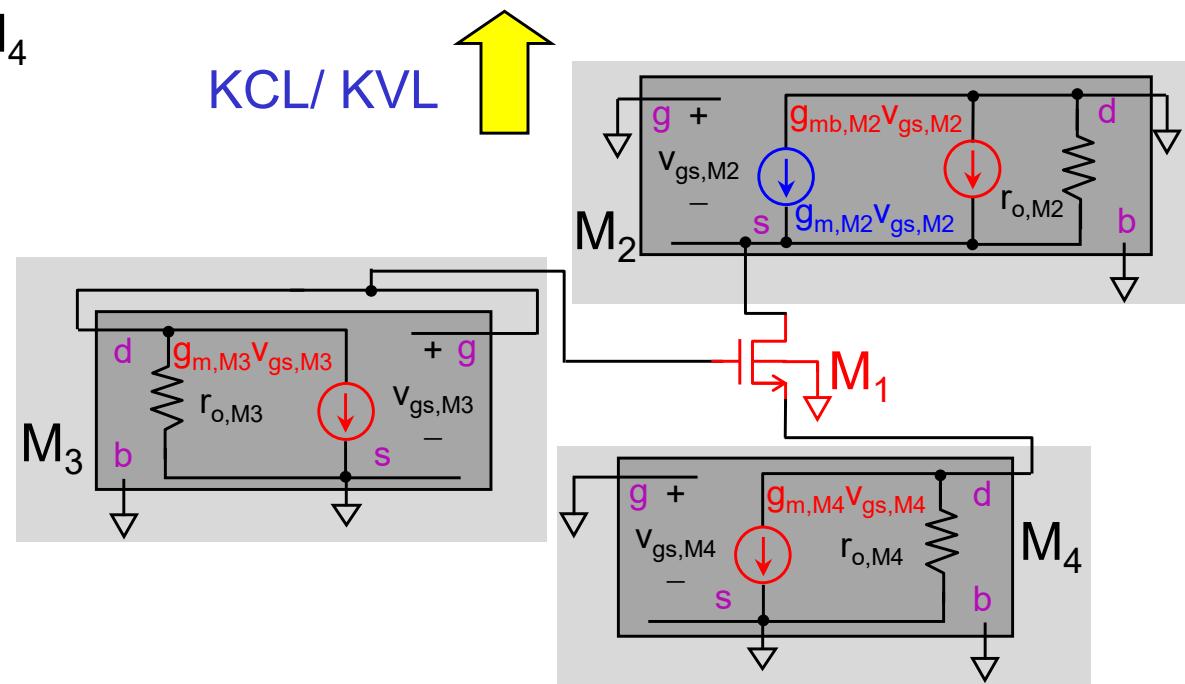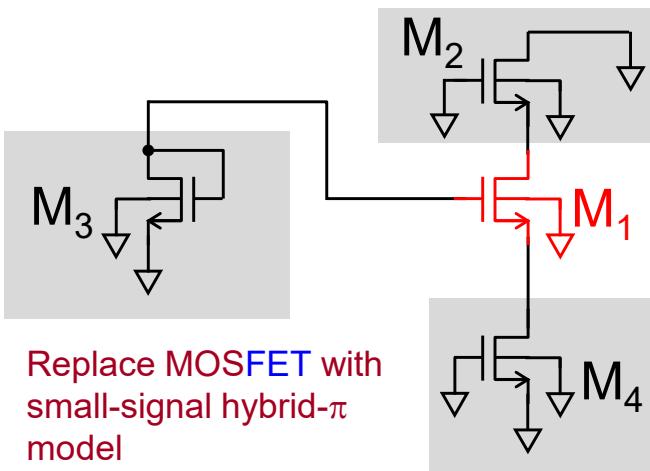Tedious simultaneous algebra and difficult to solve with number of transistors > 2



AC Analysis of Complicated Circuit


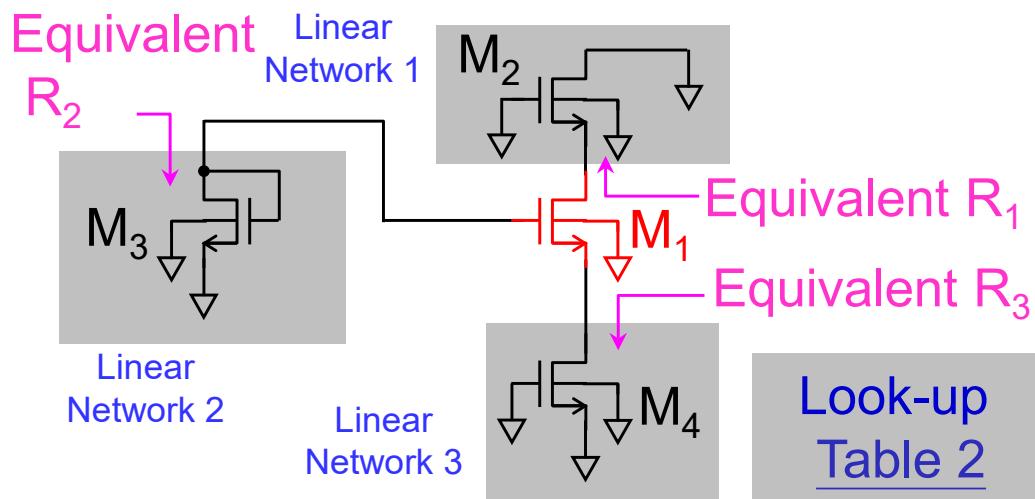
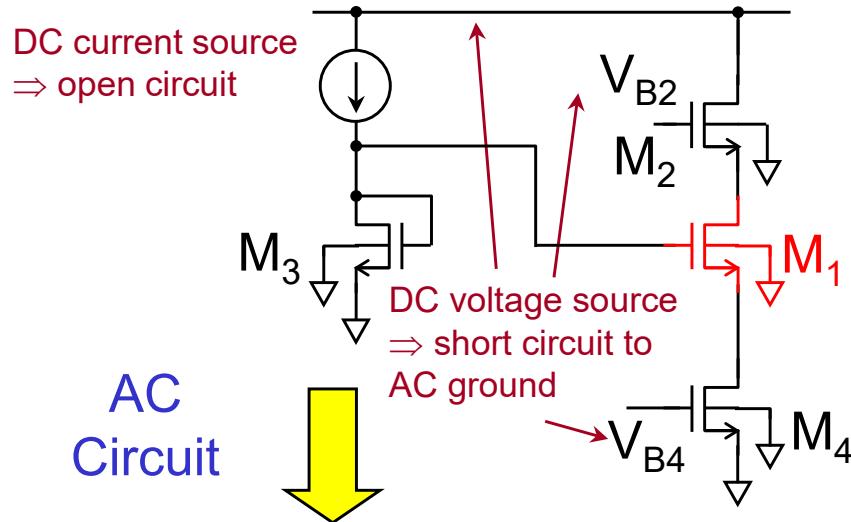


Table 2
configuration C
with $R_S=0$
 $\Rightarrow 1/(g_{m2}-g_{mb2})$

Table 2
configuration E
 $\Rightarrow 1/g_{m3}$



Table 2
configuration B
with $R_E=0$
 $\Rightarrow r_{o4}=1/(\lambda I_{D4})$

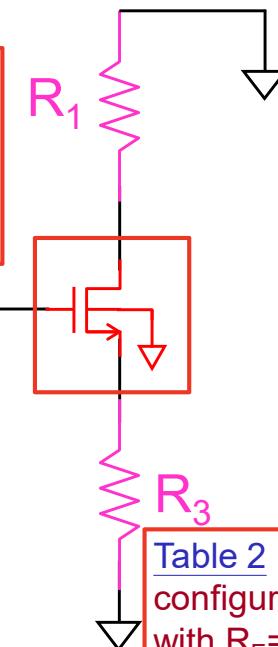Identify familiar transistor configurations and apply formula directly for the equivalent resistance





Multi-Stage Amplifier

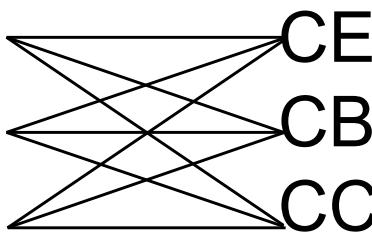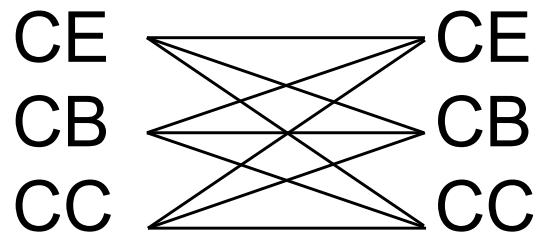Multi-stage amplifier is cascade of single-stage amplifiers-



...

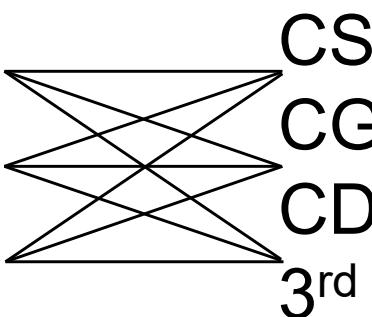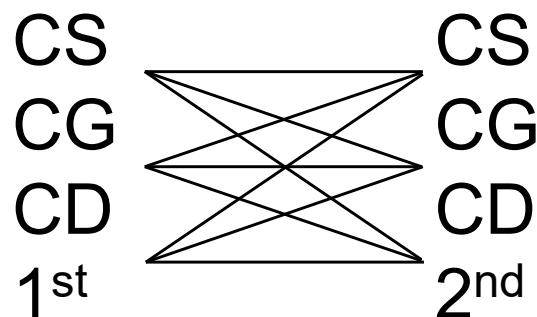1. We can mix the usage of BJT or MOS amplifier
2. We can extend by more than 3 stages
3. CE/CS with degeneration can also be used.




...

How many combinations can we have?

Why multi-stage?


- To modify R_{in} , R_{out} or the overall gain

Steps for Multi-Stage Amplifier Analysis

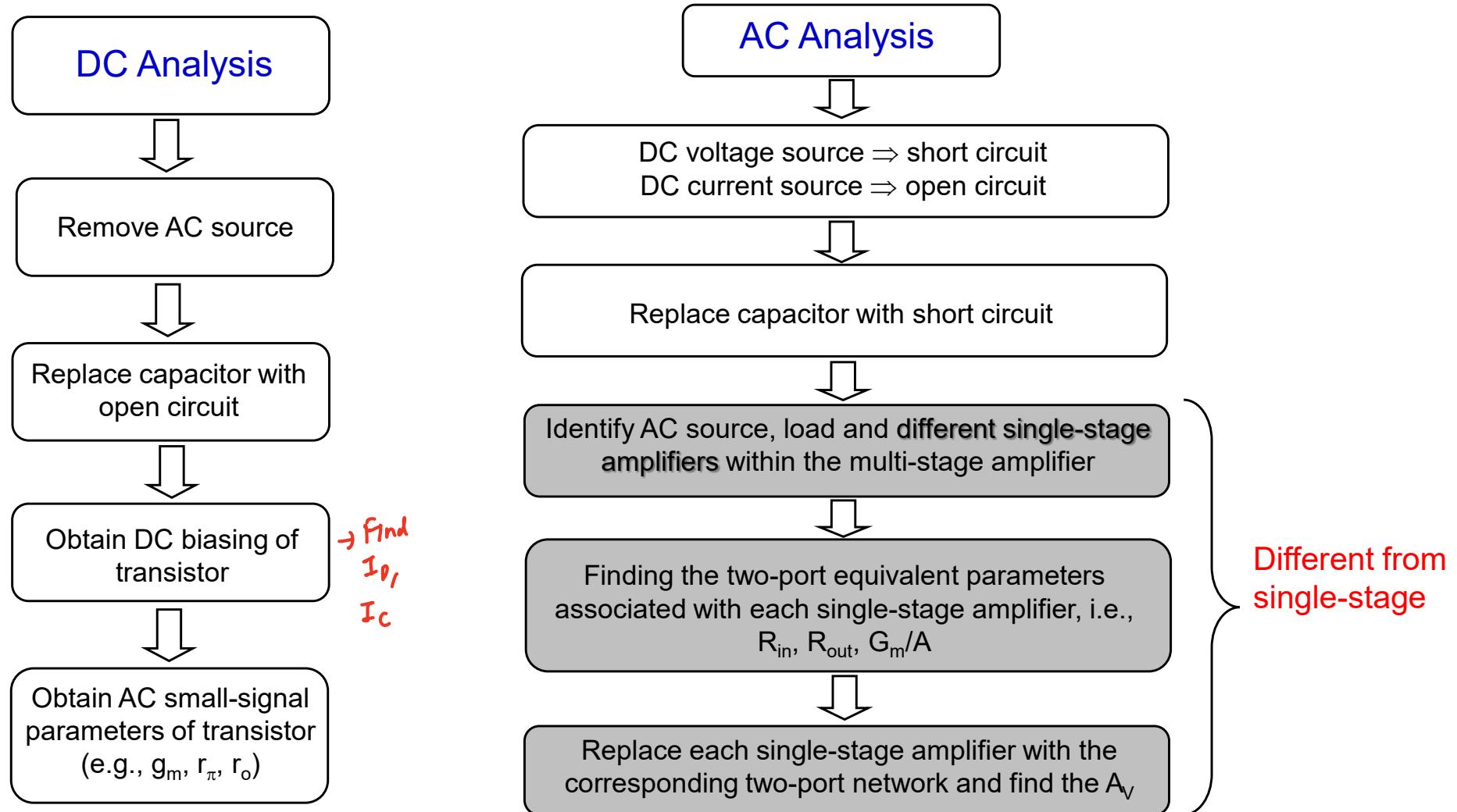


Compare above with slide SSA1-13 for steps for single-stage amplifier analysis

Steps for Two-Stage Amplifier Analysis

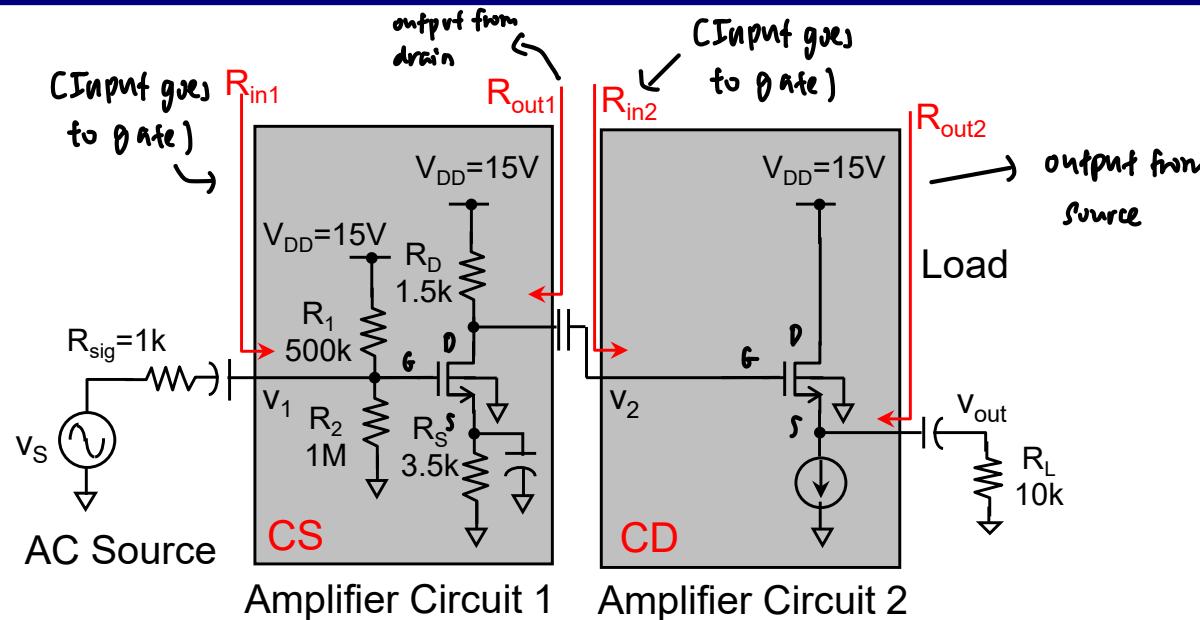

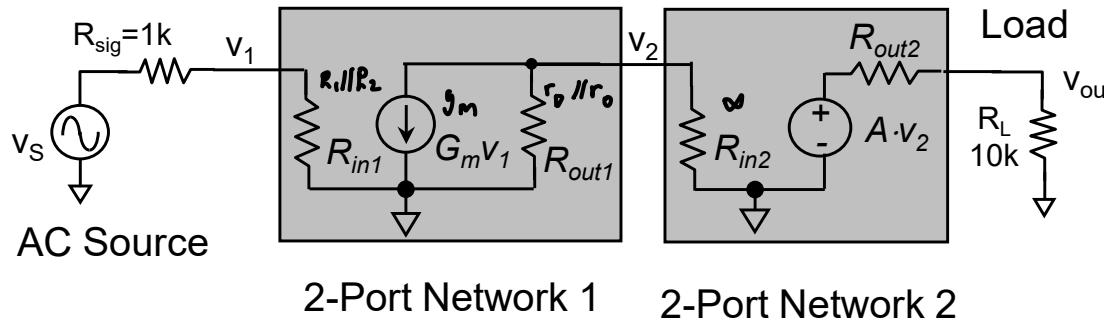Easier to analyze complicated circuit (e.g., multi-stage amplifier) as each amplifier is simplified to its equivalent 2-port network.




$$A_V = \frac{V_{out}}{V_s} = \frac{V_1}{V_s} \times \frac{V_2}{V_1} \times \frac{V_{out}}{V_2}$$

N.B. R_{in1} includes the contribution of Amplifier Circuit 2, and R_{out2} includes the contribution of Amplifier Circuit 1.

How about >2 Stage?

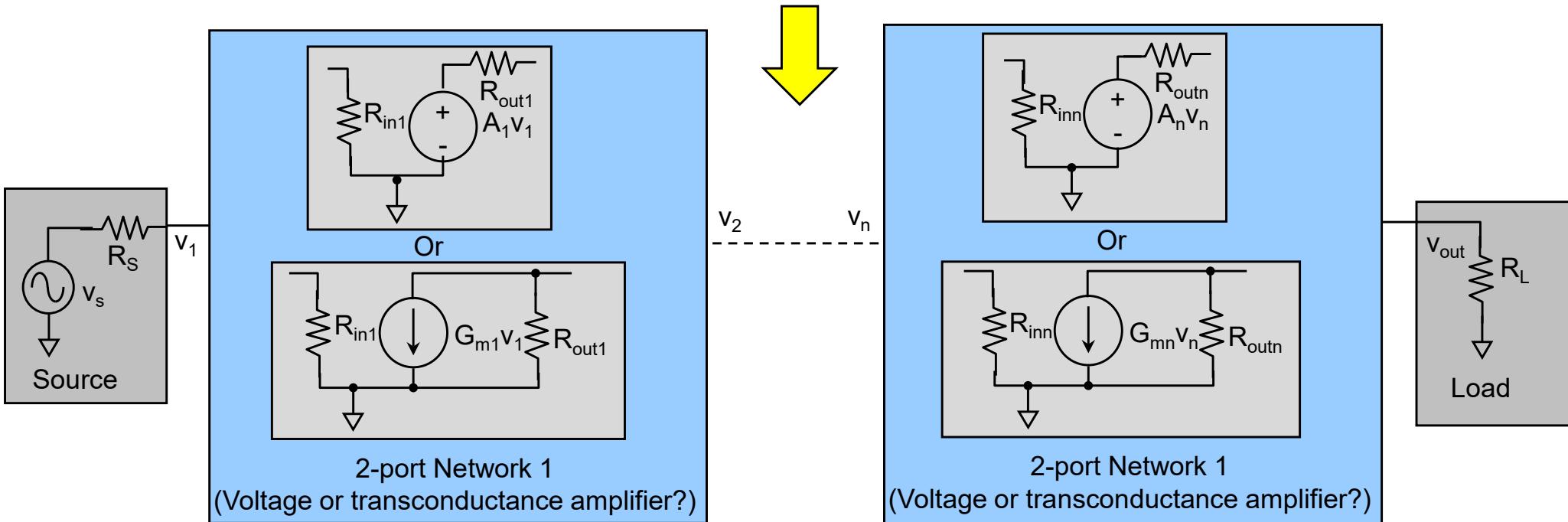
1. Transform into AC equivalent circuit
2. Identify signal path (Source to Load)
3. Identify transistors that get cut across by signal path
4. Determine the number of single-stages
5. Identify the amplifier configuration
6. Replace each stage by its 2-port network equivalent



$$\frac{V_{out}}{V_s} = \frac{V_1}{V_s} \times \frac{V_2}{V_1} \times \dots \times \frac{V_n}{V_{n-1}}$$

How about Amplifier Design?

Amplifier Analysis

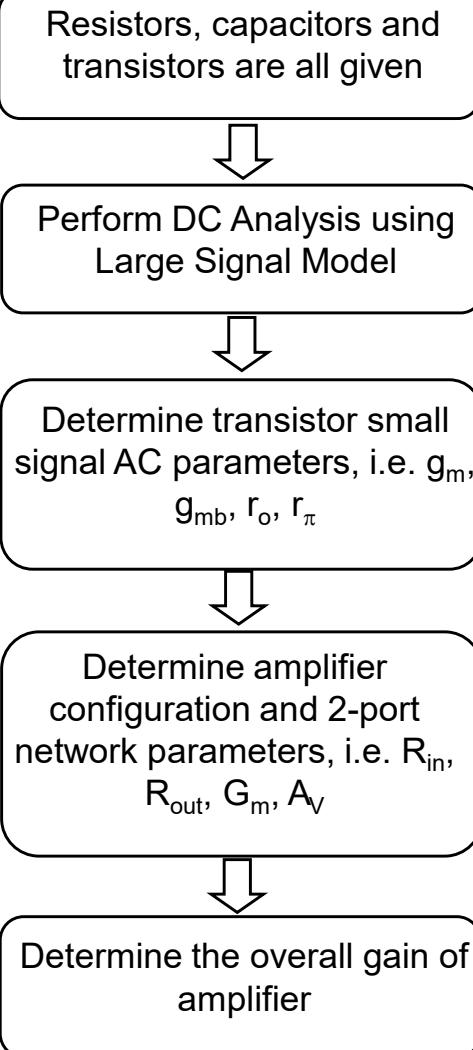

Amplifier Design

