

**NATIONAL UNIVERSITY OF SINGAPORE**  
**Department of Electrical and Computer Engineering**

**EE2027 Electronic Circuits**  
**Tutorial 2: Solution**

- Unless otherwise stated, you may assume temperature,  $T = 300$  K; thermal voltage,  $V_T = 0.025$  V and make use of the equations given in the lecture notes directly, without having to derive them.
- All the symbols are as defined in the lecture notes.

**Homework 2:**

**Homework 2 has 1 question, Question 4 of Tutorial 2. You will need to submit a softcopy of your handwritten homework to the Canvas folder: Home>Homework Assignments>HW2 half an hour after class (i.e., latest by 12.30 pm) on Thursday, 19 September 2024.**

**The softcopy submission of your homework must be in PDF format and in a single file. Name your file following the convention “Your\_Name\_HW2.pdf”. Failing to do that will mean zero mark for homework.**

**Homework questions will not be discussed in class.**

**Q1.**

- To amplify input signal of  $v_I(t) = 0.01 \times \sin(2\pi \times 10\text{kHz} \times t)$  using an inverting amplifier with gain of -10, determine the minimum required GBW for the opamp. (3 marks)
- To amplify input signal of  $v_2(t) = 0.1 \times \sin(2\pi \times 500\text{kHz} \times t)$  using an inverting amplifier with gain of -10, determine the minimum required GBW for the opamp. (3 marks)
- You are given only **one** opamp A with GBW of 200 kHz and **two** opamp B with GBW of 8 MHz. Design an opamp circuit that will give an output voltage of  $v_{out}(t) = 0.1 \times \sin(2\pi \times 10\text{kHz} \times t) + 1 \times \sin(2\pi \times 500\text{kHz} \times t)$  with the two input signals from (a) and (b). (7 marks)
- You are given only **one** opamp A with GBW of 200 kHz and **two** opamp B with GBW of 8 MHz. Design an opamp circuit that will give an output voltage of  $v_{out}(t) = 1 \times \sin(2\pi \times 10\text{kHz} \times t) + 1 \times \sin(2\pi \times 500\text{kHz} \times t)$  with the two input signals from (a) and (b). (7 marks)

**Q1: Solution**

- (a) To amplify input signal of  $v_I(t) = 0.01 \times \sin(2\pi \times 10\text{kHz} \times t)$  using an inverting amplifier with gain of -10, determine the minimum required GBW for the opamp.

$$f_{3dB,CL} = GBW \times \frac{R_1}{R_1 + R_2} \Rightarrow GBW = f_{3dB,CL} \times 11 = 110 \text{ kHz}$$

The opamp needs to have GBW of at least 110 kHz.

**(3 marks)**


- (b) To amplify input signal of  $v_2(t) = 0.1 \times \sin(2\pi \times 500\text{kHz} \times t)$  using an inverting amplifier with gain of -10, determine the minimum required GBW for the opamp.

$$f_{3dB,CL} = GBW \times \frac{R_1}{R_1 + R_2} \Rightarrow GBW = f_{3dB,CL} \times 11 = 5.5 \text{ MHz}$$

The opamp needs to have GBW of at least 5.5 MHz.

**(3 marks)**

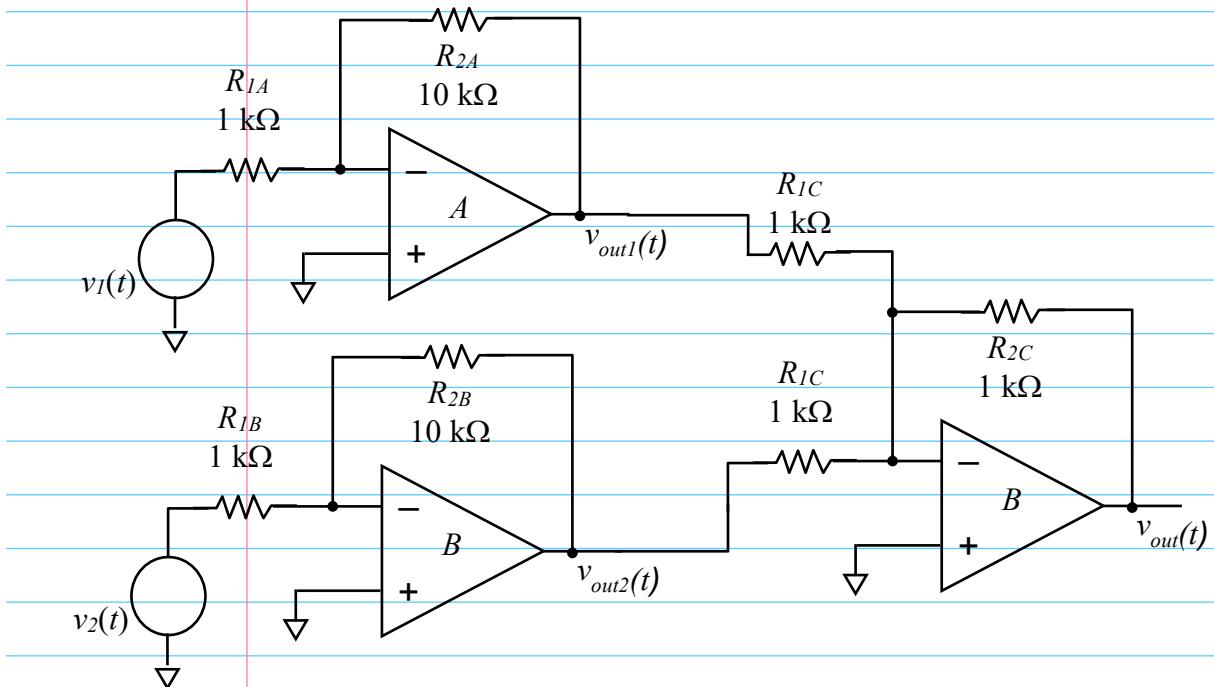- (c) You are given only **one** opamp A with GBW of 200 kHz and **two** opamp B with GBW of 8 MHz. Design an opamp circuit that will give an output voltage of  $v_{out}(t) = 0.1 \times \sin(2\pi \times 10\text{kHz} \times t) + 1 \times \sin(2\pi \times 500\text{kHz} \times t)$  with the two input signals from (a) and (b).




The first inverting amplifier using opamp A (lower GBW) with gain of -10 will give  $v_{out1}(t) = -0.1 \times \sin(2\pi \times 10\text{kHz} \times t)$ . Opamp B (higher GBW) should not be used here as it will be wasted. Opamp B (whose quantity is limited to only two pieces) is required for other parts of the circuit involving a higher frequency (i.e., 500 kHz) input signal to meet the GBW requirement.

The second inverting amplifier using opamp B (higher GBW) with gain of -10 will give  $v_{out2}(t) = -1 \times \sin(2\pi \times 500\text{kHz} \times t)$ . Opamp A cannot be used due to its lower GBW.

The third summing amplifier using opamp B (higher GBW) with gain of -1 will give  $v_{out}(t) = 0.1 \times \sin(2\pi \times 10\text{kHz} \times t) + 1 \times \sin(2\pi \times 500\text{kHz} \times t)$ . Opamp B is required here to meet the GBW requirement as one of the input signals to the summing amplifier involves a higher frequency (i.e., 500 kHz) input signal.

(7 marks)

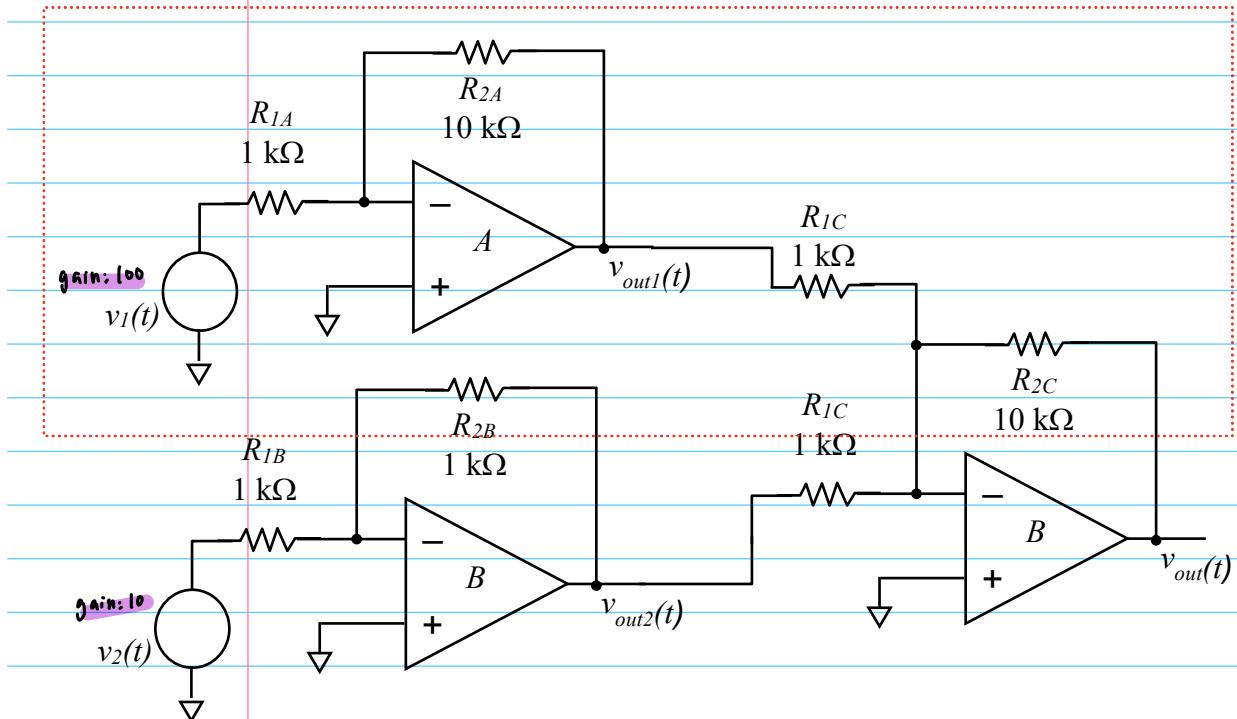- (d) You are given only **one** opamp A with GBW of 200 kHz and **two** opamp B with GBW of 8 MHz. Design an opamp circuit that will give an output voltage of  $v_{out}(t) = 1 \times \sin(2\pi \times 10\text{kHz} \times t) + 1 \times \sin(2\pi \times 500\text{kHz} \times t)$  with the two input signals from (a) and (b).



The first inverting amplifier using opamp A (lower GBW) with gain of -10 will give  $v_{out1}(t) = -0.1 \times \sin(2\pi \times 10\text{kHz} \times t)$ . Opamp B (higher GBW) should not be used here as it will be wasted. Opamp B (whose quantity is limited to only two pieces) is required for other parts of the circuit involving a higher frequency (i.e., 500 kHz) input signal to meet the GBW requirement.

The second inverting amplifier using opamp B (higher GBW) with gain of -1 will give  $v_{out2}(t) = -0.1 \times \sin(2\pi \times 500\text{kHz} \times t)$ . Opamp A cannot be used due to its lower GBW.

The third summing amplifier using opamp B (higher GBW) with gain of -10 will give  $v_{out}(t) = 1 \times \sin(2\pi \times 10\text{kHz} \times t) + 1 \times \sin(2\pi \times 500\text{kHz} \times t)$ . Opamp B is required here to meet the GBW requirement as one of the input signals to the summing amplifier involves a higher frequency (i.e., 500 kHz) input signal.

(7 marks)

- Q2. (a) Derive the equivalent resistance,  $R_x = v_x/i_x$ , for the circuit shown in Fig. Q2(a). Note that  $v_I$  is a dependent voltage source.

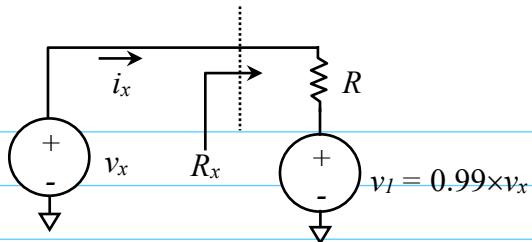


Fig. Q2(a)

- (b) The dependent voltage source,  $v_I$  of Fig. Q2(a) is implemented as shown in Fig. Q2(b) below. Derive the value of  $k$  such that  $v_I = 0.99v_x$ .

[Ans.  $k = 1.97$ ]

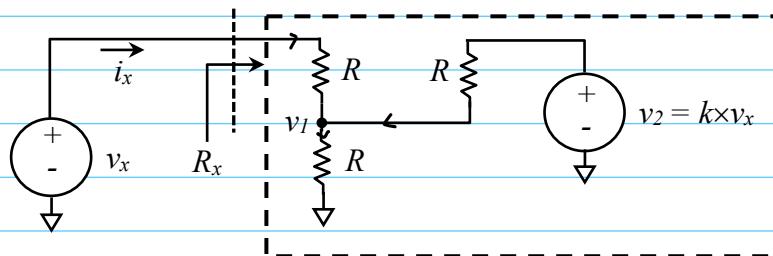


Fig. Q2(b)

- (c) Design an opamp circuit that can realize the circuit within the dashed box shown in Fig. Q2(b). You may treat  $v_x$  as an independent signal source.

- (d) The designed opamp circuit in part (c) is known as a **resistance multiplier**. It can realize a huge equivalent resistance with relatively small resistor values. Suggest and show a simple filtering circuit that can make use of this technique.

**Q2. Solution:**

- (a) Derive the equivalent resistance,  $R_x = v_x/i_x$ , for the circuit shown in Figure Q2 (a). Note that  $v_I$  is a dependent voltage source.


$$i_x = \frac{v_x - 0.99v_x}{R} = \frac{0.01v_x}{R} \Rightarrow R_x = \frac{v_x}{i_x} = 100R.$$

- (b) The dependent voltage source,  $v_I$  of Fig. Q2(a) is implemented as shown in Fig. Q2(b) below. Derive the value of  $k$  such that  $v_I = 0.99v_x$ . Derive the value  $k$  for the circuit shown in Fig. Q2 (b) such that  $v_I = 0.99v_x$ .

Apply KCL at point  $v_I$ , and apply  $v_I = 0.99v_x$  as required -

$$\begin{aligned} \frac{v_x - v_1}{R} + \frac{v_2 - v_1}{R} &= \frac{v_1}{R} \\ \frac{v_x - 0.99v_x}{R} + \frac{kv_x - 0.99v_x}{R} &= \frac{0.99v_x}{R} \\ \Rightarrow k &= 1.97 \end{aligned}$$

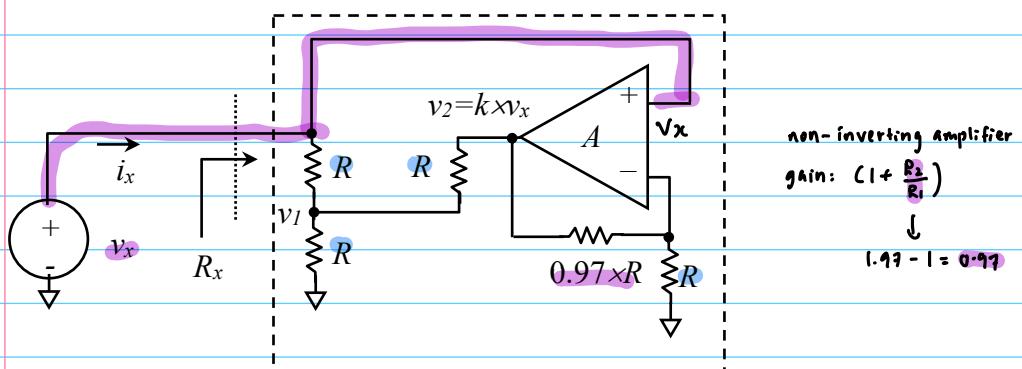- (c) Design an opamp circuit that can realize the circuit within the dashed box shown in Fig. Q2 (b). You may treat  $v_x$  as an independent signal source.




Since  $v_2 = kv_x$  where  $k$  is a positive value of 1.97, if you search through the opamp library, you can see that the **non-inverting amplifier** fits the requirement. Hence, we replace the  $v_2 = kv_x$  by a **non-inverting amplifier**.

- (d) The designed circuit in part (c) is known as a **resistance multiplier**. It can realize a huge equivalent resistance with relatively small resistor values. Suggest and show a **simple filtering circuit** that can make use of this technique.

*5 resistors multiplied to 100R (part a) equivalent*

*think of simple RC filter*

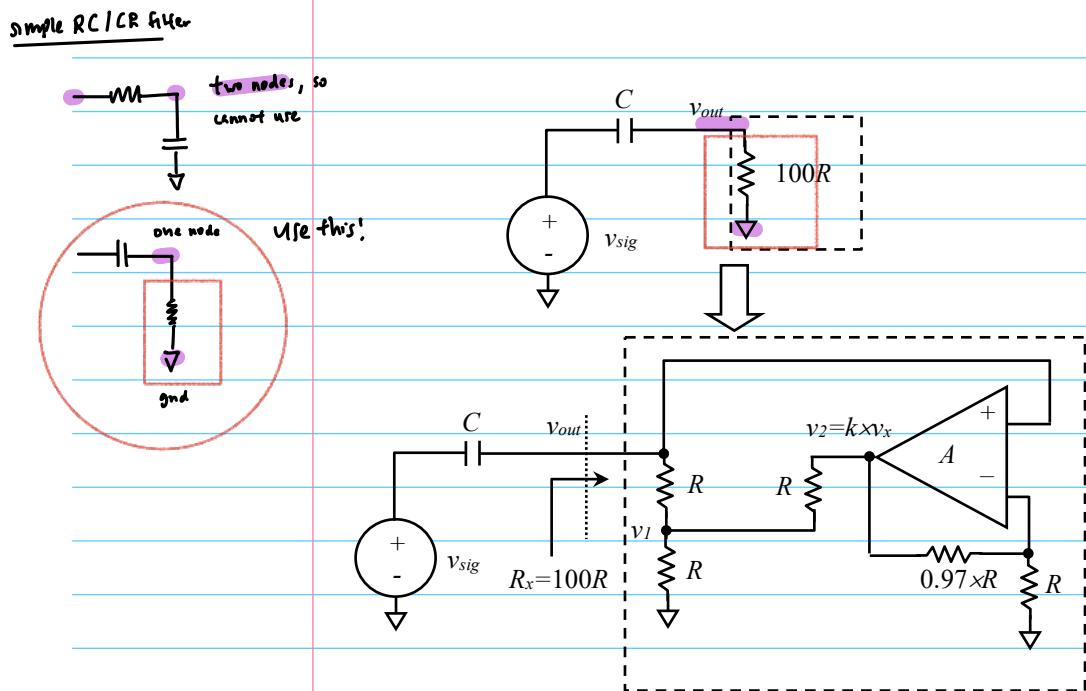As shown in part (c), the circuit in the dashed box presents an equivalent resistance of  $R_x = 100R$  between one terminal and ground, hence we can use the circuit in the dashed box to replace a resistor. As shown below, the resistor in a passive high pass filter can be replaced by the opamp circuit, between one node ( $v_{out}$ ) and ground.



Q3. Figure Q3 shows an opamp circuit composed of 3 sub-circuits, which are shown in the three boxes, labelled as A, B and C.

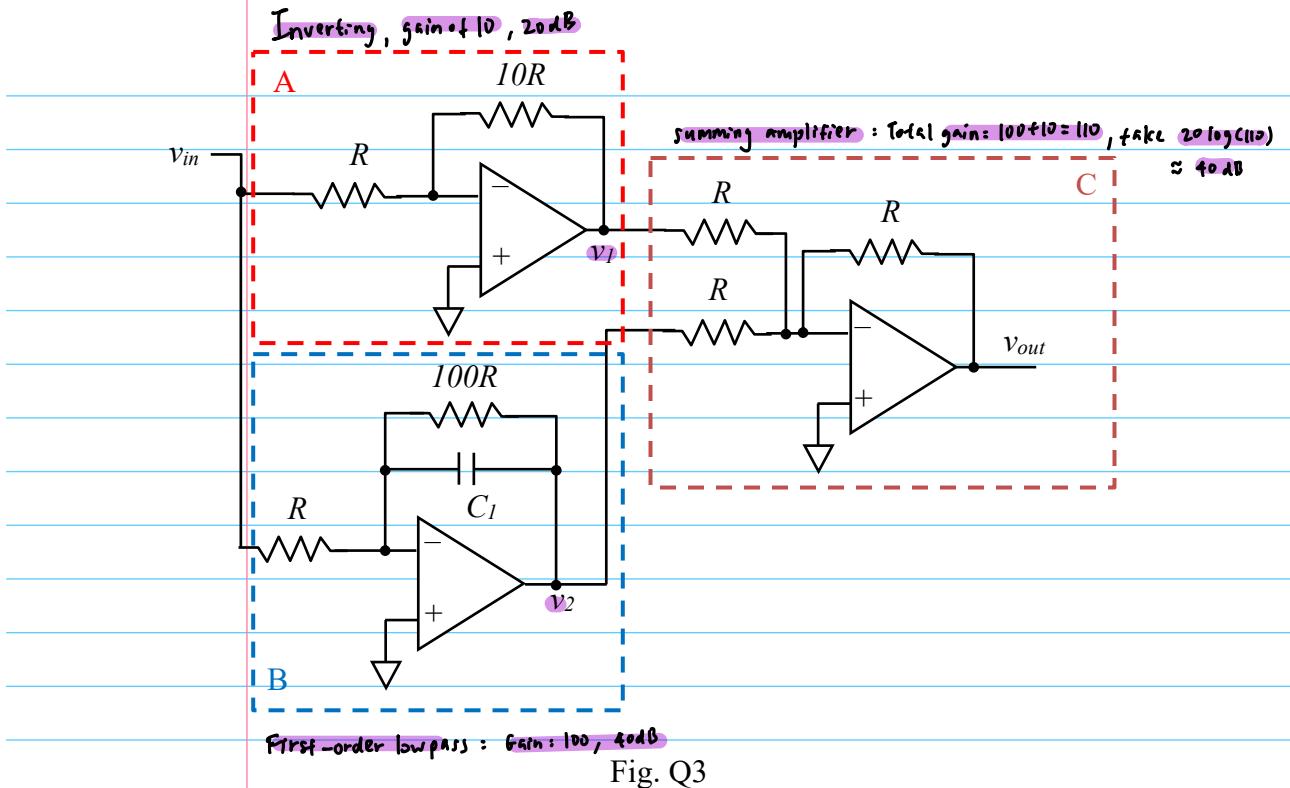


Fig. Q3

The capacitance  $C_1$  in Fig. Q3 has a value such that

$$\frac{1}{2\pi \times C_1 \times 100R} = 1 \text{ kHz.} \rightarrow \text{low pass cut-off, graph starts to go down}$$

- (a) Identify the function of each of the opamp sub-circuits.
- (b) Sketch the Bode plots of the transfer functions  $v_1/v_{in}$ ,  $v_2/v_{in}$  and  $v_{out}/v_{in}$ .

A Bode plot is a plot of the gain in decibels (dB) versus the frequency  $f$  (in  $\log_{10}$  scale). Gain (dB) =  $20 \times \log_{10}(|v_{out}/v_{in}|)$ . For example, a gain of 40 dB is equivalent to  $|v_{out}/v_{in}| = 100$ .

You may use the Semilog paper attached to sketch the Bode plots.

**Q3. Solution:**


- (a) Identify the function of each of the opamp sub-circuits.

Sub-circuit A: an inverting amplifier of  $|\text{gain}| = |v_I/v_{in}| = 10$ , or  $20 \times \log_{10}(10) = 20 \text{ dB}$ . See Bode plot of  $v_I/v_{in}$  in semilog graph below.

Sub-circuit B: a first order low pass filter of 3 dB frequency,  $f_{3dB} = \frac{1}{2\pi \times C_1 \times 100R} = 1 \text{ kHz}$ , and a low frequency  $|\text{gain}| = |v_2/v_{in}| = 100$ , or  $20 \times \log_{10}(100) = 40 \text{ dB}$ . For frequency beyond  $f_{3dB}$ , gain falls at a rate of 20 dB/decade of frequency. See Bode plot of  $v_2/v_{in}$  in semilog graph below.

Sub-circuit C: a summing amplifier, which sums the outputs of sub-circuits A and B:  $v_{out} = v_I + v_2$ . The overall circuit has a low frequency  $|\text{gain}| = |v_{out}/v_{in}| = |v_I/v_{in}| + |v_2/v_{in}| = 110$ , or  $20 \times \log_{10}(110) = 40.8 \text{ dB}$ , with the same first order frequency response as the low pass filter (sub-circuit B) from 1 to 10 kHz. See Bode plot of  $v_{out}/v_{in}$  in semilog graph below.

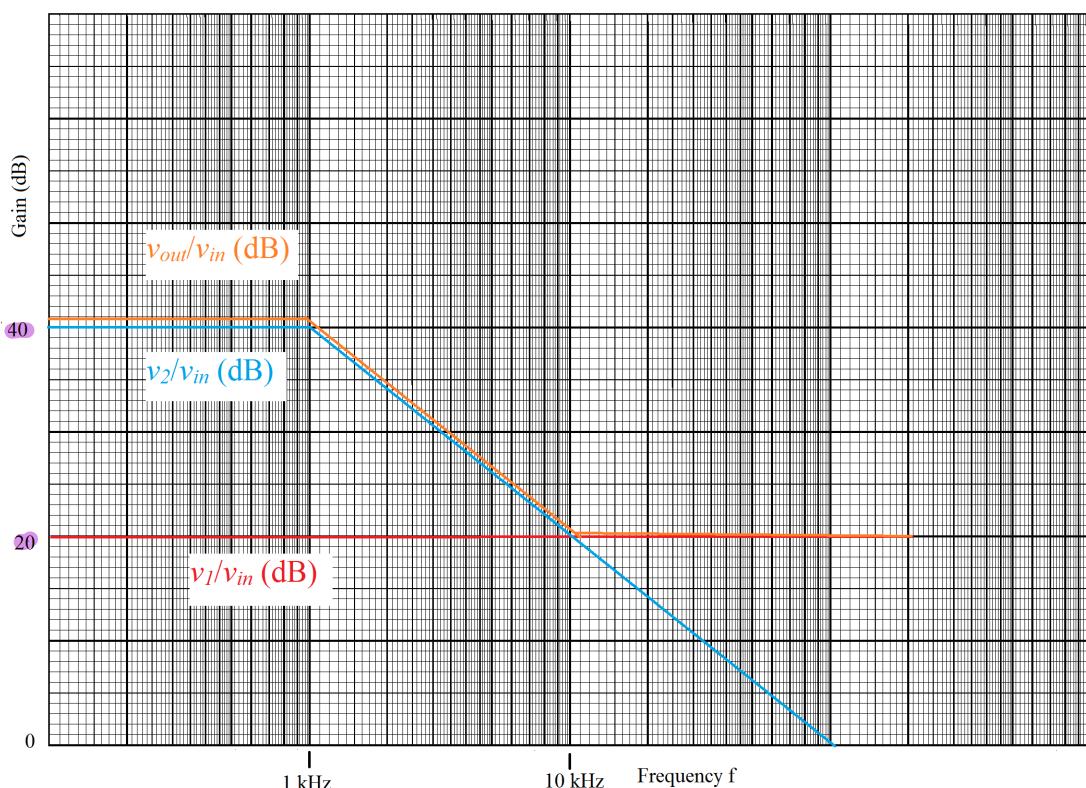- (b) Bode plots of  $v_I/v_{in}$ ,  $v_2/v_{in}$  and  $v_{out}/v_{in}$ :



- Q4. (a) Derive the equivalent impedance ( $Z_x$ ) for the opamp circuit shown in Fig. Q4(a) in terms of  $R_1$ ,  $R_2$  and  $C_3$ . Hence, show that  $Z_x$  corresponds to the impedance of a negative capacitance ( $-C_x$ ).

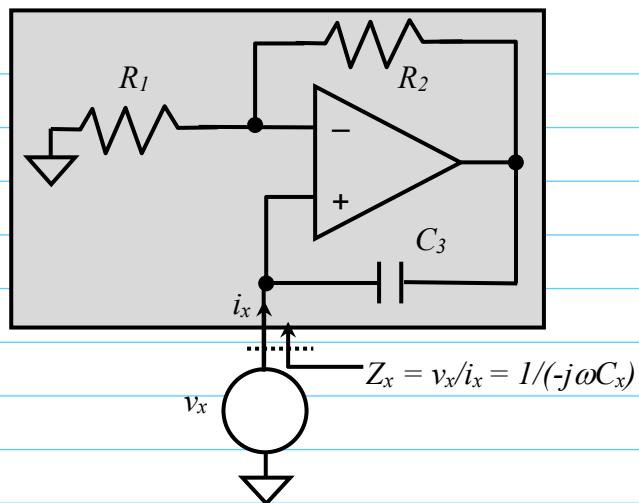


Fig. Q4(a)

- (b) The  $LC$  network shown in Fig. Q4(b) exhibits a resonant frequency of  $\frac{1}{2\pi\sqrt{LC}}$ . Using the circuit depicted in Fig. Q4(a), show how the resonant frequency of the  $LC$  network can be changed if  $R_1$  in Fig. Q4(a) is replaced by a variable resistor.

Derive also the resonant frequency in terms of the variable resistor.

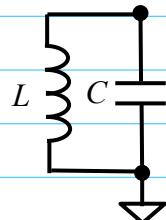


Fig. Q4(b)

**Q4. Solution:**

(a) By virtual short :

$$V_- = V_+ = v_x$$

Using  $i_- = 0$ ,  $V_o \times \frac{R_1}{R_1 + R_2} = V_- = v_x$  [ $V_o$  is the output terminal voltage of opamp]

$$\Rightarrow V_o = v_x \times \left(1 + \frac{R_2}{R_1}\right)$$


Using  $i_+ = 0$ ,  $i_x = i_c = \frac{v_x - V_o}{\frac{1}{sC_3}} = v_x \frac{\left(\frac{R_2}{R_1}\right)}{\frac{1}{sC_3}} = -v_x \frac{sC_3 R_2}{R_1}$  [ $i_c$  is the capacitor current]

$$Z_x = \frac{v_x}{i_x} = -\frac{R_1}{sC_3 R_2}$$

[Note:  $s \equiv j\omega \equiv j2\pi f$ ]

The equivalent capacitance value is  $-\frac{C_3 R_2}{R_1}$  (a negative value).

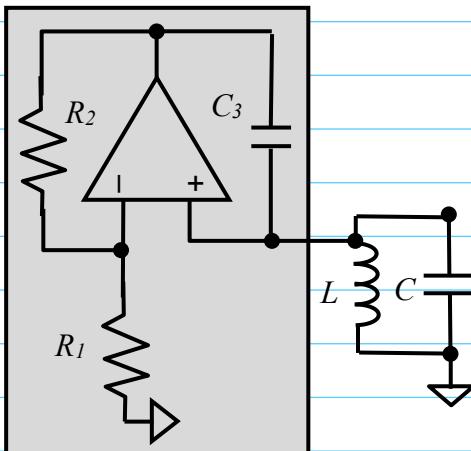(b) Connect the circuit of Fig. Q4(a) in parallel to the LC network –



Capacitance of the LC network becomes  $\left(C - \frac{C_3 R_2}{R_1}\right)$

$$\text{Resonant frequency, } f = \frac{1}{2\pi \sqrt{L \left(C - \frac{C_3 R_2}{R_1}\right)}}$$

By varying  $R_1$ , the total capacitance can be changed, and thus the resonant frequency  $f$  can be changed.

Q5.

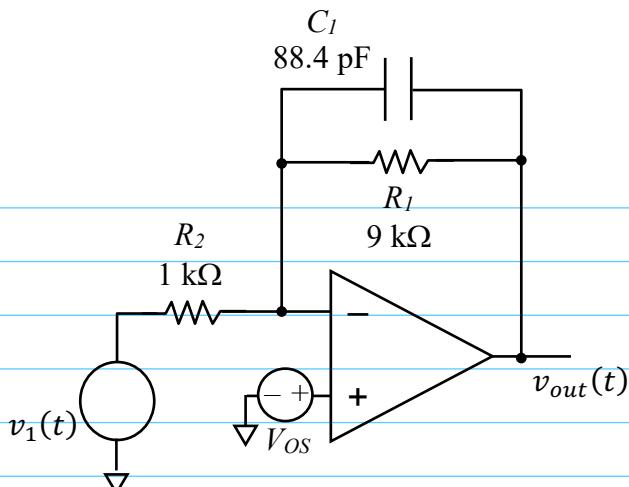


Fig. Q5 First order low-pass filter.

The opamp used in Fig. Q5 has a GBW of 2 MHz and an input offset voltage of  $V_{OS} = 20 \text{ mV}$ . The opamp is powered by  $\pm 5 \text{ V}$  supplies.

$$f_{3\text{dB}} = \frac{1}{2\pi R_1 C_1}$$

- (a) Ignoring the GBW effect of the opamp, estimate the 3dB cut-off frequency of the first order lowpass filter and its gain shown in Fig. Q5.

$$[\text{Ans. } 200 \text{ kHz}, -9 \times \frac{1}{1+j\omega \times 7.96 \times 10^{-7}}]$$

- (b) With the capacitor  $C_1$  removed from the circuit, estimate the closed-loop 3dB cut-off frequency of the resulting circuit, taking into consideration the GBW effect.

$$[\text{Ans. } 200 \text{ kHz}]$$

- (c) If the GBW effect is considered, discuss the expected gain at the cut-off frequency of part (a).

$$[\text{Ans. } 13.1 \text{ dB}]$$

- (d) If  $v_1(t)$  has a frequency well below the 3dB cut-off frequency of part (a), can we treat the capacitor  $C_1$  as an open circuit? Explain your reasoning.

- (d) If a sinusoidal voltage,  $v_1(t) = v_{pk} \times \sin(2\pi \times 10\text{kHz} \times t)$ , is applied to the circuit, estimate the maximum allowable  $v_{pk}$  such that  $v_{out}(t)$  is without distortion.

$$[\text{Ans. } 0.53 \text{ V}]$$

- (f) Suggest two methods, without changing the opamp, which can increase the maximum allowable  $v_{pk}$  in part (e).

**Q5. Solution:**

- (a) Ignoring the GBW effect of the opamp, estimate the 3dB cut-off frequency of the first order lowpass filter and its gain in Fig. Q5.

$$f_{3dB,LPF} = \frac{1}{2\pi R_1 C_1} = 200 \text{ kHz}$$

$$\text{Gain} = -\frac{R_1}{R_2} \times \frac{1}{1+j\omega R_1 C_1} = -9 \times \frac{1}{1+j\omega \times 7.96 \times 10^{-7}} \quad (\text{pg 77 notes})$$

- (b) With the capacitor  $C_1$  removed from the circuit, estimate the closed-loop 3dB cut-off frequency of the resulting circuit, taking into consideration the GBW effect.

The resulting circuit with capacitor  $C_1$  removed is an inverting amplifier. The closed-loop 3dB cut-off frequency is

$$f_{3dB,CL} = GBW \times \frac{R_2}{R_1 + R_2} = 200 \text{ kHz}$$

- (c) If the GBW effect is considered, discuss the expected gain at the cut-off frequency of part (a).

*part (b)*      *part (c)*  
At 200 kHz, as  $C_1$  will contribute -3dB and GBW will contribute another -3dB, the gain will drop to -6dB. The expected gain at 200 kHz will be:

$$20 \log_{10} \left( \frac{R_1}{R_2} \right) - 6 = 20 \log_{10}(9) - 6 = 13.1 \text{ dB}$$



- (d) If  $v_1(t)$  has a frequency well below the 3dB cut-off frequency of part (a), can we treat the capacitor  $C_1$  as an open circuit? Explain your reasoning.

Yes, the capacitor can be treated as an open circuit. This is because the gain magnitude is constant ( $= R_1/R_2$ ) for frequencies smaller than the 3dB cut-off frequency.

→ treat capacitor open circuit at low frequencies.

treat capacitor short circuit at high frequencies

- (e) If a sinusoidal voltage,  $v_1(t) = v_{pk} \times \sin(2\pi \times 10k \times t)$ , is applied to the circuit, estimate the maximum allowable  $v_{pk}$  such that  $v_{out}(t)$  is without distortion.

→ either slew-rate,  
if gain give both,  
check both,  
find the bottleneck (lower value)  
offset

Using the result of part (d), at signal frequency of 10 kHz ( $\ll f_{3dB,CL} = 200 \text{ kHz}$ ), LPF becomes effectively an inverting amplifier.

$$v_{out}(t) = V_{OS} \times \left(1 + \frac{R_1}{R_2}\right) + v_1(t) \times \left(-\frac{R_1}{R_2}\right); \text{ where } -5V < v_{out}(t) < 5V$$

$$-5V < 20mV \times 10 - 9v_{pk} \sin(2\pi \times 10k \times t) < 5V$$

$$-5.2V < -9v_{pk} \sin(2\pi \times 10k \times t) < 4.8V$$

$$-0.53V < v_{pk} \sin(2\pi \times 10k \times t) < 0.58V$$


Considering a symmetrical sinusoidal voltage,  $v_{pk}$  cannot exceed 0.53 V. Maximum allowable  $v_{pk}$  would be 0.53 V.

- (f) Suggest two methods without changing the opamp which can increase the maximum allowable  $v_{pk}$  in part (e).

↳ get rid of offset → use summing amplifier
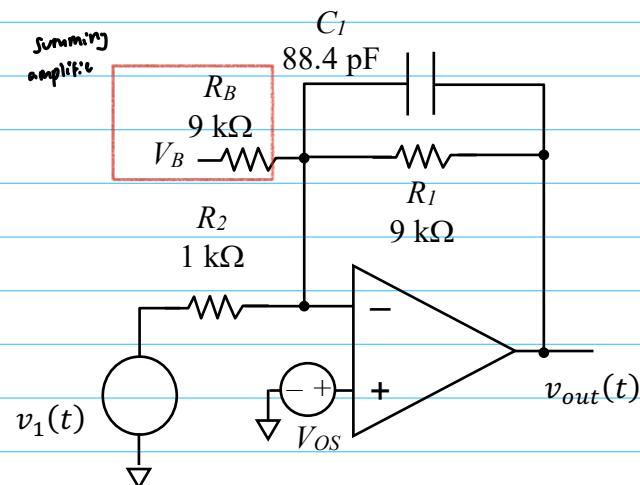
#### Method 1:

We can employ a **summing amplifier** by adding an additional resistor  $R_B$  and an additional DC voltage  $V_B$  to compensate the effect of  $V_{OS}$  -



$$v_{out}(t) = V_{OS} \times \left(1 + \frac{R_1}{R_2}\right) + v_1(t) \times \left(-\frac{R_1}{R_2}\right) + V_B \times \left(-\frac{R_1}{R_B}\right)$$


As an example, for  $R_B = 9 \text{ k}\Omega$ ,  $V_B$  of 200 mV can be added to compensate the  $V_{OS}$  effect. Maximum allowable  $v_{pk}$  would be ~0.56 V.

$v_1(t) \times \left(-\frac{R_1}{R_2}\right)$ , see part (e), 20mV offset with gain: 10 compensated

Method 2:

*Capacitor behave like open circuit in DC*

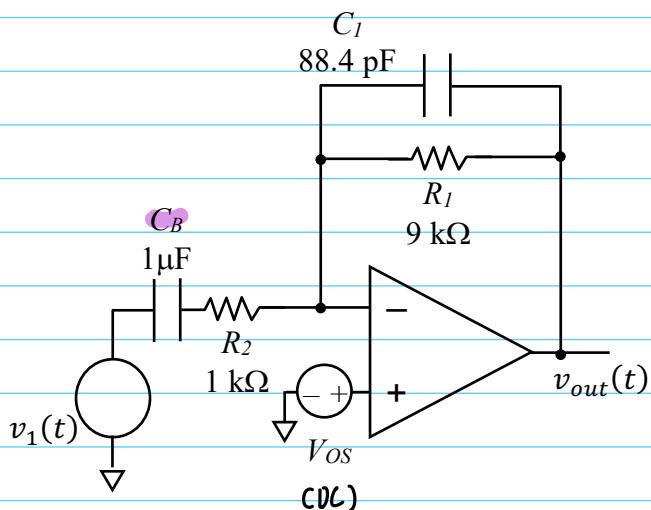We can employ a DC block capacitor  $C_B$ , as shown in the circuit below.  $C_B$  should be chosen such that its impedance is much smaller than  $R_2$  at frequency of the desired signal (i.e., 10 kHz).



$$-5V < v_{out}(t) = V_{OS} \times \left(1 + \frac{R_1}{\infty}\right) + v_1(t) \times \left(-\frac{R_1}{R_2}\right) = v_{OS} + v_1(t) \times \left(-\frac{R_1}{R_2}\right) < 5V$$

In this case,  $V_{OS}$  is not amplified by 10 times (as  $C_B$  is an open circuit under DC),  $9v_{pk}$  would now be between -4.98 and 5.02 V. Due to symmetry consideration, maximum allowable  $v_{pk}$  would be 0.55 V.

Note: when considering the effect of  $V_{OS}$ , it is DC analysis, and  $C_B$  is an open circuit.

- Q6. The opamp used in Fig. Q6 has a GBW of 0.5 MHz, a slew rate of 0.5 V/ $\mu$ s, an offset voltage of 20 mV, and a noise voltage spectral density of 20 nV/ $\sqrt{\text{Hz}}$ .

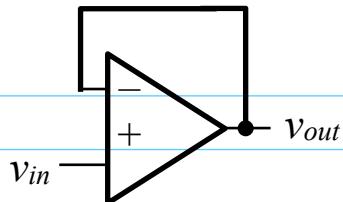


Fig. Q6

- (a) Estimate the  $f_{3dB,CL}$  of the circuit shown in Fig. Q6.

[Ans. 0.5 MHz]

- (b) What is the minimum peak voltage of  $v_{in}$  that can be fed to the circuit?

[Ans.  $v_{in,pk,min} = 25 \mu\text{V}$ ]

- (c) What is the maximum peak voltage of  $v_{in}$  that can be fed to the circuit, assuming that a signal up to  $f_{3dB,CL}$  is sent to the circuit?

[Ans.  $V_{in,pk,max} = 0.159 \text{ V}$ ]

- (d) Sketch the  $v_{out}$  using the  $v_{in}$  of part (c).

### **Q6. Solution:**

- (a) Estimate the  $f_{3dB,CL}$  for the circuit (a unity gain buffer) -

$$|\beta G(j\omega_{3dB,CL})| = 1$$

$$\Rightarrow |A(j\omega_{3dB,CL})| \approx \left| \frac{2\pi \times \text{GBW}}{j\omega_{3dB,CL}} \right| = 1$$

$$\Rightarrow f_{3dB,CL} = \text{GBW} = 0.5 \text{ MHz}$$

- (b) What is the minimum peak voltage of  $v_{in}$  that can be fed to the circuit?

$$v_{out\_noise,rms} \approx \sqrt{V_n^2 \times 0.5\text{MHz} \times \frac{\pi}{2}} = 17.7 \mu\text{V}$$

$$\Rightarrow v_{in,pk,min} \approx v_{out\_noise,rms} \times \sqrt{2} = 25 \mu\text{V}$$

- (c) What is the maximum peak voltage of  $v_{in}$  that can be fed to the circuit assuming signal up to  $f_{3dB,CL}$  is sent to the circuit?


$$\frac{dV_{out}}{dt} \approx 2\pi \times 0.5\text{MHz} \times V_{out,pk} \sin(2\pi \times 0.5\text{MHz} \times t) < 0.5 \text{ V}/\mu\text{s}$$

$$\Rightarrow V_{out,pk} < 0.159 \text{ V} \Rightarrow V_{in,pk,max} = 0.159 \text{ V}$$

Note:  $V_{out,pk}$  is not limited by  $V_{OS}$  as supply voltage is not given.

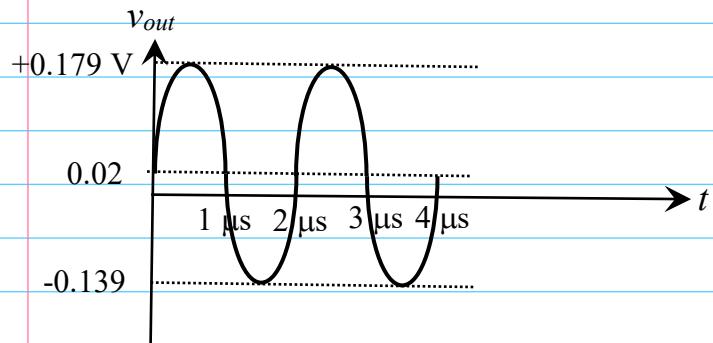- (d) Sketch the  $v_{out}$  using the  $v_{in}$  in part (c).

$v_{out}$  has a dc offset of  $V_{OS}$  -



- Q7. As shown in Fig. Q7, a triangular wave  $v(t)$ , with  $v_{pk-pk}$  of 2 V and period of  $4T$ , is fed to the two opamp circuits.

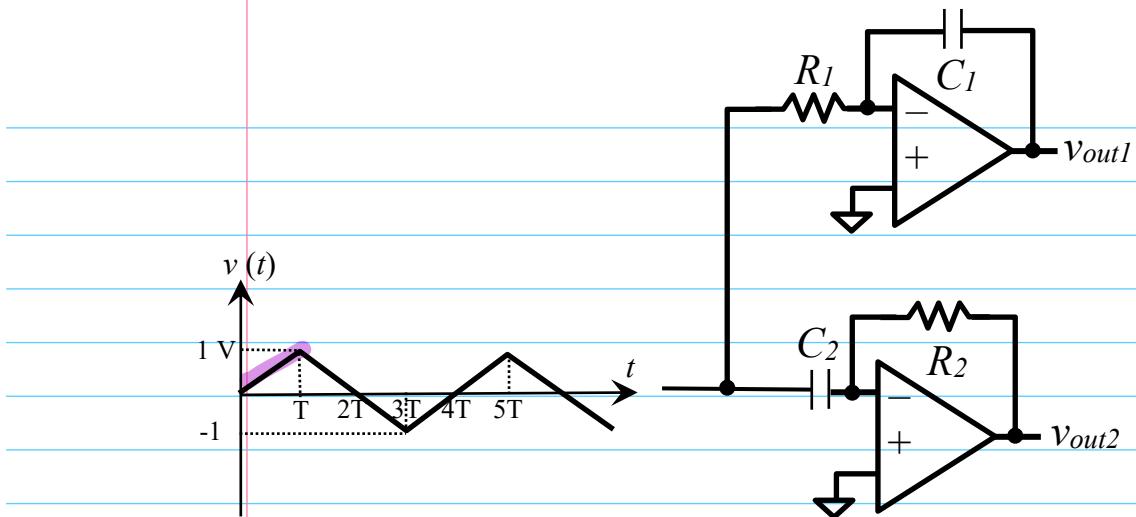


Fig. Q7


(a) Sketch and label the output waveforms,  $v_{out1}$  and  $v_{out2}$ .

$$V_{peak-to-peak} : V_p = 1V$$

(b) Derive the relationship between  $R_2$  and  $C_2$  such that  $v_{out2}$  also has  $v_{pk-pk}$  of 2 V.

### Q7. Solution:

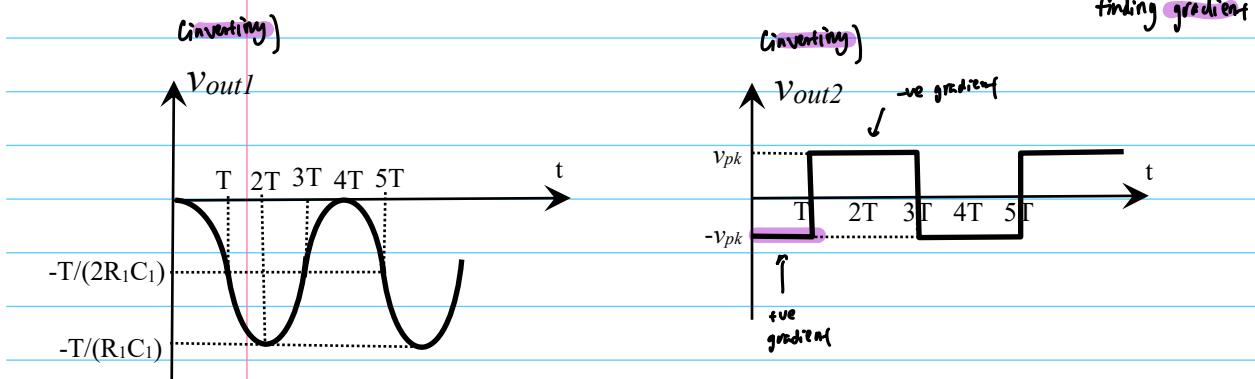(a)  $v_{out1}$  is a function of the integration of  $v(t)$ , while  $v_{out2}$  is a function of the differentiation of  $v(t)$ .



Note:  $v_{out1}$  is not sinusoidal.

$$(b) \quad v_{pk} = -R_2 C_2 \frac{dv(t)}{dt} = -R_2 C_2 \left( \frac{-2V}{2T} \right) = 1V \Rightarrow R_2 C_2 = T$$

pg 70 notes

- Q8. (a) If  $v_1(t) = \cos(2\pi \times 100000 \times t)$ , determine the  $dv_1(t)/dt$ .
- (b) If  $v_2(t) = \cos(2\pi \times 200000 \times t)$ , determine the  $dv_2(t)/dt$ .
- (c) Design an opamp circuit that can perform differentiation on  $v_1(t)$  in (a), and give rise to a peak output value of 0.1 V. Verify that the circuit obtained can be applied to  $v_2(t)$  in (b) and give rise to a peak output value of 0.2 V. [You need to specify the component values used in your opamp circuit.]
- (d) A super diode circuit is used to convert the output from (c). Sketch the resulting output voltage of the super diode circuit if  $v_1(t)$  is applied to (c). Repeat the same if  $v_2(t)$  is applied to (c). You should indicate clearly the key characteristics of the two waveforms you plot.
- (e) A RC network shown in Fig. Q8 can be connected to the super diode circuit output of (d) to form a peak detector, i.e., it can detect 0.1 V or 0.2 V, respectively from (d) if  $v_1(t)$  or  $v_2(t)$  is used. The capacitor in the RC network will charge up to the highest voltage detected at the output of the super diode circuit and hold on to this voltage if the RC time constant is large (i.e., RC network functions as a peak detector). A comparator can then be used to differentiate whether the signal is from  $v_1(t)$  or  $v_2(t)$ . Draw the whole system that consists of part (c), (d), RC network and the comparator. Suggest the threshold voltage for the comparator.

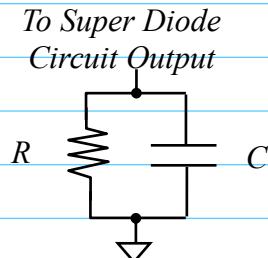


Fig. Q8

- (f) Suppose all the opamps used in (e) have offset voltage of +20 mV, comment on its impact on the overall performance for (e).

**Q8. Solution:**


- (a) If  $v_1(t) = \cos(2\pi \times 100000 \times t)$ , determine the  $dv_1(t)/dt$ .

$$\frac{dv_1(t)}{dt} = -2\pi \times 100000 \times \sin(2\pi \times 100000 \times t)$$

- (b) If  $v_2(t) = \cos(2\pi \times 200000 \times t)$ , determine the  $dv_2(t)/dt$ .

$$\frac{dv_2(t)}{dt} = -2\pi \times 200000 \times \sin(2\pi \times 200000 \times t)$$

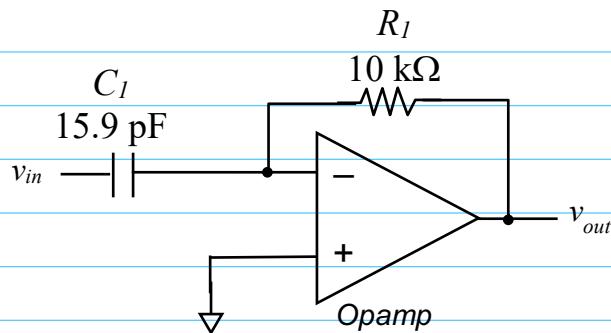- (c) Design an opamp circuit that can perform differentiation on  $v_1(t)$  in (a), and give rise to a peak output value of 0.1 V. Verify that the circuit obtained can be applied to  $v_2(t)$  in (b) and give rise to a peak output value of 0.2 V. [You need to specify the component values used in your opamp circuit.]



Using a differentiator circuit -  $v_{out}(t) = -R_1 C_1 \frac{dv_{in}(t)}{dt}$

$$|v_{out}(t)| = |R_1 C_1 \times 2\pi \times 100000 \times \sin(2\pi \times 100000 \times t)| \leq 0.1$$

$$R_1 C_1 \times 2\pi \times 100000 = 0.1$$

$$R_1 C_1 = \frac{0.1}{2\pi \times 100000}$$

Select  $R_1 = 10 \text{ k}\Omega$ , and  $C_1 = 15.9 \text{ pF}$

**[Note: Other combinations of  $R_1$  and  $C_1$  are also possible, provided  $R_1 C_1 = 1.59 \times 10^{-7}$ ]**

Verification that the circuit is applicable to (b):


$$|v_{out}(t)| = |R_1 C_1 \times 2\pi \times 200000 \times \sin(2\pi \times 200000 \times t)| \leq 0.2$$

$$\text{As, } R_1 C_1 \times 2\pi \times 200000 = 0.2 \text{ V}$$

*↗ half-wave rectifier*


- (d) A super diode circuit is used to convert the output from (c). Sketch the resulting output voltage of the super diode circuit if  $v_1(t)$  is applied to (c). Repeat the same if  $v_2(t)$  is applied to (c). You should indicate clearly the key characteristics of the two waveforms you plot.

- Frequency of  $v_1(t) = 100 \text{ kHz} \Rightarrow \text{period} = 10 \mu\text{s}$
- Frequency of  $v_2(t) = 200 \text{ kHz} \Rightarrow \text{period} = 5 \mu\text{s}$

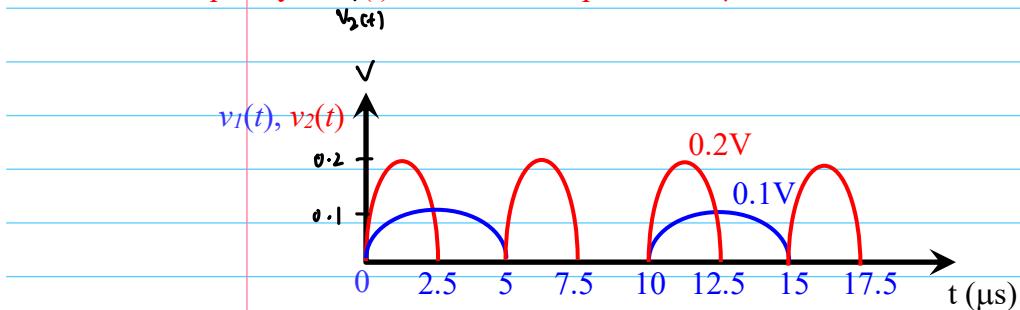Blue waveform: Output of super diode circuit for  $v_1(t)$ Red waveform: Output of super diode circuit for  $v_2(t)$ 

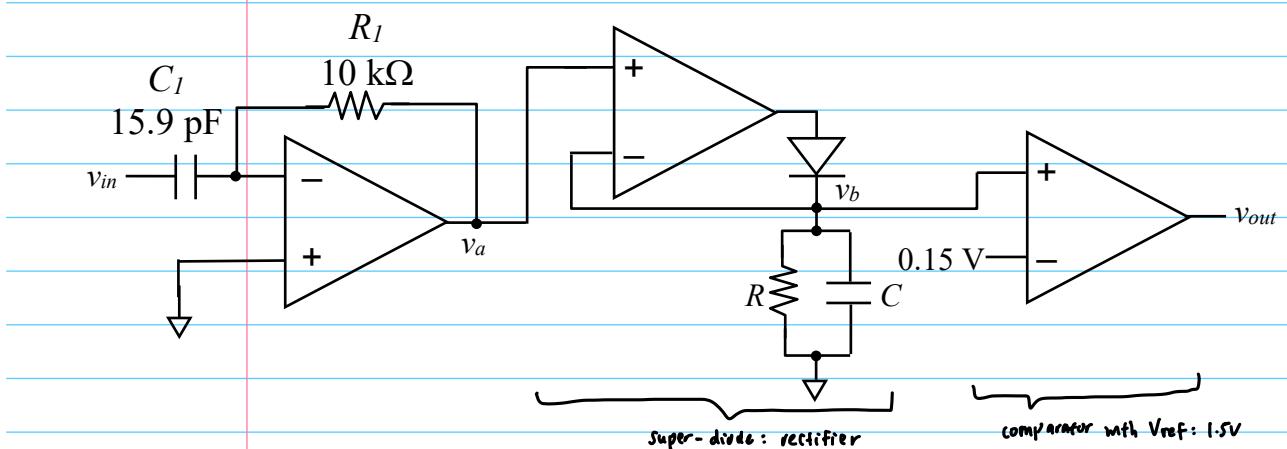- (e) A RC network shown in Fig. Q8 can be connected to the super diode circuit output of (d) to form a peak detector, i.e., it can detect 0.1 V or 0.2 V, respectively from (d) if  $v_1(t)$  or  $v_2(t)$  is used. The capacitor in the RC network will charge up to the highest voltage detected at the output of the super diode circuit and hold on to this voltage if the RC time constant is large (i.e., RC network functions as a peak detector). A comparator can then be used to differentiate whether the signal is from  $v_1(t)$  or  $v_2(t)$ . Draw the whole system that consists of part (c), (d), RC network and the comparator. Suggest the threshold voltage for the comparator.

↓  
superdiode already have  
resistor so just need to add capacitor  
to form RC network





Select threshold voltage to be 0.15 V (i.e., midway between 0.1 V and 0.2 V)  
( $V_{ref}$ )

Note:

If  $v_{in} = v_1(t)$ ,  $v_b = 0.1$  V and  $v_{out} = -V_{DD}$   
 If  $v_{in} = v_2(t)$ ,  $v_b = 0.2$  V and  $v_{out} = +V_{DD}$

- (f) Suppose all the opamps used in (e) have offset voltage of +20 mV, comment on its impact on the overall performance for (e).

When there is no input ( $v_{in} = 0$ ),  $v_a$  will exhibit +20 mV.  $v_b$  will exhibit +40 mV (20 mV due to  $v_a$ ). The non-inverting terminal  $V_+$  of the last opamp will be +60 mV. So if  $v_{in} = v_1(t)$  is sent in, it will have peak voltage of 0.16 V instead of 0.1 V. For  $v_{in} = v_2(t)$ , it will have peak voltage of 0.26 V. However, as both 0.16 V and 0.26 V will exceed the 0.15 V threshold, the circuit would not function properly.

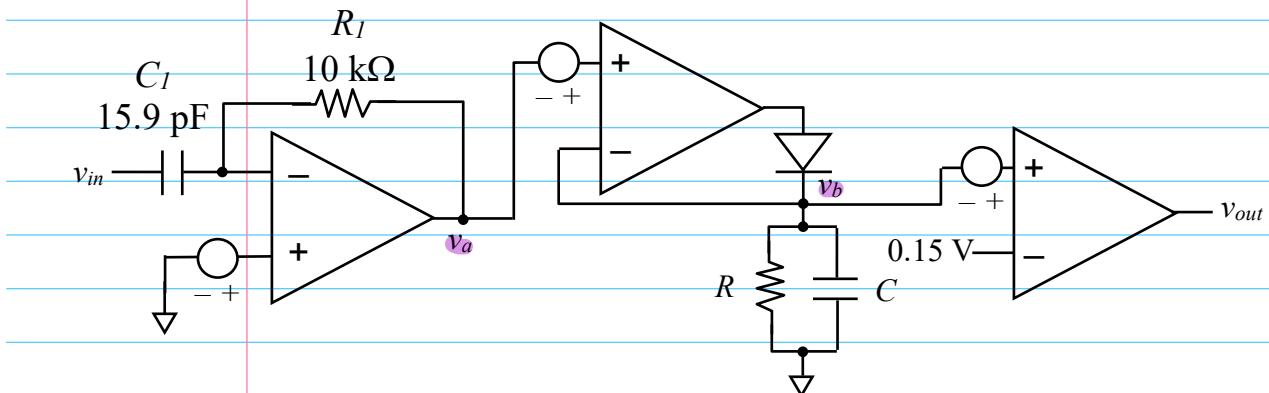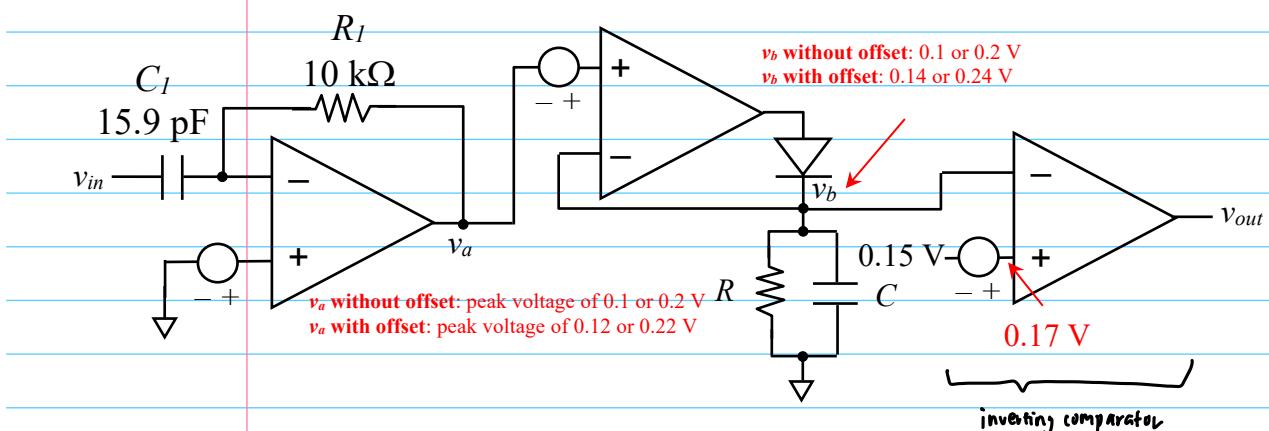Clarifying notes:

Assume the input connections of the comparator are reversed as shown above (i.e., the output of the super diode circuit  $v_b$  is applied to the inverting input of the comparator and the threshold or reference voltage is applied to the non-inverting input). As  $v_b$  will exhibit +40mV when there is no input, the peak detector output  $v_b$  with input will now be either 0.14 or 0.24 V. This will be applied directly to the inverting input of the comparator. On the other hand, due to the

reversed connection, the input threshold of 0.15 V that is applied to the non-inverting terminal, will now experience an offset voltage of +20 mV. The actual threshold voltage that appears at the non-inverting terminal will now become 0.17 V. As 0.17 V is between 0.14 and 0.24 V, the comparator will still be able to detect the output correctly. However, the output will now be inverted, i.e., when it is 0.24 V, it will output low and when it is 0.14 V, it will output high.

J

because this is an inverting  
comparator

a)  $V_i(t) = 0.01 \sin(2\pi \times 10\text{kHz} \times t)$

$$10\text{kHz} = GBW \times \frac{1}{1+10}$$

$$11 \times 10\text{kHz} = GBW$$

$$GBW = 110\text{kHz}$$

inverting amp of gain: -10

$$\downarrow$$

$$-\frac{R_2}{R_1} = -10, \text{ take } R_2 = 10 \text{ and } R_1 = 1$$

b)  $V_{i(t)} = 0.1 \sin(2\pi \times 500\text{kHz} \times t)$

$$500\text{kHz} = GBW \times \frac{1}{1+10}$$

$$GBW = 11 \times 500\text{kHz}$$

$$= 5.5\text{MHz}$$

inverting amp of gain: -10

$$\downarrow$$

$$-\frac{R_2}{R_1} = -10, \text{ take } R_2 = 10 \text{ and } R_1 = 1$$

c)  $V_{out} = 0.1 \sin(2\pi \times 10\text{kHz} \times t) + 1 \times \sin(2\pi \times 500\text{kHz} \times t)$

$\downarrow$   
gain = 10

$\downarrow$   
gain = 10

$\therefore$  input signal (a) to op-amp A with a gain (-10) ( $10\text{kHz} < \text{opamp A GBW}$ )

input signal (b) to op-amp B with a gain (-10) ( $5.5\text{MHz} < \text{opamp B GBW}$ )

$\downarrow$  output

output from (a) and (b) into summing amplifier (gain: -1) (combined  $< \text{op-amp B GBW}$ )

a)  $V_{out} = 1 \sin(2\pi \times 10\text{kHz} \times t) + 1 \times \sin(2\pi \times 500\text{kHz} \times t)$

$\downarrow$   
gain = 100

$\downarrow$   
input (c)

$\therefore$  input signal (a) to op-amp A with a gain (-10) ( $10\text{kHz} < \text{opamp A GBW}$ )

input signal (b) to op-amp B with a gain (-1) ( $5.5\text{MHz} < \text{opamp A GBW}$ )

$\downarrow$  output

output from (a) and (b) into summing amplifier (gain: -10) (combined  $< \text{op-amp B GBW}$ )

2c)

Using  $kV_L$ ,

$$V_x - I_x R - V_1 = 0$$

$$R_{2c} = \frac{V_x}{I_x}$$

$$R = \frac{V_x - V_1}{I_x}$$

$$= \frac{V_x - (0.99V_x)}{I_x}$$

$$= \frac{0.01V_x}{I_x}$$


$$R = 0.01 R_x$$

$$R_{2c} = 100 R_x$$

d)

Node  $V_1$ : KCL

$$I_x + I_2 = I_1$$

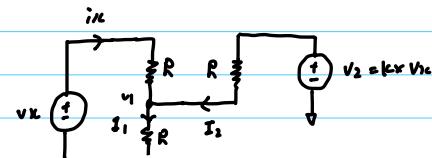

$$\frac{V_x - V_1}{R} + \frac{V_2 - V_1}{R} = \frac{V_1}{R}$$

)  $\times R$

$$V_x - 0.99V_x + kV_x - 0.99V_x = 0.99V_x$$

$$kV_x = 0.99V_x + 0.99V_x - 0.01V_x$$

$$kV_x = 1.97V_x$$


$$k = 1.97$$

e)

non-inverting op-amp with  $\frac{P_2}{P_1}$  of 0.97- positive input back to  $V_x$ 


d)

Simple circuit, passive RC / CR

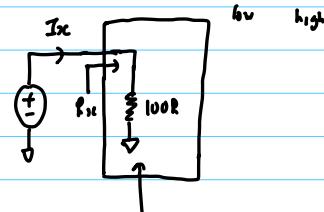

equivalent, hence only one node of the resistor can be used, either  
to ground

Hence, we use a simple high pass filter.

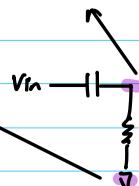

- 3a)
- A → Inverting amplifier
  - B → First-order low pass filter
  - C → Summing amplifier

b) Inverting amplifier:  $\left| \text{gain} : \left( -\frac{10}{1} \right) \right| = 10$

Db scale:  $20 \log(10) = 20 \text{ dB}$

First order low pass filter:  $\left| \text{gain} : -\left( \frac{100R}{R} \right) \right| = 100$

Db scale:  $20 \log(100) = 40 \text{ dB}$

### Summing amplifier

Gain:  $10 + 100 = 110$

Db scale:  $20 \log(110) = 40.8 \text{ dB}$

- Cut-off frequency for low-pass filter is 1 kHz (decade af  $-20 \text{ dB / decade}$ )

4a)


Ideal op-amp,  $i_+ = i_- = 0$ , (assume no input current)  
 virtual short,  $V_- = V_+ = V_{OL}$

$$V_- = V_{OL} \times \frac{R_1}{R_2 + R_1} = V_x$$

$$\begin{aligned} V_{OL} &= V_{OL} \times \frac{R_2 + R_1}{R_1} \\ &= V_x \times \left( \frac{R_2}{R_1} + 1 \right) \end{aligned}$$

Since we assume no input current

$$i_+ = i_- = 0,$$

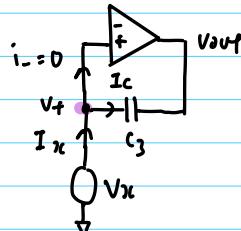

By KVL,

$$I_x = I_c$$

$$I_x = \frac{V_+ - V_{OL}}{\frac{1}{j\omega C_3}} \quad (\text{Since } V_+ = V_x)$$

$$\begin{aligned} I_x &= \frac{V_x - (V_{OL} \times \left( \frac{R_2}{R_1} + 1 \right))}{\frac{1}{j\omega C_3}} \\ &= \frac{V_x - V_x \frac{R_2}{R_1} - V_x}{\frac{1}{j\omega C_3}} \end{aligned}$$

$$= \frac{V_x (1 - \frac{R_2}{R_1} - 1)}{\frac{1}{j\omega C_3}}$$

$$I_x = -V_x \frac{\frac{R_2}{R_1}}{\frac{1}{j\omega C_3}} = -V_x \frac{R_2 j\omega C_3}{R_1}$$

$$Z_x = \frac{V_x}{I_x} = -\frac{R_1}{R_2 j\omega C_3} \quad \omega = 2\pi f$$


$\therefore$  Impedance of capacitor is:  $\frac{1}{j\omega C}$

$$\frac{1}{j\omega C} = -\frac{R_1}{R_2 j\omega C_3}$$

$$\frac{1}{C} = -\frac{R_1}{R_2 C_3} \rightarrow C = -\frac{R_2 C_3}{R_1} \quad (C \text{ has a negative impedance})$$

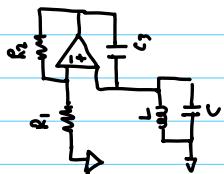4) LC resonant freq:  $\frac{1}{2\pi f_{LC}}$

Since in parallel, total capacitance is the sum of capacitance. Hence, we can add the LC network in parallel with the circuit in Fig 4a).



New resonant freq:  $\frac{1}{2\pi \sqrt{L(C - \frac{R_1 C}{R_2})}}$

∴ As  $R_1$  resistance varies, resonant frequency in the circuit will change.

$$\begin{aligned} 5a) \quad f_{3dB} &= \frac{1}{2\pi R_1 C_1} \\ &= \frac{1}{2\pi (9k)(88.4\mu)} \\ &\approx 200 \text{ kHz} \end{aligned} \quad \begin{aligned} \text{gain: } &-\frac{R_1}{R_2} \times \frac{1}{j\omega C R_1 + 1} \\ &= -\frac{9k}{1k} \times \frac{1}{j\omega (9k \cdot 9\mu)(9k) + 1} \\ &= -9 \times \frac{1}{j\omega \times 7.96 \times 10^{-9} + 1} \end{aligned}$$


b) With capacitor  $C_1$  removed, taking into consideration of GBW effect,

$$\begin{aligned} f_{3dB, CL} &= GBW \times \frac{1k}{1k \cdot 9k} \\ &= 2M \times \frac{1}{10} \\ &= 200 \text{ kHz} \end{aligned}$$

c) Gain:  $|20 \log(9)| = 19.08 \text{ dB}$

With 3dB cutoff frequency, -3dB, since GBW is same frequency, GBW effect, -3dB  
 $19.08 \text{ dB} - 3 \text{ dB cut-off} - 3 \text{ dB GBW} \approx 13.1 \text{ dB}$

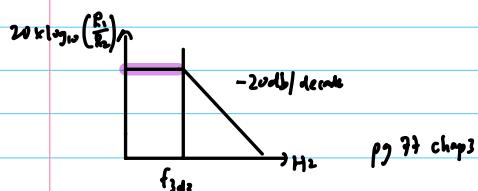d) Yes. Gain magnitude is constant ( $\frac{R_1}{R_2}$ ) for frequencies smaller than the 3dB cut-off



Low-pass filter

$\omega < 200\text{kHz}$  (inverting amp)

- e) If  $v_i(t) = V_{pk} \sin(2\pi \times 10k\text{Hz} t)$ , find max  $V_{pk}$  such that  $V_{out}$  is w/o distortion

$$V_{out(V_{in})} : -\frac{R_1}{R_2} \times V_{pk} \sin(2\pi \times 10k\text{Hz} t) \quad (inverting)$$

$$V_{out(V_{os})} = V_{os} \times \left(1 + \frac{R_1}{R_2}\right) \quad (non-inverting)$$

Since op-amp powered by  $\pm 5V$  supply

$$-5 < -\frac{R_1}{R_2} \times V_{pk} \sin(2\pi \times 10k\text{Hz} t) + V_{os} \times \left(1 + \frac{R_1}{R_2}\right) < 5$$

$$-5 < -9V_{pk} + (20m)(1 + \frac{9}{1}) < 5$$

$$-5.2 < -9V_{pk} < 4.8$$

$$-0.53V < V_{pk} < 0.58V$$

Hence max allowable is  $0.53V$ .

- f) 1) Summing amplifier

- Set  $R_2$  to  $9k\Omega$  so gain will be  $-1$ , input  $0.2V$  to cancel out  $V_{os}$

$$\therefore -\frac{R_1}{R_2} \times V_{pk} \sin(2\pi \times 10k\text{Hz} t) + V_{os} \times \underbrace{\left(1 + \frac{R_1}{R_2}\right)}_{cancel\ out} - \left(\frac{R_1}{R_2}\right) \times 0.2V$$

- 2) DC block capacitor

- Since offset is in DC, and in DC, capacitor acts as open circuit,  $V_{os}$  will not be amplified 10 times

6a)  $f_{3\text{dB}, \text{CL}} = GBW \times \frac{R_1}{R_1 + R_2}$

$= GBW \times 1$  (since it is unity gain)

$\approx 0.5\text{MHz}$

b) Min peak voltage:  $(1 + \frac{R_2}{R_1}) \times \sqrt{V_n^2 \times 0.5\text{MHz} \times \frac{\pi}{2}}$

 $= (1) \times \sqrt{(20\text{n})^2 \times 0.5\text{MHz} \times \frac{\pi}{2}}$

$= 17.7\mu\text{V} \rightarrow \text{rms}$

$V_p = 17.7\mu\text{V} \times \sqrt{2}$

$\approx 25\mu\text{V}$


c) Max  $\rightarrow$  slew rate / GBW

$2\pi f \times V_{\text{out, pk}} \sin(2\pi(0.5\text{MHz})t) < 0.5\text{V}/\mu\text{s}$

$2\pi(0.5\text{MHz}) \times V_{\text{out}} < 0.5\text{V}/\mu\text{s}$

$2\pi(0.5\text{MHz}) \times V_{\text{out}} < 0.5 \times 10^6$



$V_{\text{out}} < 0.159\text{V}$

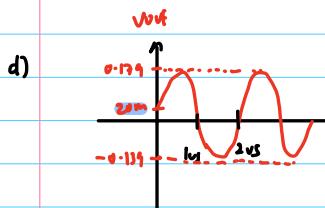

input offset = 20mV

period  $\frac{1}{f} = \frac{1}{0.5\text{MHz}}$   
 $= 2\mu\text{s}$

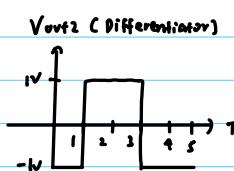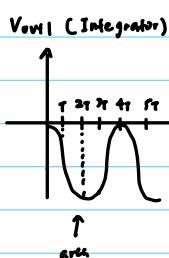e)  $V_{\text{out1}} \rightarrow \text{Integrator} \rightarrow \text{area under curve}$   
 $V_{\text{out2}} \rightarrow \text{Differentiator} \rightarrow \text{gradient of graph}$  } both inverting



When +ve gradient, +ve output,  
when -ve gradient, -ve output

f) For  $V_{\text{out2}}$  to have  $V_{pp} = 2\text{V}$ ,  $V_p = 1\text{V}$

$$V_p = -R_2 C_2 \frac{d(V_t)}{dt} = 1\text{V}$$

$$= -R_2 C_2 \left(\frac{2\text{V}}{2\mu\text{s}}\right) = 1\text{V} \Rightarrow R_2 C_2 = T$$

d)  $v_1(t) = \cos(2\pi \times 100000 \times t)$

$$\frac{dv_1(t)}{dt} = -2\pi \times 100000 \times \sin(2\pi \times 100000 \times t)$$

b)  $v_2(t) = \cos(2\pi \times 200000 \times t)$

$$\frac{dv_2(t)}{dt} = -2\pi \times 200000 \times \sin(2\pi \times 200000 \times t)$$

c)  $V_{out}(t) = -RL \frac{dV_{in}(t)}{dt}$

$$0.1V = -RL (-2\pi \times 100000)$$

$$RL = \frac{0.1}{2\pi \times 100000}$$

$$= 1.59 \times 10^{-7}$$

$$R = \frac{1.59 \times 10^{-7}}{1 \times 10^{-9}}$$


$$= 159 \Omega$$

∴ Hence, we can choose a  $1nF$  capacitor, and  $159\Omega$  resistor

check for  $V_3(t)$

$$-(1nF)(159\Omega) \times -2\pi \times 200000 \approx 0.2V$$

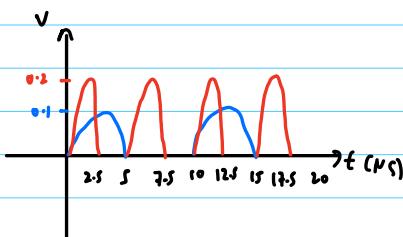
d) Super diode acts as half-wave rectifier.



$$\text{period} = \frac{1}{1m} = 10 \mu s$$

$$\text{period} = \frac{1}{2m} = 5 \mu s$$

e)

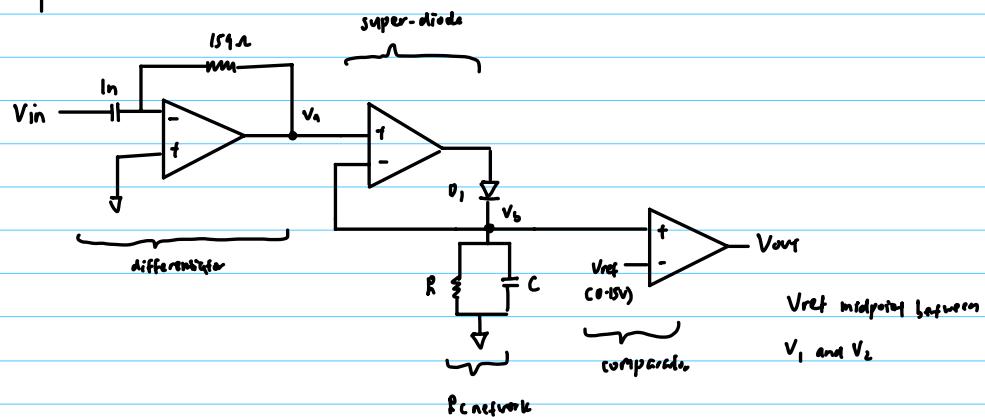

{) If all op-amps have offset voltage of 20mV, in the third op-amp, the non-inverting terminal will have a offset voltage total of 60mV. Hence, when added with the input signal,  $V_{in}$  (0.1, 0.2), the resulting input to the comparator will either be 0.16V or 0.26V. Since both these voltages are higher than the comparators threshold voltage (0.15V), the comparator will not work.