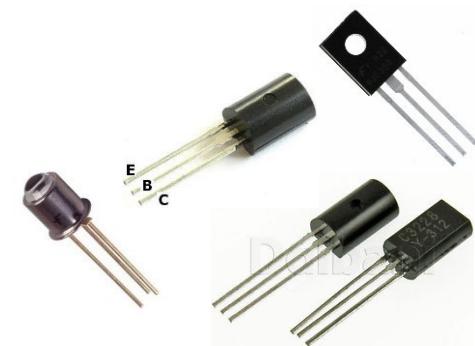


Bipolar Junction Transistor (BJT)

Bipolar Junction Transistor (BJT)


1. Introduction
2. Modes of Operation: Forward Active, Saturation, Cut-Off and Reverse Active
3. Forward Active Current-Voltage Characteristic
4. Large-Signal Model and dc Analysis
5. Amplifier Circuit
6. Small-Signal Model (Simplified Hybrid- π) and ac Analysis
7. Other Hybrid- π Small-Signal Models




Reference

- Sedra and Smith, Microelectronic Circuits, Fifth Edition, Oxford (2004), pp. 159 – 168, 173 - 183, 203 - 241.

BJT – Introduction (Structure)

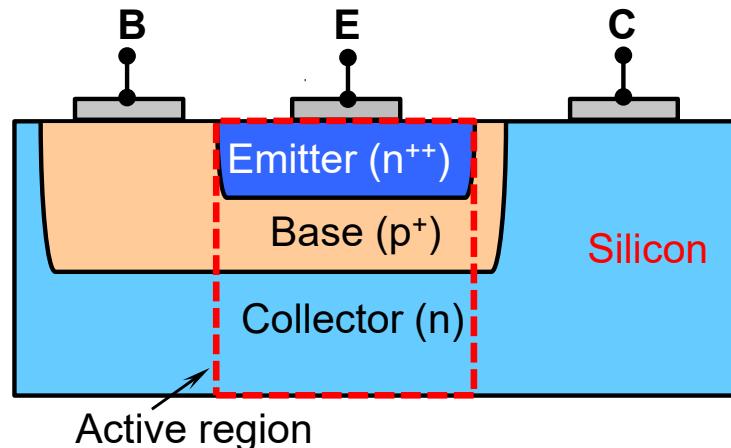


Active region of npn BJT:

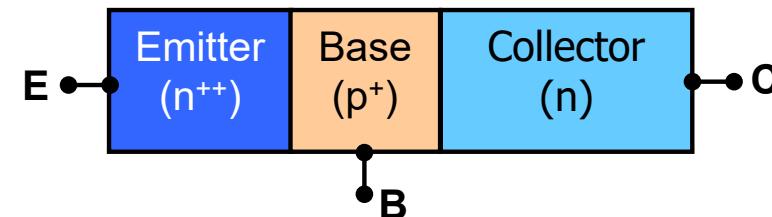


- ❑ Bipolar junction transistor (BJT) is a 3-terminal device made using a single crystal semiconductor (typically silicon), just like the *pn*-junction diode.
- ❑ BJT is made with **3 doped semiconductor regions**, namely **emitter**, **base** and **collector**, corresponding to the 3 terminals.
- ❑ Left figure above shows a schematic cross-sectional view of an npn BJT, where the emitter is n-type, base is p-type and collector is n-type.
- ❑ The **active region** of the BJT is the region under (and including) the emitter. This is the part of the device that provides, for example, the **amplifying function** of the BJT. The rest of the structure is to facilitate the movement of the currents into or out of the transistor. We will focus on the active region of BJT.

BJT – Introduction (Structure)

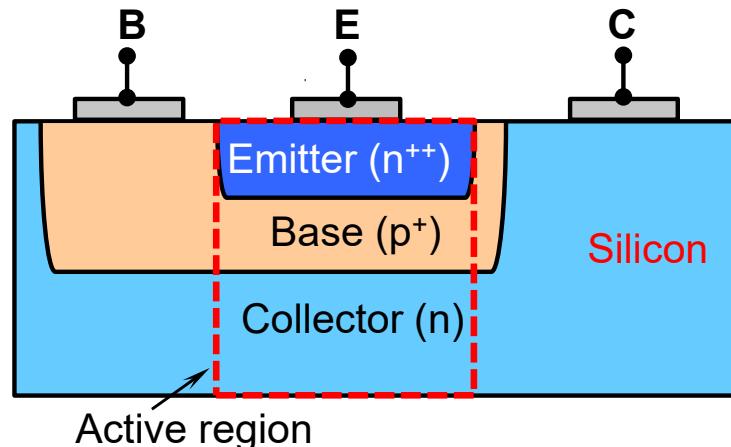


Active region of npn BJT:

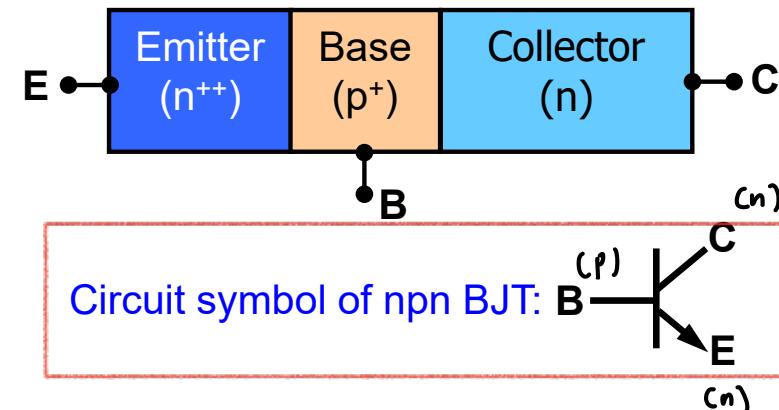


- BJT is not a symmetrical device, in particular, impurities added to the emitter is at a much higher concentration than that added to collector. Hence, **emitter** is indicated as **n⁺⁺-type** (**very heavily doped** and has many more electrons) and **collector** as **n-type**.
- Concentration of impurities (of a different type from that for emitter/collector) added to base is in between those of emitter and collector. Base is thus indicated as **p⁺-type**.
- BJT comprises two **back-to-back pn-junctions***: emitter-base junction and base-collector junction. The **two pn-junctions must be close enough to each other to interact**, and this requires the base to be **thin**.

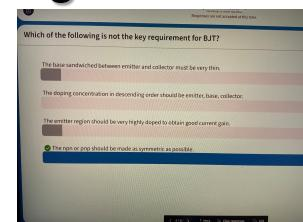* BJT cannot be made by connecting two *pn*-junctions back-to-back.




BJT – Introduction (npn vs pnp BJT)


Active region of npn BJT:

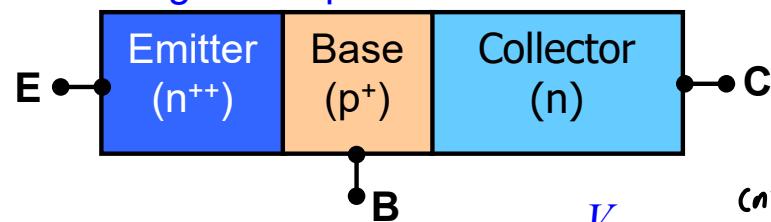


Circuit symbol of npn BJT:

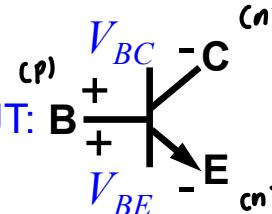

Active region of pnp BJT:

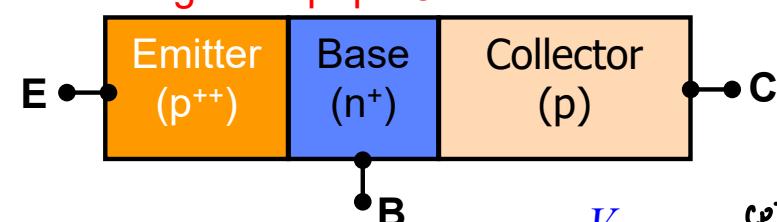

Circuit symbol of pnp BJT:

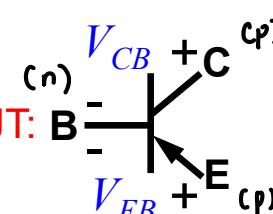

- The emitter-base junction and base-collector junction can be either forward biased or reverse biased.
- There are two types of BJT: npn and pnp (as shown above). Note the difference between the 2 structures and circuit symbols.
- For pnp BJT, the emitter is p++-type, base is n+-type and collector is p-type.
- Both npn and pnp BJTs perform similar functions: **amplification** and **switching**. Their difference lies in the **biasing polarity** of the two junctions when operating. For a given mode of operation, the current directions and voltage polarities are exactly opposite between npn and pnp BJTs.
- Note that BJT is a **nonlinear device**, just like the **pn-junction**.

Bipolar Junction Transistor (BJT)

Bipolar Junction Transistor (BJT)

1. Introduction
2. Modes of Operation: Forward Active, Saturation, Cut-Off and Reverse Active
3. Forward Active Current-Voltage Characteristic
4. Large-Signal Model and dc Analysis
5. Amplifier Circuit
6. Small-Signal Model (Simplified Hybrid- π) and ac Analysis
7. Other Hybrid- π Small-Signal Models




Reference

- Sedra and Smith, Microelectronic Circuits, Fifth Edition, Oxford (2004), pp. 159 – 168, 173 - 183, 203 - 241.

BJT – Modes of Operation


- BJT has 2 *pn-junctions* (emitter-base junction and collector-base junction), and each *pn-junction* can be either forward biased or reverse biased, hence there are 4 possible permutations of the biasing arrangement for a BJT. These correspond to different modes of operation of the BJT, as shown in the table below for an npn BJT*:

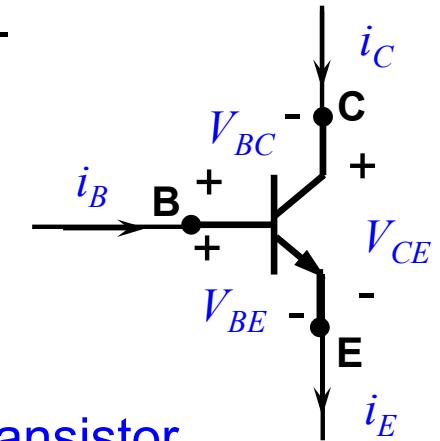Modes of operation of the npn bipolar junction transistor



Mode of Operation	Emitter-Base Junction	Collector-Base Junction	Application
Cut-off	Reverse biased ($V_{BE} < 0$ for npn)	Reverse biased ($V_{BC} < 0$ for npn)	Logic - OFF State
Forward Active	Forward biased ($V_{BE} > 0$ for npn)	Reverse biased ($V_{BC} < 0$ for npn)	Amplifier
Saturation	Forward biased ($V_{BE} > 0$ for npn)	Forward biased ($V_{BC} > 0$ for npn)	Logic - ON State
Reverse Active	Reverse Biased ($V_{BE} < 0$ for npn)	Forward Biased ($V_{BC} > 0$ for npn)	Not used

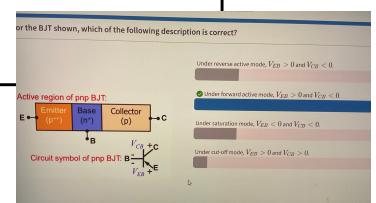
* A similar table for pnp bipolar junction transistor is shown in the [Appendix A](#).



BJT – Modes of Operation (for reference)

Some definitions:

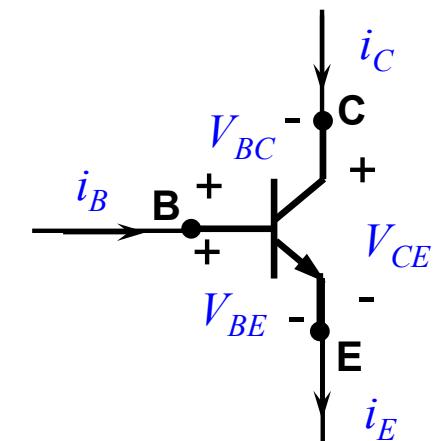- Voltage at the base with-respect-to the emitter (i.e., the **base-emitter junction voltage**) - V_{BE}
- Voltage at the base with-respect-to the collector (i.e., the **base-collector junction voltage**) - V_{BC}
- Voltage at the collector with-respect-to the emitter - V_{CE} ($= V_{BE} - V_{BC}$) or $V_{CE} = V_{CB} + V_{BE}$ or $V_{CE} = V_{CB} - V_{EB}$



Cut-off operation (used as the OFF-state in logic circuit):

- Both **emitter-base junction** and **base-collector junction** are **reverse biased**.
- $V_{BE} < 0$ and $V_{BC} < 0$ for npn BJT.
- Practically no current flows in the BJT. Between collector and emitter is practically an open circuit.


Saturation operation (Used as the ON-state in logic circuit):

- Both **emitter-base junction** and **base-collector junction** are **forward biased**.
- $V_{BE} > 0$ (~ 0.7 V) and $V_{BC} > 0$ (~ 0.7 V) for npn BJT.
- Large current flows in the BJT. Between collector and emitter is practically a **short circuit**, and V_{CE} is a small voltage.

BJT – Modes of Operation (for reference)

□ Forward active operation (used in amplifier circuit):

- Emitter-base ($n^{++}p^+$) junction is forward biased and base-collector (p^+n) junction is reverse biased.
- $V_{BE} > 0$ and $V_{BC} < 0$ for npn BJT.
- BJT works as a controlled current regulator. The main current through the BJT flows between the emitter and collector, i_C , and it is controlled by the base-emitter junction voltage, v_{BE} (or equivalently, the base current, i_B). This is transistor action and is made possible by an n^{++} -type emitter and p^+ -type base, and a thin base. See slides BJT-11 and -12.



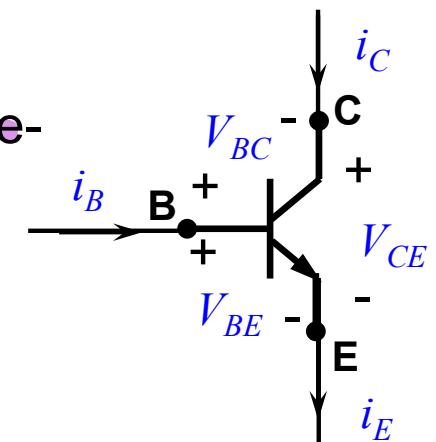


□ Reverse active operation (not used):

- Emitter-base ($n^{++}p^+$) junction is reverse biased and base-collector (p^+n) junction is forward biased.
- $V_{BE} < 0$ and $V_{BC} > 0$ for npn BJT.
- This mode of operation is not useful, as it does not provide amplification, unlike the forward active operation. This is owing to the non-symmetrical nature of BJT, specifically, collector being n-type while emitter is n^{++} -type.

BJT – Modes of Operation


- The circuit below shows an npn BJT in common-emitter configuration. The common-emitter IV characteristics are also plotted, which shows the relationships between the collector current, i_C , and the collector-emitter voltage, v_{CE} , for different base currents, i_B , (or equivalently different v_{BE}).
- The regions corresponding to the forward active, saturation and cut-off modes of operation are as indicated in the plot below.
- We shall be focusing on BJT in forward active operation.

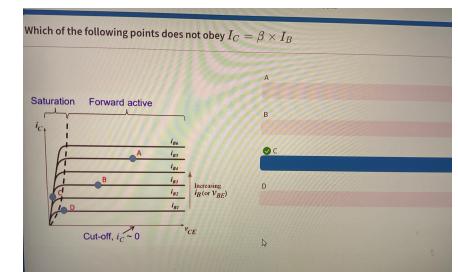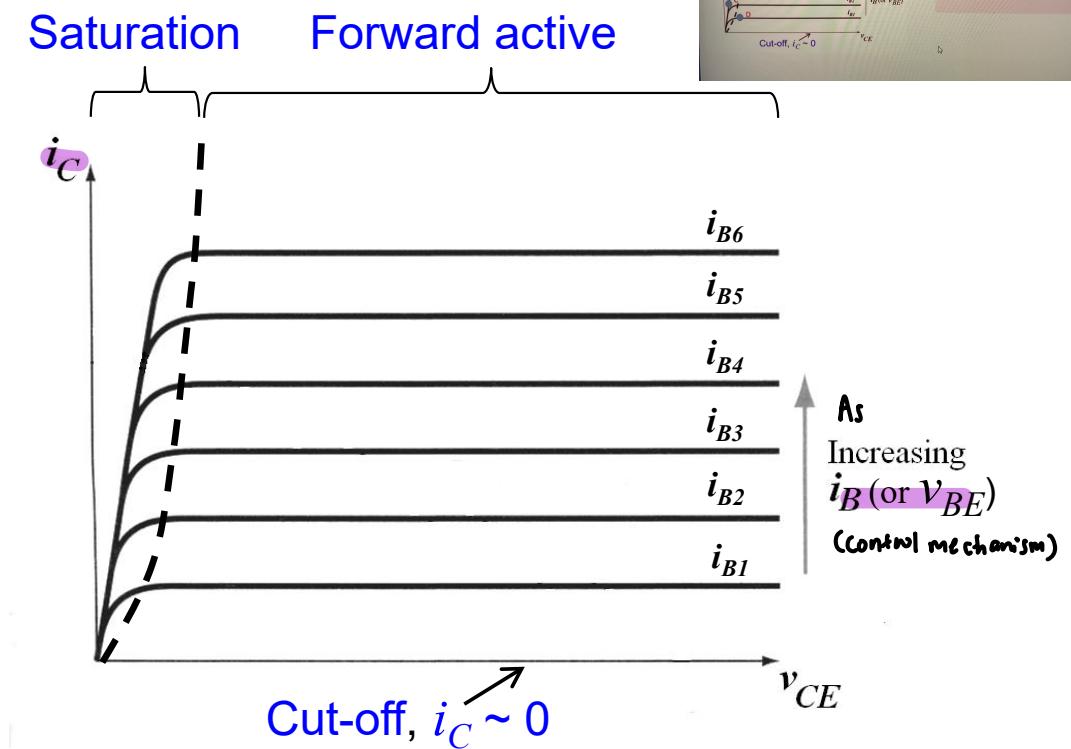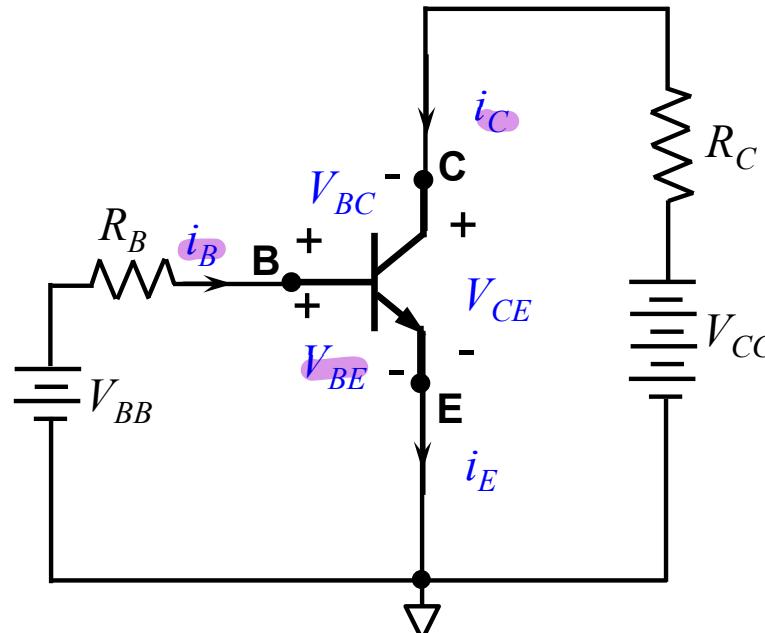

Bipolar Junction Transistor (BJT)

Bipolar Junction Transistor (BJT)

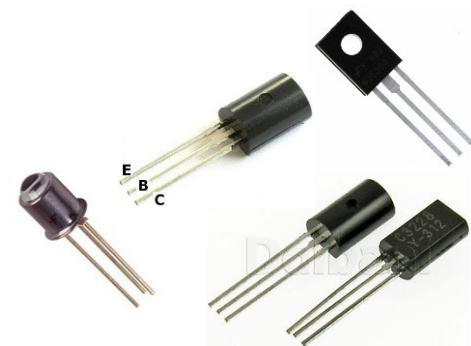1. Introduction
2. Modes of Operation: Forward Active, Saturation, Cut-Off and Reverse Active
3. **Forward Active Current-Voltage Characteristic**
4. Large-Signal Model and dc Analysis
5. Amplifier Circuit
6. Small-Signal Model (Simplified Hybrid- π) and ac Analysis
7. Other Hybrid- π Small-Signal Models



Reference

- Sedra and Smith, Microelectronic Circuits, Fifth Edition, Oxford (2004), pp. 159 – 168, 173 - 183, 203 - 241.



BJT – Forward Active IV Characteristic

- Discussion will be based on an npn BJT, which applies to a pnp BJT as well, except for the bias voltage polarities and current directions (see Appendix B). ~~**~~
- In forward active operation, emitter-base junction is forward biased and base-collector junction is reverse biased: $v_{BE} > 0$ and $v_{BC} < 0$ for an npn BJT. The collector current, i_C , which flows into the collector and through the reverse-biased base-collector junction is controlled by v_{BE} -


$$i_C = I_S e^{v_{BE}/V_T} \quad (3.1)$$

- The base current, i_B , which flows into the base and through the forward-biased base-emitter junction is

$$i_B = \frac{I_S}{\beta} e^{v_{BE}/V_T} \quad (3.2)$$

- In the above, I_S is the saturation current; V_T is the thermal voltage ($V_T = kT/q \approx 0.025$ V at $T = 300$ K); and β is the common-emitter current gain ($\beta = i_C/i_B$).
- From equations (3.1) and (3.2) -
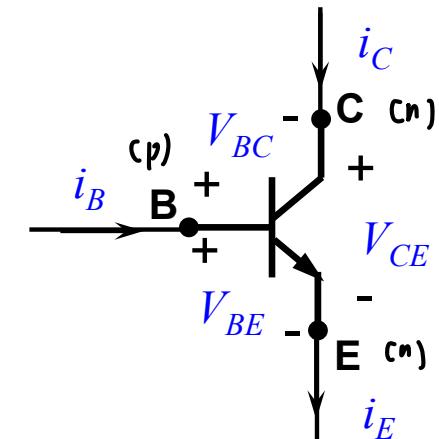
$$i_C = \beta i_B \quad \rightarrow \text{only true for forward active mode} \quad (3.3)$$




BJT – Forward Active IV Characteristic

- From equation (3.1): BJT works as a controlled current regulator, where the main current, i_C , that flows through the reverse-biased base-collector junction does not depend on v_{BC} , but is controlled by the voltage across a close by forward-biased base-emitter junction, v_{BE} . This is transistor action.
- Alternatively, i_C is seen to be controlled by i_B in equation (3.3). Typically, i_C is much greater than i_B , e.g., 100 times.
- By Kirchhoff's Current Law (KCL), the emitter current is

$$i_E = i_C + i_B = I_b(\beta + 1) \quad (3.4)$$

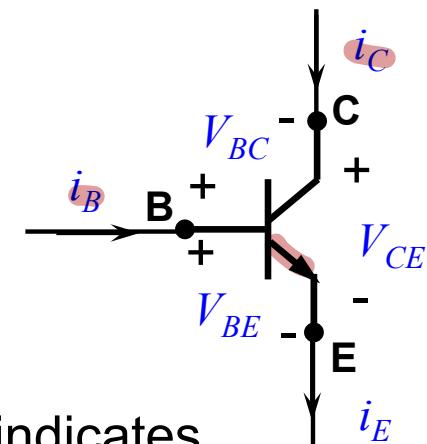- i_E flows out of emitter for npn BJT.
- The arrow head at the emitter in the BJT circuit symbol indicates the direction of current flow in forward active operation.



or


$$i_E = i_C + \frac{i_C}{\beta} = \left(\frac{\beta+1}{\beta} \right) i_C$$

$$i_C = \frac{\beta}{\beta+1} i_E \approx 100-200$$

Hence approx, $i_C \approx i_E$

BJT – Forward Active IV Characteristic (Ideal)

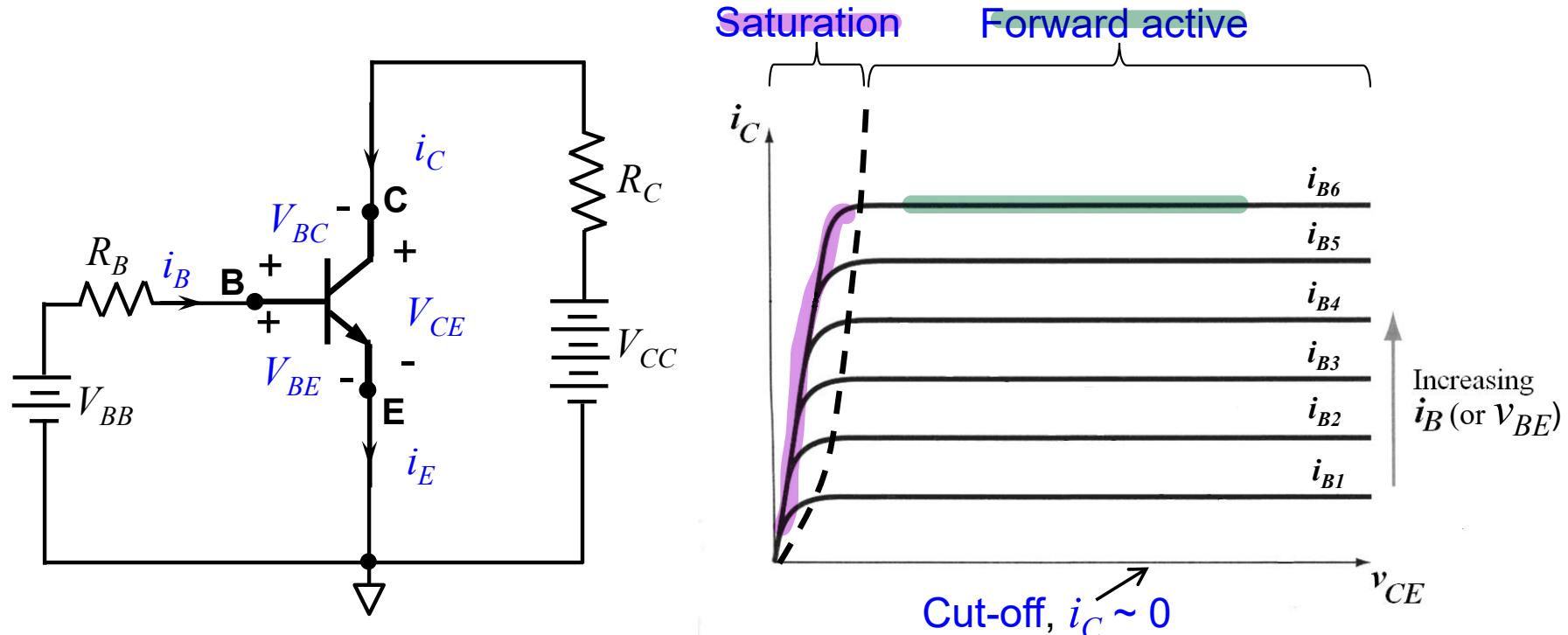Ideal common-emitter IV characteristics of an npn BJT -




In forward active operation, emitter-base junction is forward biased, hence $v_{BE} \approx 0.7$ V; while base-collector junction is reverse biased, $v_{BC} < 0$ for npn BJT.

- From eqns. (3.1) and (3.3), i_C is a strong function of v_{BE} (or i_B).
- $v_{CE} = v_{CB} + v_{BE} \approx v_{CB} = -v_{BC}$ for $v_{CE} \gg v_{BE} \approx 0.7$ V. ↗ much greater than
- From eqn. (3.1), i_C is not dependent on v_{BC} , hence not dependent on v_{CE} in forward active operation, where $v_{CE} \gg v_{BE} \approx 0.7$ V.

BJT – Forward Active IV Characteristic (Non-Ideal)

- In a real (non-ideal) BJT, i_C is not independent on v_{BC} (hence v_{CE}) in forward active operation. This is known as the **Early Effect***.
- The i_C - v_{CE} characteristics would then have a slight upward slope, as shown in the figure below.
- When all i_C - v_{CE} characteristics are projected to the negative v_{CE} -axis, they meet approximately at the same voltage, $-V_A$.
 - V_A is known as the **Early voltage**, and is typically large, e.g., ~ 100 V.
- Expression for i_C - v_{CE} is then modified to:
- The additional factor, $\frac{v_{CE}}{V_A}$, accounts for the dependence of i_C on v_{CE} , or **Early effect**.

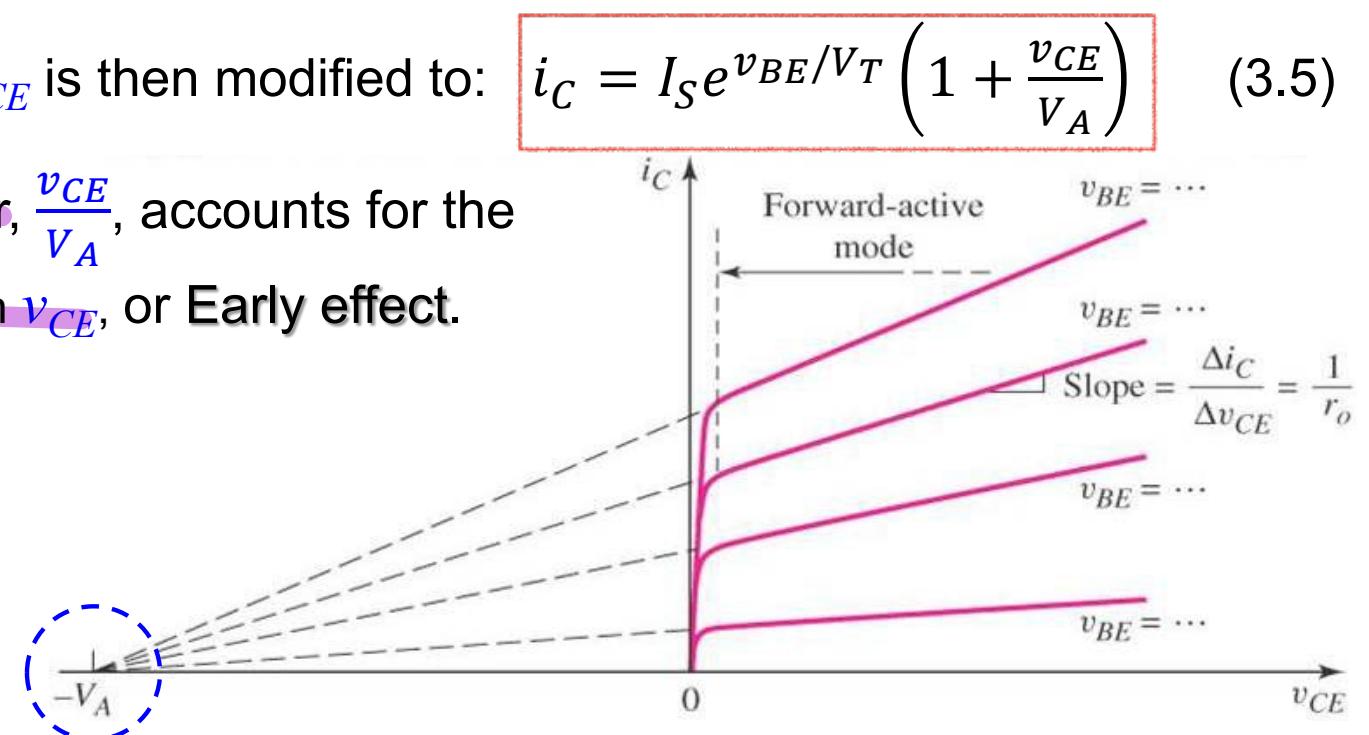

*Early Effect is also known as the base-width modulation.

Bipolar Junction Transistor (BJT)

Bipolar Junction Transistor (BJT)

1. Introduction
2. Modes of Operation: Forward Active, Saturation, Cut-Off and Reverse Active
3. Forward Active Current-Voltage Characteristic
4. Large-Signal Model and dc Analysis
5. Amplifier Circuit
6. Small-Signal Model (Simplified Hybrid- π) and ac Analysis
7. Other Hybrid- π Small-Signal Models



Reference

- Sedra and Smith, Microelectronic Circuits, Fifth Edition, Oxford (2004), pp. 159 – 168, 173 - 183, 203 - 241.


* * * * * BJT – Large-Signal Model (npn BJT)

- For an npn BJT in forward active operation: $v_{BE} > 0$ and $v_{BC} < 0$.

- $i_C = I_S e^{v_{BE}/V_T}$ (3.1)


- $i_B = \frac{I_S}{\beta} e^{v_{BE}/V_T}$ (3.2)

- $i_C = \beta i_B$ (3.3)

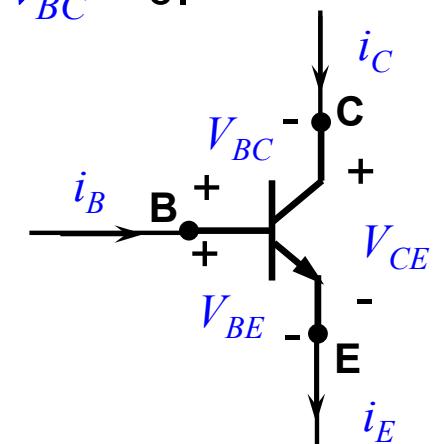


- We can model an npn BJT using

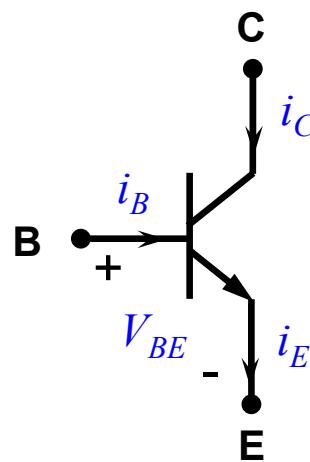- $i_B = \frac{I_S}{\beta} e^{v_{BE}/V_T}$ → a diode (between the emitter-base junction)
- $i_C = \beta i_B$ → a dependent current source




is equivalent to

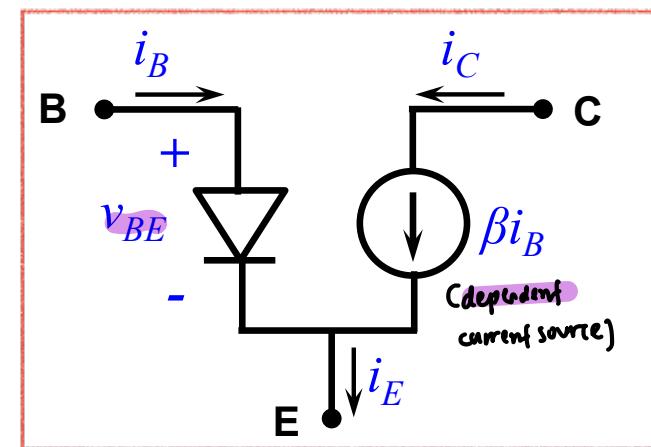



under forward active,
 v_{BE} (emitter-base)
forward biased (diode),
 V_{CE} (collector-emitter)
is constant current (pg 12)

BJT – Large-Signal Model (npn BJT)

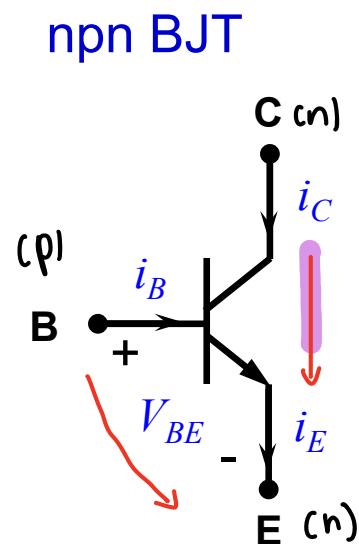- As the emitter-base junction is forward biased, $v_{BE} \approx 0.7 \text{ V}$, it can be modeled by a constant voltage source (using the constant-voltage-drop model for a forward biased pn-junction).




is equivalent to

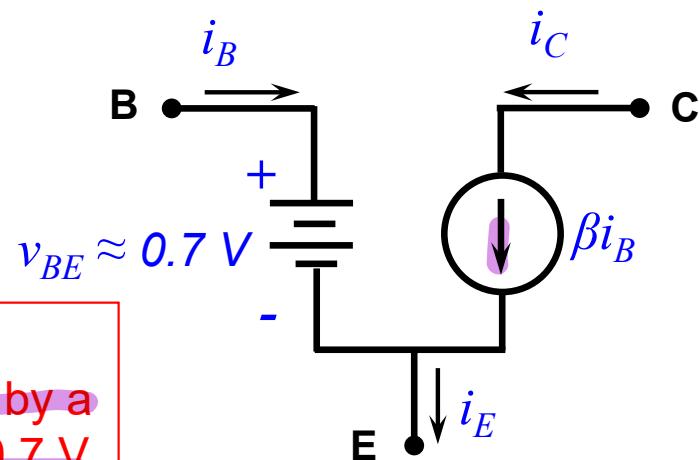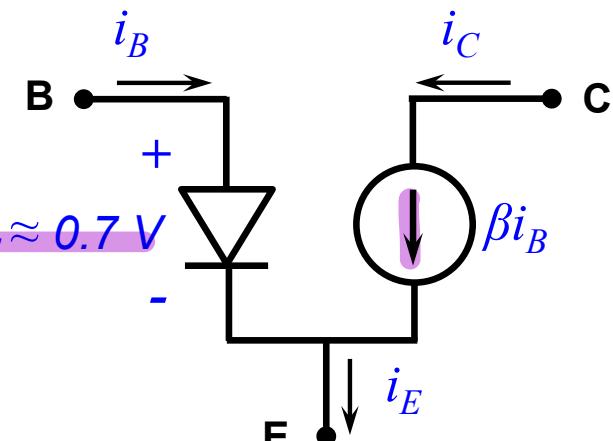


The forward biased base-emitter junction is modeled by a constant-voltage-drop of $\sim 0.7 \text{ V}$

BJT – Large-Signal Model (pnp BJT)

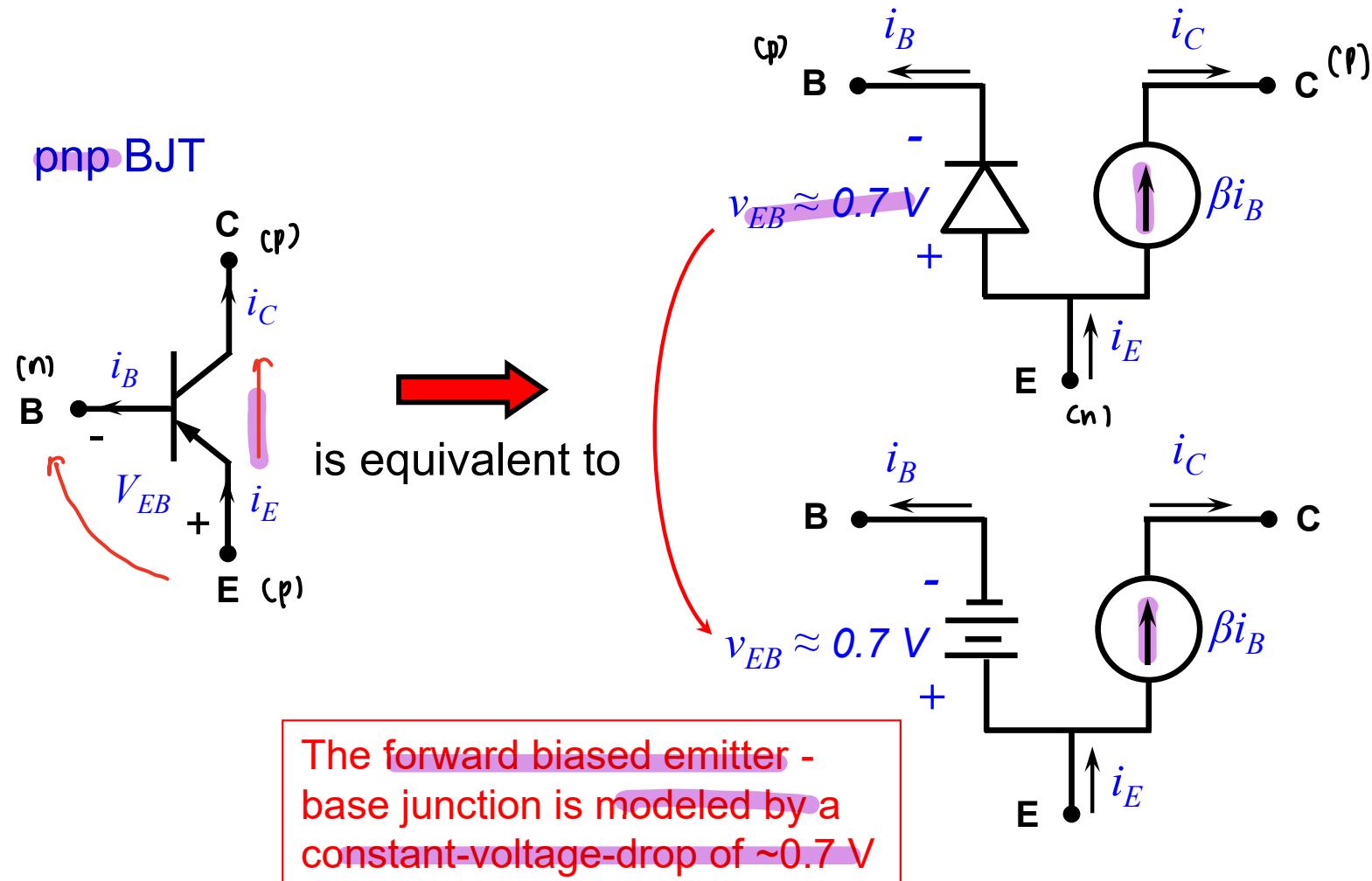- Large-signal model of a pnp BJT: polarities of voltages and directions of currents are opposite to those of an npn BJT.





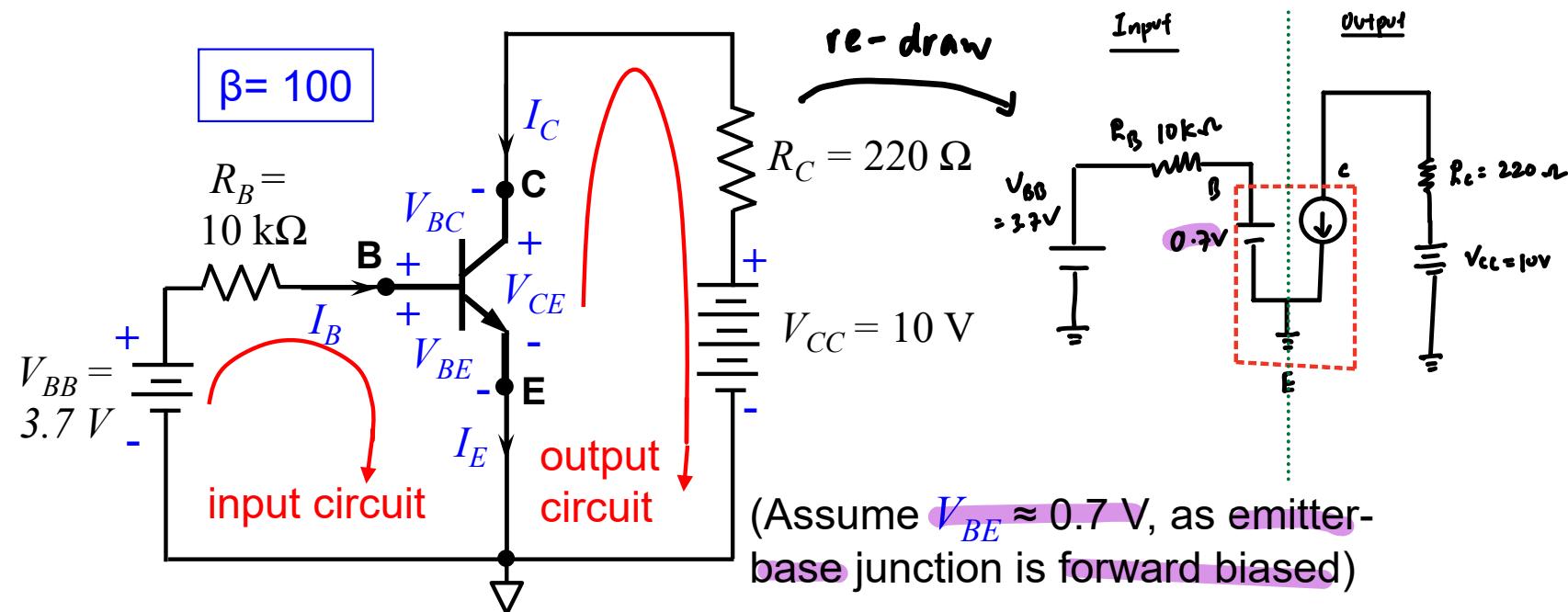BJT – Operating Point (Bias Point): DC Analysis



- We want to determine the dc operating point (also known as bias point) voltages and currents of the common-emitter amplifier circuit shown above.
- Note: all currents and voltages in above circuit are dc values and are denoted by capital letter symbol and capital subscript: for examples, I_B for base current and V_{BE} for base-emitter junction voltage.
- Input circuit, using KVL: $I_B = \frac{V_{BB} - V_{BE}}{R_B} \approx \frac{3.7 - 0.7}{10k} = 0.3 \text{ mA} = 300 \mu\text{A}$
- Output circuit, using KVL: $V_{CC} = I_C R_C + V_{CE}$ (known as the load line)

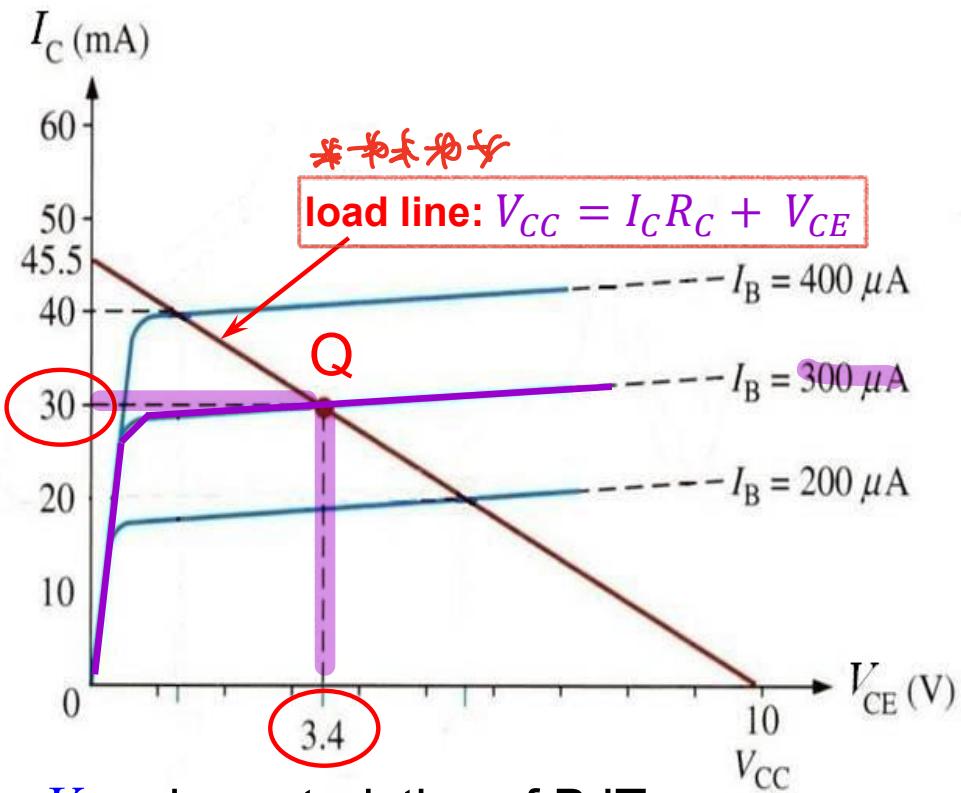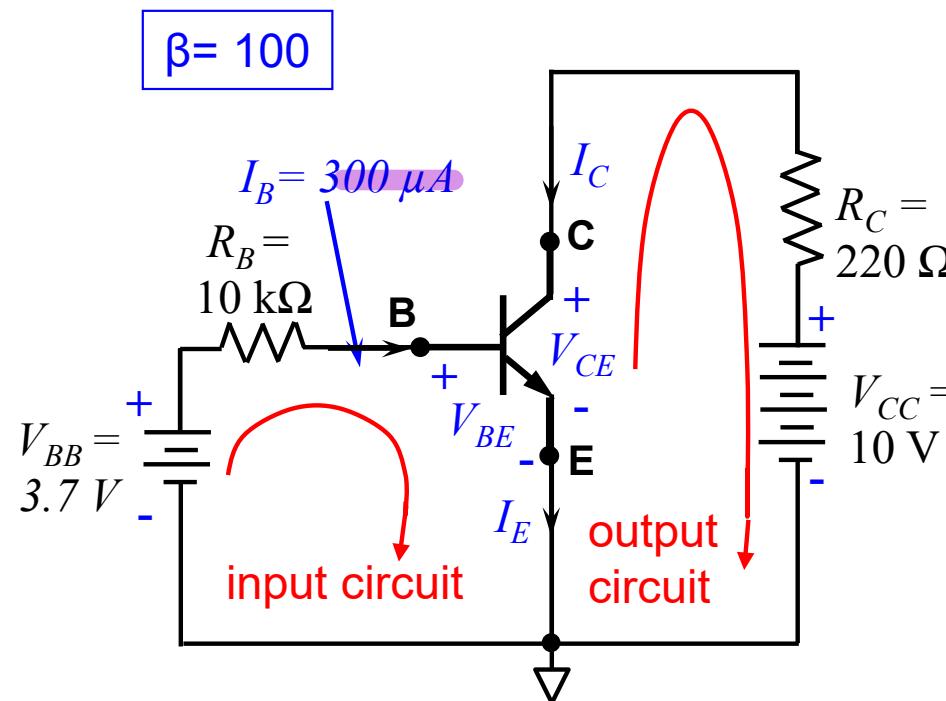BJT – Operating Point (Bias Point): DC Analysis





- I_C and V_{CE} are also governed by the I_C - V_{CE} characteristics of BJT shown above for different I_B).
 - BJT is operating at $I_B = 300 \mu A$, as determined earlier.
 - Operating point of BJT (point Q) is the intersection between its I_C - V_{CE} characteristic for $I_B = 300 \mu A$ and the output circuit load line:
- $$V_{CC} = I_C R_C + V_{CE} \quad \text{or} \quad I_C = (V_{CC} - V_{CE}) / R_C$$
- At the operating point, Q: $I_C = 30 \text{ mA}$ and $V_{CE} = 3.4 \text{ V}$ (determined graphically).

BJT – Calculation of Operating Point

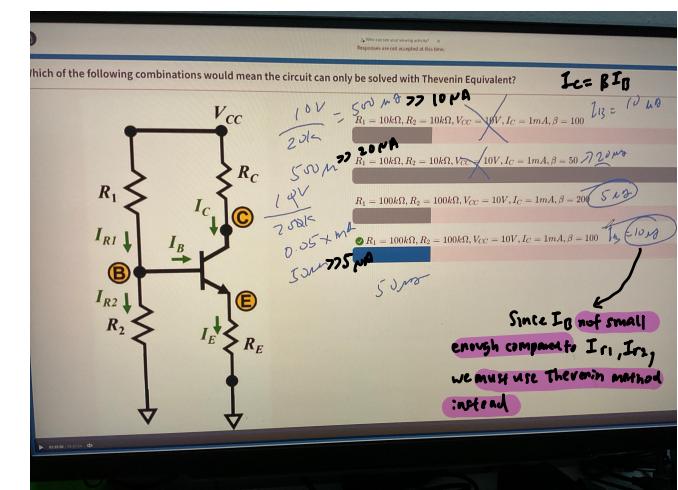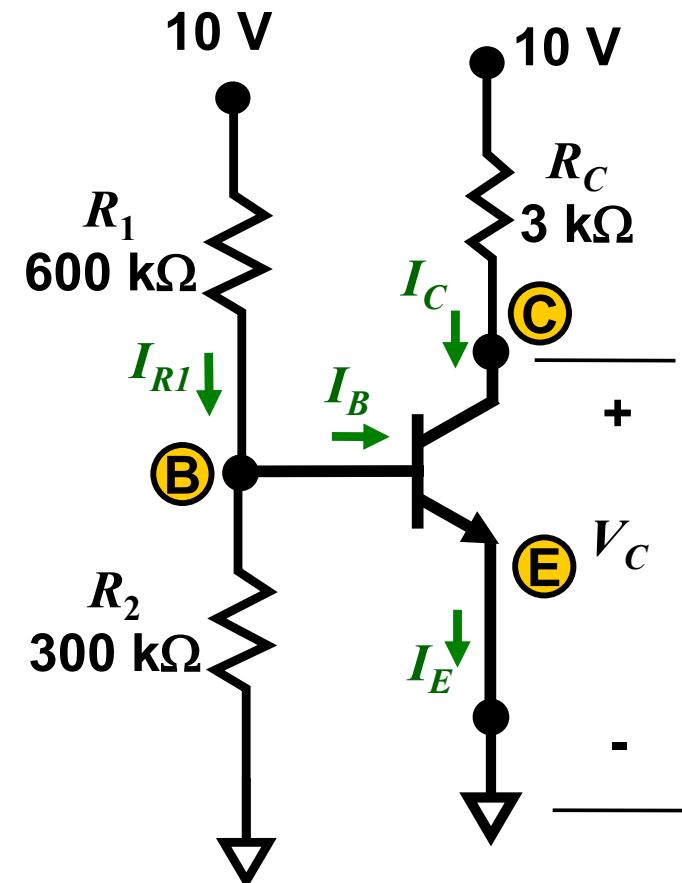Example 1 (Thevenin equivalent method) → Use this if method 2 assumption (pg 25) fails


Find the currents I_C , I_B , and I_E , and the voltage V_C using the large-signal model for the BJT, assuming that it is operating in the forward active region. The value of β for the BJT is 100.




BJT – Calculation of Operating Point

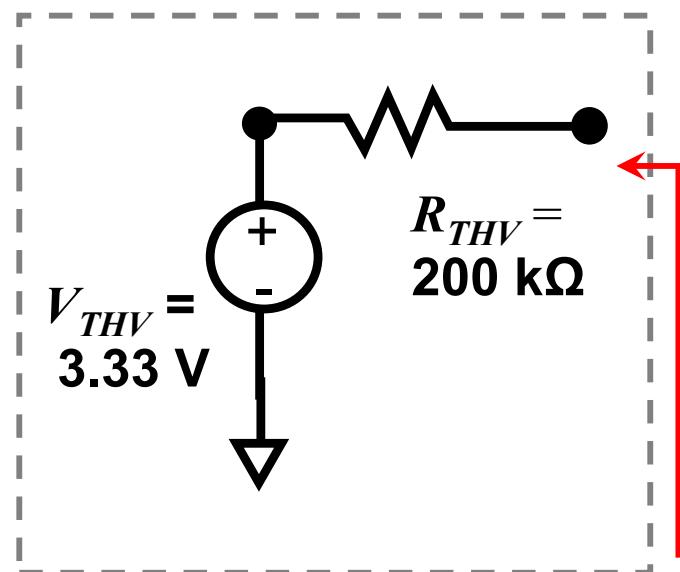Example 1 (Thevenin equivalent method)

- First, we obtain the Thevenin Equivalent Circuit of the base-biasing circuit, shown in the dashed grey box:



is equivalent to

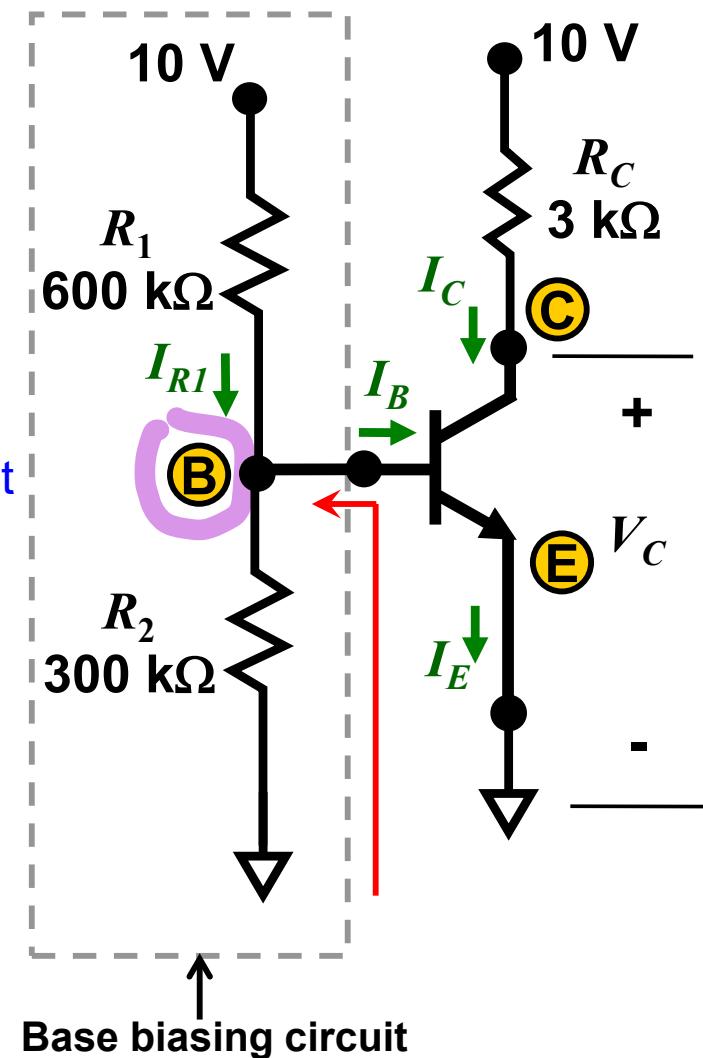

$$V_{THV} = \frac{R_2}{R_1 + R_2} \times 10 = 3.33 \text{ V}$$


$$R_{THV} = R_1 // R_2 = 200 \text{ k}\Omega.$$

Note: With the base biasing circuit replaced by its Thevenin's equivalent circuit, the above circuit has the same topography as the circuit of slide BJT-20.

BJT – Calculation of Operating Point

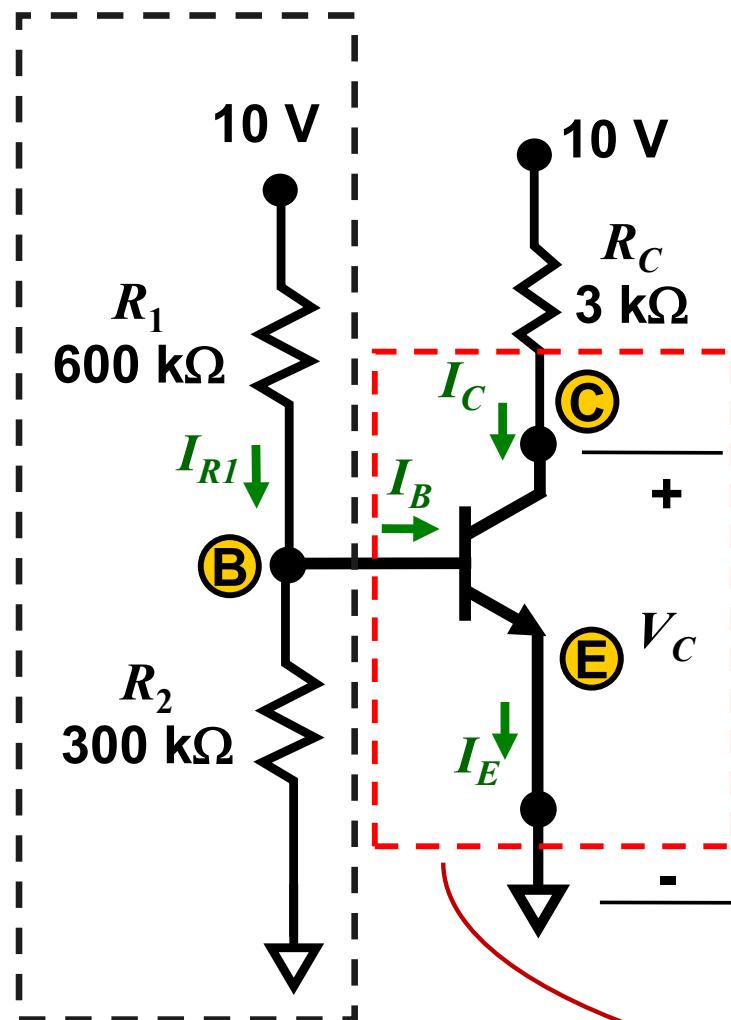Example 1 (Thevenin equivalent method)


- Next, we replace the npn BJT by its large-signal model (Forward active).



Thevenin equivalent of the base biasing circuit

After finish finding values, need to check:
 $V_{BE} > 0$ (Forward bias)
 $V_{BC} < 0$ (Reverse)

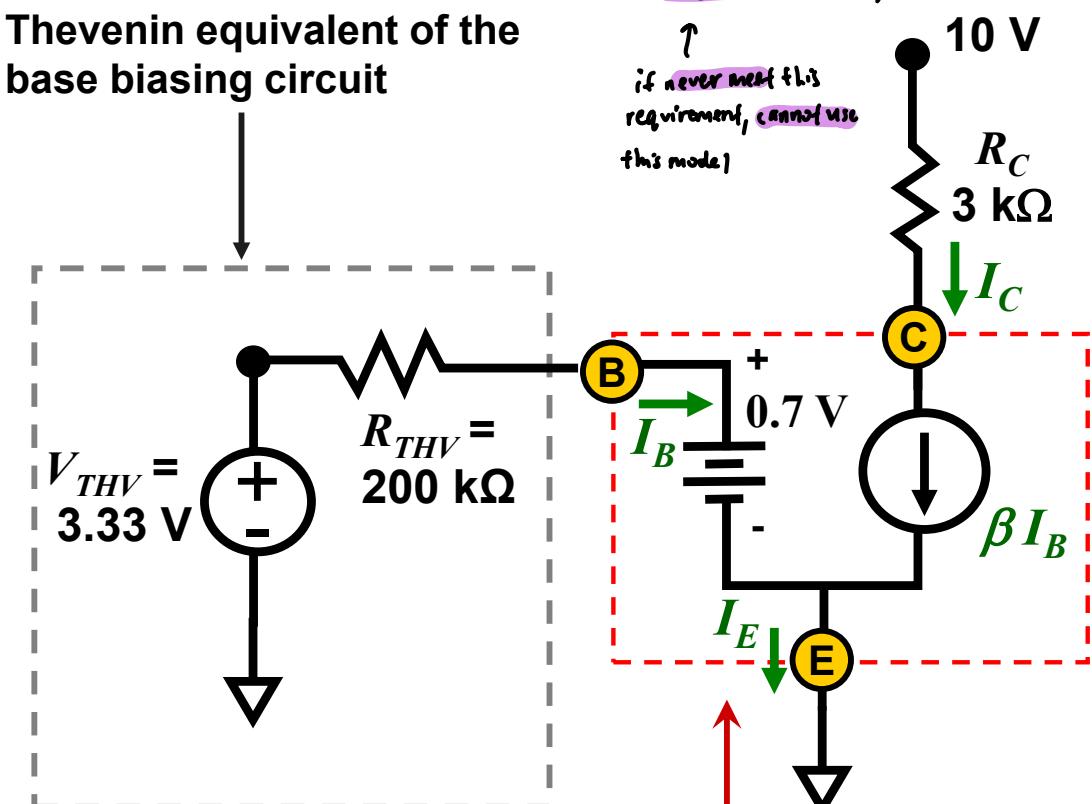
\uparrow
 if never meet this requirement, cannot use this model



Large-Signal Model for npn BJT

BJT – Calculation of Operating Point

Example 1 (Thevenin equivalent method)

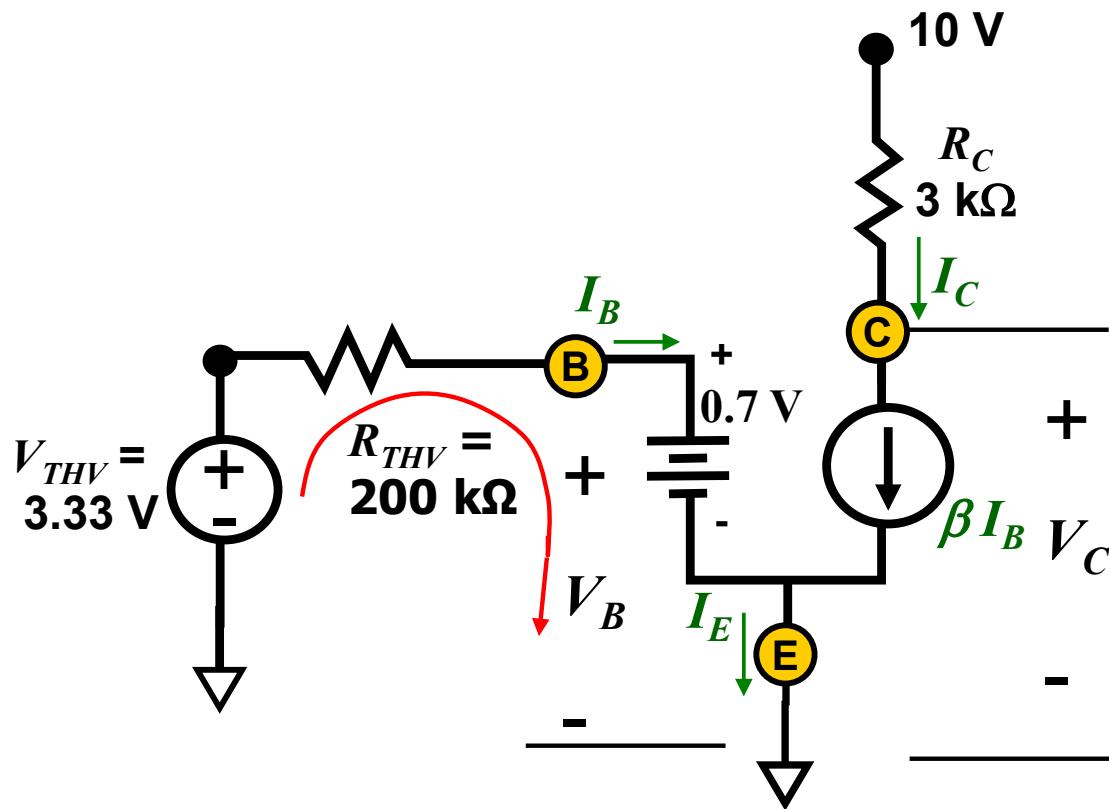

$$I_B = \frac{3.33 \text{ V} - 0.7 \text{ V}}{200 \text{ k}\Omega} = 0.0132 \text{ mA.}$$

$$I_C = \beta I_B = 100 \times 0.0132 \text{ mA} = 1.32 \text{ mA.}$$

$$I_E = (\beta + 1)I_B = 101 \times 0.0132 \text{ mA} = 1.33 \text{ mA.}$$

$$V_C = 10 \text{ V} - 3 \text{ k} \times (1.32 \text{ mA}) = 6.04 \text{ V.}$$

Check: Base voltage, $V_B = V_{BE} = 0.7 \text{ V.}$


Base-collector voltage $V_{BC} = V_B - V_C = 0.7 \text{ V} - 6.04 \text{ V} = -5.34 \text{ V,}$

Since the base-emitter pn junction is forward biased, and the base-collector pn junction is reverse biased, the npn BJT is in operating in the forward active region.

BJT – Calculation of Operating Point

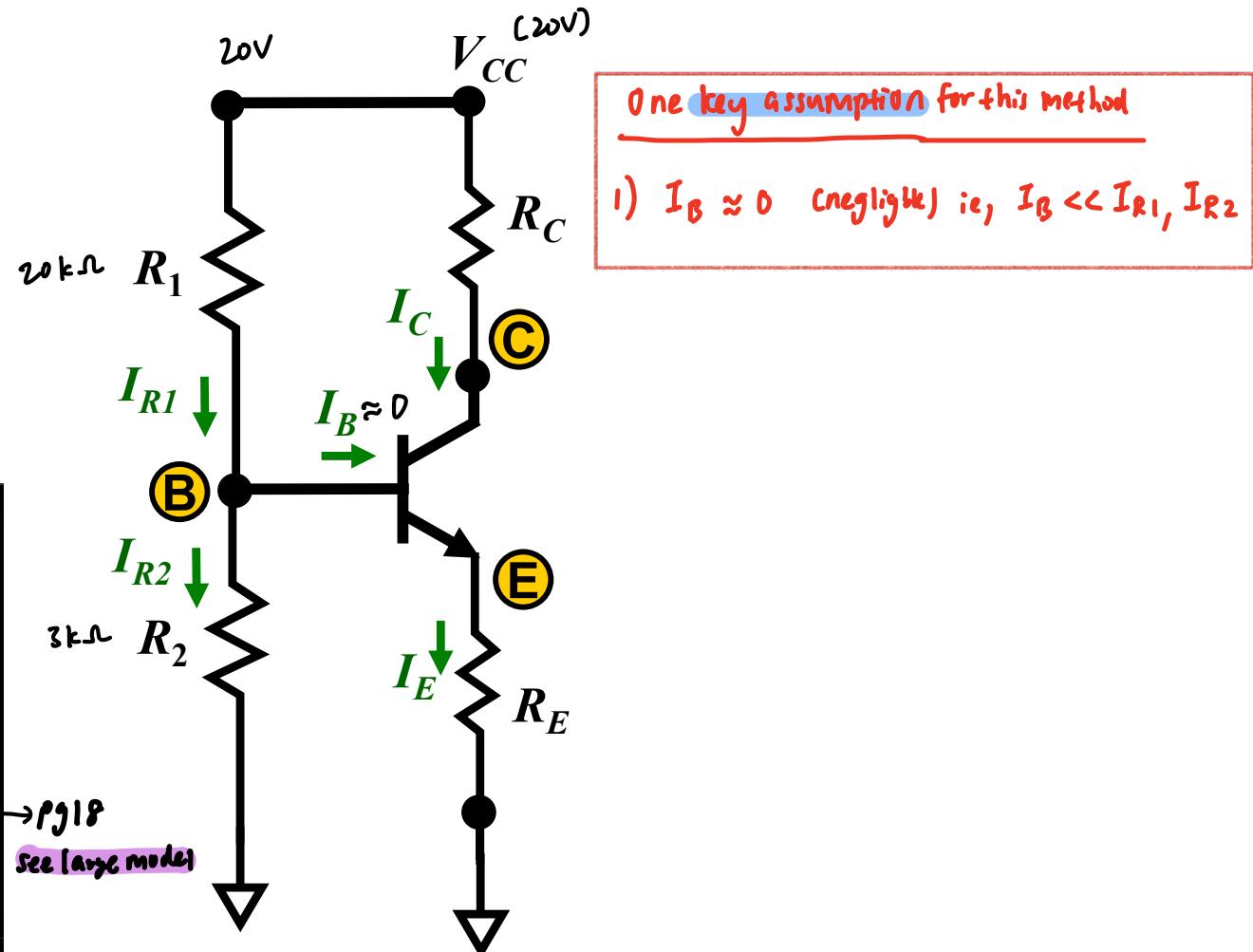
Example 2 (Voltage divider method)

The circuit below has $V_{CC} = 20$ V, $R_C = 5$ k Ω , $R_E = 1$ k Ω , $R_1 = 20$ k Ω , and $R_2 = 3$ k Ω . The value of β for the BJT is 100. Assume BJT is operating in the forward active region, determine the values of I_C and I_B using the large-signal model for the BJT



BJT – Calculation of Operating Point

Example 2 (Voltage divider method)

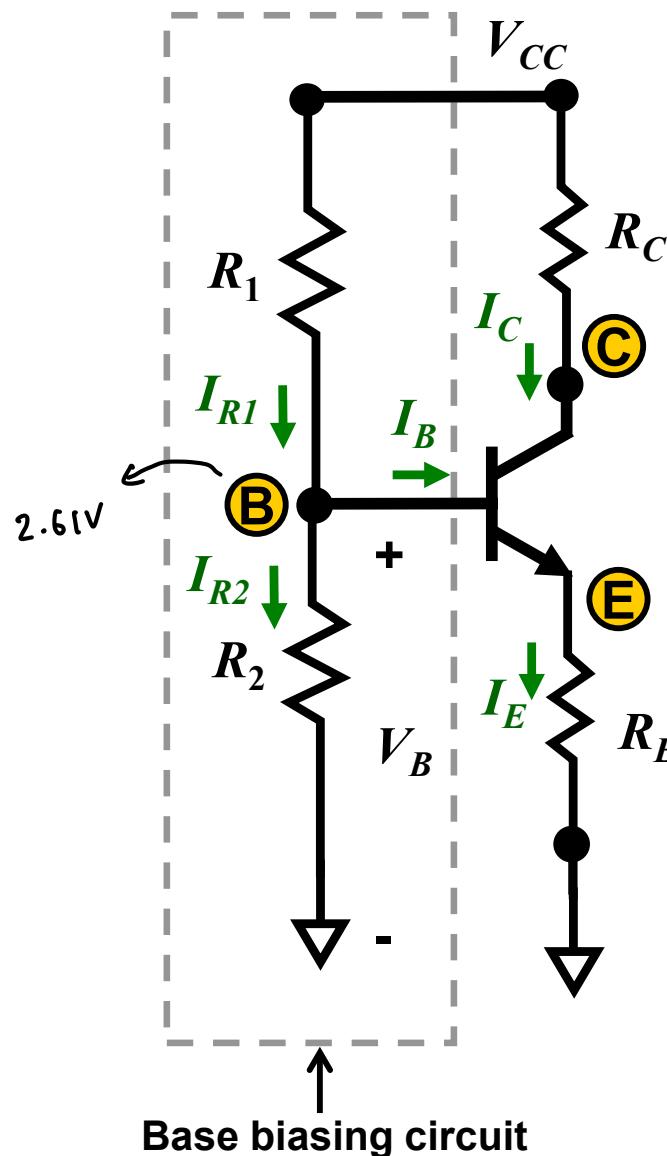


Given : $V_{CC} = 20 \text{ V}$, $R_C = 5 \text{ k}\Omega$, $R_E = 1 \text{ k}\Omega$, $R_1 = 20 \text{ k}\Omega$, and $R_2 = 3 \text{ k}\Omega$.

Assuming that I_B is small compared to I_{R1} and I_{R2} , we apply the voltage division rule to obtain


$$I_{R1} \approx I_{R2} \approx \frac{V_{CC}}{R_1 + R_2} = \frac{20 \text{ V}}{20 \text{ k}\Omega + 3 \text{ k}\Omega} = 0.87 \text{ mA}$$
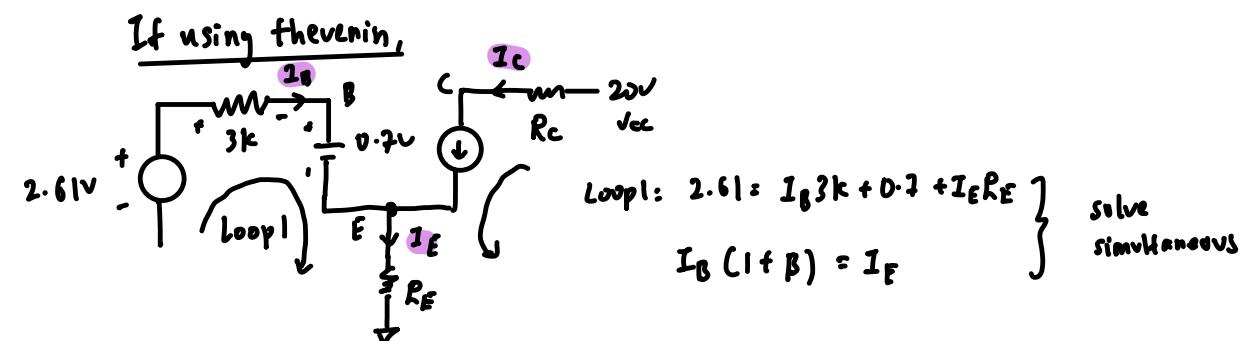
$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{3 \text{ k}\Omega}{(20 + 3) \text{ k}\Omega} 20 \text{ V} = 2.61 \text{ V}$$



BJT – Calculation of Operating Point

Example 2 (Voltage divider method)

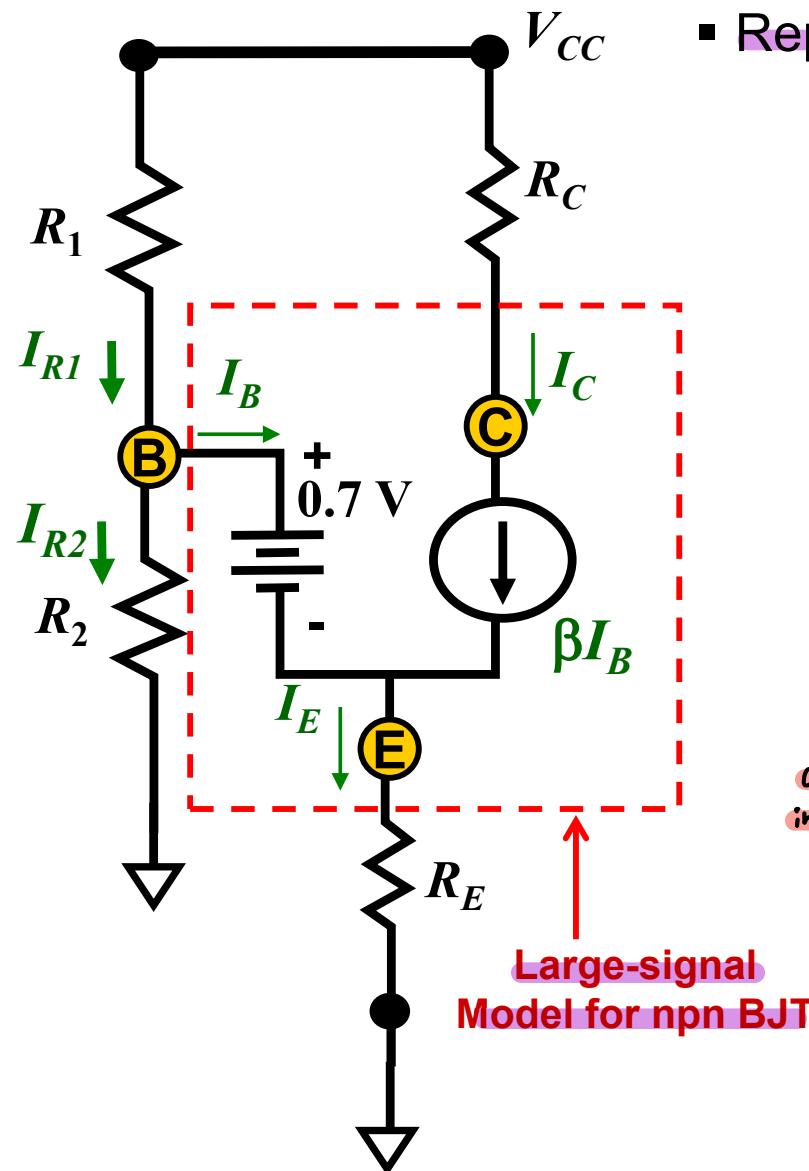

- Replace the npn BJT by its large-signal model.

$$V_E = V_B - V_{BE} = 2.61 - 0.7 = 1.91 \text{ V.}$$

\hookrightarrow constant voltage drop

$$\text{Thus, } I_E = V_E / R_E = V_E / 1 \text{ k}\Omega = 1.91 \text{ mA.}$$

$\stackrel{100}{\curvearrowleft}$ constant

$$I_C = [\beta / (\beta + 1)] I_E = [100/101] \times 1.91 \text{ mA}$$

$$= 1.89 \text{ mA.}$$

$\hookrightarrow I_C + \frac{I_C}{\beta} = I_E \rightarrow I_C (1 + \frac{1}{\beta}) = I_E$

$$I_C = \beta I_B$$

$$I_B = I_C / \beta = 0.0189 \text{ mA} = 18.9 \mu\text{A}$$

Check: I_B (0.0189 mA), is indeed much smaller than I_{R1} and I_{R2} (≈ 0.87 mA). Voltage divider assumption is valid.


\checkmark
Check assumption
in pg 25

Note: If I_B is not small compared to the currents flowing through R_1 and R_2 , the voltage divider rule cannot be applied.

We would then need to use the Thevenin equivalent method.

BJT – Calculation of Operating Point

Example 2 (Voltage divider method)

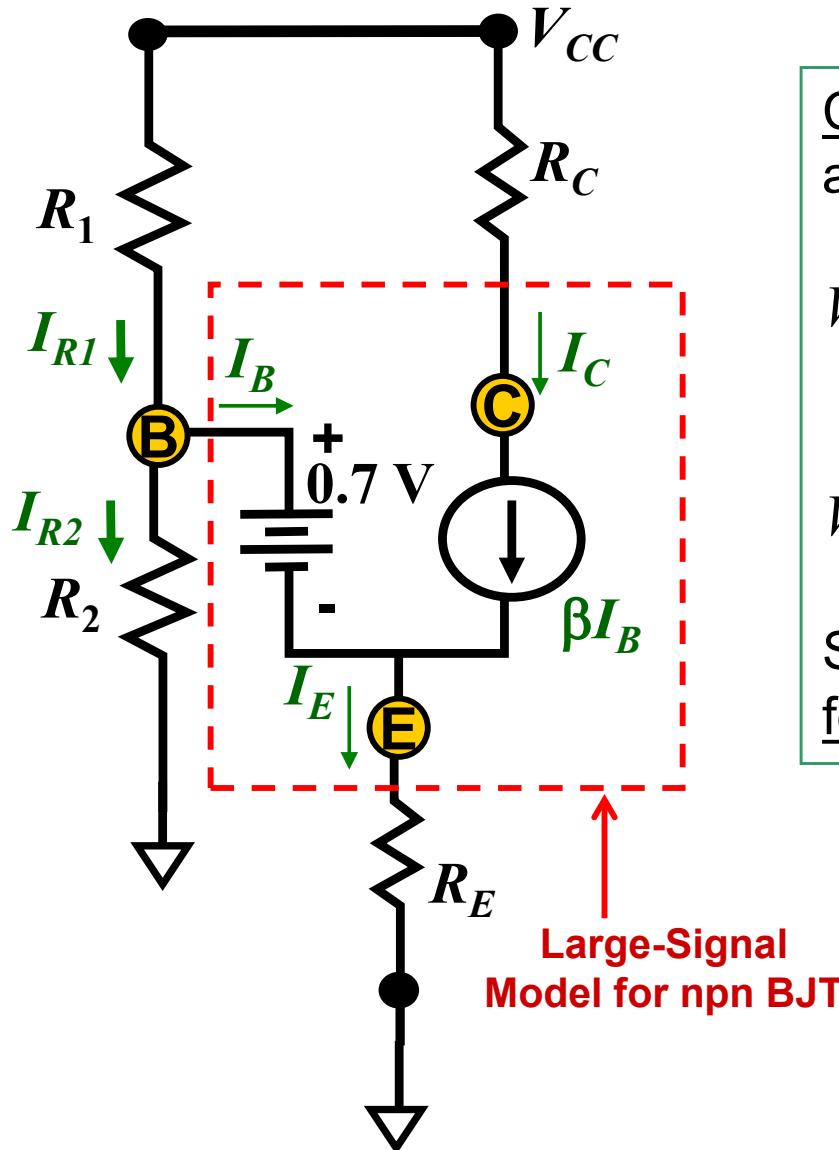

Check that the BJT is indeed in the forward-active region of operation:

$$\begin{aligned} V_C &= V_{CC} - I_C R_C = 20 - 1.89 \text{ mA} \times 5 \text{ k}\Omega \\ &= 10.55 \text{ V}. \end{aligned}$$


$$V_{BC} = V_B - V_C = 2.61 - 10.55 = -7.94 \text{ V}.$$

Since $V_{BC} < 0$ and $V_{BE} > 0$, the npn BJT is in the forward active region of operation.

Bipolar Junction Transistor (BJT)

Bipolar Junction Transistor (BJT)

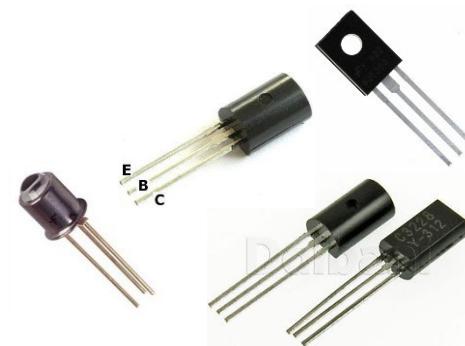1. Introduction
2. Modes of Operation: Forward Active, Saturation, Cut-Off and Reverse Active
3. Forward Active Current-Voltage Characteristic
4. Large-Signal Model and dc Analysis
5. **Amplifier Circuit**
6. Small-Signal Model (Simplified Hybrid- π) and ac Analysis
7. Other Hybrid- π Small-Signal Models





Reference

- Sedra and Smith, Microelectronic Circuits, Fifth Edition, Oxford (2004), pp. 159 – 168, 173 - 183, 203 - 241.



BJT – Amplifier Circuit

- In an amplifier circuit, BJT is biased in the forward active region. In addition to dc sources, V_{BB} and V_{CC} , an ac (small-signal) source, v_s , is applied to the input circuit, as shown in the common-emitter amplifier circuit below. v_s can be considered as a small add-on to V_{BB} .
- Two types of operation: dc and ac (small-signal) operations.
- The dc sources, V_{BB} and V_{CC} bias the BJT to operate in the forward active region and set the bias point (point Q) around which the small ac signal operates.

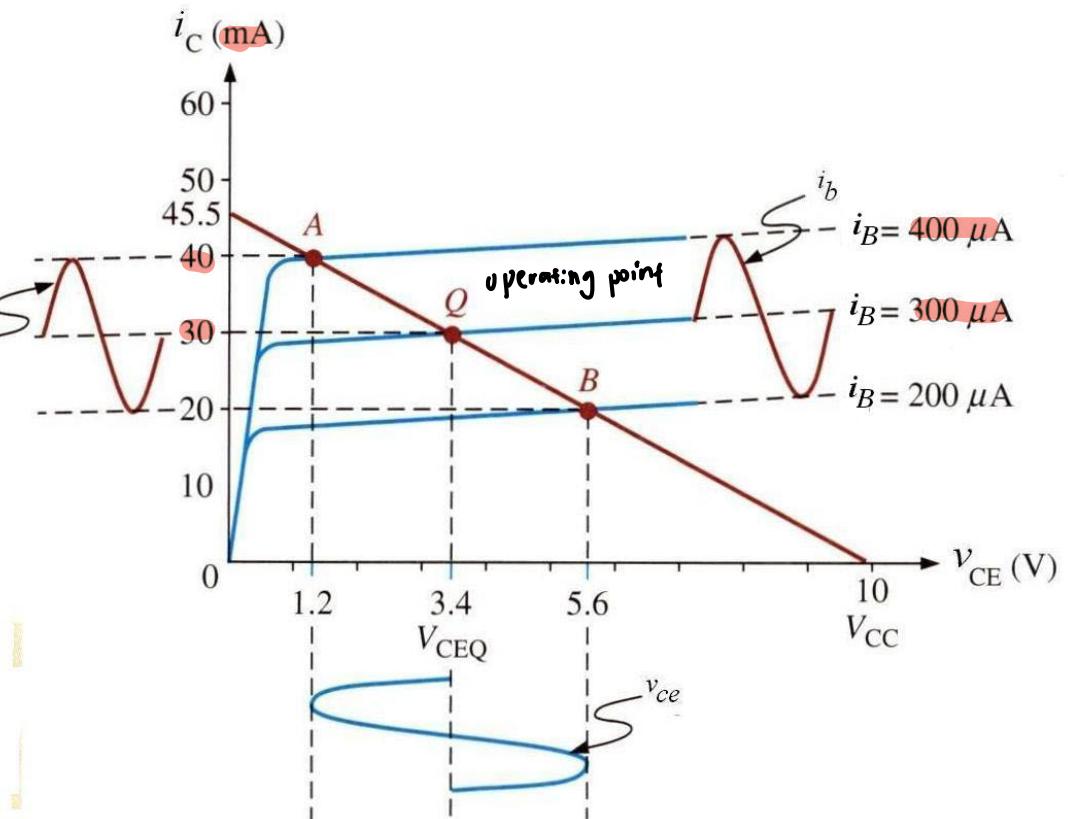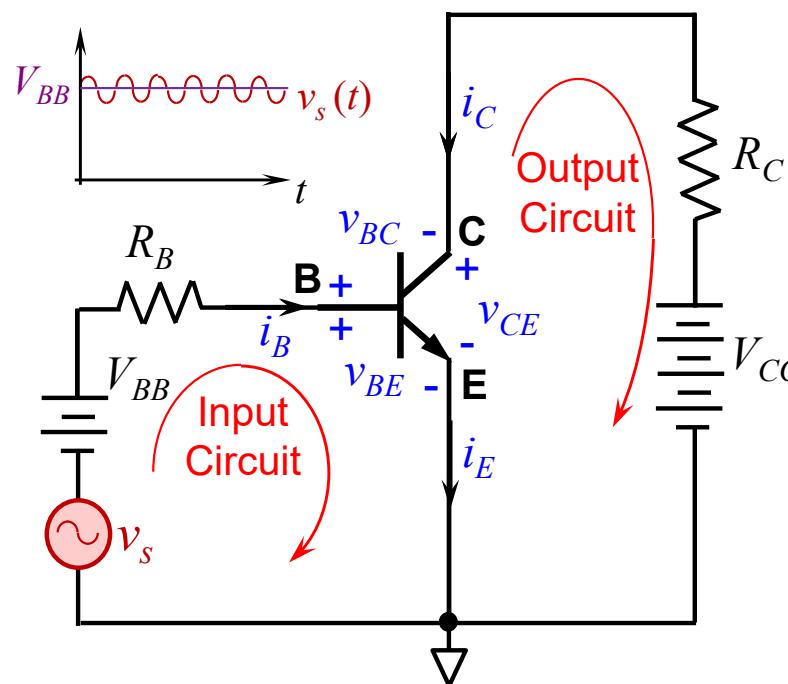

BJT – Amplifier Circuit



- The dc bias point (Q) currents and voltages (I_B , I_C , V_{CE}) can be determined using the BJT large-signal model, in the absence of the ac (small-signal) source, v_s .
- In the presence of ac (small-signal) source, v_s , the total base current, i_B , in the input circuit has an ac (small-signal) value, i_b , in addition to the dc value, I_B :
 - $i_B = I_B + i_b$
- As a result, total collector current, i_C , and total collector-emitter voltage, v_{CE} , of the output circuit will be similarly changed, with the addition of a small-signal i_c and v_{ce} , respectively:
 - $i_c = I_c + i_c$ and $v_{CE} = V_{CE} + v_{ce}$

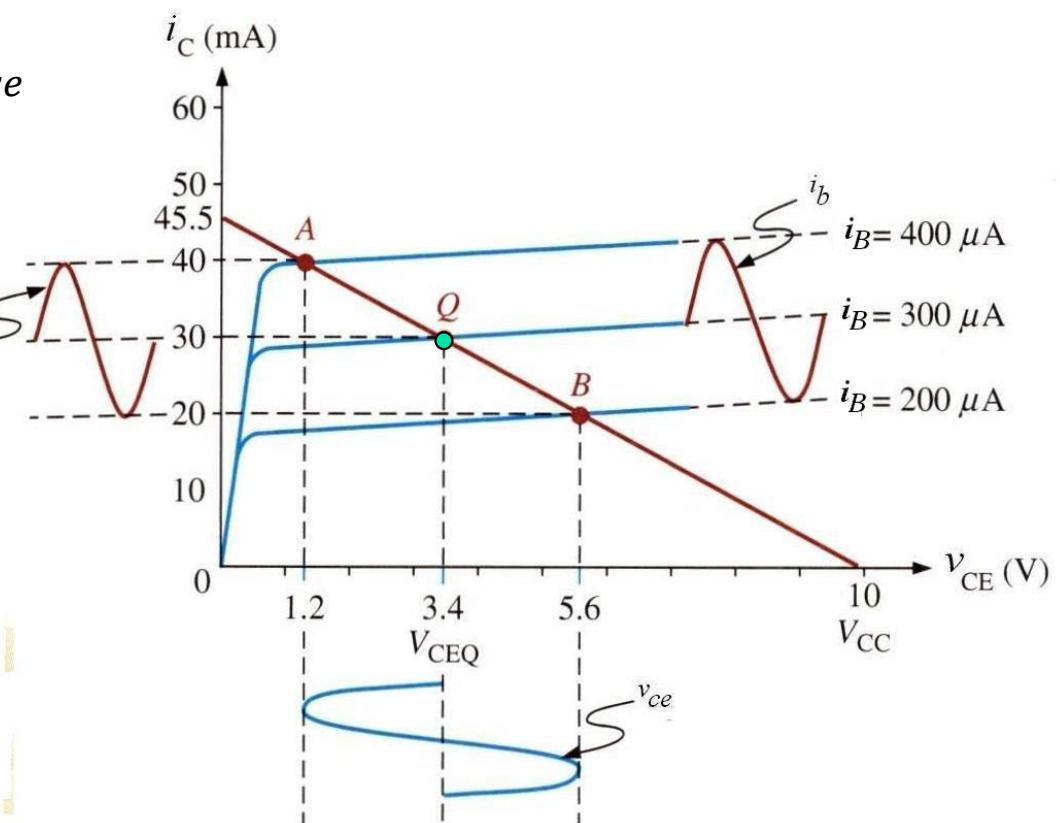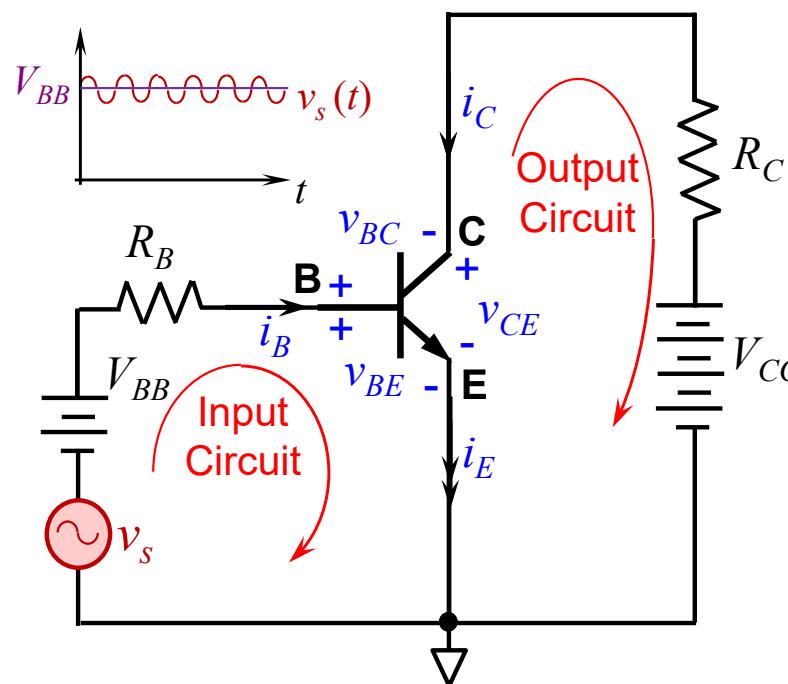

BJT – Amplifier Circuit

Notations for dc and ac values (examples)

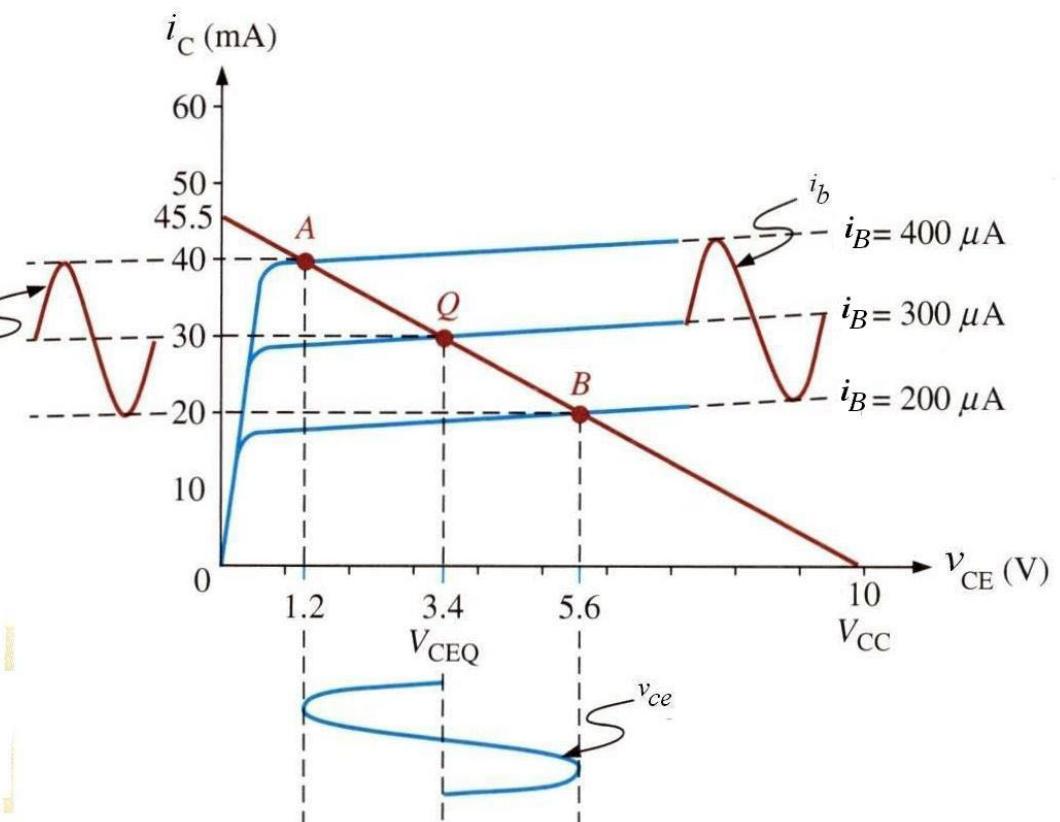
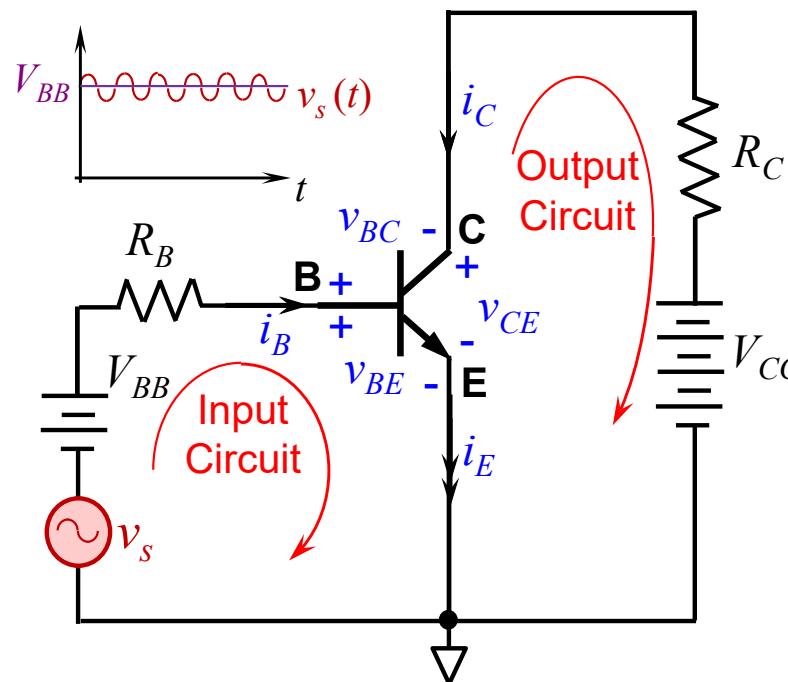
- dc current:
Capital symbol I_C Capital subscript
- ac current:
Lower case symbol i_c Lower case subscript
- Total current:
Lower case symbol $i_C = I_C + i_c$ Capital subscript



BJT – Amplifier Circuit

The common-emitter amplifier circuit below will demonstrate signal amplification, graphically with the help of the IV-characteristics.

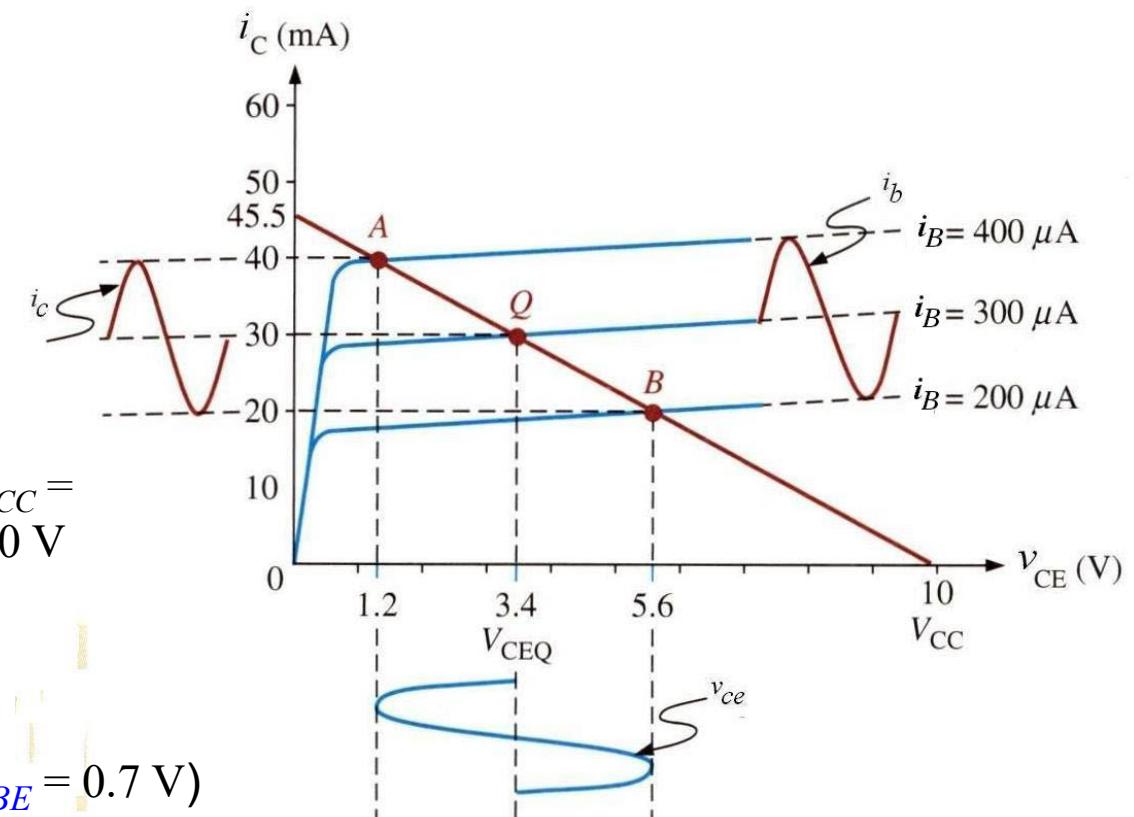
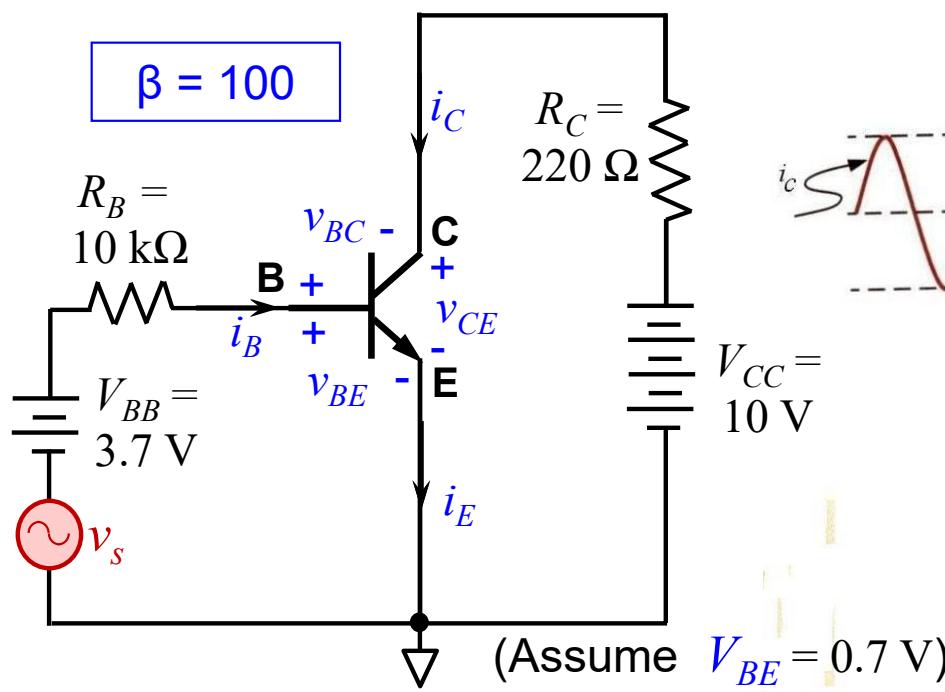
- Without the ac (small-signal) source, i.e., $v_s = 0$ -
 - No ac (small-signal) values: $i_b = 0$, $i_c = 0$, and $v_{ce} = 0$.
 - $i_B = I_B = 300 \mu\text{A}$, $i_C = I_C = 30 \text{ mA}$, and $v_{CE} = V_{CE} = 3.4 \text{ V}$ (see slides BJT 19 & BJT-20 for dc operation analysis). These are dc biasing currents and voltages.
 - Point Q, the dc bias point.




BJT – Amplifier Circuit

With ac source v_s -

- When $i_b = 100 \mu\text{A}$, $i_B = I_B + i_b = 300 \mu\text{A} + 100 \mu\text{A} = 400 \mu\text{A}$.
 - Point A: $i_C = I_C + i_c = 40 \text{ mA}$, and $v_{CE} = V_{CE} + v_{ce} = 1.2 \text{ V}$.
- When $i_b = -100 \mu\text{A}$, $i_B = I_B + i_b = 300 \mu\text{A} - 100 \mu\text{A} = 200 \mu\text{A}$.
 - Point B: $i_C = I_C + i_c = 20 \text{ mA}$, and $v_{CE} = V_{CE} + v_{ce} = 5.6 \text{ V}$.
- Small-signal $i_b = 100 \mu\text{A}$ leads to small-signal $i_c = 10 \text{ mA}$, which is 100 (β) times bigger. This is **signal amplification**.

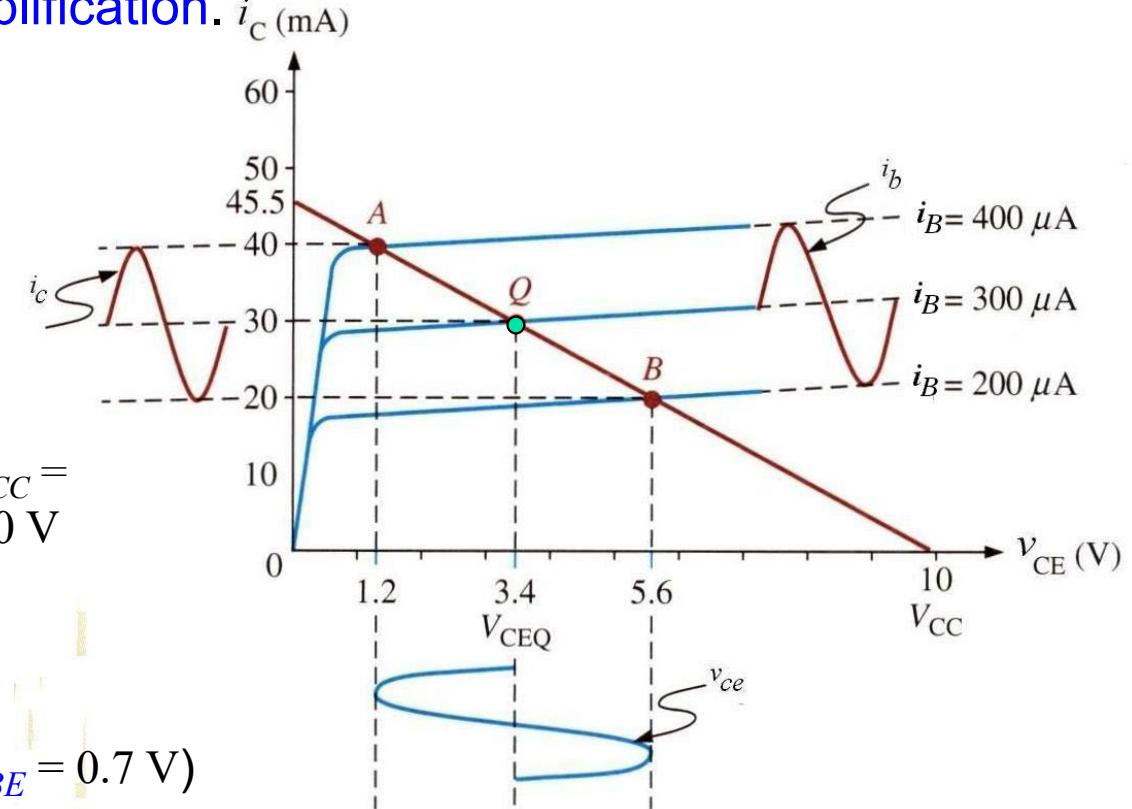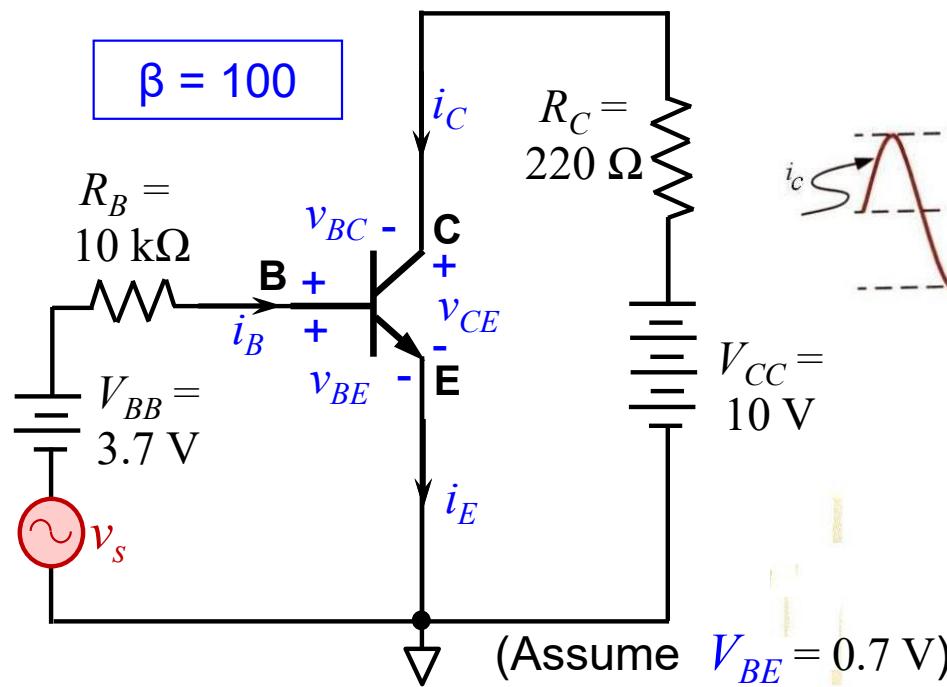

BJT – Amplifier Circuit (The Principles)


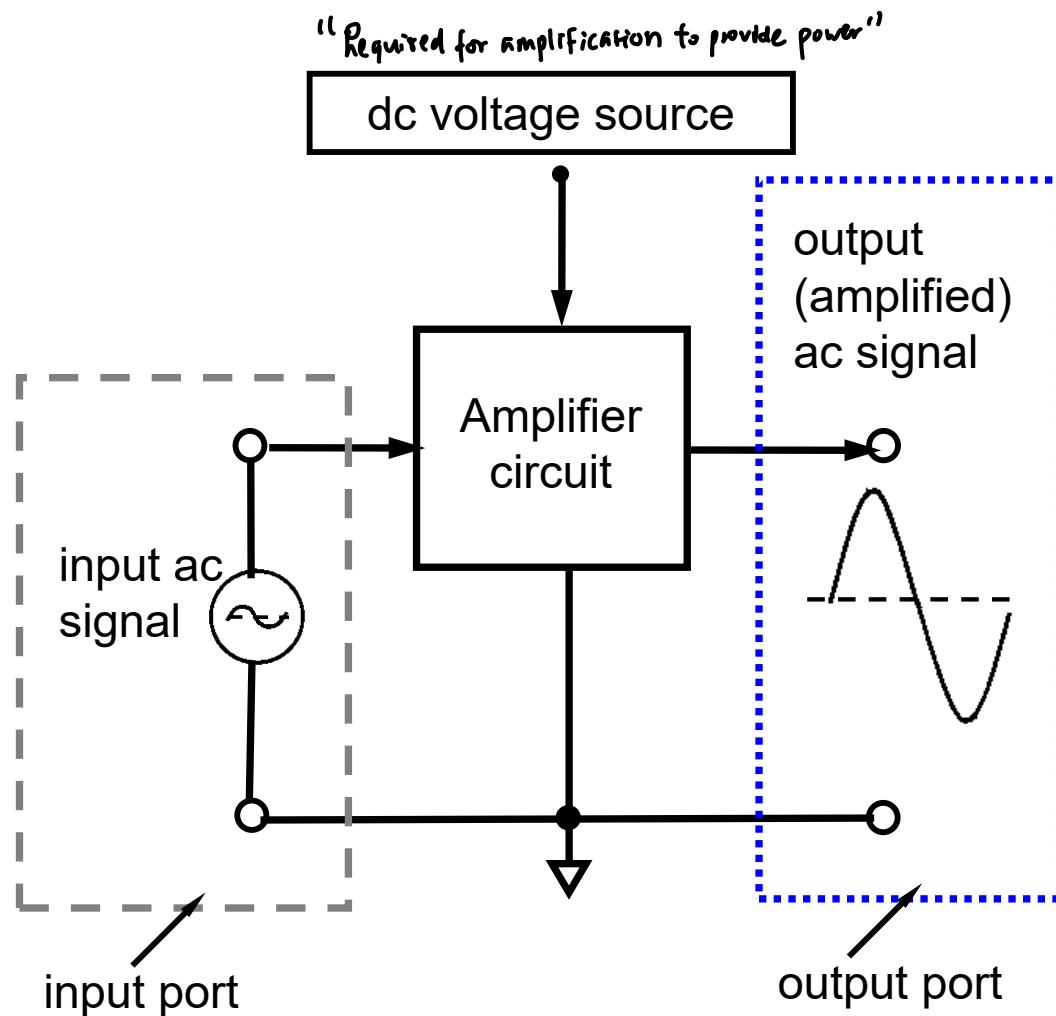


- Amplifier circuit is a 2-port network with the dc voltage source that supplies power to the entire circuit, while the ac signal is applied to the input port.
- The transistor in the amplifier circuit acts as a **control device**, which controls the flow of power from the dc source, to produce an enhanced (amplified) ac signal at the output port.
- The output ac signal is of the **same waveform** as the input ac signal, but is of larger amplitude (in current, voltage, or power).

BJT – Amplifier Circuit (Inappropriate Bias Point)

With R_B reduced to $7.5 \text{ k}\Omega$ -




- dc base current, $I_B = (V_{BB} - V_{BE}) / R_B = (3.7 - 0.7)/7.5\text{k} = 400 \mu\text{A}$. Bias point Q.
- With ac source v_s - when $i_b = 100 \mu\text{A}$, $i_B = I_B + i_b = 400 \mu\text{A} + 100 \mu\text{A} = 500 \mu\text{A}$.
 - Intersection between load line and BJT characteristics moves to point A, where the BJT no longer operates in the forward active region.
- The ac signal waveforms of i_c and v_{ce} are distorted.

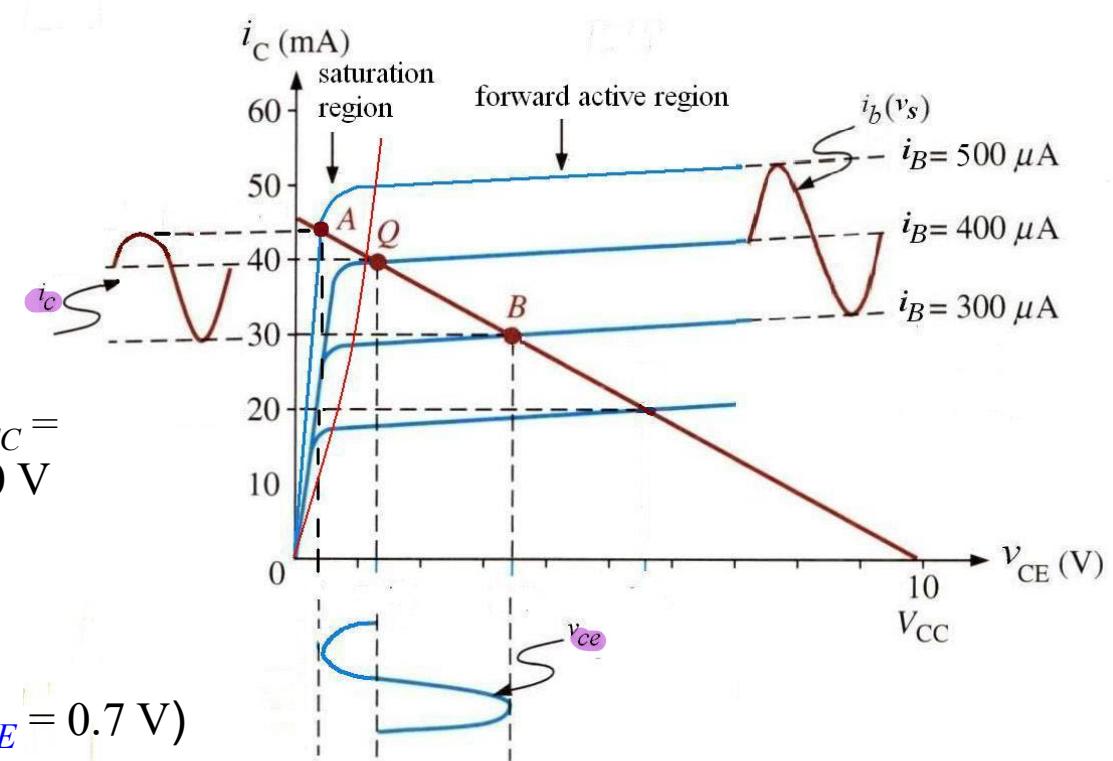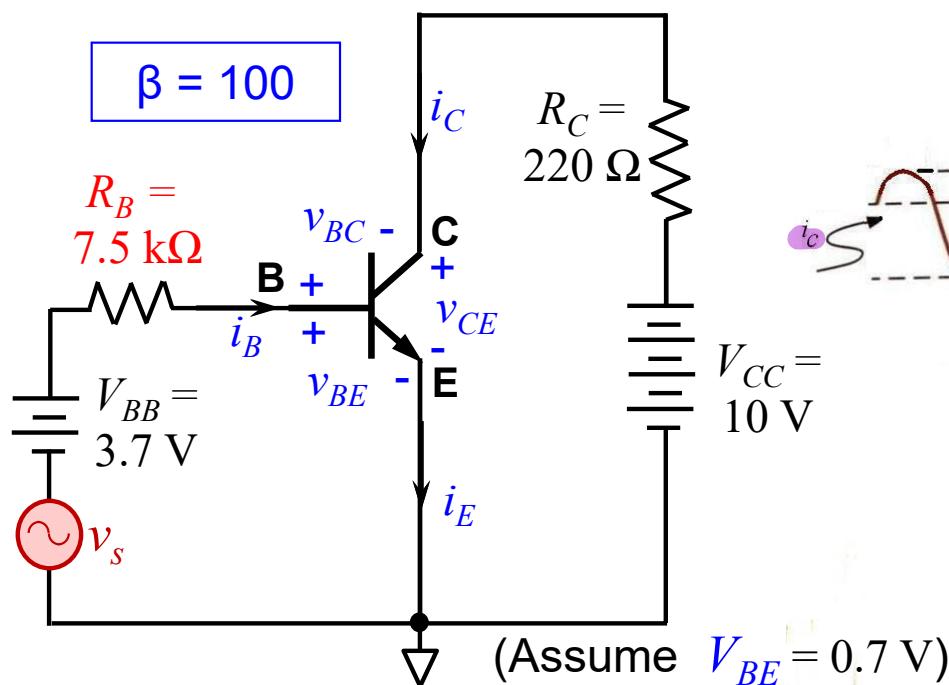

BJT – Amplifier Circuit (Inappropriate Bias Point)

With R_B increased to 30 k Ω -

- dc base current, $I_B = (V_{BB} - V_{BE}) / R_B = (3.7 - 0.7)/30k = 100 \mu A$. Bias point Q.
- With ac source v_s , assuming $i_b = 200 \mu A$. At some point during the negative half-cycle of i_b the intersection between load line and BJT characteristics is at point B.
 - ac signal i_c is clipped at 0 A, as total i_c cannot be negative.
 - ac signal v_{ce} is clipped at 10 V, as total v_{CE} cannot exceed the power supply voltage.

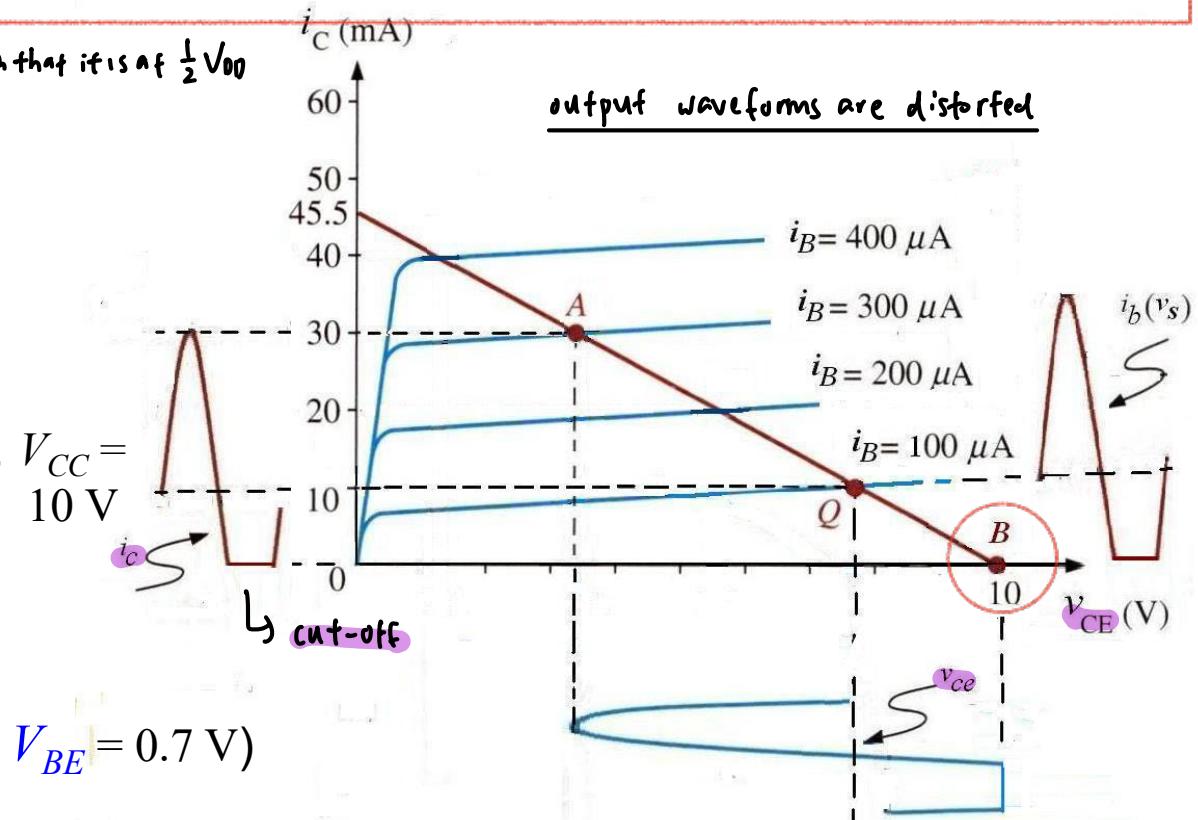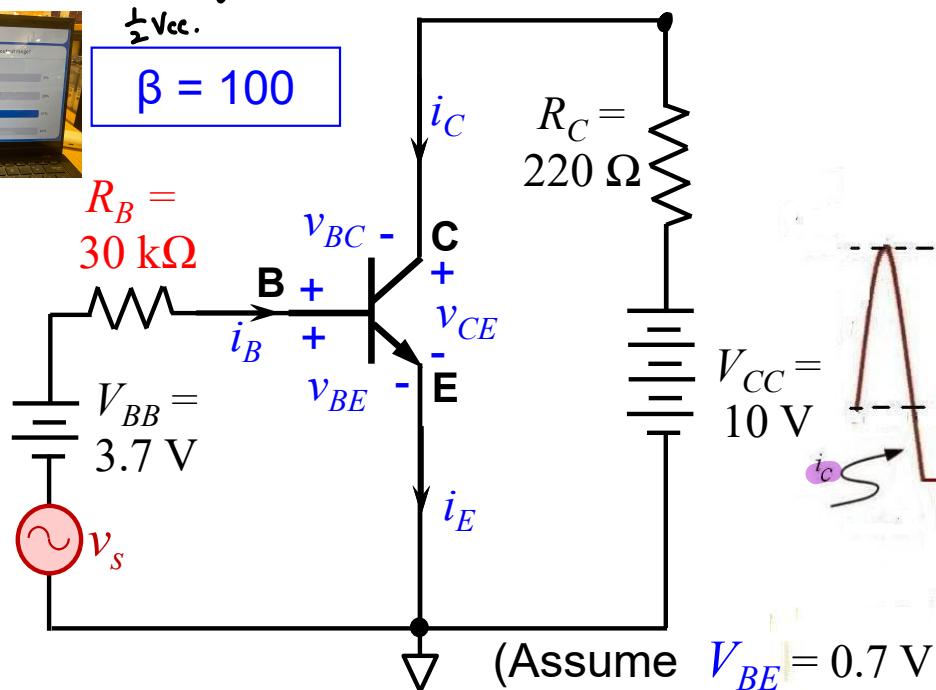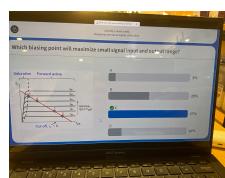

Bipolar Junction Transistor (BJT)

Bipolar Junction Transistor (BJT)

1. Introduction
2. Modes of Operation: Forward Active, Saturation, Cut-Off and Reverse Active
3. Forward Active Current-Voltage Characteristic
4. Large-Signal Model and dc Analysis
5. Amplifier Circuit
6. Small-Signal Model (Simplified Hybrid- π) and ac Analysis
7. Other Hybrid- π Small-Signal Models




Reference

- Sedra and Smith, Microelectronic Circuits, Fifth Edition, Oxford (2004), pp. 159 – 168, 173 - 183, 203 - 241.

BJT – Small-Signal Model

To develop a small-signal model of BJT operating in the **forward active region**.

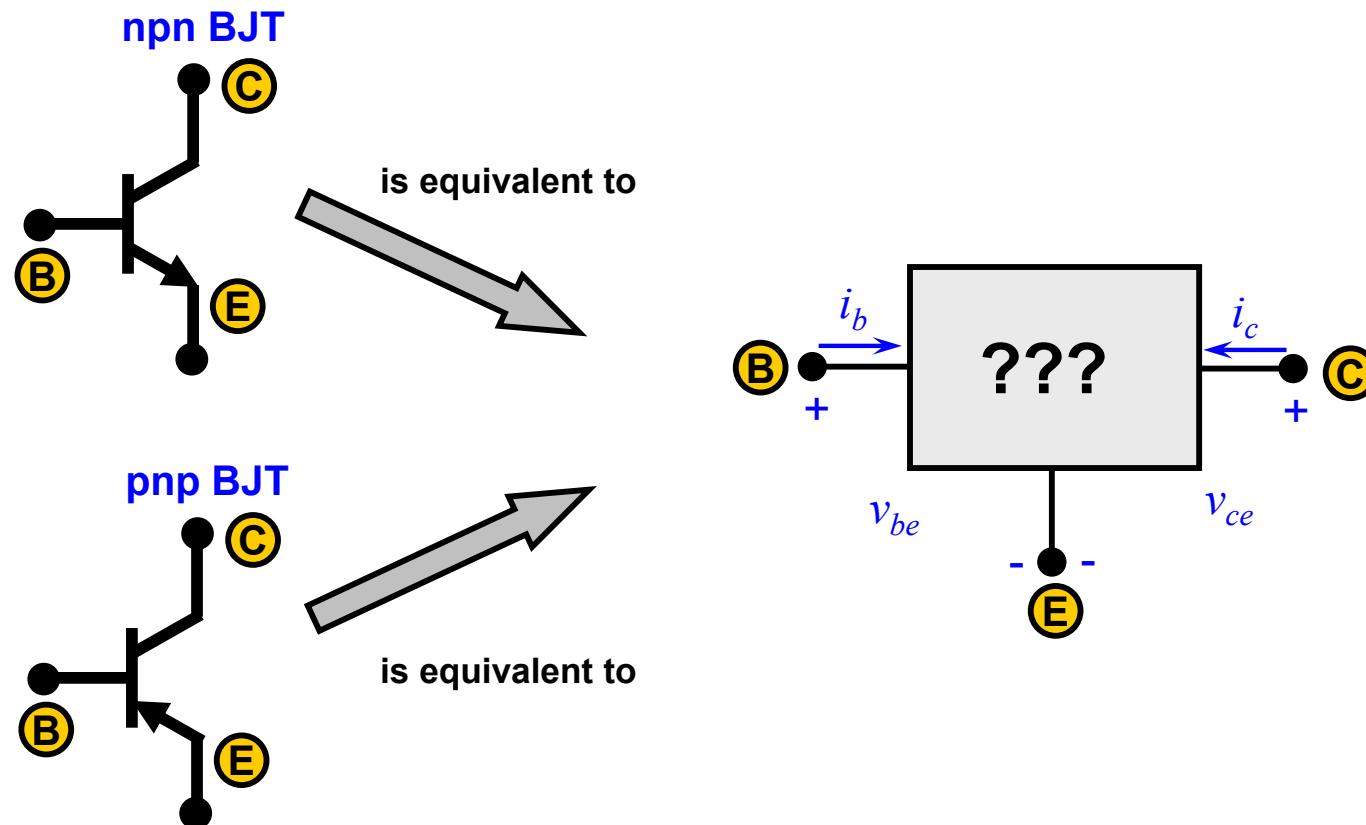- We seek **linear relationships*** among the **small-signal ac components** of the base current, collector current, base-emitter voltage and collector-emitter voltage - i_b , i_c , v_{be} , and v_{ce} (at a bias point).



* In the development of the small-signal model of a *pn*-junction diode, we obtain an approximate linear relationship between its small-signal current, i_d , and its small-signal voltage, v_d , at a bias point (see slides pn-30 to pn-35, in particular, equations (2.12) and (2.14)).

BJT – Small-Signal Model Parameter - g_m

- From equation (3.1), collector current -


$$i_C = I_S e^{v_{BE}/V_T}$$

- At the dc bias point (point Q), dc collector current - $I_C = I_S e^{V_{BE}/V_T}$

- A linear relationship between a small change in the collector current, Δi_C , and a small change in the base-emitter voltage, Δv_{BE} , can be found by linearizing the i_C - v_{BE} characteristic.

- A small change in i_C w.r.t a small change in v_{BE} , can be approximated by the derivative of i_C w.r.t v_{BE} -

$$\frac{\Delta i_C}{\Delta v_{BE}} \Big|_{V_{BE}} = \frac{i_c}{v_{be}} \Big|_{V_{BE}} \approx \frac{\partial i_C}{\partial v_{BE}} \Big|_{V_{BE}} = \frac{I_S e^{V_{BE}/V_T}}{V_T} = \frac{I_C}{V_T} = g_m \quad (3.6)$$

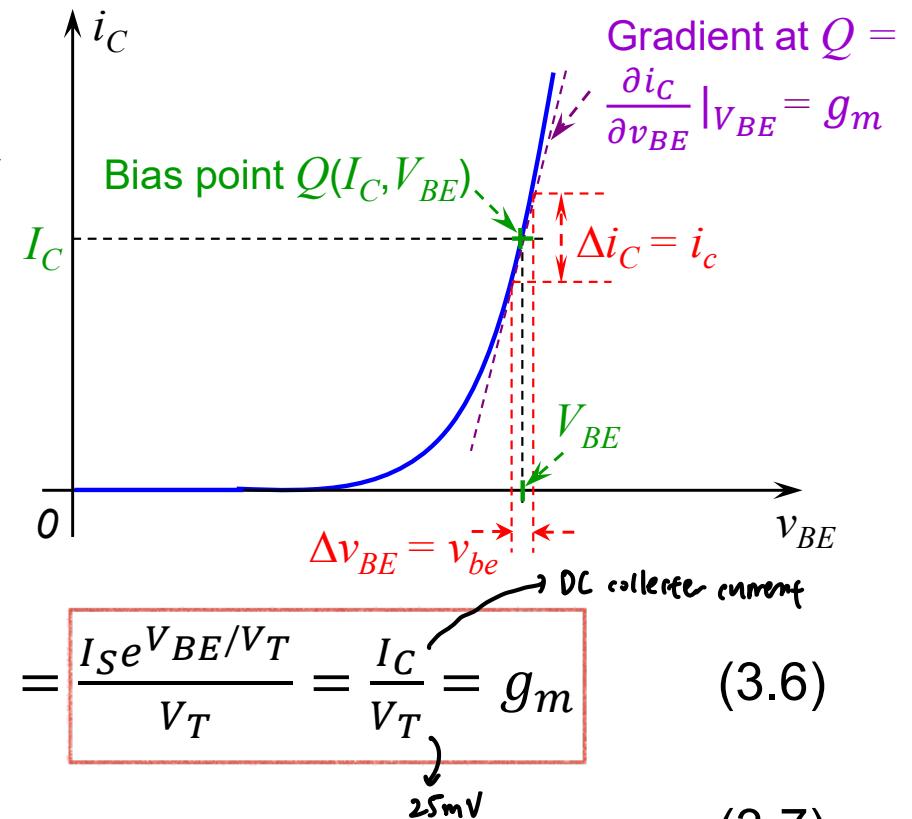

- Transconductance :
$$g_m = \frac{i_c}{v_{be}} = \frac{I_C}{V_T}$$

- Transconductance, g_m , models a small change in the collector current, i_c , caused by a small change in base-emitter voltage, v_{be} .

BJT – Small-Signal Model Parameter - r_π

- From equation (3.2), base current -

$$i_B = \frac{I_S}{\beta} e^{v_{BE}/V_T} \quad \therefore I_C = \beta I_B$$

- At the dc bias point (point Q), dc base current - $I_B = \frac{I_S}{\beta} e^{v_{BE}/V_T}$

- A small change in i_B w.r.t a small change in v_{BE} , can be approximated by the derivative of i_B w.r.t v_{BE} -

$$\frac{\Delta i_B}{\Delta v_{BE}} \Big|_{V_{BE}} = \frac{i_b}{v_{be}} \Big|_{V_{BE}} \approx \frac{\partial i_B}{\partial v_{BE}} \Big|_{V_{BE}} = \frac{I_S e^{V_{BE}/V_T}}{\beta V_T} = \frac{I_C}{\beta V_T} = g_\pi \quad (3.8)$$


$\frac{g_m}{\beta}$
 $\frac{1}{r_\pi}$

- Taking the reciprocal of g_π , input resistance: \rightarrow happen at the base

$$r_\pi = \frac{1}{g_\pi} = \frac{v_{be}}{i_b} = \frac{\beta V_T}{I_C} = \frac{\beta}{g_m} = \frac{v_{be}}{i_b} \quad (3.9)$$

- Hence, $\beta = g_m r_\pi$ (3.10)

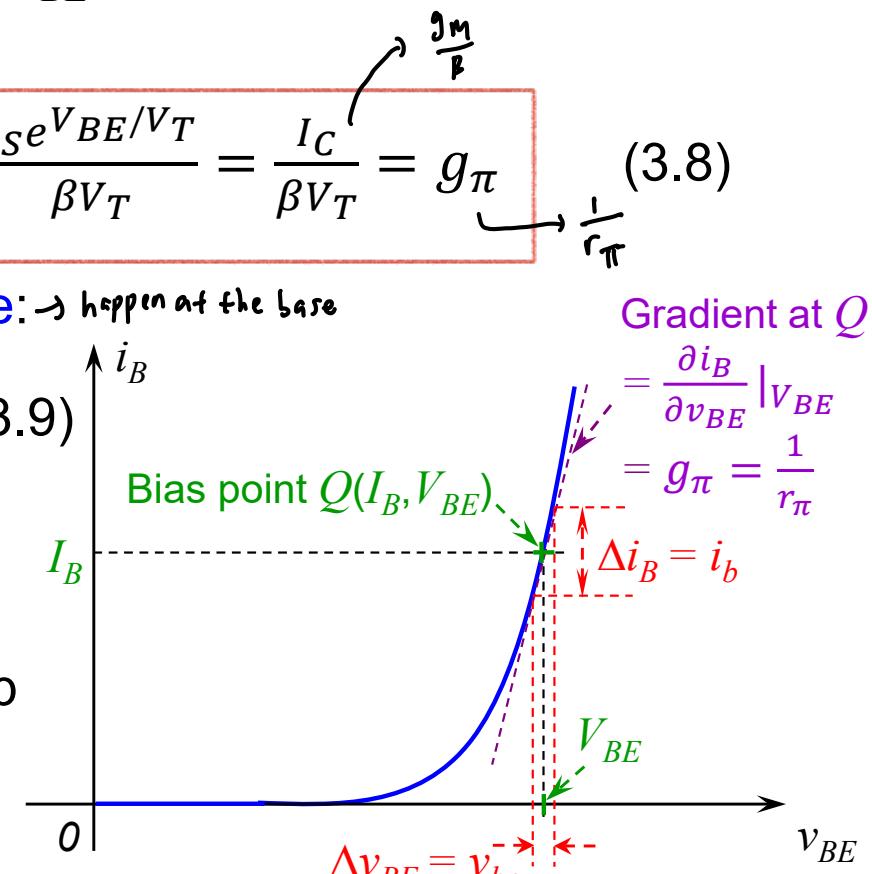- Input resistance, r_π , models the relationship between a small change in the base current, i_b , and a small change in base-emitter voltage, v_{be} .



BJT – Small-Signal Model Parameters (Summary)

- Equation (3.7) - Transconductance, g_m , models a small change in the collector current, i_c , caused by a small change in base-emitter voltage, v_{be} –

$$i_c = g_m v_{be} \quad [g_m = \frac{I_C}{V_T}] \quad (3.7)$$

AC I_C current \curvearrowleft
 Small change in collector current \nearrow
 Small change in base-emitter voltage \searrow
DC - bias point I_C

- Equation (3.9) - Input resistance, r_π , models the relationship between a small change in the base current, i_b , and a small change in base-emitter voltage, v_{be} –


$$v_{be} = r_\pi i_b \quad [r_\pi = \frac{\beta V_T}{I_C}] \quad (3.9)$$

Small change in base-emitter voltage \nearrow
 Small change in base current \searrow

- Equation (3.10) - $\beta = g_m r_\pi$ (3.10)


- Combine equations (3.7), (3.9) and (3.10) -
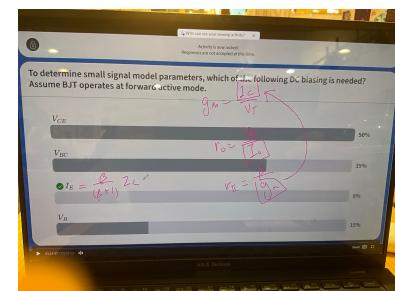
$$i_c = g_m v_{be} = g_m r_\pi i_b = \beta i_b \quad (3.11)$$




BJT – Small-Signal Model (Simplified Hybrid- π)

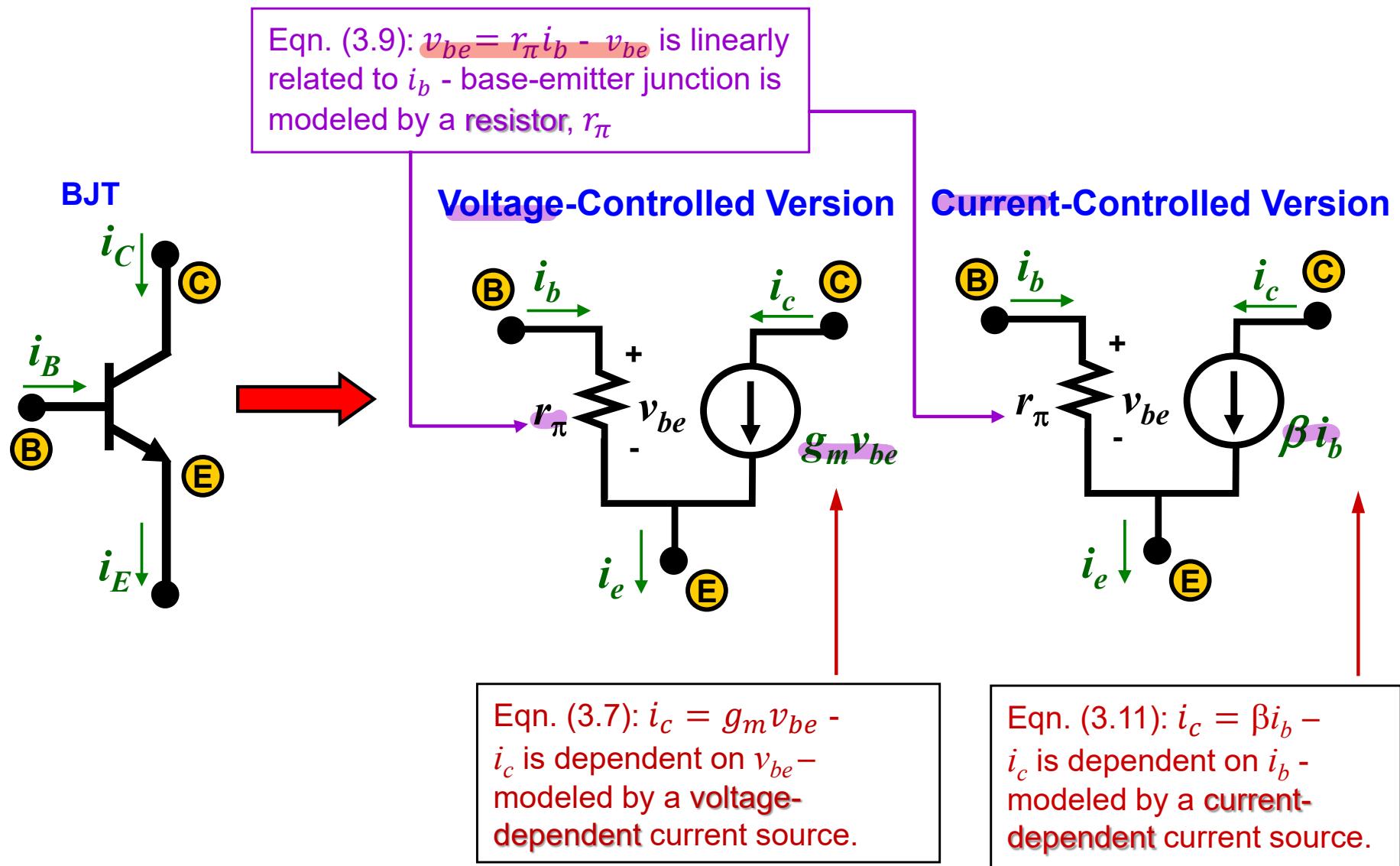- Small-signal model of BJT is developed using equations (3.7), (3.9), (3.11) -




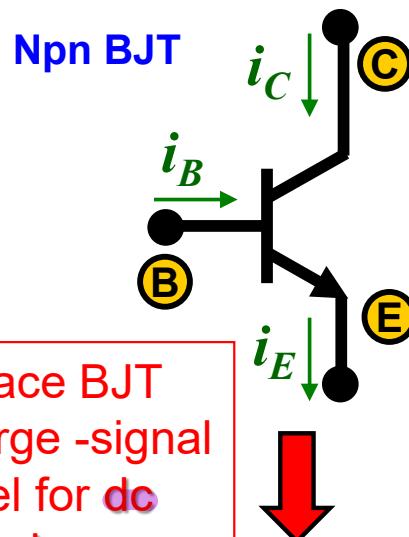BJT – Forward Active Mode Models (Summary)



Replace BJT by large -signal model for dc analysis

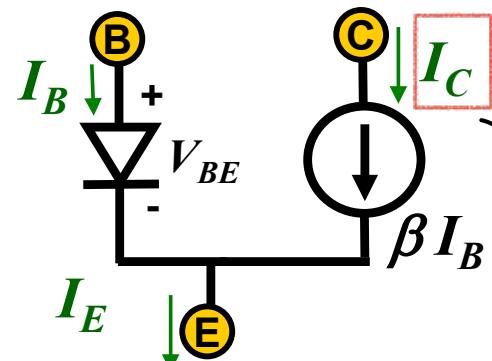Replace BJT by hybrid- π Model for small-signal analysis




Large-Signal Model of the npn BJT


$$g_m = \frac{I_C}{V_T}$$

$$r_\pi = \frac{\beta}{g_m}$$

Voltage-Controlled Version

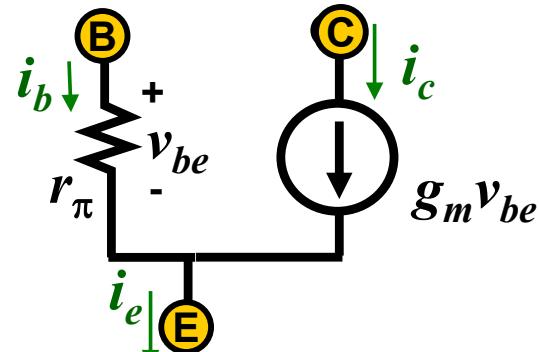



Current-Controlled Version

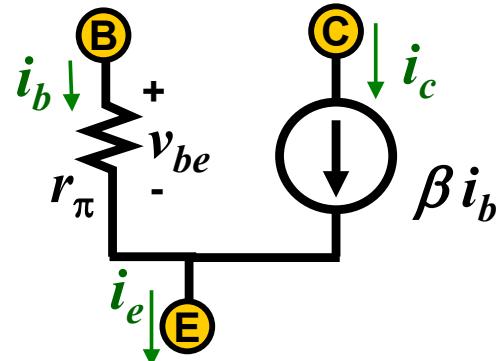

Small-Signal model (Simplified hybrid- π) of the npn BJT

BJT – Amplifier Circuit Operation & Analysis

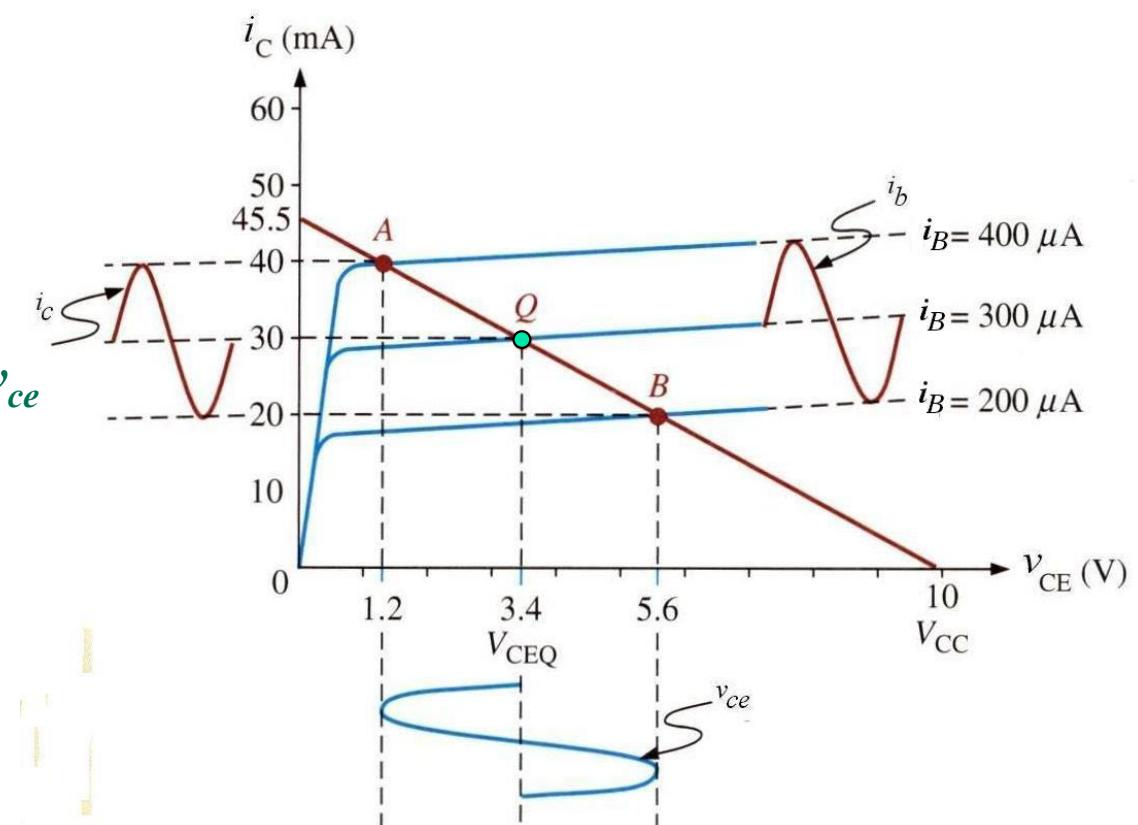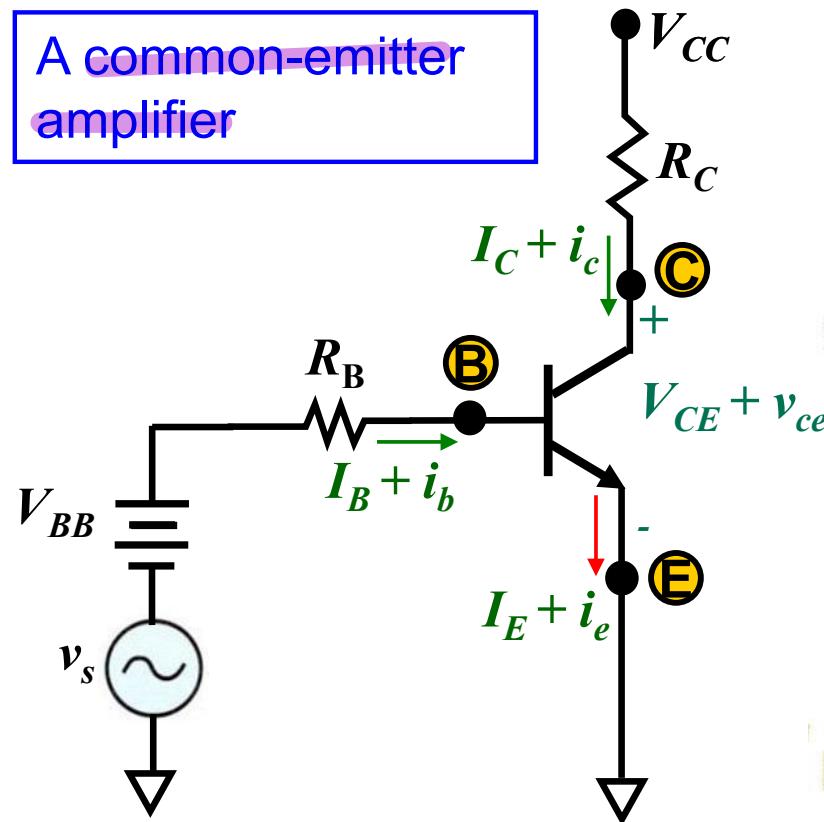
- The operation of an amplifier circuit is shown in the i_C - v_{CE} curve below, where the dc bias point (Q) and the small signals i_b , i_c and v_{ce} are indicated.
- In the presence of an ac (small-signal) source, v_s -
 - $i_B = I_B + i_b$, $i_C = I_C + i_c$, and $v_{CE} = V_{CE} + v_{ce}$
 - i_B , i_C and v_{CE} all have a small-signal component and they vary with time.



STEP 1


BJT – Amplifier Circuit Operation (dc Analysis)

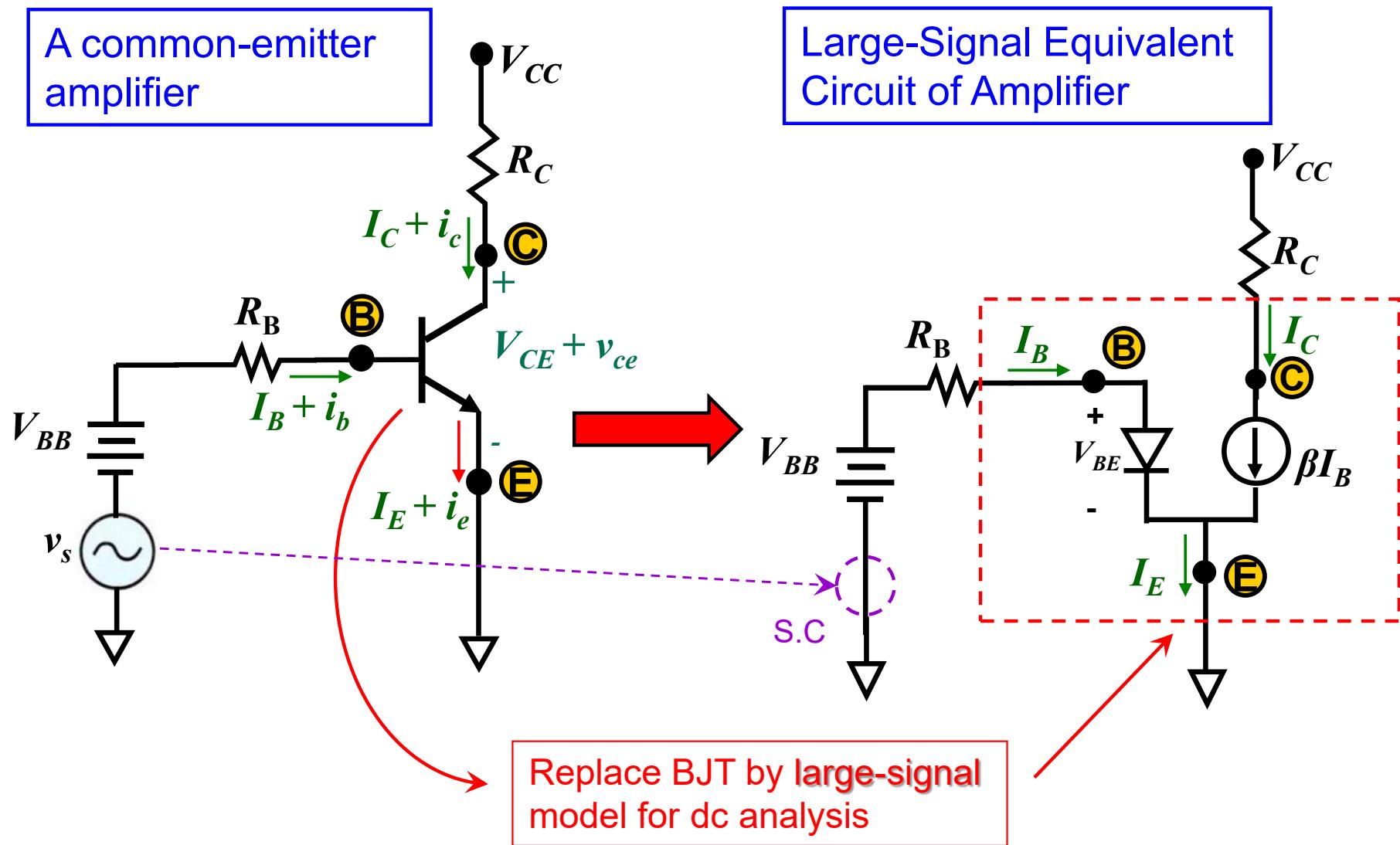- The dc bias point of the amplifier can be determined using the large-signal equivalent circuit, in the absence of the ac (small signal) source, v_s .




BJT – Amplifier Circuit Operation (ac Analysis)

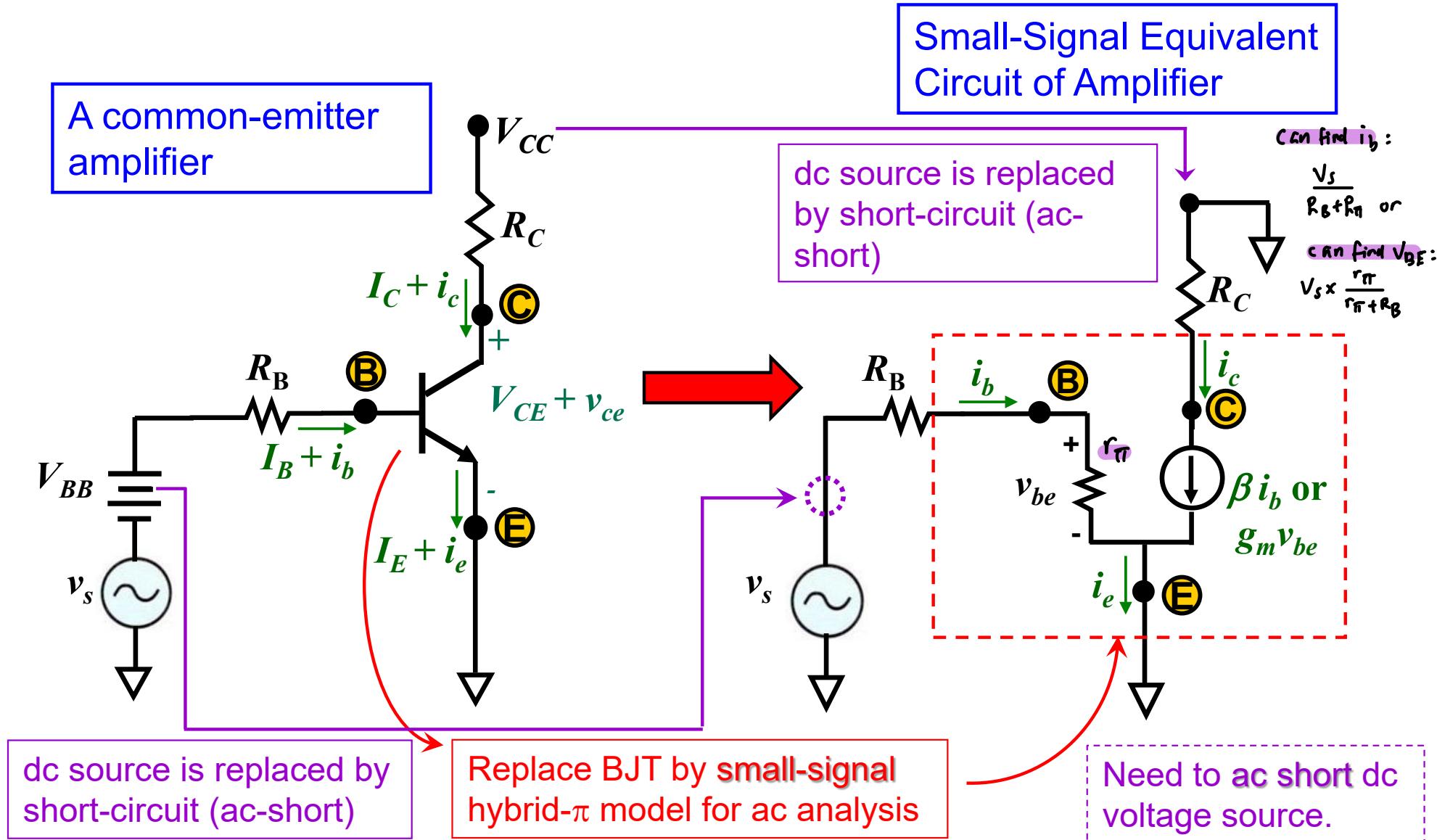- The small-signal ac analysis of the amplifier is carried out using the small-signal equivalent circuit, and dc voltage sources need to be ac short.




BJT – Small-Signal Model (pnp)

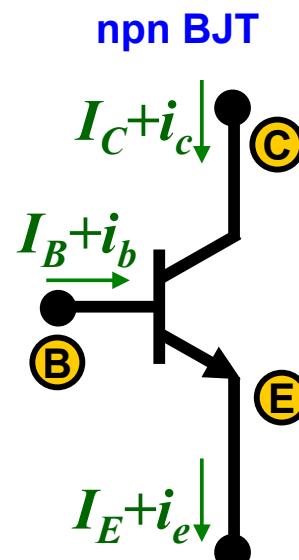

The change in collector current for the npn BJT is positive when there is an increase in the collector current flowing into the collector
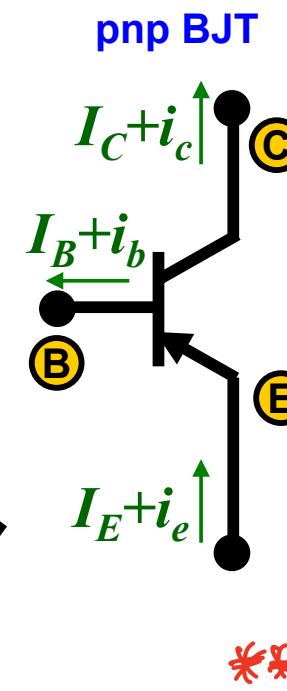
$$\downarrow i_c = g_m v_{be} = \beta i_b$$




The change in collector current for the pnp BJT is positive when there is an increase in the collector current flowing out of the collector

$$\downarrow i_c = g_m v_{eb} = \beta i_b$$


Replace the BJT by the simplified hybrid- π model for small-signal analysis

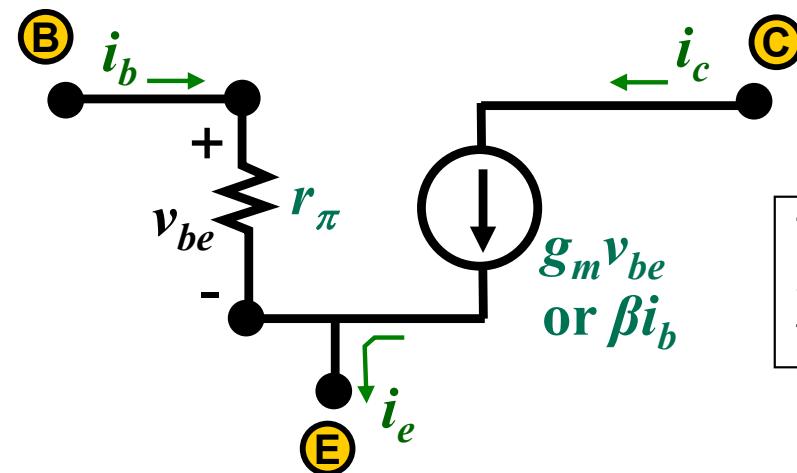Simplified Hybrid- π Model for npn BJT or pnp BJT



This Hybrid- π Model is in its simplest form here. We will use this simplest form by default.


BJT – Small-Signal Model (pnp vs npn)

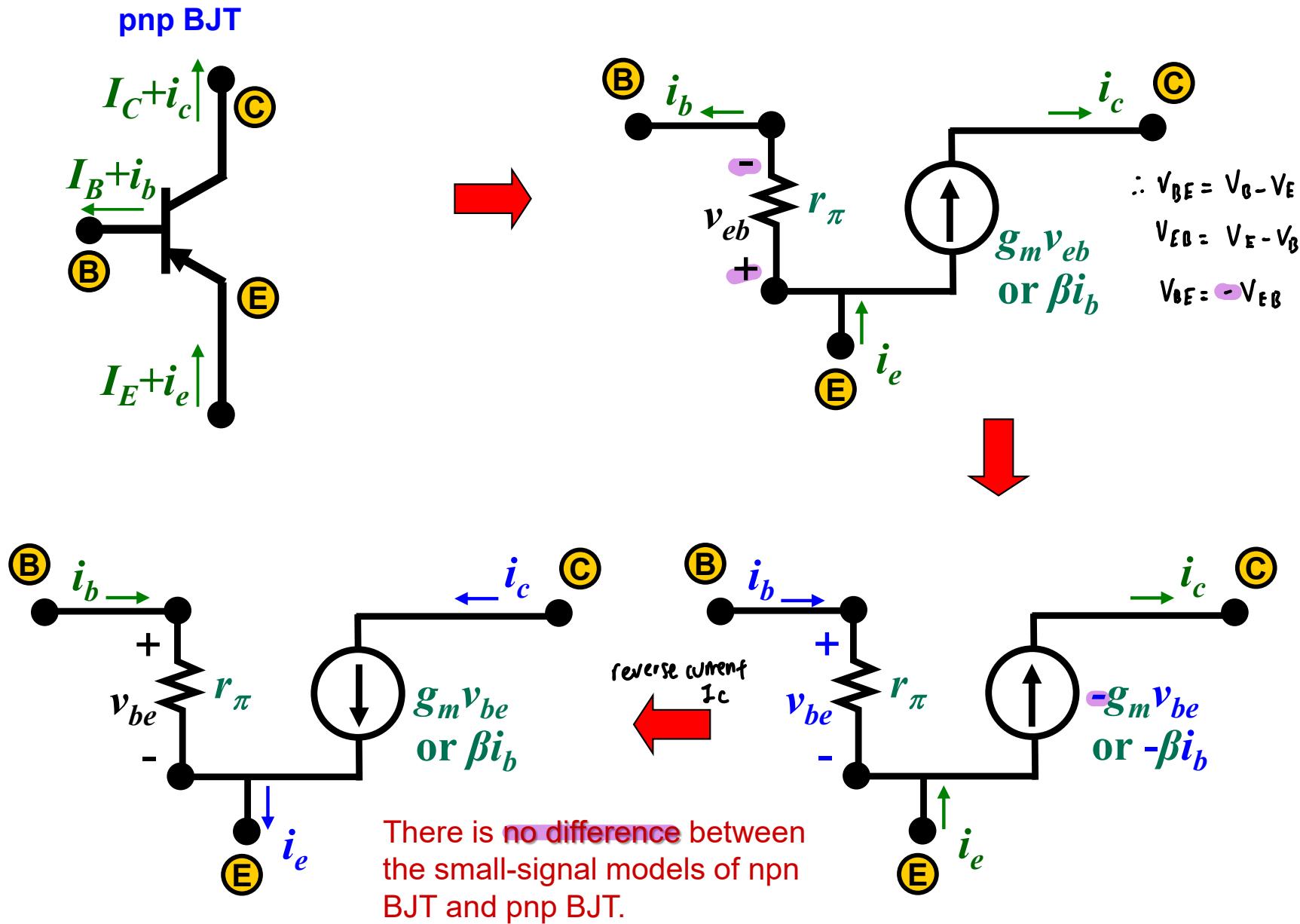

Bipolar Junction Transistor (BJT)

Bipolar Junction Transistor (BJT)

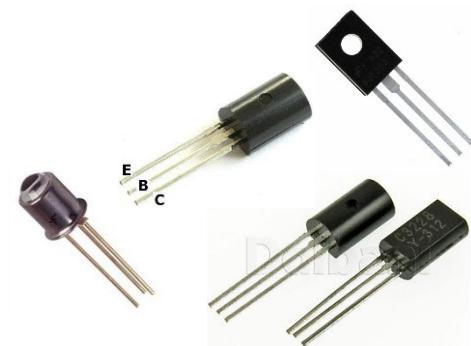1. Introduction
2. Modes of Operation: Forward Active, Saturation, Cut-Off and Reverse Active
3. Forward Active Current-Voltage Characteristic
4. Large-Signal Model and dc Analysis
5. Amplifier Circuit
6. Small-Signal Model (Simplified Hybrid- π) and ac Analysis
7. Other Hybrid- π Small-Signal Models



Reference

- Sedra and Smith, Microelectronic Circuits, Fifth Edition, Oxford (2004), pp. 159 – 168, 173 - 183, 203 - 241.

BJT – Small-Signal Model (Simplified Hybrid- π)



- In simplified hybrid- π model, Early effect was ignored and collector current,

$$i_C = I_S e^{v_{BE}/V_T}, \quad (3.1)$$

is a function of only the base-emitter junction voltage, v_{BE} : $i_C = f(v_{BE})$.

- Small-signal collector current, i_c , is directly due to small-signal base-emitter junction voltage, v_{be} :

$$i_c = \frac{\partial i_C}{\partial v_{BE}} |_{V_{BE}} \times v_{be} = g_m \times v_{be} \quad (\text{see } \underline{\text{slide BJT-40}}, \text{ equation (3.6)})$$

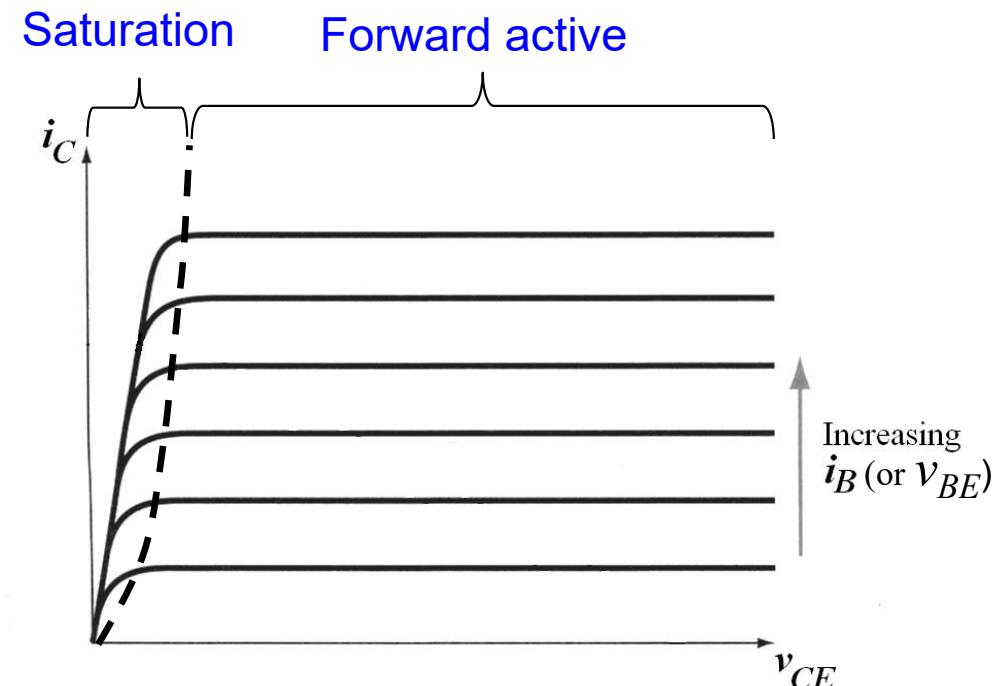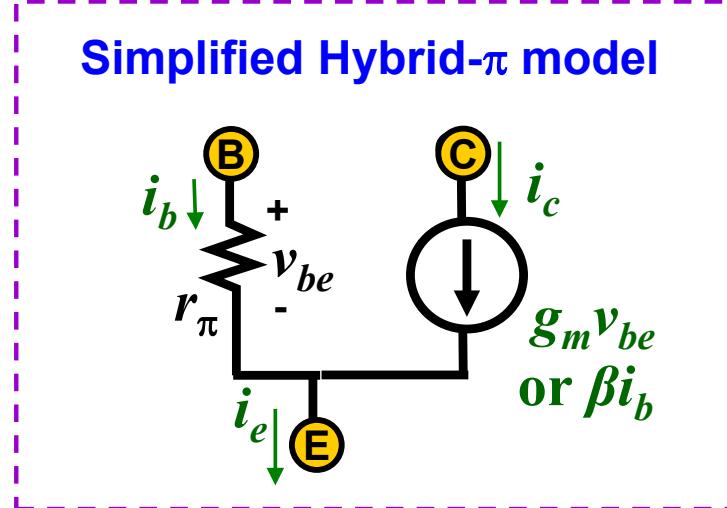

BJT – Small-Signal Model (Hybrid- π)

- With Early effect (see slide BJT-14), collector current becomes

$$i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A} \right), \quad (3.5)$$

is also a function of collector-emitter voltage, v_{CE} , in addition to v_{BE} :

$$i_C = f(v_{BE}, v_{CE}).$$


- Small-signal collector current, i_c , will then be contributed by the small-signal collector-emitter voltage, v_{ce} , as well, in addition to that contributed by v_{be} -

$$\Delta i_c = i_c \approx \underbrace{\frac{\partial i_c}{\partial v_{BE}}|_{V_{BE}} \times v_{be}}_{\text{Contribution of } v_{be}} + \underbrace{\frac{\partial i_c}{\partial v_{CE}}|_{V_{CE}} \times v_{ce}}_{\text{Contribution of } v_{ce}} \quad (3.12)^*$$

Contribution of v_{be}

Contribution of v_{ce}

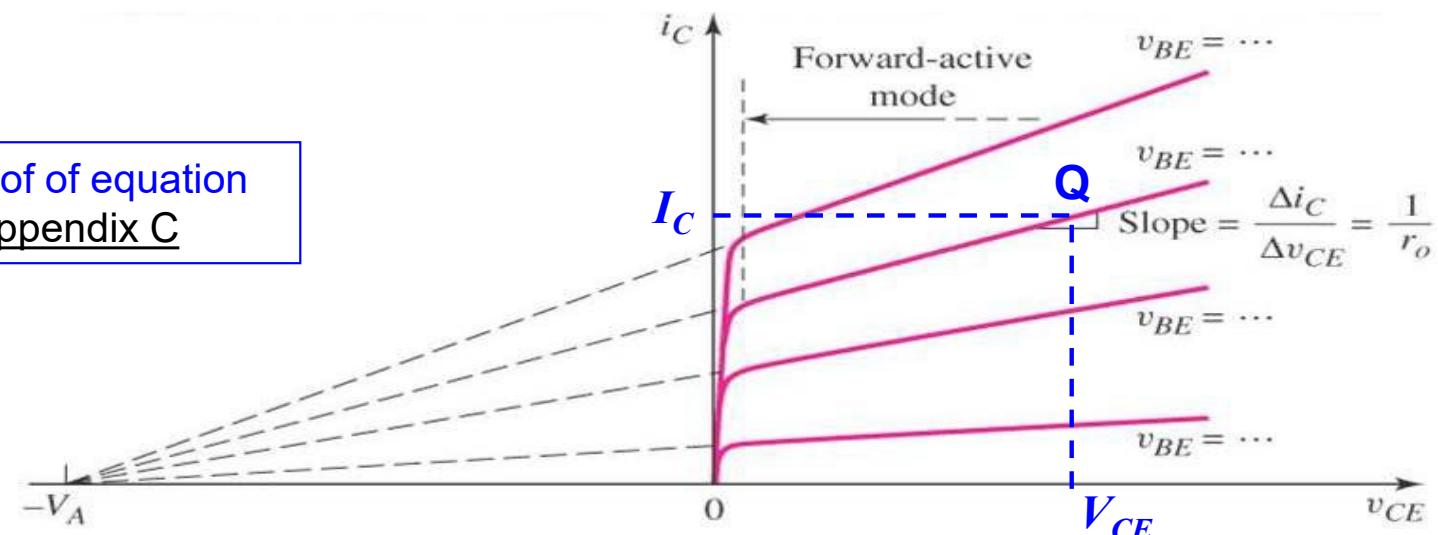* Mathematical proof of equation (3.12) is given in Appendix C



BJT – Small-Signal Model (Hybrid- π)

- Equation (3.5) -


$$i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A} \right)$$

- For given V_{BE} and V_{CE} (point Q), when v_{CE} changes, i_C will change. Change in i_C owing to a small change in v_{CE} is related to the slope (or derivative) of the corresponding i_C - v_{CE} curve as follows –

$$\frac{\Delta i_C}{\Delta v_{CE}} = \frac{i_c}{v_{ce}} = \frac{\partial i_C}{\partial v_{CE}} \Big|_{V_{CE}, V_{BE}} = \frac{I_S}{V_A} e^{V_{BE}/V_T} \approx \frac{I_C}{V_A} = \frac{1}{r_o} \quad (3.13)$$

- Output resistance: $r_o = \frac{v_{ce}}{i_c} = \frac{V_A}{I_C} \rightarrow$ early voltage if not given assume ∞ (3.14)

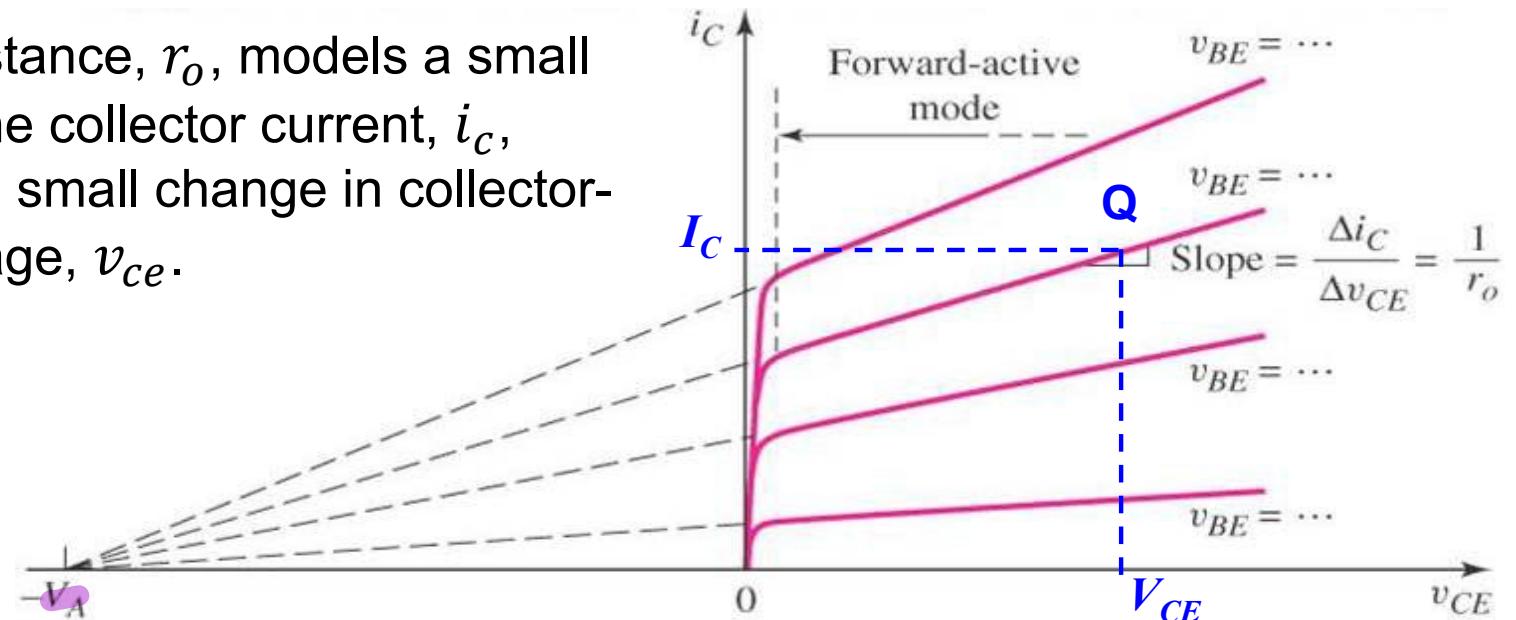- Output resistance, r_o , models a small change in the collector current, i_C , caused by a small change in collector-emitter voltage, v_{ce} .




BJT – Small-Signal Model (Hybrid- π)

- From equation (3.12) –

$$i_c = \frac{\partial i_C}{\partial v_{BE}}|_{V_{BE}} \times v_{be} + \frac{\partial i_C}{\partial v_{CE}}|_{V_{CE}} \times v_{ce}$$

or, $i_c = g_m v_{be} + v_{ce}/r_o = \beta i_b + v_{ce}/r_o$ (3.15)

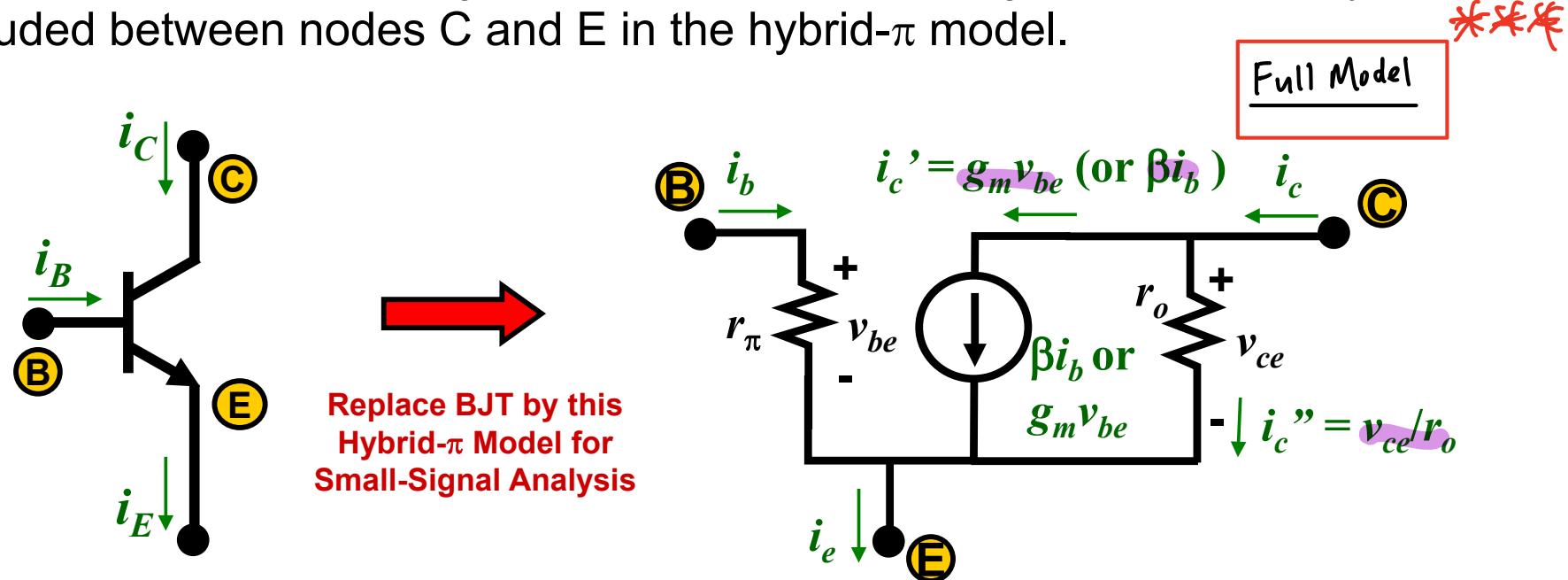
- The term v_{ce}/r_o accounts for the dependence of i_C on v_{CE} (or Early effect).
- To model the increase in i_C owing to an increase in v_{CE} , a resistance r_o is included between nodes C and E in the hybrid- π model.



Note: In EE2027, you can assume that r_o is infinite by default. However, if the Early voltage V_A is given, then r_o should be calculated and included in the small-signal analysis.

BJT – Full Hybrid- π Model at High Frequency

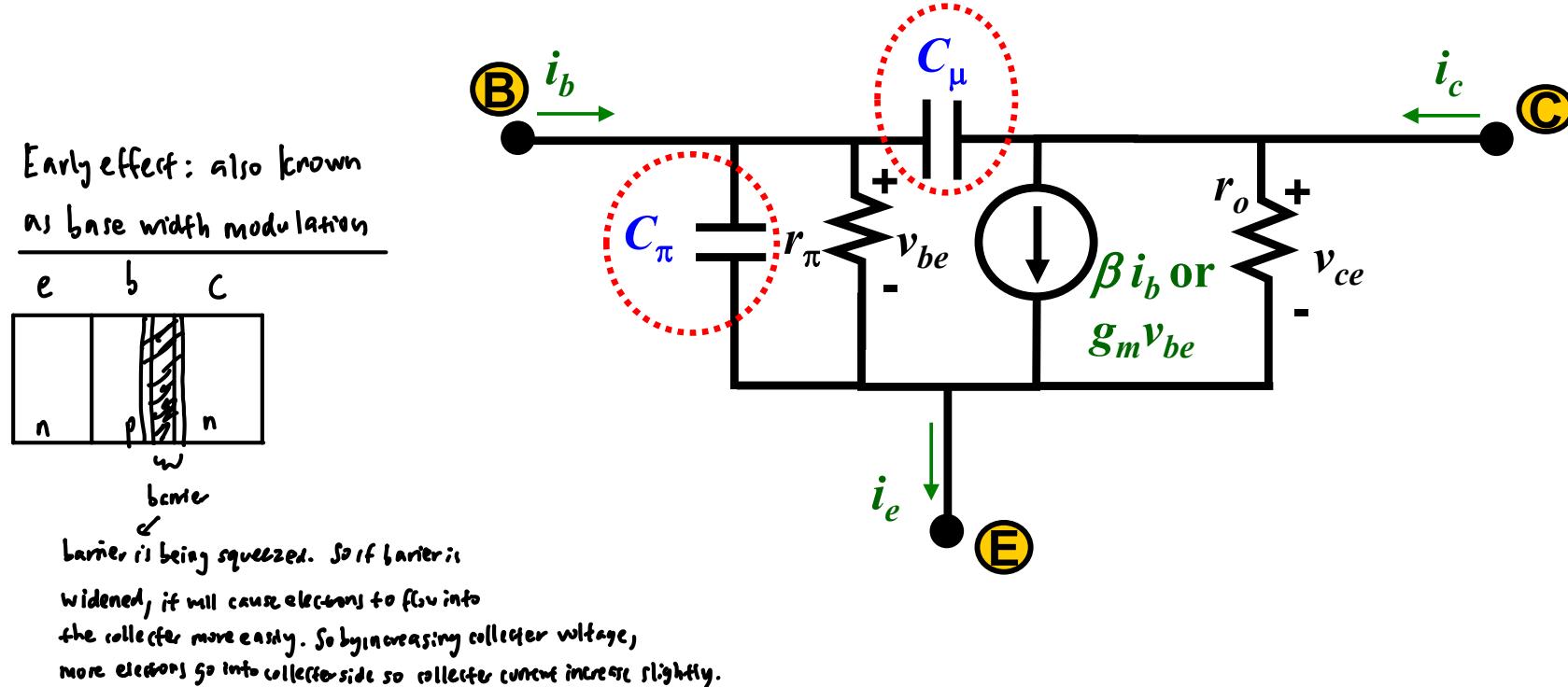- BJTs have capacitances associated with base-emitter and base-collector *p-n*-junctions, which have charge storage.
- At high frequencies, two parasitic capacitors have to be included: C_π and C_μ , respectively across the base-emitter and base-collector junctions.



Note: We introduce the existence of these capacitances C_μ and C_π here, and their inclusion in the Hybrid- π Model is only necessary when high frequency response is discussed. We will ignore these capacitances (in the pF range) for low frequency signals.

BJT - Topics Discussed

□ **Structure:** 3 regions/terminals - emitter, base and collector

□ **Operation regions:** Forward active, saturation, cut-off

□ **i_C - v_{CE} curves**

□ **Forward active IV characteristics (npn BJT):**

- $i_C = I_S e^{v_{BE}/V_T}, \quad i_B = \frac{I_S}{\beta} e^{v_{BE}/V_T}, \quad i_C = \beta i_B$

□ **Forward active i_C with Early Effect (npn BJT):** $i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A} \right)$

□ **npn vs pnp BJT:** same functions, opposite bias voltage polarities and current directions


□ **Forward active large-signal model & dc analysis**

- Thevenin equivalent vs voltage divider method for base biasing circuit

□ **Forward active small-signal model:** $g_m = \frac{I_C}{V_T}, \quad r_\pi = \frac{\beta V_T}{I_C}, \quad r_o = \frac{V_A}{I_C}$

APPENDICES

APPENDIX A – Operation of pnp BJT

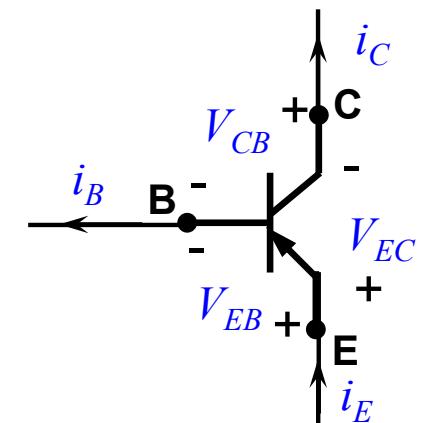

Modes of operation of the pnp bipolar junction transistor

Mode of Operation	Emitter-Base Junction	Collector-Base Junction	Applications
Cut-off	Reverse biased ($V_{EB} < 0$ for pnp)	Reverse biased ($V_{CB} < 0$ for pnp)	Logic-OFF State
Forward Active	Forward biased ($V_{EB} > 0$ for pnp)	Reverse biased ($V_{CB} < 0$ for pnp)	Amplifier
Saturation	Forward biased ($V_{EB} > 0$ for pnp)	Forward biased ($V_{CB} > 0$ for pnp)	Logic - ON State
Reverse Active	Reverse Biased ($V_{EB} < 0$ for pnp)	Forward Biased ($V_{CB} > 0$ for pnp)	Not used

* For the same mode of operation, the current directions and voltage polarities of pnp BJT are exactly opposite from those of npn BJT.

APPENDIX B – IV Characteristic of pnp BJT

- For pnp BJT in forward active operation –

- Emitter-base junction is forward biased: $v_{EB} > 0$.
- Collector-base junction is reverse biased: $v_{CB} < 0$.
- Collector current, i_C , is controlled by v_{EB} –

$$i_C = I_S e^{v_{EB}/V_T} \text{ (flows out of the collector)}, \quad (\text{B.1})$$

- Base current, i_B , is given by

$$i_B = \frac{I_S}{\beta} e^{v_{EB}/V_T} \text{ (flows out of the base)}, \quad (\text{B.2})$$


where I_S is the saturation current,

V_T is the thermal voltage and $V_T = kT/q \approx 0.025$ at $T = 300$ K, and β is the common-emitter current and $\beta = i_C/i_B$.

- From equations (B.1) and (B.2):

$$i_C = \beta i_B \quad (\text{B.3})$$

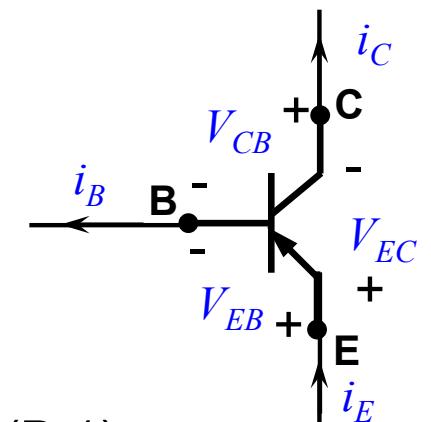- Emitter current: $i_E = i_C + i_B$ (flows into the emitter). (B.4)



APPENDIX C – Non-Ideal i_C -Expression

- With Early effect (see slide BJT-14), collector current in forward active region is given by

$$i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A} \right) = f(v_{BE}, v_{CE}) \quad (\text{C.1})$$

- We can express the total (instantaneous) currents and voltages in terms of the dc (operating point) and ac (signal) currents and voltages, that is

- $i_C = I_C + i_c$
- $v_{BE} = V_{BE} + v_{be}$
- $v_{CE} = V_{CE} + v_{ce}$

- Hence, $i_C = I_C + i_c = f(v_{BE}, v_{CE}) = f(V_{BE} + v_{be}, V_{CE} + v_{ce}) \quad (\text{C.2})$

- Expand equation (C.2) as a Taylor series and neglecting higher order terms for small v_{be} and v_{ce} -

$$\begin{aligned} i_C &= I_C + i_c = f(V_{BE} + v_{be}, V_{CE} + v_{ce}) \\ &\approx f(V_{BE}, V_{CE}) + \frac{\partial i_C}{\partial v_{BE}}|_{V_{BE}} \times v_{be} + \frac{\partial i_C}{\partial v_{CE}}|_{V_{CE}} \times v_{ce} \end{aligned}$$

- As $I_C = f(V_{BE}, V_{CE})$, small signal collector current

$$i_c \approx \frac{\partial i_C}{\partial v_{BE}}|_{V_{BE}} \times v_{be} + \frac{\partial i_C}{\partial v_{CE}}|_{V_{CE}} \times v_{ce}. \quad (\text{C.3})$$