

## ***Diode (Semiconductor pn-Junction)***

---


### **Diode (Semiconductor pn-Junction)**

1. Introduction
2. Operation Regions: Forward-Bias, Reverse-Bias, and Breakdown
3. Current-Voltage Characteristic
4. Modeling the Diode: Large-Signal Model and Small-Signal Model
5. The Diode Circuit(s): Rectifier and Voltage Regulator
6. Charge Stored and Capacitive Effect


### **Reference**

- ❑ A.D. Sedra & K.C. Smith, “Microelectronic Circuits – Theory and Application”, 5<sup>th</sup> Edition (International Version), Oxford University Press, Chapter 2.

# Diode – Introduction (Structure)

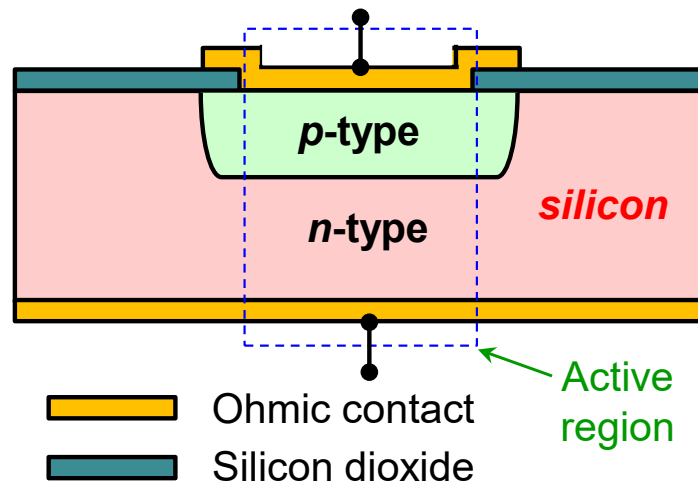

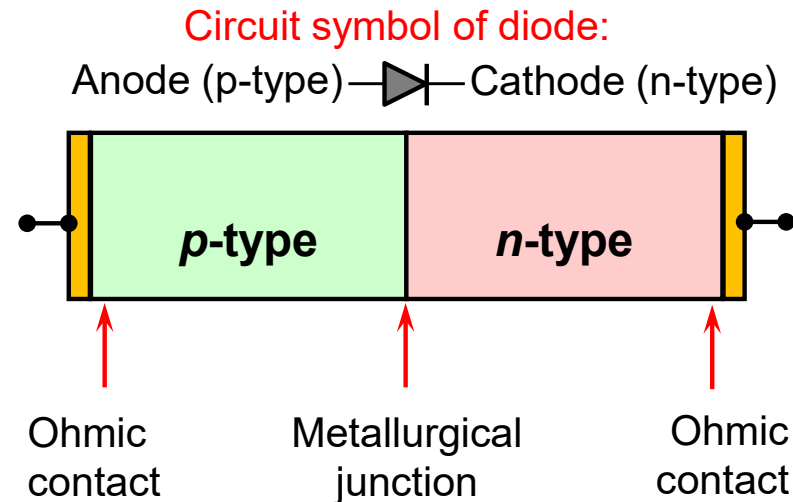**Realistic cross-section of fabricated silicon *pn*-junction diode**



**Simplified structure (active region) & circuit symbol of a semiconductor *pn*-junction.**

The diode to be discussed is a **semiconductor *pn*-junction**.

- ❑ Made using a **single crystal** semiconductor (typically **silicon**), with impurities added to one side to contain many **negative charge carriers (electrons)**, called an ***n*-type semiconductor**; and to the other side to contain many **positive charge carriers (holes)**, called a ***p*-type semiconductor**.
- ❑ In a semiconductor, there are two types of charge carriers: **electrons** (with charge of  $-1.602 \times 10^{-19}$  C) and **holes** (with charge of  $+1.602 \times 10^{-19}$  C). This is in contrast to metals, which have only electrons.

# Diode – Introduction (Semiconductor)


- ❑ Semiconductors have electrical conductivities (or resistivity) **between** that of metals (conductors) and insulators.
- ❑ Unlike metal and insulator, a **unique property of semiconductor** is that **impurities** can be added (in a controlled manner) into it –
  - to make it *n*-type or *p*-type, and
  - to change its conductivity (or resistivity) and carrier concentration.

$$R = \rho \frac{l}{A}$$

	Material	Typical Resistivity* (Ω-cm)	Typical Carrier Concentration (cm <sup>-3</sup> )
Metal	Copper Gold Aluminum Stainless Steel 316)	1.69×10 <sup>-6</sup> 2.20×10 <sup>-6</sup> 2.67×10 <sup>-6</sup> 70-78×10 <sup>-6</sup>	} ~10 <sup>23</sup> (electron)
Semiconductor	Germanium Silicon Gallium Arsenide	46 2.3×10 <sup>5</sup> 10 <sup>8</sup>	} Wide range up ~10 <sup>18-19</sup> (with impurity added)
Insulator	Silicon Nitride Silicon Dioxide Polyimide	10 <sup>14</sup> 10 <sup>14</sup> -10 <sup>16</sup> 10 <sup>18</sup>	} Negligible

\* Resistivity is reciprocal of conductivity. Temperature ~ 300 K (room temperature).

# Diode – Introduction (Semiconductor)

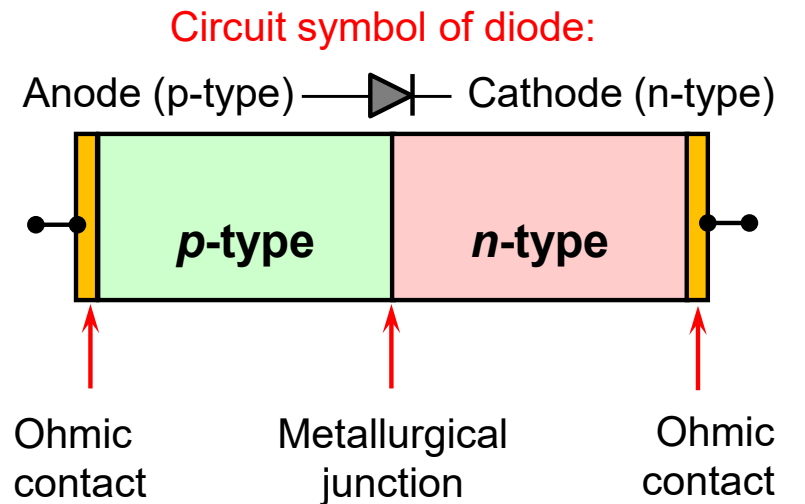

**Simplified structure and circuit symbol of a semiconductor pn junction.**

IIIA	IVA	VA	VI
5 <b>B</b> 10.81	6 <b>C</b> 12.01	7 <b>N</b> 14.01	
13 <b>Al</b> 26.98	14 <b>Si</b> 28.09	15 <b>P</b> 30.97	
31 <b>Ga</b> 69.72	32 <b>Ge</b> 72.61	33 <b>As</b> 74.92	
49 <b>In</b> 114.8	50 <b>Sn</b> 118.7	51 <b>Sb</b> 121.8	
81	82	83	


p-type impurities in Si → (points to B, Al, Ga)

n-type impurities in Si → (points to P, As, Sb)

- ❑ The process of adding impurities to semiconductor is known as **doping**. ⚡ ⚡
- ❑ Impurities added to semiconductor to make it *n*-type and *p*-type are different.  
For silicon (a group IV element) –
  - *p*-type impurity is a group III element (Boron, Aluminium and Gallium).
  - *n*-type impurity is a group V element (Phosphorus, Arsenic and Antimony).
- ❑ The process of doping can also change a *p*-type semiconductor to *n*-type semiconductor, and vice versa. For example, by adding more *n*-type impurities to an originally *p*-type semiconductor, it can be changed to *n*-type. This allows the making of *pn*-junction, and transistors (BJT and MOSFET).
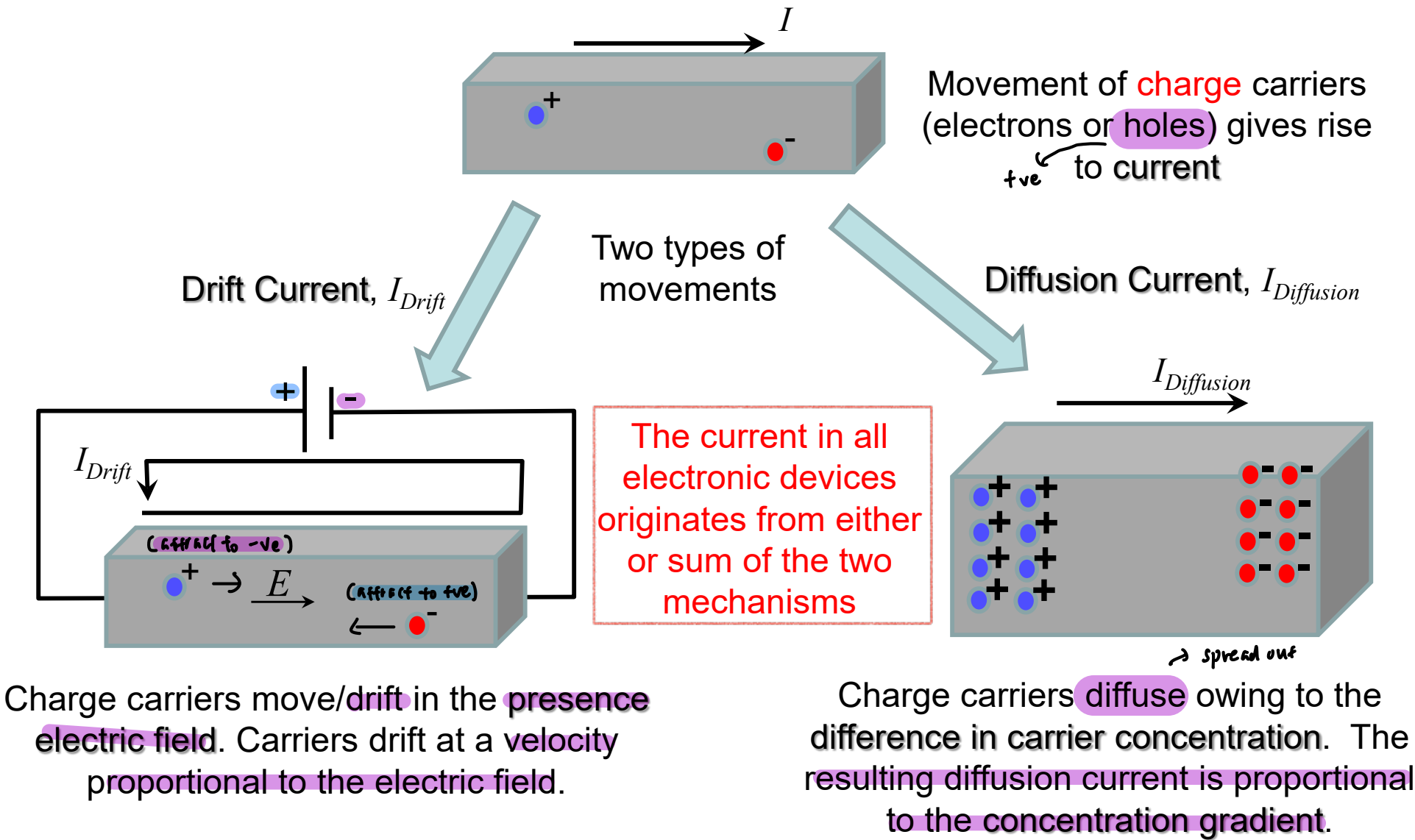
# Diode – Introduction (Origin of Current)

- Take note there are two types of charge carrier movement, leading to two types of current: drift and diffusion.



# Diode – Introduction (Carriers and Carrier Movement in Devices)


Devices	Dominant Carrier Movement Mechanism	Type of Carriers
Resistor	Drift	<ul style="list-style-type: none"> <li>▪ Electrons (Metal)</li> <li>▪ Electrons and holes (Semiconductor)</li> </ul>
Diode	Diffusion	<ul style="list-style-type: none"> <li>▪ Electrons and holes</li> </ul>
BJT (Bipolar Junction Transistor)	Diffusion	<ul style="list-style-type: none"> <li>▪ Electrons and holes</li> </ul>
MOSFET (Metal Oxide Semiconductor Field Effect Transistor)	Drift	<ul style="list-style-type: none"> <li>▪ Electrons (NMOS)</li> <li>▪ Holes (PMOS)</li> </ul>

→ one side p-type  
one side n-type  
(diffuse)
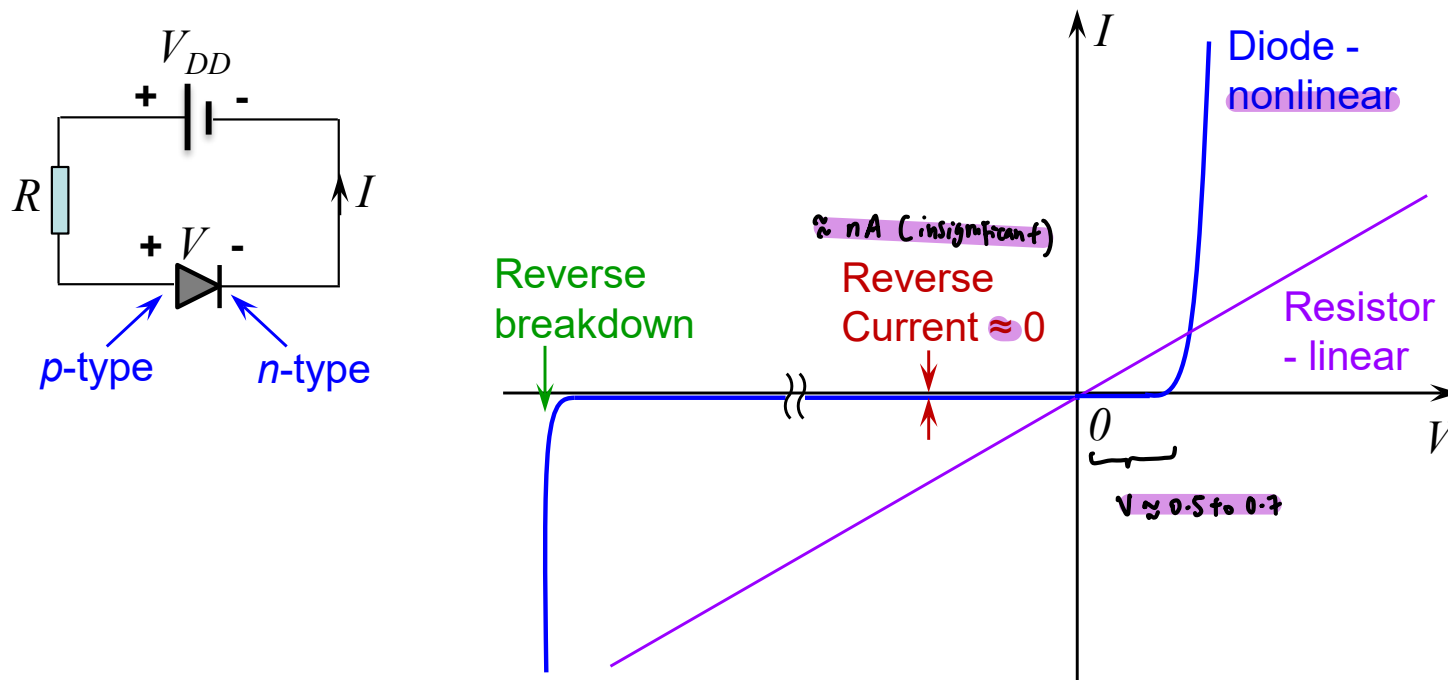
## Diode – Introduction (IV Characteristic)

Diode (semiconductor *pn*-junction) is the simplest (2-terminal) and most fundamental *nonlinear* circuit element.

- ❑ It allows a current flow through it easily in one direction (known as the forward direction,  $V > 0$ ), but not in the opposite direction (known as the reverse direction,  $V < 0$ ), except for the reverse breakdown region.
- ❑ Unlike a resistor, which is a *linear* element that has a linear current-voltage relation.
- ❑ Diode can be used as a switch and in a rectifier circuit to convert ac into dc.



## ***Diode (Semiconductor pn-Junction)***

---

### **Diode (Semiconductor pn-Junction)**


1. Introduction
2. Operation Regions: Forward-Bias, Reverse-Bias, and Breakdown
3. Current-Voltage Characteristic
4. Modeling the Diode: Large-Signal Model and Small-Signal Model
5. The Diode Circuit(s): Rectifier and Voltage Regulator
6. Charge Stored and Capacitive Effect

### **Reference**

- ❑ A.D. Sedra & K.C. Smith, “Microelectronic Circuits – Theory and Application”, 5<sup>th</sup> Edition (International Version), Oxford University Press, Chapter 2.




# Diode – Forward Bias Operation

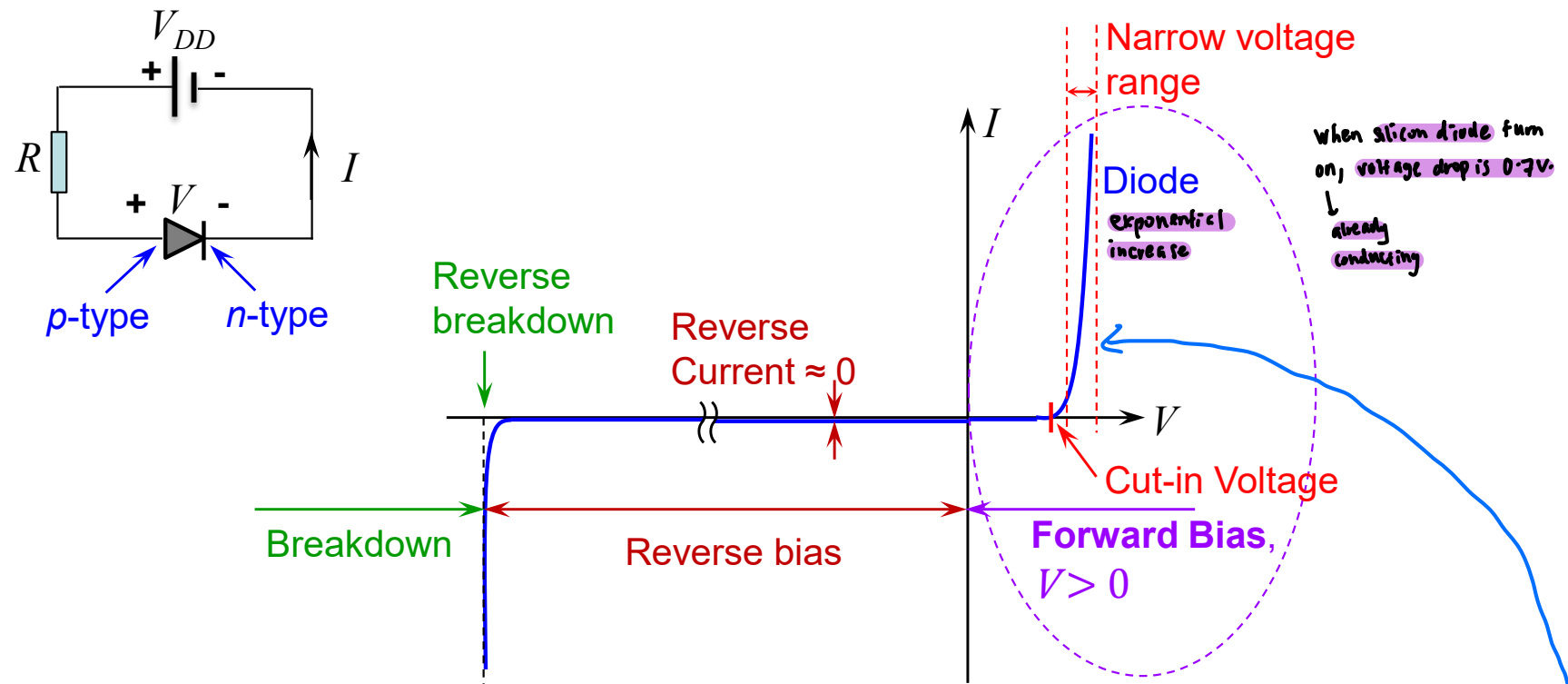


- ❑ Under **forward-bias** ( $V > 0$ ), an external voltage is applied such that the **p-type terminal** is at a higher (positive) voltage with respect to the **n-type terminal**.
  - **Forward current flows** through the diode from the **p-type** to **n-type** side.
- ❑ The **forward current remains small** ( $\approx 0$  practically) until the **cut-in voltage**, and **increases quickly** with a small increase in  $V$  thereafter.
- ❑ With a substantial forward current, the voltage drop across the diode lies in a **narrow range**.
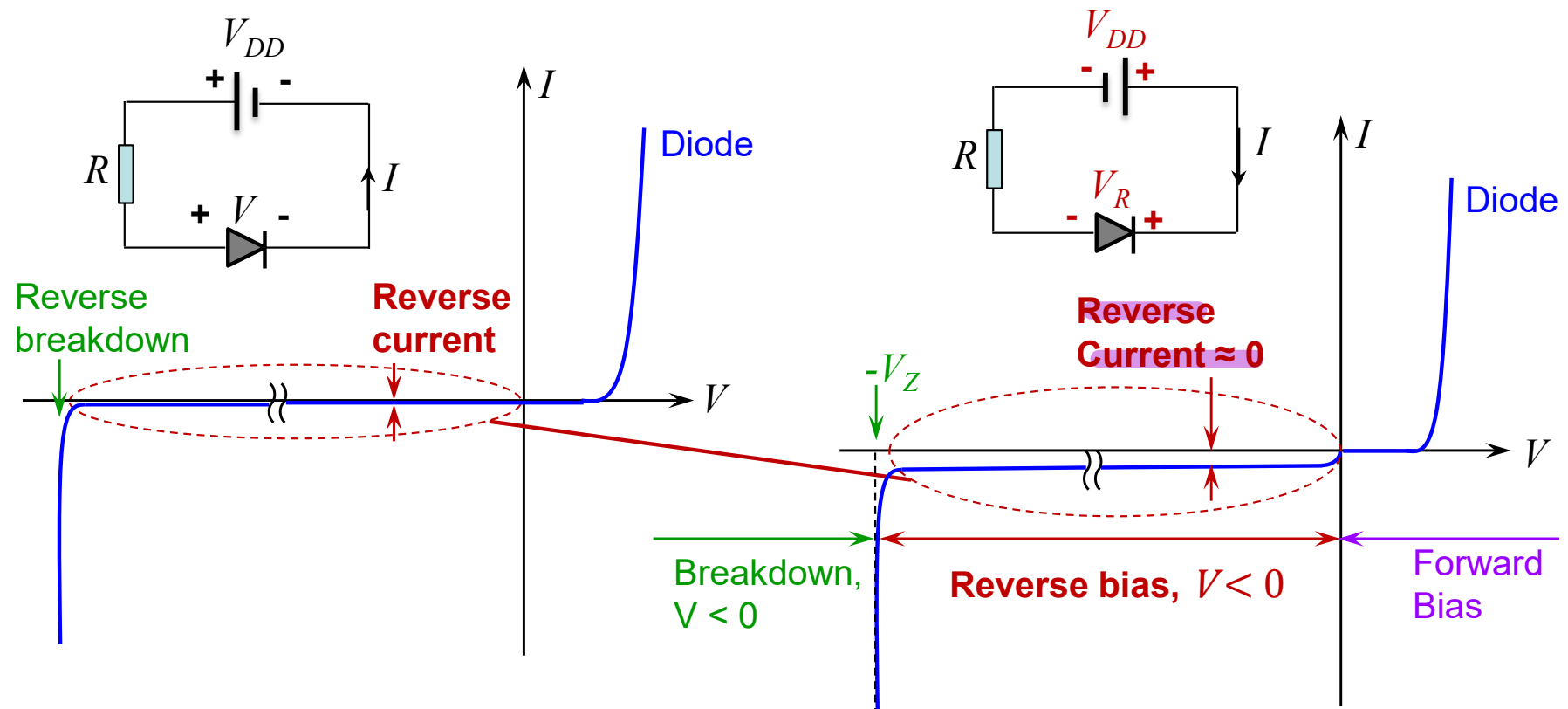
# Diode – Reverse Bias Operation (Non-Breakdown Region)




- ❑ Under **reverse-bias** ( $V < 0$ ), an external voltage is applied such that the *p*-type terminal is at a lower (or negative) voltage with respect to the *n*-type terminal.
  - Reverse current flows through the diode from the *n*-type to *p*-type side.
- ❑ For reverse bias voltage magnitude,  $|V| = V_R < V_Z$ , the **breakdown voltage**, reverse current is very small and can be treated practically as **zero**, meaning the diode is equivalent to an **open circuit**.
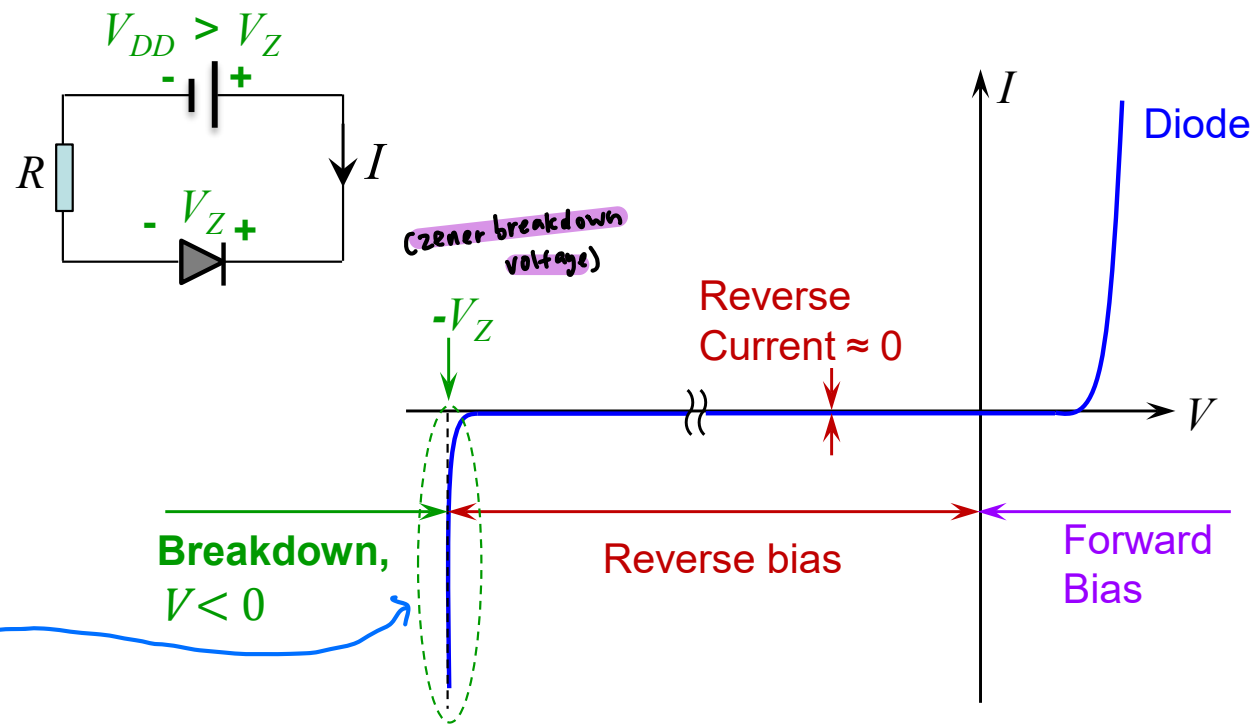
# Diode – Reverse Bias Operation (Breakdown Region)



- ❑ With an external voltage supply that reverse biases the diode,  $V_{DD} > V_Z$  (breakdown voltage), the diode reverse current is no longer  $\approx 0$ , but can be very large, while its voltage is practically not changed and stays at  $-V_Z$ . This condition is known as **breakdown**.
- ❑ Under breakdown operating condition, the voltage across the pn junction diode is 'clamped' at  $-V_Z$ . Minus sign highlights that breakdown is a reverse biased condition.
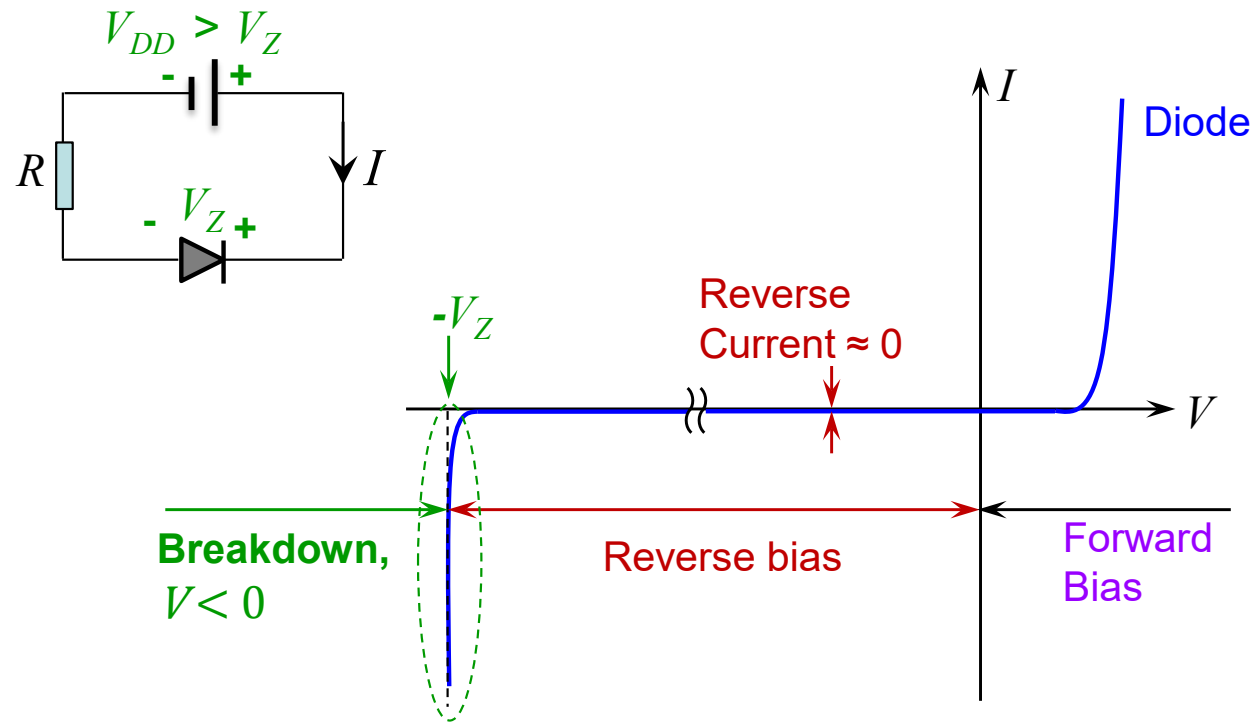
# Diode – Reverse Bias Operation (Breakdown Region)



- Operation in the breakdown region **does not** destroy the diode, provided the current through it is kept below a certain level, such that the power dissipation ( $V \times I$ ) is below what the diode can handle.
- While operating in the breakdown region, current can be limited by connecting a resistor,  $R$ , of suitable value in series with the  $pn$  junction diode -

$$P = VI / P = I^2 R / P = \frac{V^2}{R}$$

$$I = \frac{V_{DD} - V_Z}{R}$$

## ***Diode (Semiconductor pn-Junction)***

---


### **Diode (Semiconductor pn-Junction)**

1. Introduction
2. Operation Regions: Forward-Bias, Reverse-Bias, and Breakdown
3. **Current-Voltage Characteristic**
4. Modeling the Diode: Large-Signal Model and Small-Signal Model
5. The Diode Circuit(s): Rectifier and Voltage Regulator
6. Charge Stored and Capacitive Effect

### **Reference**

- ❑ A.D. Sedra & K.C. Smith, “Microelectronic Circuits – Theory and Application”, 5<sup>th</sup> Edition (International Version), Oxford University Press, Chapter 2.

# Diode – Current-Voltage Characteristic

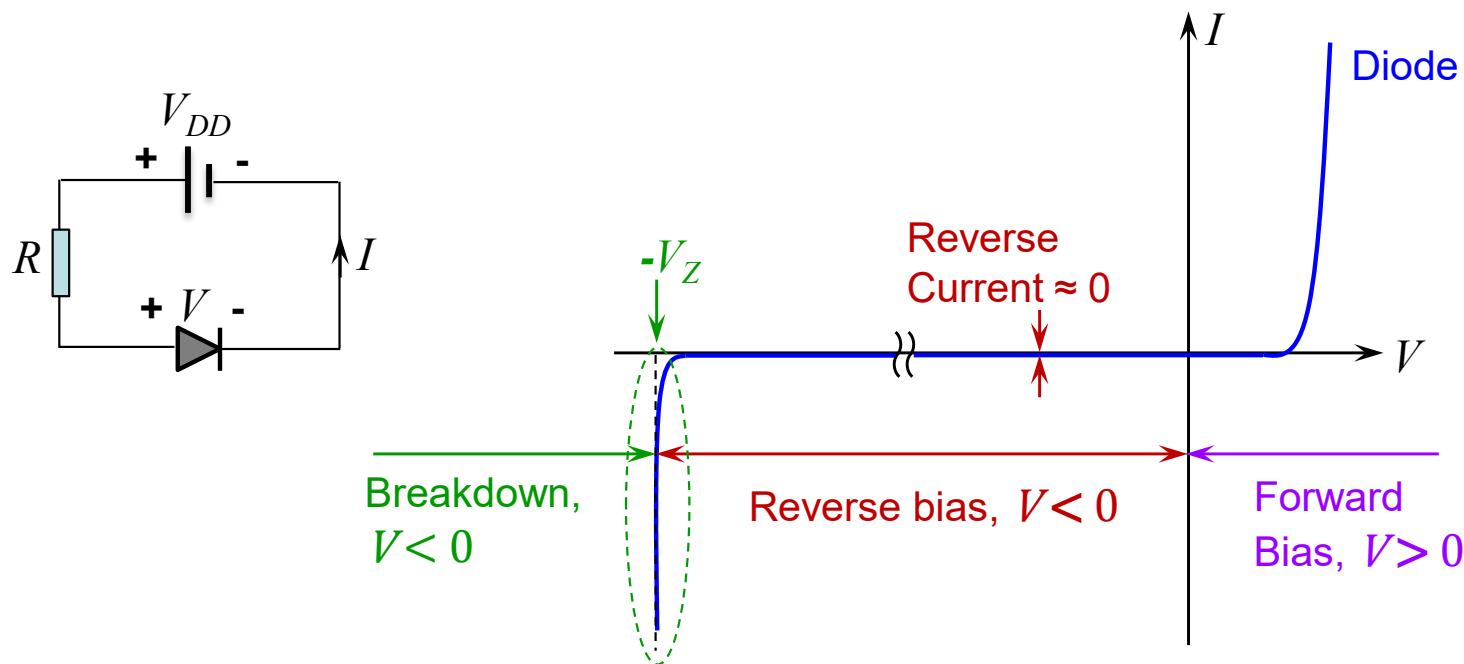

Current-voltage ( $I$  $V$ ) relationship of a “real”  $pn$ -junction diode -


$$I = I_S \left( e^{\frac{V}{nV_T}} - 1 \right)$$

between 1 ~ 2

(2.1)

- ☐  $V$  is the **voltage** across the diode:  $V > 0$  for forward bias and  $V < 0$  for reverse bias.
- ☐  $I$  is the **current** flowing through the diode:  $I > 0$  for forward bias and  $I < 0$  for reverse bias.  
(take more convenient value when doing calculation)
- ☐  $V_T$  is the **thermal voltage**,  $V_T = kT/q = 0.0259 \text{ V} \approx 0.025 \text{ V}$  at  $T = 300 \text{ K}$ .  
(27°C)

# Diode – Current-Voltage Characteristic

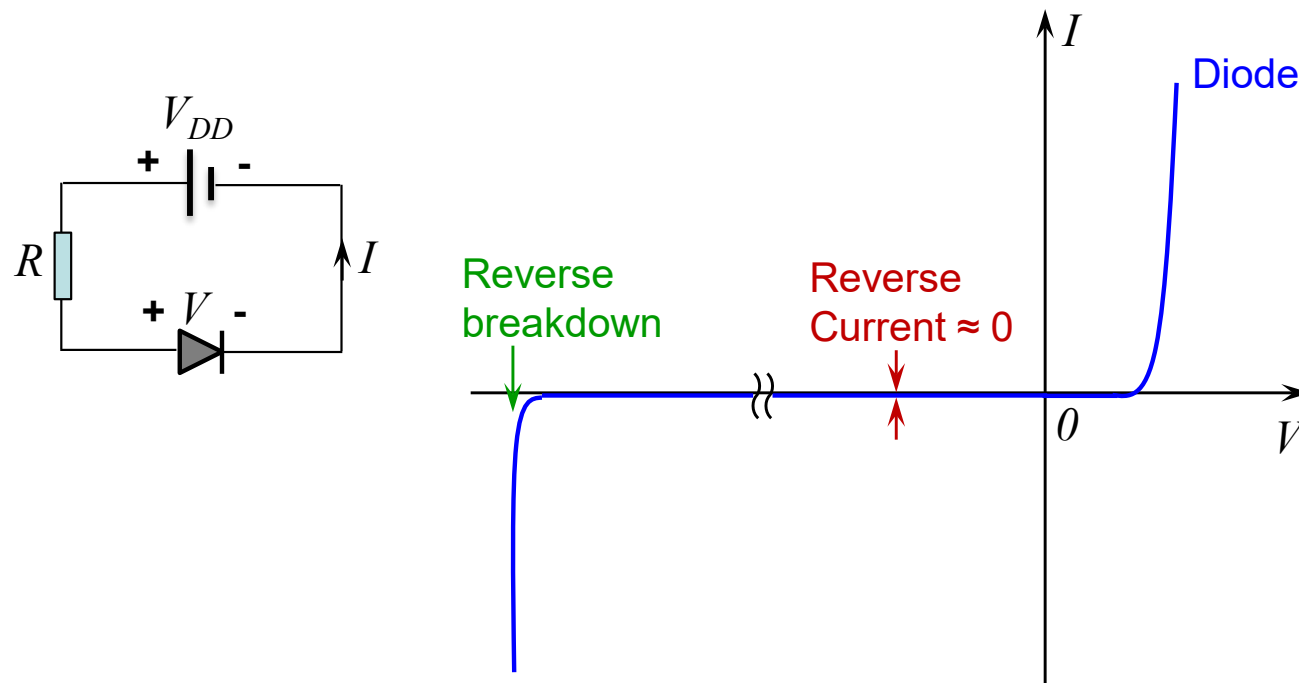


Current-voltage ( $IV$ ) relationship of a “real”  $pn$ -junction diode -

$$I = I_S \left( e^{\frac{V}{nV_T}} - 1 \right) \quad (2.1)$$

- $n$  is the **exponential factor**, and has a value between 1 and 2, depending on the material and physical structure of the semiconductor  $pn$ -junction.
  - For an **ideal  $pn$ -junction diode**,  $n = 1$ .
- $I_S$  is the **reverse saturation current**, a parameter of the diode and it is a strong function of temperature. It increases with increasing temperature.
 

(  $\uparrow T$ ,  $\uparrow I_S$  )
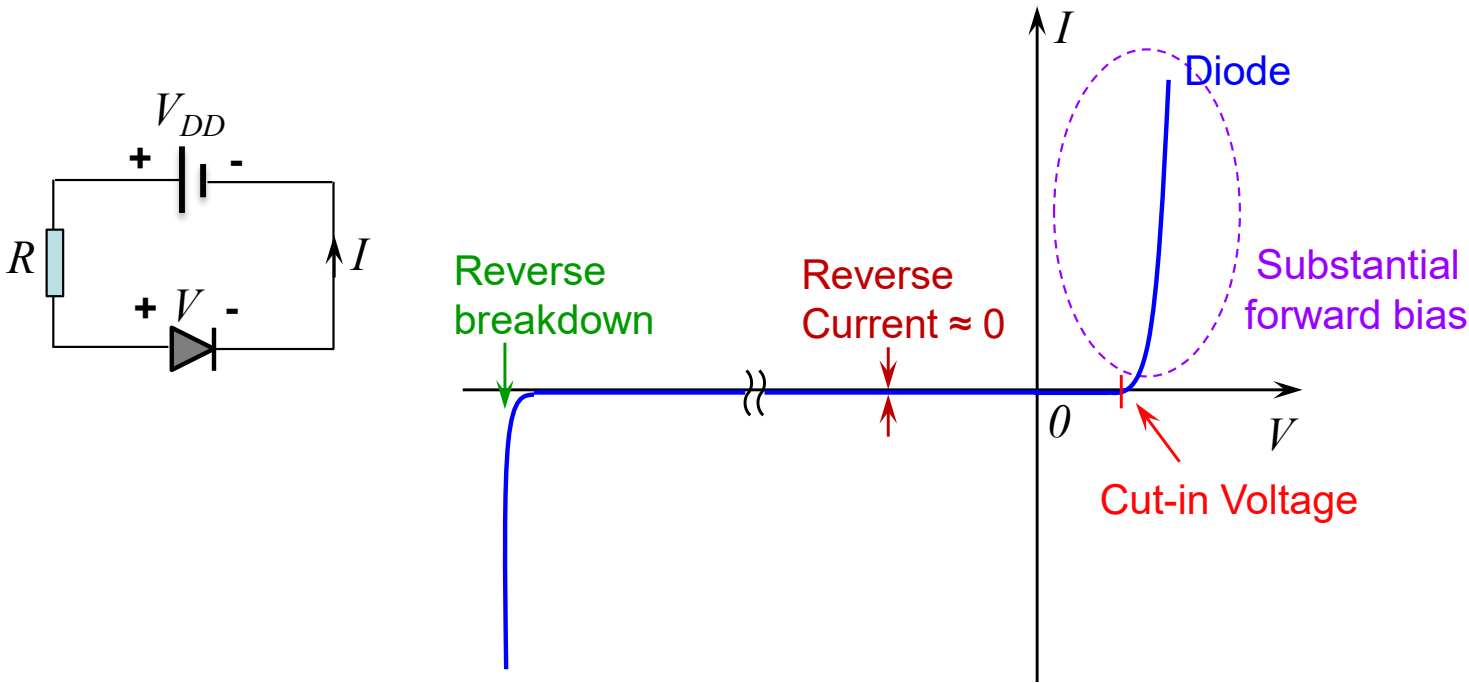
# Diode – Current-Voltage Characteristic (Forward Bias)



Current-voltage ( $IV$ ) relationship of a “real”  $pn$ -junction diode -

$$I = I_S \left( e^{\frac{V}{nV_T}} - 1 \right) \tag{2.1}$$

□ For **substantial forward bias** ( $V > \text{cut-in voltage} > 0$ ),  $e^{\frac{V}{nV_T}} \gg 1$  and  $\downarrow$  much greater than 1

$I = I_S \left( e^{\frac{V}{nV_T}} - 1 \right) \approx I_S e^{\frac{V}{nV_T}}$


 $\rightarrow$  1 becomes negligible (2.2a)

or  $V \approx nV_T \ln(I/I_S)^*$   $\rightarrow$  taking  $\log_e$  both sides (2.2b)

\*A linear relation between  $V$  and  $\ln(I)$ .


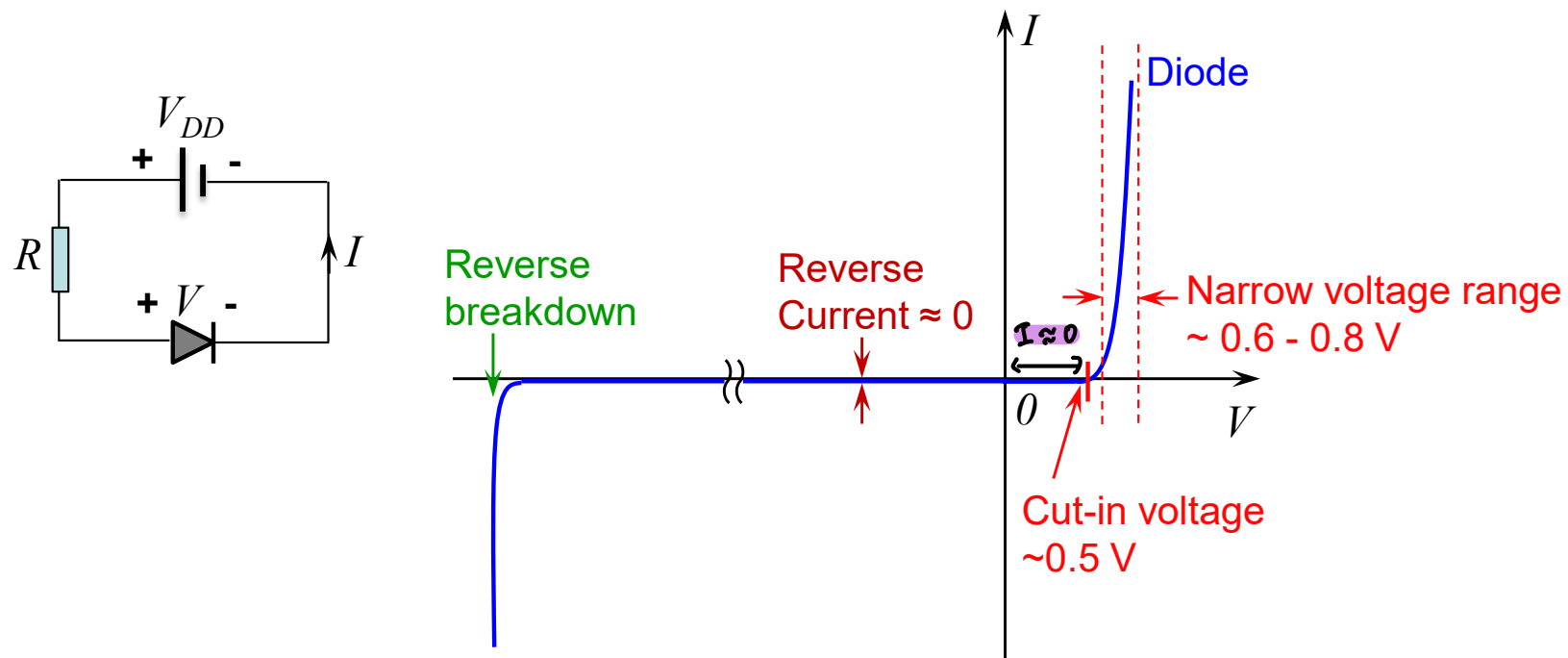
# Diode – Current-Voltage Characteristic (Forward Bias)




Current-voltage ( $IV$ ) relationship of a “real”  $pn$ -junction diode -

$$I = I_S \left( e^{\frac{V}{nV_T}} - 1 \right) \quad (2.1)$$

□ Owing to the **exponential**  $IV$  relationship –

- $I \approx 0$  for  $V < \sim 0.5$  V (known as the **cut-in voltage**)
- For a **fully conducting  $pn$ -junction diode** ( $V > \sim 0.5$  V and with **substantial current** flowing through), the **voltage drop across it lies in a narrow range**,  $\sim 0.6$  to  $0.8$  V.  $\Rightarrow$  take avg:  $0.7$  V
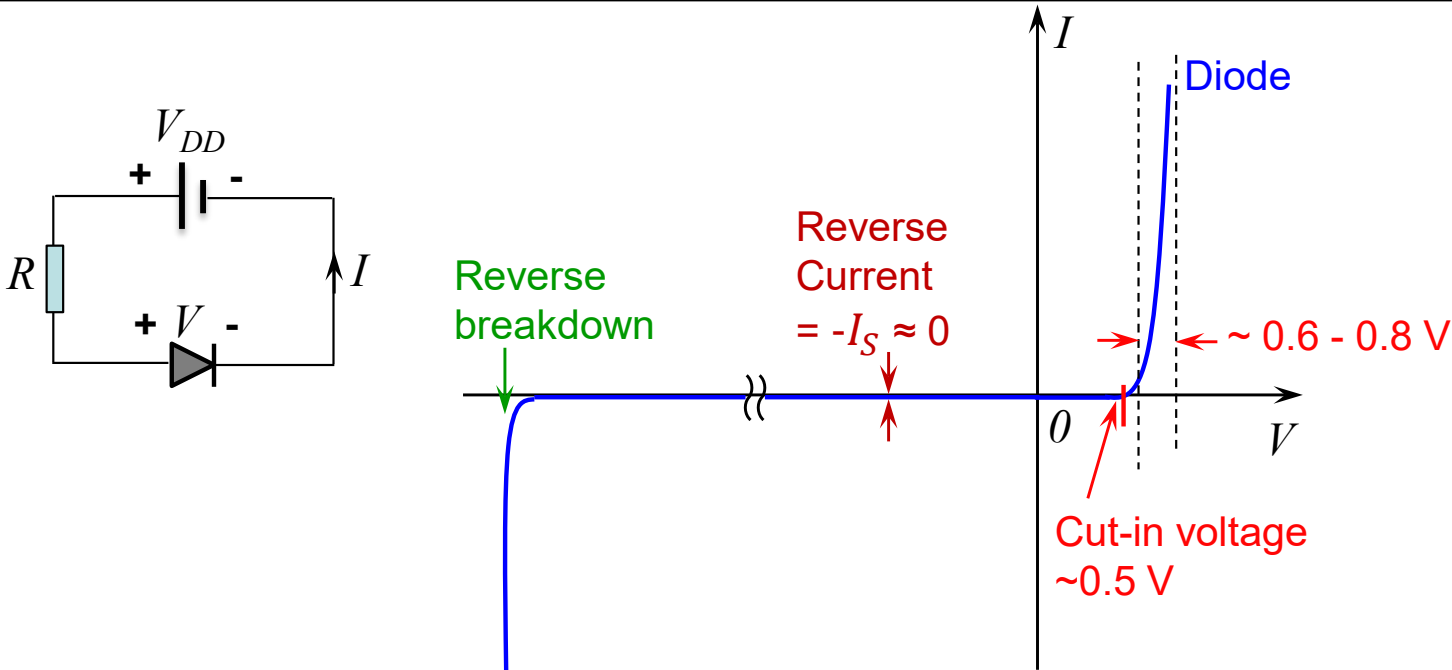
# Diode – Current-Voltage Characteristic (Reverse Bias)



Current-voltage ( $IV$ ) relationship of a “real”  $pn$ -junction diode -

$$I = I_S \left( e^{\frac{V}{nV_T}} - 1 \right) \tag{2.1}$$

- In **reverse bias**,  $V < 0$ , for  $|V| > \text{a few times } nV_T$ ,  $e^{\frac{V}{nV_T}} \ll 1$  and  
 $I = I_S \left( e^{\frac{V}{nV_T}} - 1 \right) \approx -I_S$  (for Non- breakdown region)  
↓ much less than

- Reverse current is a **constant** independent on  $V$ , having a magnitude of  $I_S$ , the reverse saturation current, a very small number (practically zero).

**N.B.** Equation (2.1) does **not** predict the **breakdown** characteristic.

## ***Diode (Semiconductor pn-Junction)***

---


### **Diode (Semiconductor pn-Junction)**

1. Introduction
2. Operation Regions: Forward-Bias, Reverse-Bias, and Breakdown
3. Current-Voltage Characteristic
4. Modeling the Diode: Large-Signal Model and Small-Signal Model
5. The Diode Circuit(s): Rectifier and Voltage Regulator
6. Charge Stored and Capacitive Effect

### **Reference**

- ❑ A.D. Sedra & K.C. Smith, “Microelectronic Circuits – Theory and Application”, 5<sup>th</sup> Edition (International Version), Oxford University Press, Chapter 2.
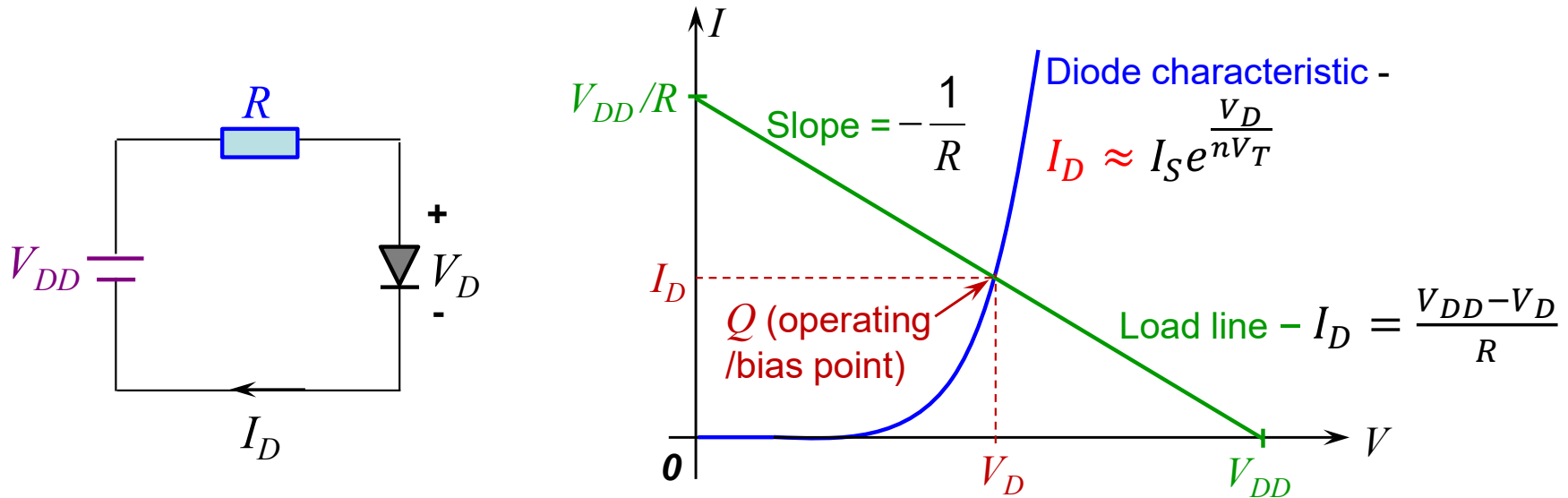
# Diode – Modeling the Diode – Large-Signal Model




## Why the need to model diode?

- Consider the analysis of the above simple circuit shown, which uses a diode in forward bias. Assuming  $V_{DD} > 0.5$  V, the  $IV$  characteristic of the diode is

$$I_D = I_S \left( e^{\frac{V_D}{nV_T}} - 1 \right) \approx I_S e^{\frac{V_D}{nV_T}} \quad \text{based on pg 16} \quad (2.3)$$

- $I_D$  and  $V_D$  are the current through the diode and voltage across the diode, respectively.
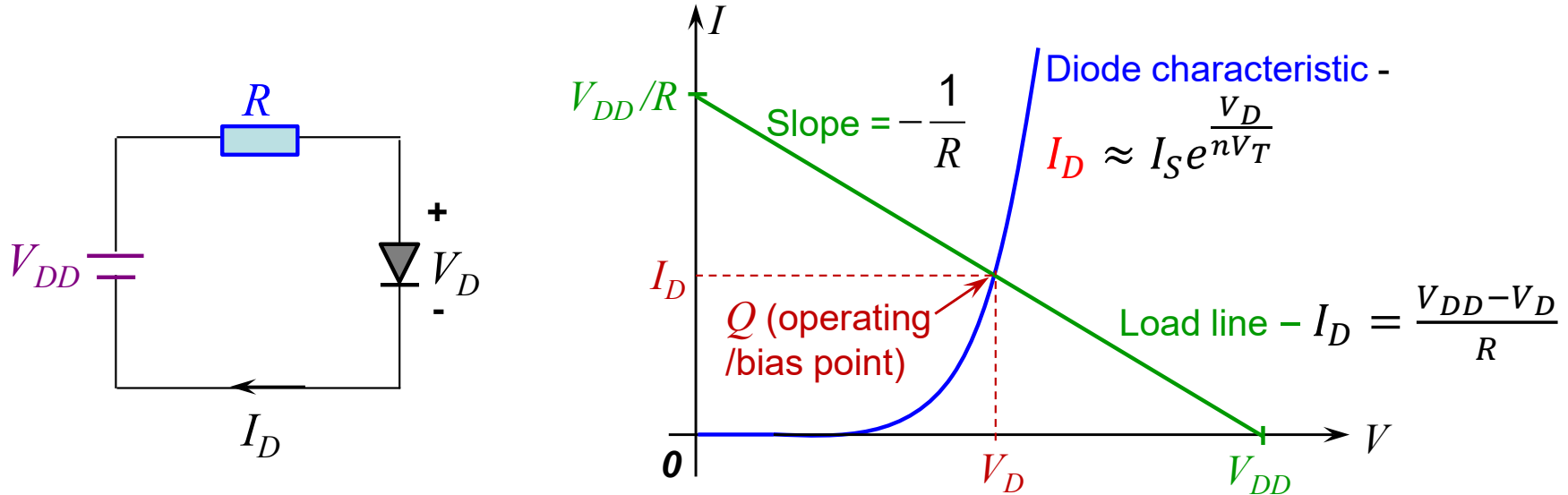
# Diode – Modeling the Diode – Large-Signal Model



- ❑  $I_D$  and  $V_D$  are **also** governed by the Kirchhoff Voltage Law (KVL) –


Load line: 
$$I_D = \frac{V_{DD} - V_D}{R} \quad (2.4)$$

- ❑ Equation (2.4) is known as the **load line** of the circuit.
- ❑  $I_D$  and  $V_D$  **cannot** be determined easily by solving equations (2.3) and (2.4) simultaneously, owing to the **exponential  $IV$  characteristic** of the *pn*-junction diode.
- ❑ They can be **determined by the intersection of equations (2.3) and (2.4) graphically** (as shown above).
- ❑ They can also be solved using a simple **iterative procedure** (see work example).

# Diode – Modeling the Diode – Large-Signal Model
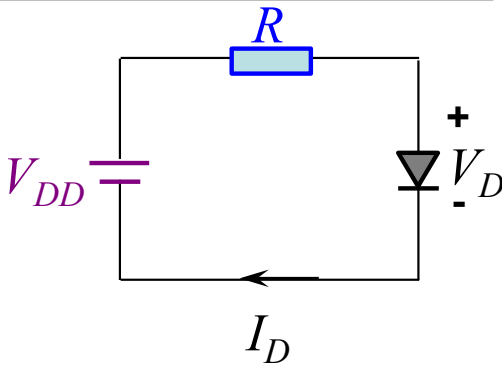
## Work Example - Iterative Method

Determine the current  $I_D$  and voltage  $V_D$  of the circuit shown below by means of iteration for  $V_{DD} = 5\text{ V}$  and  $R = 1\text{ k}\Omega$ . It is given that the diode has a current of 1 mA at a voltage of 0.6 V and that its voltage drop changes by 0.1 V for every decade change in current.



- ❑  $I_D$  and  $V_D$  are governed by equations (2.3) and (2.4).
- ❑ We need to find  $nV_T$  first in order to use the diode equation (2.3) in the iteration process.

take loge both sides  $\rightarrow I_D \approx I_S e^{\frac{V_D}{nV_T}}$  ( $V_{DD} = 5\text{ V} \Rightarrow$  diode operates in substantial forward bias)

$\Rightarrow V_D \approx nV_T \ln(I_D/I_S)$

- ❑ Given that at  $V_D = 0.6\text{ V}$ ,  $I_D = 1\text{ mA} \Rightarrow 0.6\text{ V} = nV_T \ln(1\text{ mA}/I_S)$

- ❑ Subtracting the above two equations yields

$\ln\left(\frac{x}{y}\right) = \ln x - \ln y$

$V_D - 0.6\text{ V} = nV_T \ln(I_D/I_S) - nV_T \ln(1\text{ mA}/I_S)$

$\Rightarrow V_D - 0.6\text{ V} = nV_T \ln(I_D/1\text{ mA})$

$nV_T (\ln I_D - \ln I_S) - nV_T (\ln 1\text{ mA} - \ln I_S)$   
 $= nV_T (\ln I_D - \ln I_S - \ln 1\text{ mA} + \ln I_S)$   
 $= nV_T (\ln I_D - \ln 1\text{ mA})$

## Diode – Modeling the Diode – Large-Signal Model

- Given that  $V_D$  changes by 0.1 V for every decade change in  $I_D$ , i.e., for  $(V_D - 0.6 \text{ V}) = 0.1 \text{ V}$ ,  $I_D / 1 \text{ mA} = 10$ , leading to

$$V_D - 0.6 \text{ V} = nV_T \ln(I_D / 1 \text{ mA}) \Rightarrow 0.1 = nV_T \ln(10) \\ \Rightarrow nV_T = 0.043$$

The iteration process proceeds as follows -

- ① 1) We first assume  $V_D = V_{D0} = 0.7 \text{ V}$ , the mid voltage value of the range shown on slide pn-17 ( $\sim 0.6 - 0.8 \text{ V}$ ), which is based on the diode characteristic, i.e., equation (2.3).
- 2) Next, substitute  $V_D = V_{D0} = 0.7 \text{ V}$  into equation (2.4), the KVL equation, we make an initially estimate for  $I_D (= I_{D0})$  -

$$I_{D0} = \frac{V_{DD} - V_{D0}}{R} = \frac{5 - 0.7}{1000} = 4.3 \text{ mA}$$

- 3) Using the estimated  $I_{D0} = 4.3 \text{ mA}$ , a better estimate for  $V_D (= V_{D1})$  is obtained using the diode equation -

$$V_D - 0.6 \text{ V} = nV_T \ln(I_D / 1 \text{ mA}) \Rightarrow V_{D1} - 0.6 \text{ V} = 0.043 \ln(4.3 \text{ mA} / 1 \text{ mA}) \\ \Rightarrow V_{D1} = 0.6627 \text{ V}$$

## Diode – Modeling the Diode – Large-Signal Model

---

- 4) Substitute  $V_{D1} = 0.6627$  V into equation (2.4), a better estimate for  $I_D (= I_{D1})$  is obtained

$$I_{D1} = \frac{V_{DD} - V_{D1}}{R} = \frac{5 - 0.6627}{1000} = 4.3373 \text{ mA}$$

- 5) Thus, after the 1<sup>st</sup> iteration  $I_{D1} = 4.3373$  mA and  $V_{D1} = 0.6627$  V. The 2<sup>nd</sup> iteration proceeds in a similar manner, by repeating steps 3 and 4:

$$V_{D2} - 0.6 \text{ V} = 0.043 \ln(4.3373 \text{ mA} / 1 \text{ mA}) \Rightarrow V_{D2} = 0.6631 \text{ V}$$


$$I_{D2} = \frac{V_{DD} - V_{D2}}{R} = \frac{5 - 0.6631}{1000} = 4.3369 \text{ mA}$$

- 6) 2<sup>nd</sup> iteration yields  $I_{D2} = 4.3369$  mA and  $V_{D2} = 0.6631$  V, which are close to values obtained after the 1<sup>st</sup> iteration (less than 0.06% difference), hence further iterations are not necessary, as the values of  $V_D$  and  $I_D$  have converged.

□ Take note that equations (2.3) and (2.4) are used alternately.



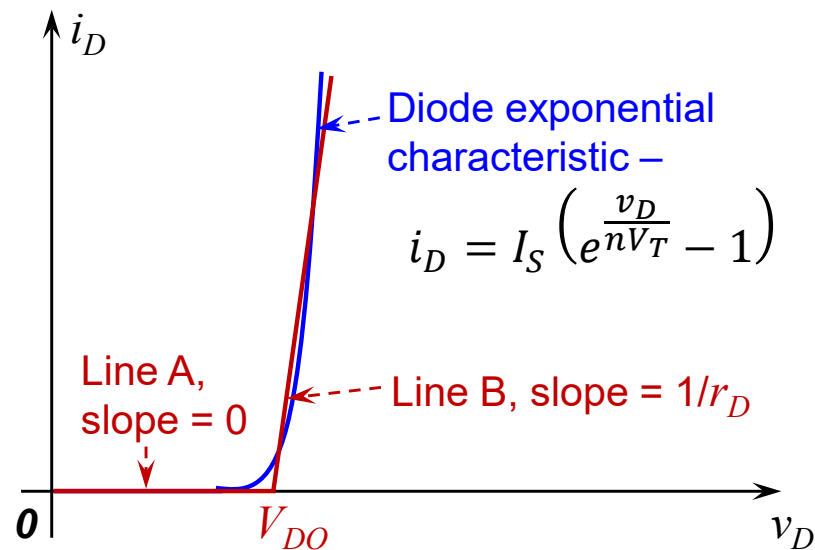
# Diode – Modeling the Diode – Large-Signal Model



## Why the need to model diode?

- ❑ For more complex circuits, the analysis by means of the graphical method may not be possible and the iterative method may be too tedious owing to the **exponential**  $IV$  characteristic of diode.
- ❑ To speed up circuit analysis, **simpler model** for the diode is used. This is at the **expense** of precise results.
- ❑ The forward bias diode exponential characteristic can be approximated by two straight lines: Line A with **zero slope**, and Line B with a **slope  $1/r_D$** . This approximation is known as the **piecewise-linear model**.
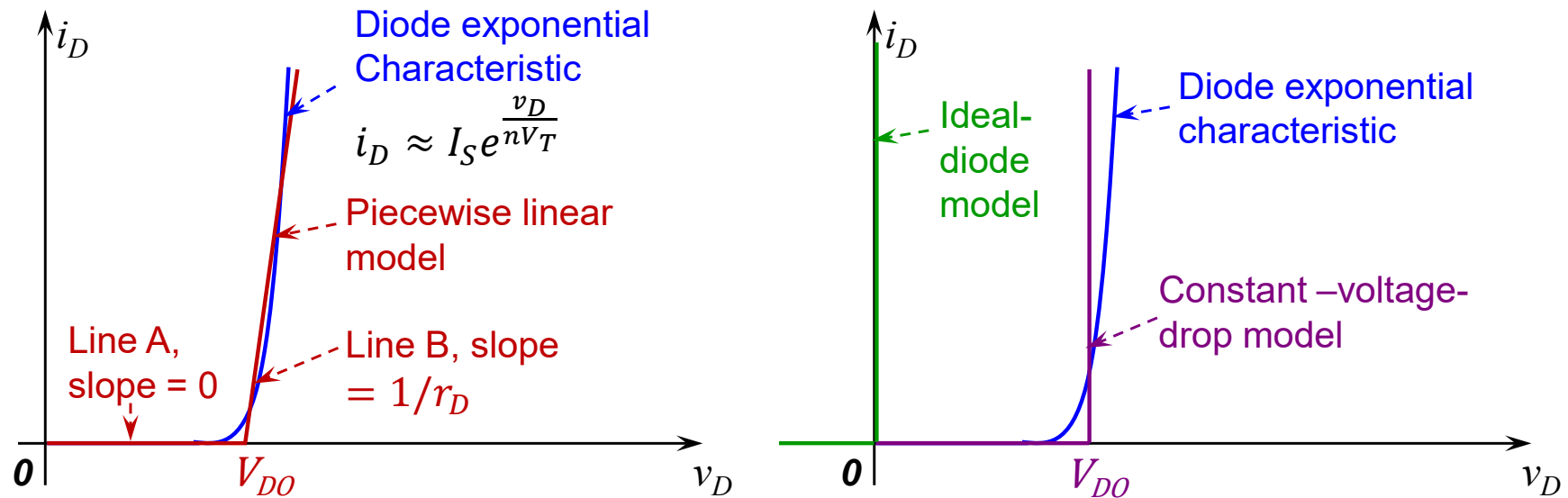
# Diode – Modeling the Diode - Large-Signal Model



## Large-signal model


### □ The piecewise-linear model:

- $i_D = 0$ ,  $v_D \leq V_{DO}$  (Line A) (2.5)
- $i_D = (v_D - V_{DO})/r_D$ ,  $v_D \geq V_{DO}$  (Line B) (2.6)
- $V_{DO}$  and  $r_D$  are model parameters. Choice of lines A and B (or  $V_{DO}$  and  $r_D$ ) is not unique.
- Closer approximation obtained by restricting the operation range.

### □ The ideal-diode model: $V_{DO} = 0$ and $r_D = 0$ .

### □ The constant-voltage-drop model: $r_D = 0$ and $V_{DO}$ is usually taken as 0.7 V.
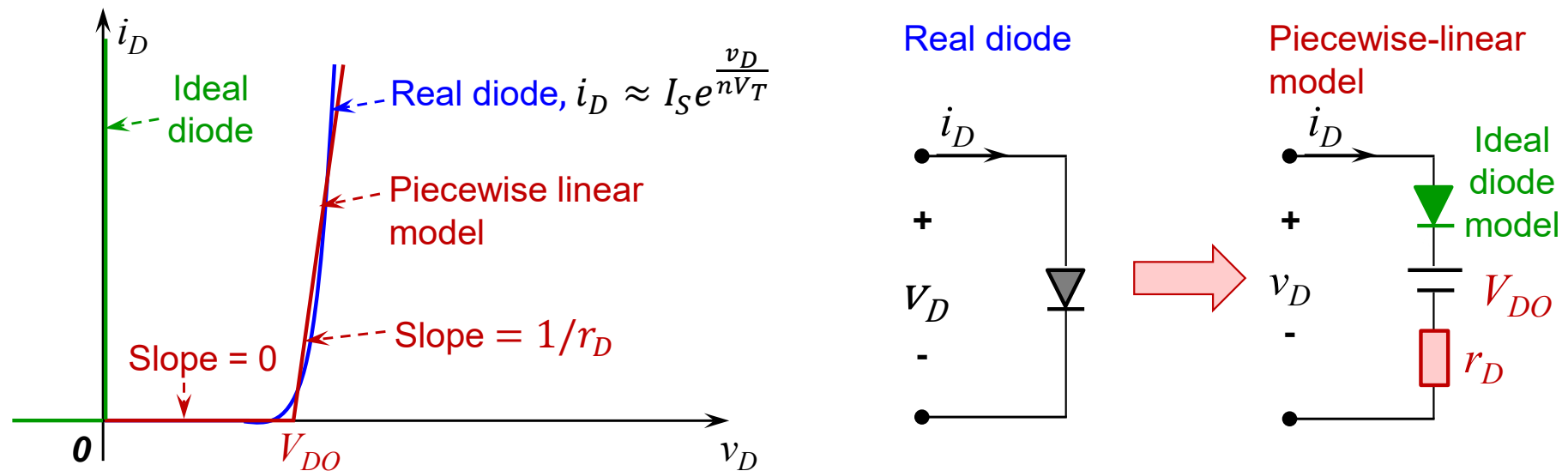
# Diode – Modeling the Diode - Large Signal Model



## The large-signal model

- ❑ In the equivalent circuit of the **piecewise-linear model** of diode, an **ideal diode model** is included to restrict  $i_D$  flow in the forward bias direction only.
- ❑ The large signal model can be used to replace the diode in the dc (large signal) circuit analysis (see work example to follow).
- ❑ Symbols for diode current and voltage have been replaced by  $i_D$  and  $v_D$ . They represent the 'total' current and voltage of a diode and will be elaborated in subsequent slides.

## Diode – Modeling the Diode - Large-Signal Model

### Work Example - Using Constant-Voltage-Drop Model (for DC Analysis)

Determine the current  $I_D$  and voltage  $V_D$  of the circuit shown below for  $V_{DD} = 5\text{ V}$  and  $R = 1\text{ k}\Omega$ . It is given that the diode has a current of 1 mA at a voltage of 0.6 V and that its voltage drop changes by 0.1 V for every decade change in current.

- Since  $V_{DD} = 5\text{ V}$ , diode operates in substantial forward bias


$\Rightarrow V_D = V_{D0} \approx 0.7\text{ V}$  (using the Constant-Voltage-Drop Model)

$$I_D = \frac{V_{DD} - V_D}{R} \approx \frac{5 - 0.7}{1\text{k}} = 4.3\text{ mA (by means of KVL equation)}$$


- Errors incurred in comparison to results obtained using iterative method:

- $I_D$ : 4.3 mA versus 4.3369 mA  $\Rightarrow$  -0.85% error
- $V_D$ : 0.7 V versus 0.6631 V  $\Rightarrow$  +5.56% error

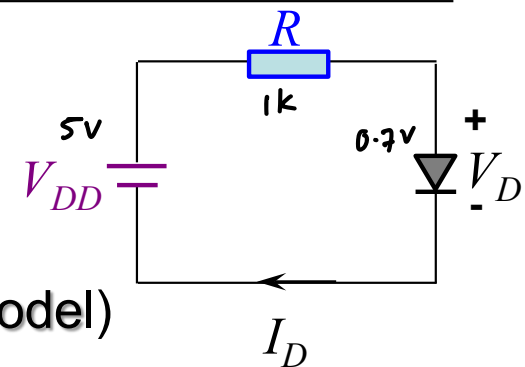- Analysis is much easier using the constant-voltage-drop model for diode! At the expense of small error.




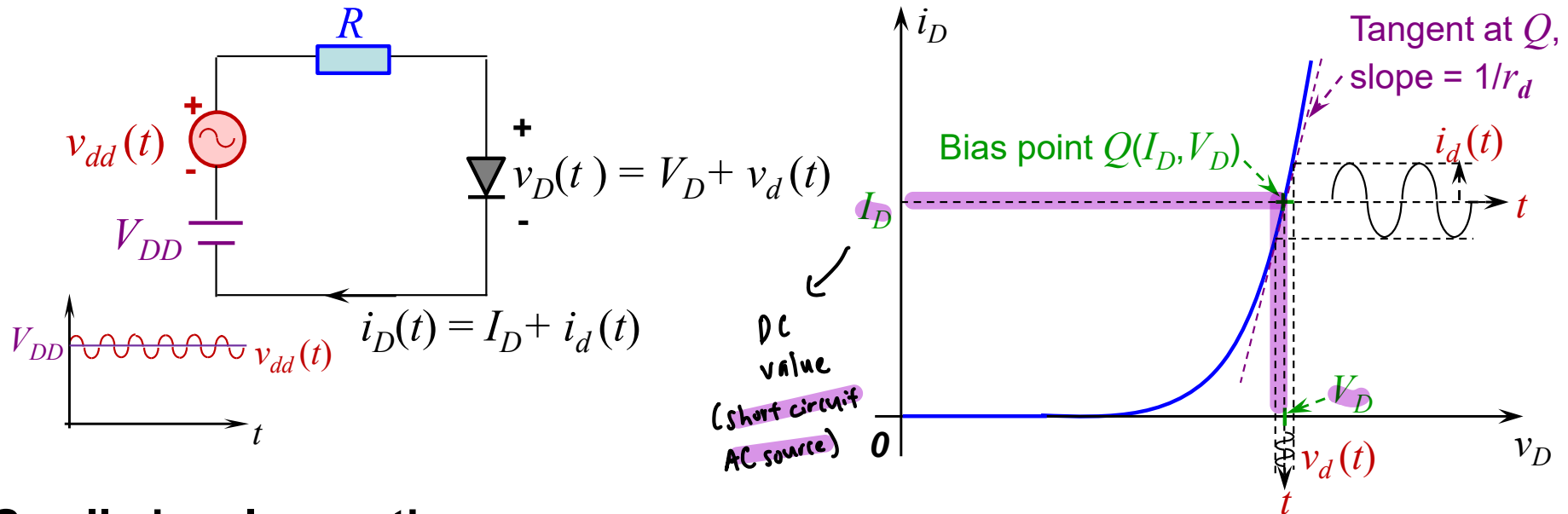
# Diode – Modeling the Diode - Small-Signal Model



## Small-signal operation

- ❑ There are circuits with time varying signal in addition to the dc supply ( $V_{DD}$ ), as shown in the circuit above, where  $v_{dd}(t)$  is an ac signal with a small amplitude. The circuit analysis is complicated owing to the non-linear nature of the diode.
  - ❑ Concept of **small-signal operation**: a small amplitude time varying signal, such as a small ac signal,  $v_{dd}(t)$ , can be considered as a small add-on to the dc supply,  $V_{DD}$ . Analysis of circuit can then be divided into two parts:
    - dc analysis – consider only the effect of dc supply,  $V_{DD}$ .
    - ac (small signal) analysis – consider only the effect of small ac signal,  $v_{dd}(t)$ .
- The solutions are added together using superposition to give the total effect.

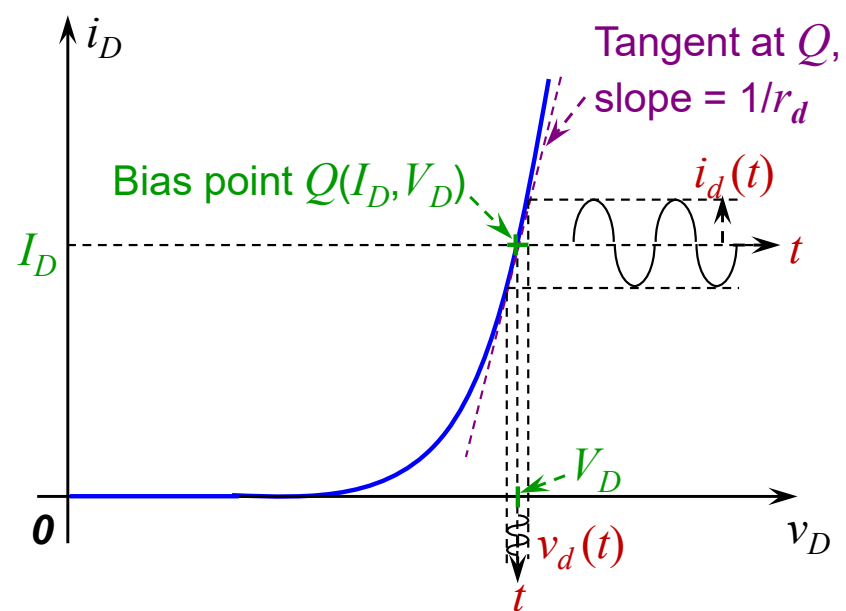
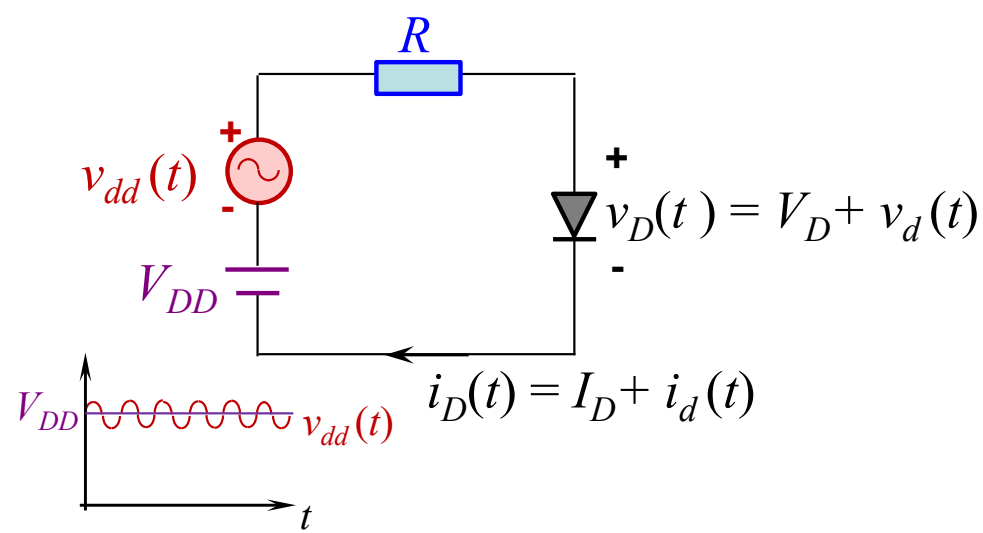
# Diode – Modeling the Diode (dc and ac symbols)



## Notations for dc and ac values (examples)

- ☐ **dc current:**  
Capital Symbol  $\nearrow I_D \nwarrow$  Capital subscript
- ☐ **ac current:**  
Lower case symbol  $\nearrow i_d \nwarrow$  Lower case subscript
- ☐ **Total current:**  
Lower case symbol  $\nearrow i_D = I_D + i_d \nwarrow$  Capital subscript

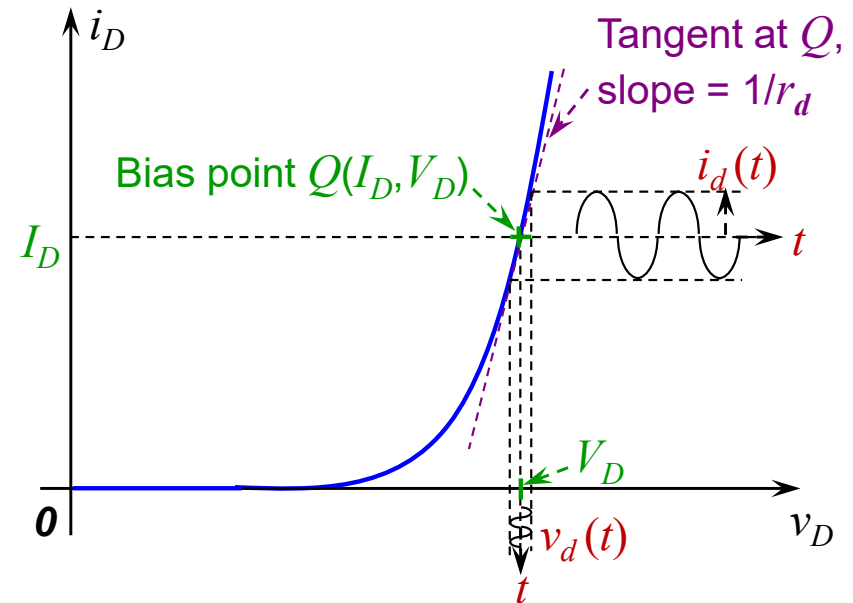
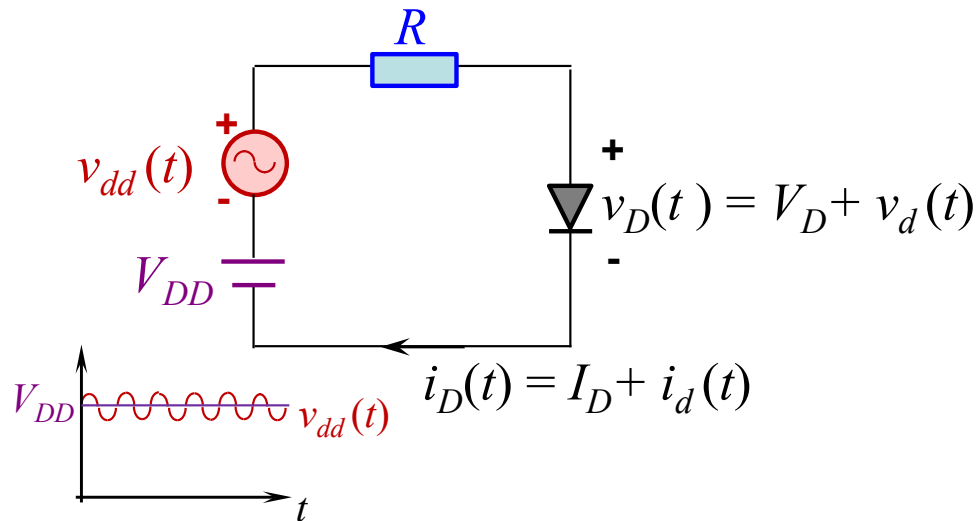
# Diode – Modeling the Diode - Small-Signal Model



## Small-signal operation AC signal

- ❑ **dc analysis:** The dc source,  $V_{DD}$ , is used to bias the diode to operate at a point on its forward  $IV$  characteristic,  $Q(I_D, V_D)$ , known as the **bias point**, around which the diode small ac signals,  $v_d(t)$  and  $i_d(t)$ , operate.
  - The dc bias point  $Q(I_D, V_D)$  can first be determined using the large-signal model, and in the **absence** of the small-signal ac source,  $v_{dd}(t)$ .
- ❑ **ac (small-signal) analysis:** How do we analyze the diode small-signal operation around the bias point,  $Q(I_D, V_D)$ ?
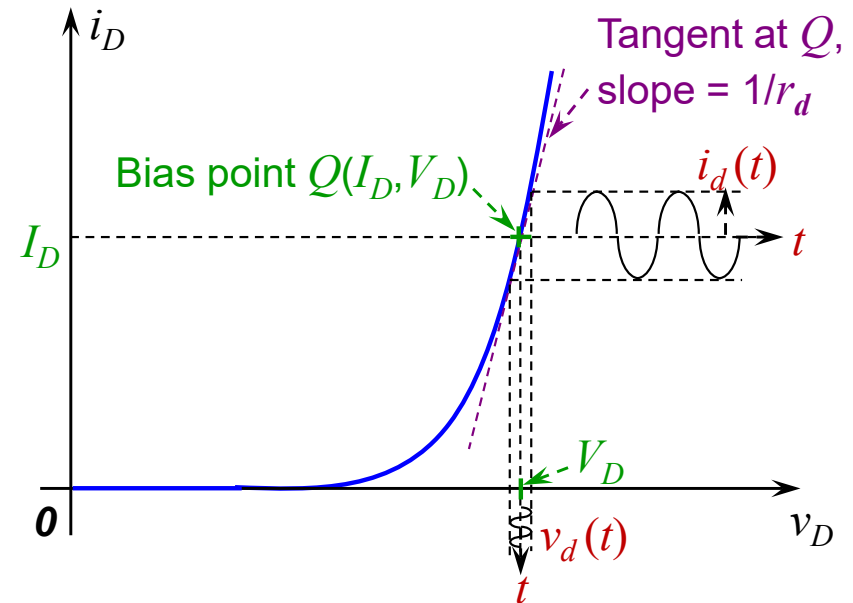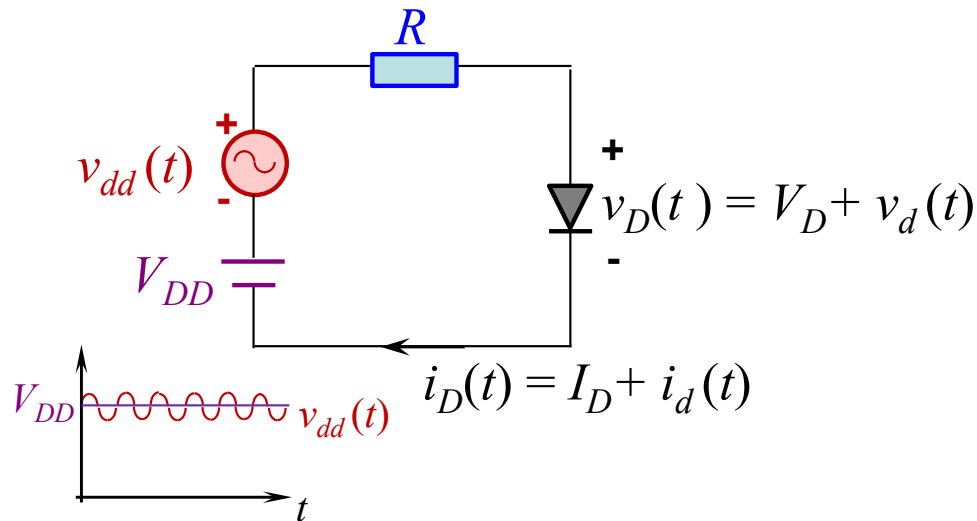
# Diode – Modeling the Diode - Small-Signal Model



## Small-signal operation

□ In the presence of  $V_{DD}$  and  $v_{dd}(t)$ , the **total** instantaneous diode voltage and current,  $v_D(t)$  and  $i_D(t)$ , are plotted above and given as follows -

- $v_D(t) = V_D + v_d(t)$   $\rightarrow$  DC + AC signal (2.7)



- $i_D(t) = I_D + i_d(t)$  (2.8)

□  $V_D$  and  $I_D$  are the diode dc bias voltage and current, respectively. They are the values **without** the small-signal ac source  $v_{dd}(t)$  and are related as follows –

- $I_D \approx I_S e^{\frac{V_D}{nV_T}} \rightarrow \text{pg 16}$  (2.9)


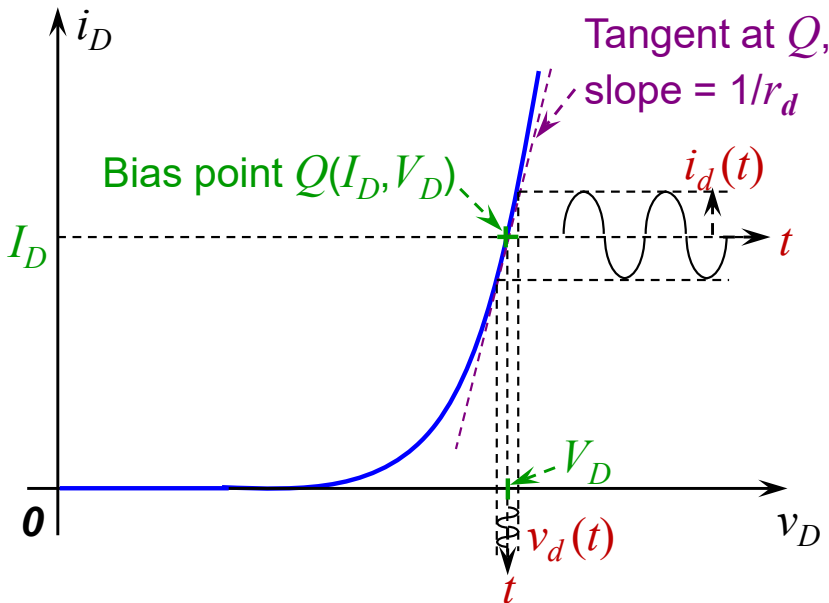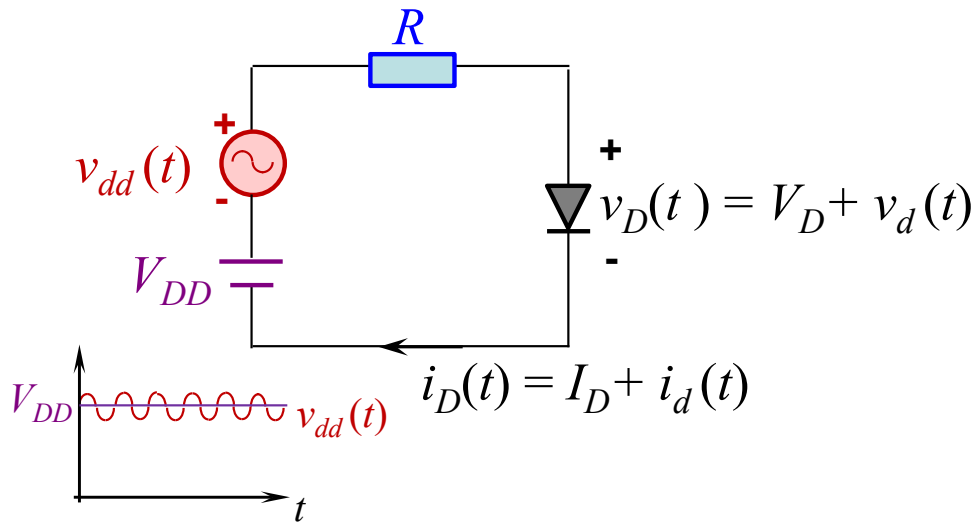
# Diode – Modeling the Diode - Small-Signal Model



## Small-signal operation

□ With small-signal source  $v_{dd}(t)$  applied, the total instantaneous current,  $i_D(t)$ , is



$$\blacksquare \quad i_D(t) = I_S e^{\frac{v_D(t)}{nV_T}} = I_S e^{\frac{V_D + v_d(t)}{nV_T}} = I_S e^{\frac{V_D}{nV_T}} e^{\frac{v_d(t)}{nV_T}} = I_D e^{\frac{v_d(t)}{nV_T}} \quad (2.10)$$

□ Since  $v_{dd}(t)$  is a small-signal source,  $v_d(t)$  is expected to be small, known as the small-signal voltage of the diode; and for  $v_d(t) \ll nV_T$ ,  $\xrightarrow{\text{much smaller}}$

$$\blacksquare \quad i_D(t) = I_D e^{\frac{v_d(t)}{nV_T}} \approx I_D \left[ 1 + \frac{v_d(t)}{nV_T} \right] = I_D + \frac{I_D}{nV_T} v_d(t) \quad (2.11)$$

• Note:  $e^x \approx 1 + x$ , for  $x \ll 1$ .  $i_D(t)$
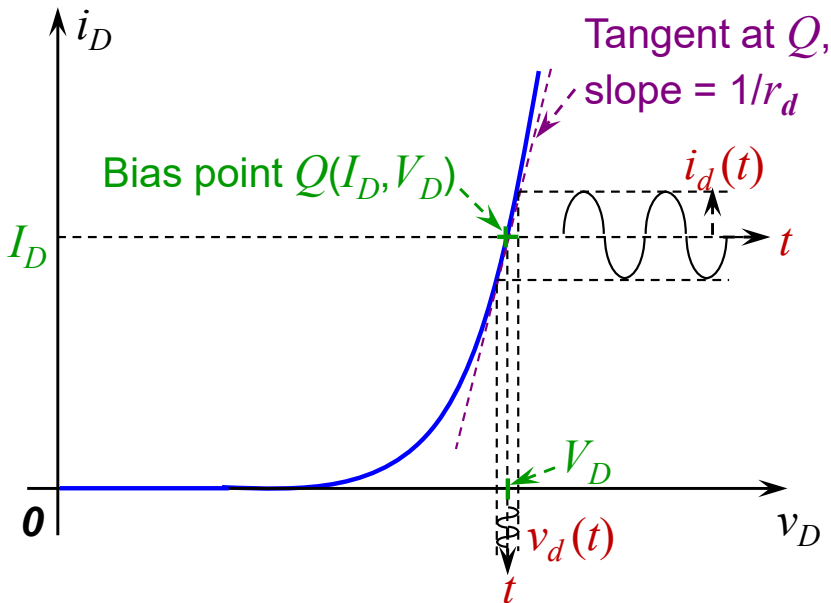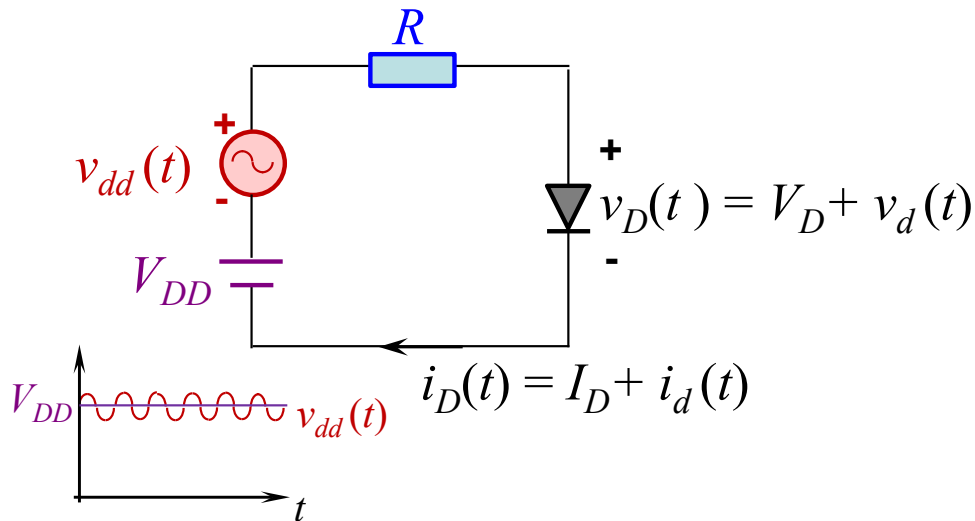
# Diode – Modeling the Diode - Small-Signal Model



## Small-signal operation

- ❑ From equation (2.11) - for small  $v_{dd}(t)$ , the total instantaneous current,  $i_D(t)$ , is the **sum (superposition)** of two components: a dc  $I_D$ , and an ac  $\frac{I_D}{nV_T} v_d(t)$ .
- ❑ The total instantaneous diode current  $i_D(t)$  is also given by equation (2.8), hence the small-signal current of the diode,  $i_d(t)$ , is given by


■  $i_d(t) = \frac{I_D}{nV_T} v_d(t) = \frac{1}{r_d} v_d(t)$  (2.12)

■  $r_d = \frac{nV_T}{I_D} \rightarrow \text{constant}$  (2.13)

*\*\*\**  $r_d$  (constant voltage drop model)

- ❑  $r_d$  has the dimension of resistance and is called the **diode small-signal resistance**.  
(N.B.  $r_d$  is different from  $r_D$  in slide pn-26, a large-signal model parameter)
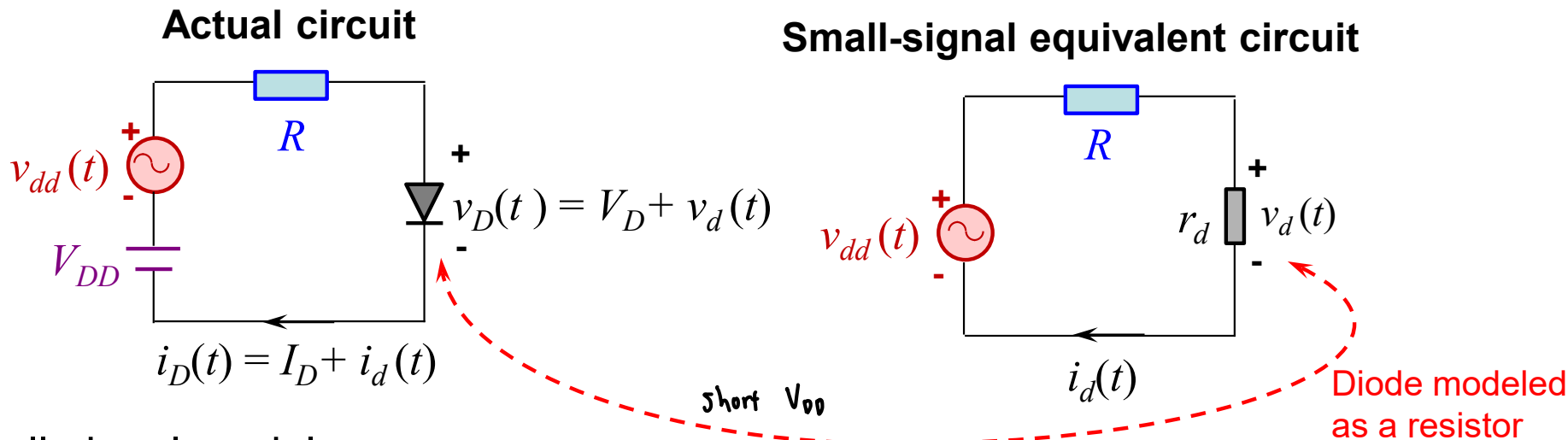
# Diode – Modeling the Diode - Small Signal Model



## Small-signal model

❑ From equation (2.12) - diode small-signal current,  $i_d(t)$ , is **directly** and **linearly** related to its **small-signal voltage**,  $v_d(t)$ , via  $r_d$  (similar to a resistor) -

▪ 
$$i_d(t) = \frac{I_D}{nV_T} v_d(t) = \frac{1}{r_d} v_d(t) \tag{2.12}$$



❑ For small-signal operation (around a dc bias point), the diode can be replaced (or modeled) by a **resistor**,  $r_d$ , as shown in the circuit on the right above. There is no need for detailed calculation with time and the dc source,  $V_{DD}$ , is replaced by a short circuit (known as ac short).

▪ Diode small-signal current can be determined using KVL: 
$$i_d(t) = \frac{v_{dd}(t)}{R+r_d}$$
  
\*\*\* need to find DC current

❑ The **bias point**  $I_D$  is needed to find  $r_d$ , as seen in equation (2.13):  $r_d = \frac{nV_T}{I_D}$ .

# Diode – Modeling the Diode - Small Signal Model

## Small-signal equivalent circuit

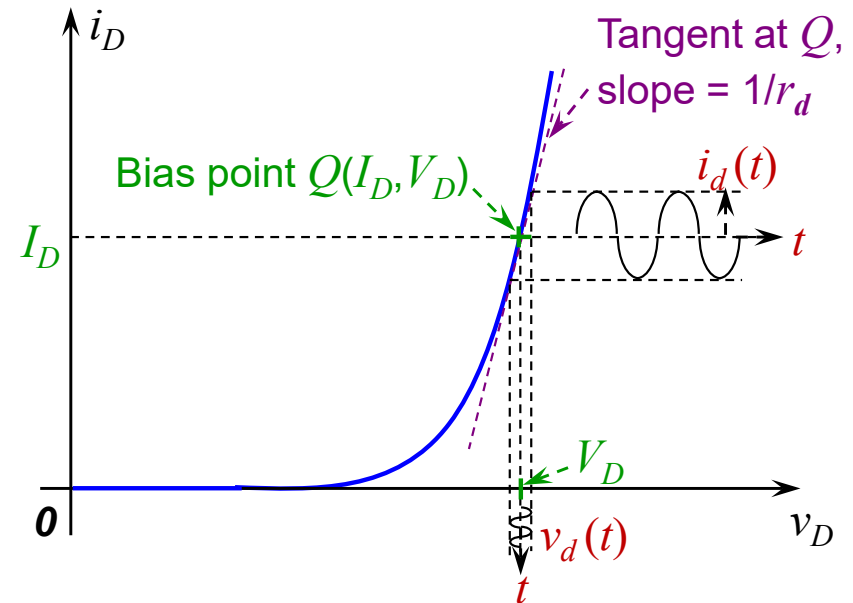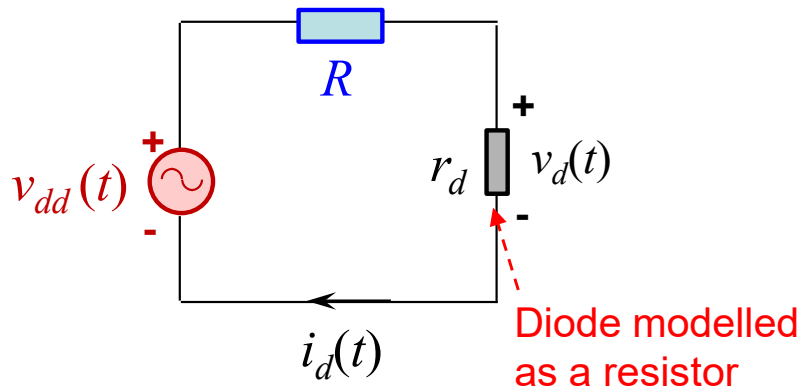

## Small signal model

- It has been seen that small-signal analysis can be performed **separately** from dc analysis with the diode modelled as a linear component **resistor**,  $r_d$ , and the dc source,  $V_{DD}$ , replaced by a short circuit.
- From above  $IV$  characteristic - the **slope** at the dc bias point  $Q(I_D, V_D)$  gives approximately the **inverse** of diode small-signal resistance,  $r_d$  -

$$\frac{di_D}{dv_D} \bigg|_{v_D=V_D} = \frac{1}{r_d} = \frac{i_d}{v_d} = \frac{I_D}{nV_T} \quad (2.14)$$

- $r_d$  is also known as the diode **incremental resistance**.
- In developing the small-signal model of diode (non-linear), we have a **linear** relationship between its small-signal voltage,  $v_d$ , and small-signal current,  $i_d$ .

## ***Diode (Semiconductor pn-Junction)***

---


### **Diode (Semiconductor pn-Junction)**

1. Introduction
2. Operation Regions: Forward-Bias, Reverse-Bias, and Breakdown
3. Current-Voltage Characteristic
4. Modeling the Diode
5. The Diode Circuit(s): Rectifier and Voltage Regulator
6. Charge Stored and Capacitive Effect

### **Reference**

- A.D. Sedra & K.C. Smith, “Microelectronic Circuits – Theory and Application”, 5<sup>th</sup> Edition (International Version), Oxford University Press, Chapter 2.

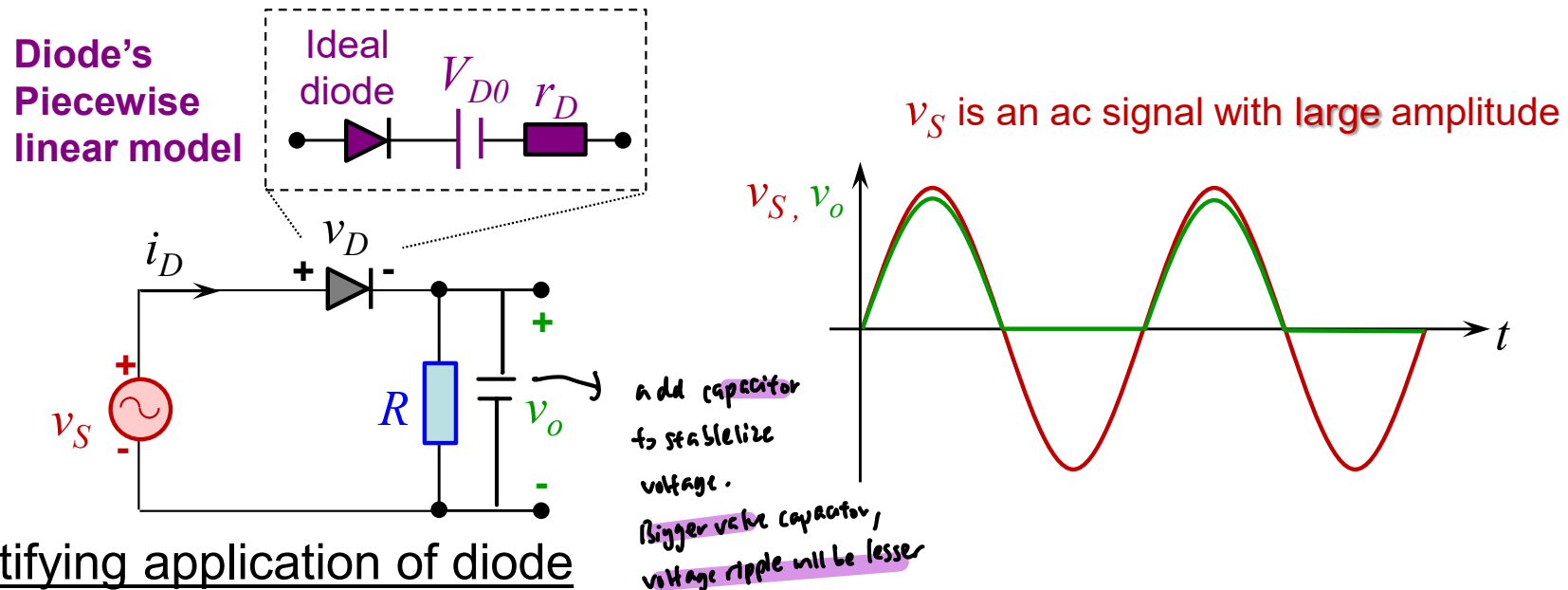
## Diode – Diode Circuit(s): Half-Wave Rectifier



### Rectifying application of diode

- ❑ During the **positive** half-cycles of  $v_S$ , current flows through the diode in the **forward** direction, hence  $v_o \cong v_S - V_{D0}$  ( $\gg i_D r_D$ ) where AC source amplitude is  $v_S$ .
- ❑ During the **negative** half-cycles of  $v_S$ , the diode does not conduct, thus  $v_o = 0$ .
- ❑ Although  $v_S$  alternates in polarity and has a **zero average value**,  $v_o$  is **unipolar / unidirectional** and has a **finite average value** or a **dc component**.
- ❑ Above circuit is known as a **half-wave rectifier** as it utilizes alternate half-cycles of input sinusoidal AC source  $v_S$ .


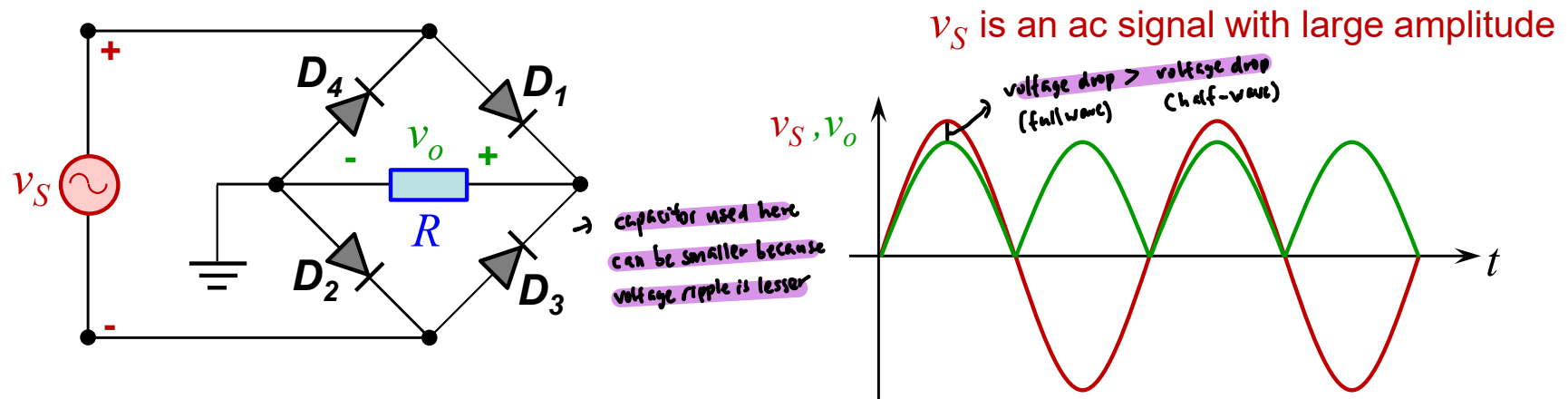
## Diode – Diode Circuit(s): Full-Wave Rectifier



### Full-wave bridge rectifier

- ❑ Full-wave rectifier utilizes both positive and negative half-cycles of input signal.
- ❑ Four diodes connected in Wheatstone bridge configuration is used.
- ❑ During the positive half-cycles of  $v_S$ , current conducts through diode  $D_1$ , load resistor  $R$  and diode  $D_2$ . In the meantime,  $D_3$  and  $D_4$  are reverse biased.
- ❑ During the negative half-cycles of  $v_S$ , current conducts through diode  $D_3$ , load resistor  $R$  and diode  $D_4$ , while diode  $D_1$  and  $D_2$  are reverse biased.
- ❑ Note that -  $v_o \cong v_S - 2 \times V_{D0}$ .
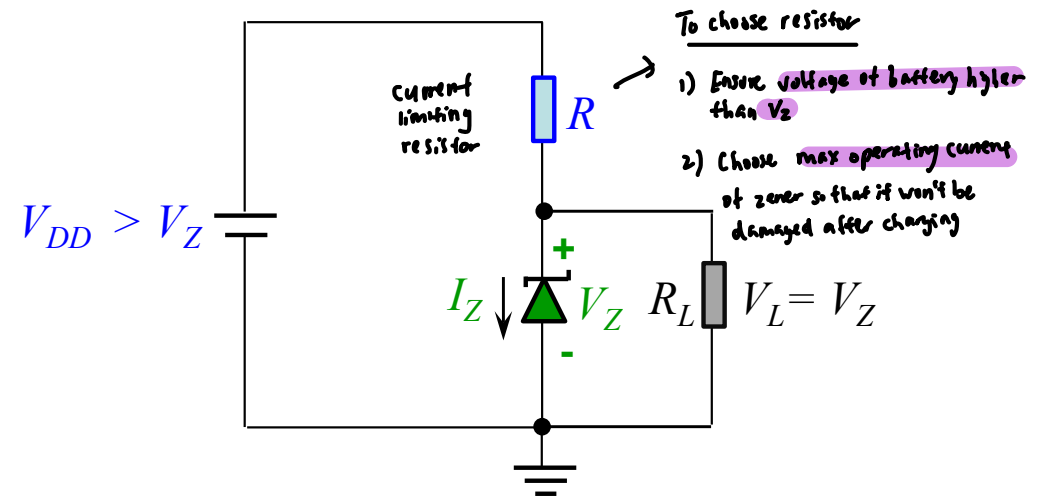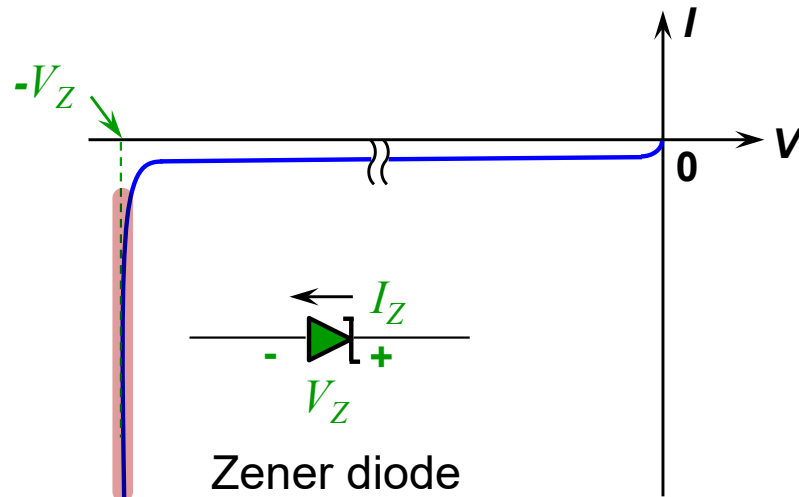
# Diode – Diode Circuit(s): Voltage Regulator



## Zener diode as a voltage reference

- ❑ Zener diodes are special diodes designed to operate in the breakdown region and they can be used in the design of voltage regulator (a circuit that provides a  $V_Z$  constant dc voltage between its terminals). Zener diodes are specified with  $V_Z$ , the breakdown voltage.
- ❑ In the above circuit, as long as  $V_{DD} > V_Z$  (meaning Zener diode operates in the breakdown region), the voltage across the load  $R_L$  is kept constant (or regulated) at  $V_L = V_Z$  by the Zener diode. Note that  $I_Z \neq 0$ .
- ❑ Virtually replaced by specially designed ICs that perform voltage regulation much more effectively and greater flexibility.



## ***Diode (Semiconductor pn-Junction)***

---

### **Diode (Semiconductor pn-Junction)**


1. Introduction
2. Operation Regions: Forward-Bias, Reverse-Bias, and Breakdown
3. Current-Voltage Characteristic
4. Modeling the Diode
5. The Diode Circuit(s): Rectifier and Voltage Regulator
6. Charge Stored and Capacitance Effect

### **Reference**

- ❑ A.D. Sedra & K.C. Smith, “Microelectronic Circuits – Theory and Application”, 5<sup>th</sup> Edition (International Version), Oxford University Press, Chapter 2.
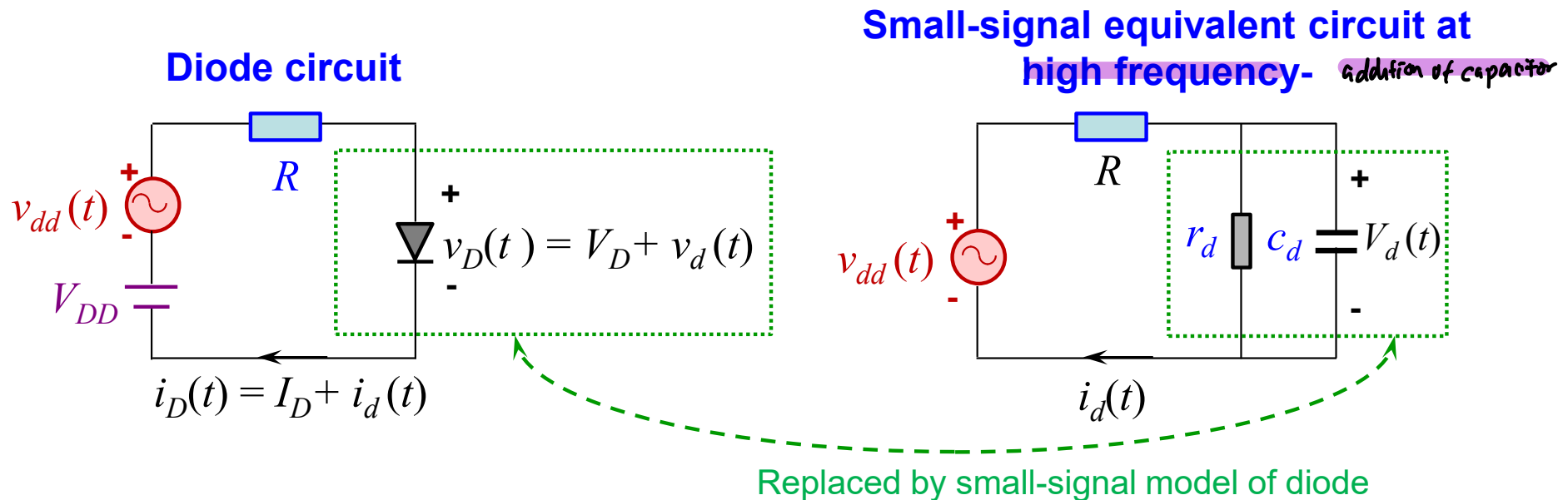
## Diode – Charge Stored and Capacitive Effect

- ❑ *pn*-junction exhibits **capacitive effect**, as there are charges stored within it and which is a function of the voltage applied across the *pn*-junction,  $v_D$ .
- ❑ As the charges stored do not vary linearly with  $v_D$ , unlike a parallel plate capacitor. Only small-signal capacitance ( $= dQ/dv_D$ ) can be defined for a *pn*-junction diode.
- ❑ At high-frequencies, **capacitive effect must be included in the small-signal model** of a *pn*-junction, as shown below -



## Diode – Topics Discussed

---

- ❑ Basics: Structure, semiconductor versus metal/insulator, n- versus p-semiconductor, doping, drift versus diffusion current
- ❑ Operation regions: forward bias (below cut-in and substantial forward bias), reverse bias (non-breakdown & breakdown)
- ❑ IV characteristic:  $I_D = I_S \left( e^{\frac{V_D}{nV_T}} - 1 \right)$
- ❑ Large signal model ( $r_D$ ,  $V_{D0}$ ) & dc large-signal analysis
- ❑ Small signal model ( $r_d = \frac{nV_T}{I_D}$ ) & ac small-signal analysis
- ❑ Rectifiers: half-wave versus full-wave rectifier
- ❑ Zener diode & voltage regulator
- ❑ Capacitive effect – to be included at high-frequency.

# Semiconductor pn-Junction Diodes Vs Vacuum Tube Diodes

## Semiconductor pn-Junction Diodes -



## Vacuum Diodes -

