

Mid-term Quiz AY2324S2

ⓘ This is a preview of the published version of the quiz

Started: 4 Apr at 21:41

Quiz instructions

This Quiz has 4 questions -


- 2 Multiple Answers/Choice questions. with negative marking for Multiple Answers questions.
- 2 Fill-in-Multiple-Blanks questions. For numerical answers that are not whole numbers and larger than unity, express them to 2 decimal places with roundup, e.g., fill in 12.34 for 12.3354, 12.30 for 12.3. For numerical answers that are smaller than unity, express them to 2 significant figures, e.g. fill in 0.067 for 0.0666.

The duration of the Quiz is 60 minutes and the total mark is 100.

⋮

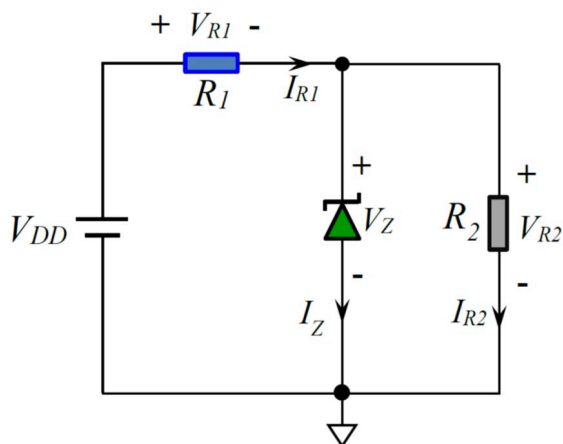Question 1 10 pts

A voltage regulator circuit is shown below, where V_Z is the breakdown voltage of the Zener diode. Which of the following statement(s) is(are) TRUE?



☐ For fixed values of V_{DD} , R_1 and V_Z , and $V_{DD} > V_Z$, the Zener current I_Z can be increased by decreasing the value of R_2 .


☐ If V_{R2} , obtained using the voltage divider method by assuming that the Zener diode is an open circuit, is smaller than V_Z , it can be implied that the Zener diode is operating in the breakdown region with V_{R2} clamped at V_Z .

☒ If the power rating of the Zener diode is 0.8 W, it is safe to operate the voltage regulator circuit continuously if $V_{DD} > V_Z = 5$ V and $I_Z = 100$ mA.

☒ For fixed values of V_{DD} , R_2 and V_Z , and $V_{DD} > V_Z$, the Zener current I_Z can be increased by decreasing the value of R_1 .

⋮

Question 2 10 pts

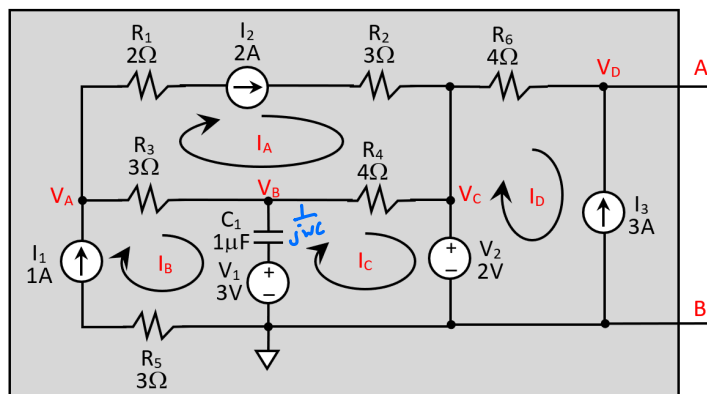

$I_A =$ [Select] 2 A, $I_B =$ [Select] 1 A, $I_C =$ [Select] 1 A, $I_D =$ [Select] -3 A.

$V_C =$ [Select] 2 V, $V_B =$ [Select] -2 V, $V_A =$ [Select] -5 V, $V_D =$ [Select] 14 V.


(Manually marked)

The whole network can be transformed into Thevenin Equivalent with:

$V_{THV} =$ [Select] **14** V , $R_{THV} =$ [Select] **4** Ω

⋮

Question 3 40 pts

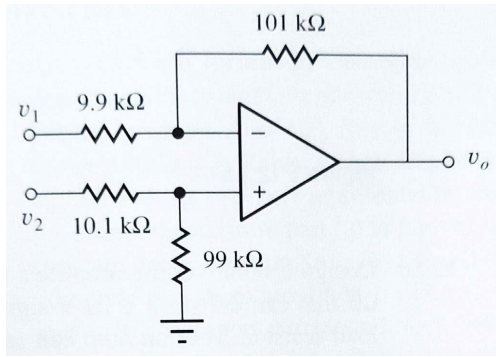


The input voltages, v_1 and v_2 , in the opamp amplifier circuit shown above are given as follows:

$$v_1 = 10 \sin(120\pi t) + 0.25 \sin(5000\pi t)$$

$$v_2 = 10 \sin(120\pi t) - 0.25 \sin(5000\pi t)$$

Common-mode differential/2

Assume that the opamp is ideal.

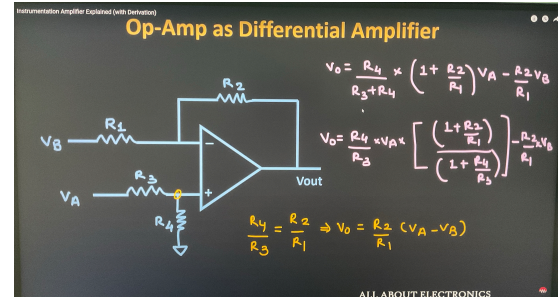

(a) Applying ideal opamp analysis, an expression for the output voltage v_o in terms of the input voltages, v_1 and v_2 , is found to be:

$$v_o = -10.202 v_1 + 10.165 v_2$$

$$a) \quad v_o = \left(-\frac{101k}{9.9k}\right) v_1 + \left(\frac{99k}{10.1k+99k}\right) \times \left(1 + \frac{101k}{9.9k}\right) v_2$$

$$= -10.202 v_1 + 10.165 v_2 //$$

(b) From the given input voltages, v_1 and v_2 above, the differential-mode input voltage v_{id} is:

$$v_{id} = 0.5 \sin(5000 \pi t)$$

$$\text{(or) } -0.5$$

$$v_{id} = v_1 - v_2 \text{ (or) } v_2 - v_1$$

(c) From the given input voltages, v_1 and v_2 above, the common-mode input voltage v_{icm} is:

$$v_{icm} = 10 \sin(120 \pi t)$$

$$v_{icm} = (v_1 + v_2) / 2$$

$$v_o = -0.37 \sin(120\pi t) - 5.09 \sin(5000\pi t)$$

$$-10.202 (10 \sin(120\pi t) + 0.25 \sin(5000\pi t)) + 10.165 (10 \sin(120\pi t) - 0.25 \sin(5000\pi t))$$

$$= -102.02 \sin(120\pi t) - 2.5505 \sin(5000\pi t) + 101.65 \sin(120\pi t) - 2.54125 \sin(5000\pi t)$$

$$= -0.37 \sin(120\pi t) - 5.091 \sin(5000\pi t)$$

(d) From the results in parts (a) and (b) above, the differential-mode gain A_{OL} is calculated to be -10.18 (or) 10.18

$$A_{OL} = \frac{V_{od}}{V_{id}} = \frac{-5.09}{-0.5}$$

$$A_{OL} = -5.09 / 0.5 \text{ (or) } -5.09 / (-0.5)$$

(e) From the results in parts (a) and (c) above, the differential-mode gain, the common-mode gain A_{CM} is calculated to be -0.037 (or) 0.037

$$A_{CM} = \frac{V_{o,CM}}{V_{i,CM}} = \frac{-0.37}{10}$$

$$A_{CM} = -0.37 / 10$$


(f) From the results in parts (d) and (e) above, the common-mode rejection ratio (CMRR) is calculated to be 48.8 dB.

$$CMRR = 20 \log \left(\frac{A_{OL}}{A_{CM}} \right) = 20 \log \left(\frac{10.18}{0.037} \right)$$

$$= 48.79 \text{ dB}$$

⋮

Question 4 40 pts

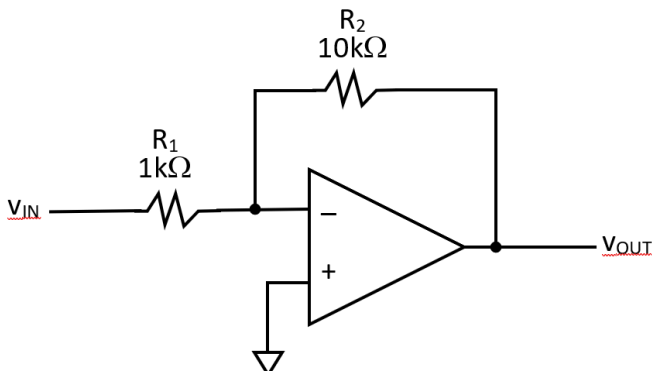

The opamp has GBW of 1 MHz, slew rate of $0.5 \text{ V}/\mu\text{s}$, $v_n = 100 \text{ nV}/\sqrt{\text{Hz}}$.

- 1) The closed-loop 3dB bandwidth of the inverting amplifier shown above is **90.91** kHz. $f_{3dB,CL} = GBW \times \frac{R_1}{R_1 + R_2} = 1M \times \frac{1k}{1k + 10k} = 90.911k$
- 2) When v_{IN} is $0.1 \times \sin(2\pi \times 50k \times t)$, the v_{OUT} will be amplified to peak amplitude of **1 or -1** V with frequency of 50 kHz without any issue. \rightarrow inverting with gain: 10 $(-\frac{R_2}{R_1})$
- 3) The resulting rms output noise due to opamp for this inverting amplifier would be **415.7** μ V. $V_{out,n} = \sqrt{(V_n)^2 \times f_{3dB} \times \frac{\pi}{2}} \times (1 + \frac{R_2}{R_1}) = 415.7 \mu V$
- 4) If the opamp is slew rate limited when the output has peak amplitude of 1V, the maximum frequency the inverting amplifier can handle is **79.58** kHz. $2\pi f \times 1 < 0.5V/\mu s$
kHz. $f < 79.57 kHz$
- 5) If the opamp is slew rate limited with the maximum allowable frequency being 50 kHz, the output peak amplitude allowable for v_{OUT} would be **1.59** V, and the input peak amplitude allowable for v_{IN} would be **159.15** mV. $V_{in} = \frac{V_{out}}{gain} = \frac{1.59}{10} = 159.15 mV$
 $2\pi(50k) \times V_p < 0.5V/\mu s$
 $V_p < 1.59V$
- 6) The output peak amplitude is 1V. In order for the inverting amplifier to have identical maximum operating frequency determined by both the GBW and slew rate, the resulting $R_1/(R_1+R_2)$ ratio should be **0.0796**. Hence, R_1 should be 1 k Ω and R_2 should be **11.57** k Ω .

Saved at 21:42

Submit quiz

$$2\pi f \times 1 < 0.5V/\mu s$$

$$f < 79.57 kHz$$

Since they want identical max operating frequency,

$$79.58k = 1M \times \frac{R_1}{R_1 + R_2}$$

$$\frac{R_1}{R_1 + R_2} = 0.07958$$

$$\approx 0.0796$$

$$\frac{1k}{1k + R_2} \approx 0.0796$$

$$1k = 0.0796(1k) + 0.0796 R_2$$

$$0.0796 R_2 = 920.4$$

$$R_2 = 11.56 k\Omega$$