

NATIONAL UNIVERSITY OF SINGAPORE
Department of Electrical and Computer Engineering

EE2027 Electronic Circuits
Tutorial 4: Solution

- Unless otherwise stated, you may assume temperature, $T = 300$ K; thermal voltage, $V_T = 0.025$ V and make use of the equations given in the lecture notes directly, without having to derive them.
- All the symbols are as defined in the lecture notes.

Homework 4:

Homework 4 is Questions 5 of Tutorial 4. You will need to submit a softcopy of your handwritten homework to Canvas>Homework Submissions>HW4 half an hour after class (i.e., latest by 4:30 pm) on Tuesday, 16 April 2024. Failing to do that will mean zero mark for homework.

The softcopy submission of your homework must be in PDF format (in a single file) and named using the convention “<Your Name>_HW4”.

Homework questions will not be discussed in class.

Q1. Figure Q1 shows a single-stage BJT amplifier circuit. The BJT Q_1 has $\beta = 100$.

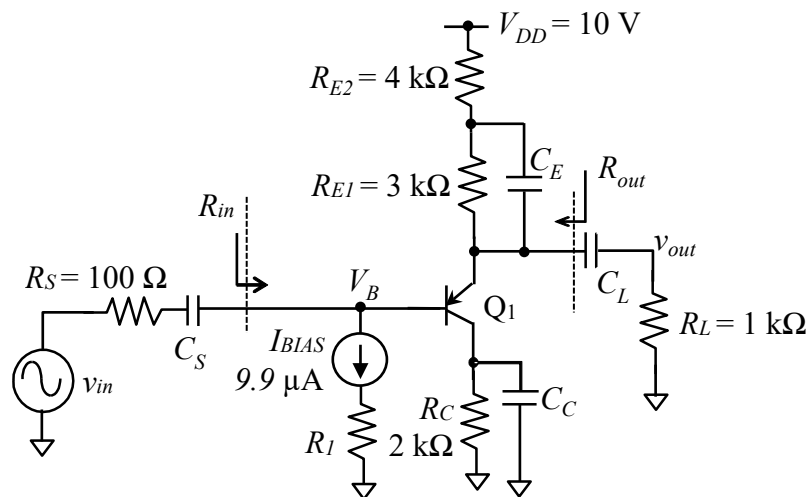


Fig. Q1

- Find the DC base voltage of Q_1 (V_B) and R_I . Verify any assumption you make in the calculation. (Note: The voltage drop across the DC current source, I_{BIAS} , has been designed to be approximately 0 V.) [Ans: $V_B = 2.3$ V, $R_I = 232$ kΩ]
- Draw the small-signal equivalent of the circuit in Fig. Q1 and identify the amplifier configuration.

- (c) Calculate the two-port network parameters of the amplifier, and draw the equivalent two-port network of the amplifier. Ans: [$R_{in} \approx 82.4 \text{ k}\Omega$, $R_{out} \approx 25.7 \text{ }\Omega$]

- (d) Estimate the voltage gain, v_{out}/v_{in} . [Ans: $v_{out}/v_{in} \approx 0.97$]

Q1. Solution:

BJT Q₁ is of the pnp type.

(a) DC analysis:

Assume BJT Q₁ is working in *forward active operation*, $V_{EB} \approx 0.7 \text{ V}$.

$$I_B = I_{BIAS} = 9.9 \text{ }\mu\text{A}; I_E = (\beta + 1)I_B = 1 \text{ mA}.$$

$$V_E = V_{DD} - I_E R_E = 10 - 7 = 3 \text{ V}.$$

$$V_B = V_E - 0.7 = 2.3 \text{ V}.$$


$$R_I = V_B / I_B = 232 \text{ k}\Omega \text{ [Voltage drop across DC current source, } I_{BIAS}, \approx 0]$$

$$V_C = I_C \times R_C = 990 \text{ }\mu\text{A} \times 2 \text{ k}\Omega = 1.98 \text{ V}.$$

$$V_{BC} = V_B - V_C = 2.3 - 1.98 = 0.32 \text{ V} > 0.$$


Check:

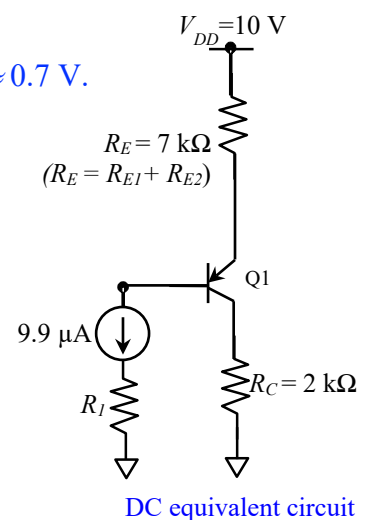Base-emitter junction is in forward bias. Base-collector junction is in reverse bias. BJT Q₁ is working in forward active operation.



(b) The amplifier configuration is Common Collector (CC).

The small-signal equivalent circuit is:

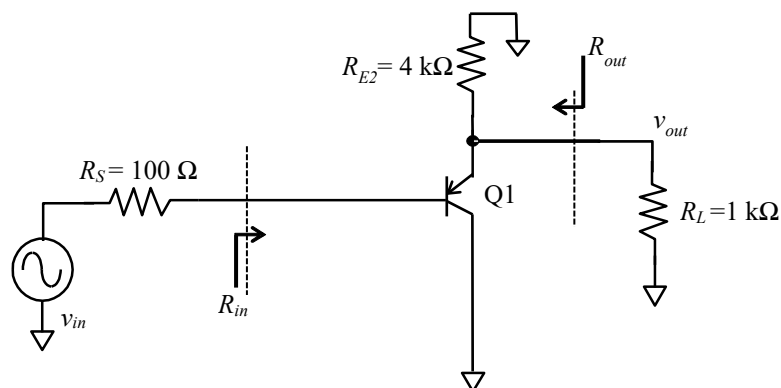

BJT Q₁ can also be replaced by its small-signal model in the above figure.

(c)

$$g_{m,Q1} = I_C / V_T = 0.99\text{mA} / 0.025 = 39.6 \text{ mA/V (or } 40 \text{ mA/V assuming } I_C \approx I_E)$$

$$r_{\pi,Q1} = \beta / g_{m,Q1} = 100 / 39.6\text{mA/V} = 2.52 \text{ k}\Omega \text{ (or } 2.5 \text{ k}\Omega \text{ assuming } I_C \approx I_E)$$

$$r_{o,Q1} = V_A / I_C = \infty \text{ (} V_A \text{ is not given, by default, } V_A = \infty)$$

With the help of Table 1, Configuration A –

$$R_{in} = [r_{\pi,Q1}(1 + g_{m,Q1}\{R_{E2} // R_L\})] = [2.52\text{k} \times (1 + 39.6\text{mA/V} \times \{4\text{k} // 1\text{k}\})] = 82.4 \text{ k}\Omega$$


With the help of Table 1, Configuration C –

$$R_{out} = R_{E2} // \left[(R_S + r_{\pi,Q1}) / (1 + \beta_{Q1}) \right] // r_{o,Q1} = 4\text{k} // [(0.1\text{k} + 2.52\text{k}) / (1 + 100)] // \infty = 25.7 \text{ }\Omega$$

With the help of Table 3, Configuration C –

$$A_v = \frac{v_{out}}{v_i} = \left[\frac{g_{m,Q1}(R_{E2} // R_L)}{1 + g_{m,Q1}(R_{E2} // R_L)} \right] = \left[\frac{39.6\text{mA/V}(4\text{k} // 1\text{k})}{1 + 39.6\text{mA/V}(4\text{k} // 1\text{k})} \right] = 0.97$$

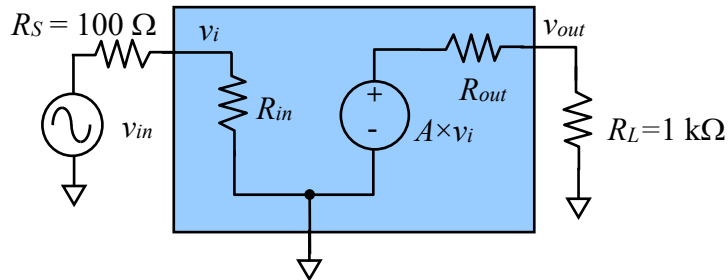The 2-port network of the amplifier (Voltage amplifier) is as follows -



Note: $A_v = \frac{v_{out}}{v_i}$ is not A in the 2-port network equivalent Voltage Amplifier (see figure above).

$$v_{out} = \frac{R_L}{R_L + R_{out}} \times A v_i$$

$$\Rightarrow A = \frac{v_{out}}{v_i} \times \frac{R_L + R_{out}}{R_L} = A_v \times \frac{R_L + R_{out}}{R_L} = 1.067$$

(d) Estimate the voltage gain v_{out} / v_{in} .

With the help of Table 3, configuration C –

$$\frac{v_{out}}{v_{in}} = \frac{v_i}{v_{in}} \times \frac{v_{out}}{v_i} = \frac{R_{in}}{R_{in} + R_S} \left\{ \frac{g_{m,Q1}(R_{E2} // R_L)}{1 + g_{m,Q1}(R_{E2} // R_L)} \right\} \approx \frac{82.4\text{k}}{0.1 + 82.4\text{k}} \times \frac{39.6\text{mA/V} \times (4\text{k} // 1\text{k})}{1 + 39.6\text{mA/V} \times (4\text{k} // 1\text{k})} = 0.97$$

- Q2. Consider the amplifier shown in Fig. Q2. The npn bipolar junction transistor has the following parameter values: $\beta = 100$, $V_A = 100$ V.

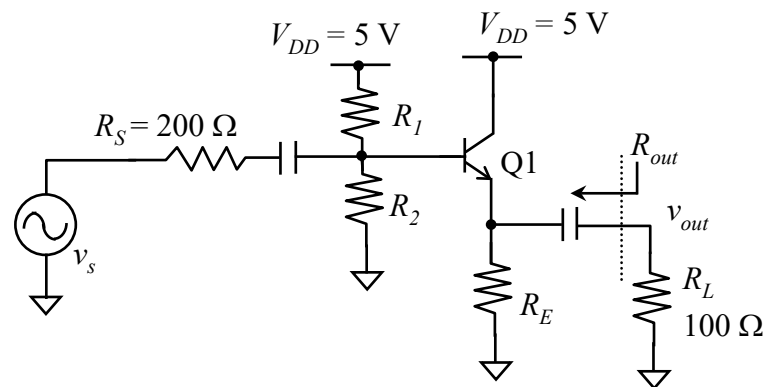


Fig. Q2

- For the maximum power transfer to load, R_L , what should R_{out} be?
[Ans: $R_{out} = 100 \Omega$]
- To have the desired R_{out} of part (a), what should the specified $g_{m,Q1}$ be? (You may need to make some assumption for resistors R_1 , R_2 and R_E)
[Ans: $g_{m,Q1} = 10 \text{ mA/V}$]
- What is the amplifier configuration? Sketch the equivalent 2-port network of the amplifier circuit in Fig. Q2.
- Set $R_1 = 100 \text{ k}\Omega$ and $R_E = 5 \text{ k}\Omega$, calculate R_2 to complete the design.
[Ans: $R_2 = 64 \text{ k}\Omega$]
- Calculate the input resistance of the amplifier, R_{in} .
[Ans: $R_{in} \approx 13.2 \text{ k}\Omega$]
- Calculate the voltage gain v_{out}/v_s .
[Ans: $v_{out}/v_s \approx 0.49$]

Q2. Solution:

- (a) For the maximum power transfer to load, R_L , R_{out} must be designed to have the same value as R_L , so $R_{out} = 100 \Omega$.

- (b) $R_{out} = R_E // R_X$, where R_X is the equivalent resistance looking into the emitter of Q_1 .

Resultant resistance connected to the base of Q_1 is $R_S // R_1 // R_2 \approx R_S$ (since $R_S = 200 \Omega$, which is small, we can assume $R_S \ll R_1, R_2$).


From Table 1, look into emitter, Configuration C –

$$R_X \approx \frac{R_S // R_1 // R_2}{\beta + 1} + \frac{1}{g_{m,Q1}} \approx \frac{1}{g_{m,Q1}} \quad [\text{if } R_S \text{ is small}]$$

To have the desired $R_{out} = 100 \Omega$, we can assume $R_E \gg \frac{1}{g_{m,Q1}} \Rightarrow R_{out} = R_E // R_X \approx$

$$\frac{1}{g_{m,Q1}} = 100 \Omega \Rightarrow g_{m,Q1} = 10 \text{ mA/V}$$

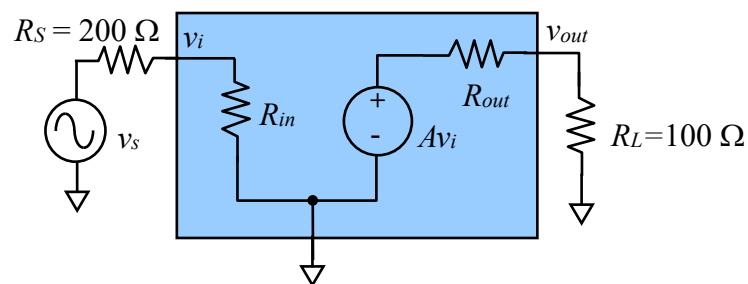- (c) The amplifier configuration is Common Collector (CC) and its equivalent 2-port network is as follows -



$$R_{out} = R_L \approx \frac{1}{g_{m,Q1}} = 100 \Omega$$

- (d) Need to find base voltage of BJT Q_1 .

Since $R_E = 5 \text{ k}\Omega \gg \frac{1}{g_{m,Q1}}$ [assumption made earlier in part (b) is valid], $R_{out} = 100 \Omega$,

then $g_{m,Q1} = 10 \text{ mA/V}$.

$$g_{m,Q1} = \frac{I_{C,Q1}}{V_T} \Rightarrow I_{C,Q1} = g_{m,Q1} V_T = 0.25 \text{ mA} \approx I_{E,Q1}$$

$$I_{E,Q1} = \frac{V_E}{R_E} \Rightarrow V_E = 1.25 \text{ V}$$

$$V_B = V_E + V_{BE} \approx V_E + 0.7 = 1.95 \text{ V}$$

Using the voltage divider method, base voltage of BJT Q₁ -

$$V_B = \frac{5R_2}{R_1 + R_2}, \text{ Since } R_1 = 100 \text{ k}\Omega, \text{ then } R_2 = 64 \text{ k}\Omega. [\text{Note: } R_1, R_2 \gg R_S = 200 \text{ }\Omega]$$

$$I_1 \approx I_2 = \frac{5}{100k + 64k} = 30 \mu\text{A} \gg I_B = 2.5 \mu\text{A} \Rightarrow \text{Voltage divider method is valid.}$$

(e)

$$g_{m,Q1} = 10 \text{ mA/V} \Rightarrow I_{C,Q1} = g_{m,Q1} V_T = 0.25 \text{ mA}$$

$$r_{o,Q1} = V_{A,Q1} / I_{C,Q1} = 400 \text{ k}\Omega$$

$$r_{\pi,Q1} = \beta_{Q1} / g_{m,Q1} = 10 \text{ k}\Omega$$

$$R_{out} \approx \frac{1}{g_{m,Q1}} = 100 \text{ }\Omega$$

With the help of Table 1, Configuration A –

$$\begin{aligned} R_{in} &= R_1 // R_2 // [r_{\pi,Q1} (1 + g_{m,Q1} \{R_E // R_L\})] \\ &= 100k // 64k // [10k \times (1 + 10m \times \{5k // 0.1k\})] = 13.2 \text{ k}\Omega \end{aligned}$$

(f) Calculate the voltage gain, v_{out} / v_s .

With the help of Table 3, configuration C –

$$\begin{aligned} A_v &= \frac{v_{out}}{v_s} = \frac{v_i}{v_s} \times \frac{v_{out}}{v_i} \\ &= \frac{R_{in}}{R_{in} + R_s} \left\{ \frac{g_{m,Q1} (R_E // R_L)}{1 + g_{m,Q1} (R_E // R_L)} \right\} \approx \frac{13.2}{0.2 + 13.2} \times \frac{10m \times 0.098k}{1 + 10m \times 0.098k} = 0.49 \end{aligned}$$

- Q3. Figure Q3 shows a single-stage amplifier with current mirror biasing. For the two p -channel MOSFETs, $V_{THP1} = V_{THP2} = -1$ V, $\lambda_{P1} = \lambda_{P2} = 0$, $K_{p,M1} = K_{p,M2} = 2 \text{ mA V}^{-2}$. For the pnp BJT, $\beta = 100$, $V_A = 100$ V.

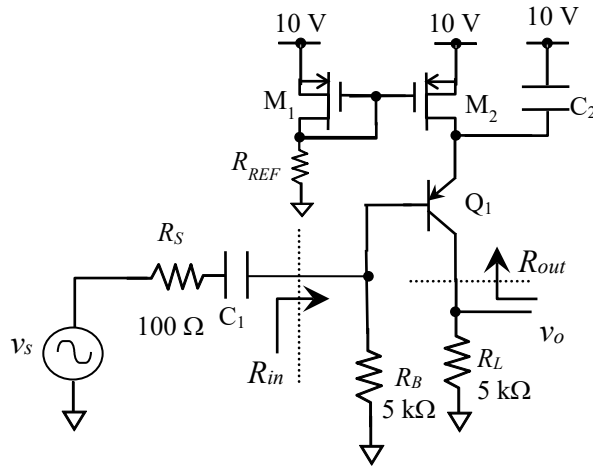


Fig. Q3

- Design R_{REF} such that $I_{D,M1} = 1$ mA. [Ans: $R_{REF} = 8.29 \text{ k}\Omega$]
- Calculate the small signal parameters of Q1, i.e., $g_{m,Q1}$, $r_{\pi,Q1}$ and $r_{o,Q1}$.
- Identify the configuration of the single-stage amplifier.
- Determine the parameters, G_m , R_{in} and R_{out} of the two-port network of the amplifier.
- Determine the gain v_o/v_s of the amplifier using the 2-port network parameters derived in part (d). [Ans: $v_o/v_s \approx -180$]

Q3. Solution:

- (a) Note: M_1 and M_2 form a current mirror current source and they do not provide amplification function.

$V_G = V_D$ for $M_1 \Rightarrow M_1$ in saturation operation.

$$V_S = 10 \text{ V}; I_{D,M1} = K_p (|V_{GS}| - |V_{THP}|)^2$$

$$1 \text{ mA} = 2 \text{ mA V}^{-2} (10 - 1 \text{ mA} \times R_{REF} - 1)^2$$

$$R_{REF} = 9 \pm 0.707 = 9.707 \text{ or } 8.293 \text{ k}\Omega$$

$$R_{REF} = 9.707 \text{ k}\Omega, V_G = 9.707 \text{ V}, |V_{GS}| = 0.293 \text{ V} < |V_{THP}|, \text{ invalid.}$$

$$\therefore R_{REF} = 8.293 \text{ k}\Omega$$

(b)

$$I_C \approx I_E = I_{D,M2} = I_{D,M1} = 1 \text{ mA}$$

$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ m}}{0.025} = 40 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{40 \text{ m}} = 2.5 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{100}{1 \text{ m}} = 100 \text{ k}\Omega$$

(c) The configuration of the single-stage amplifier is Common Emitter (CE).


(d) $G_m = g_m = 40 \text{ mA/V}$ (Table 3, Configuration A)

With the help of Table 1, Configuration A, with emitter shorted to ground

$$R_{in} = R_B // r_\pi = 5 \text{ k} // 2.5 \text{ k} = 1.67 \text{ k}\Omega$$

With the help of Table 1, Configuration B, with emitter shorted to ground

$$R_{out} = r_o = 100 \text{ k}\Omega$$

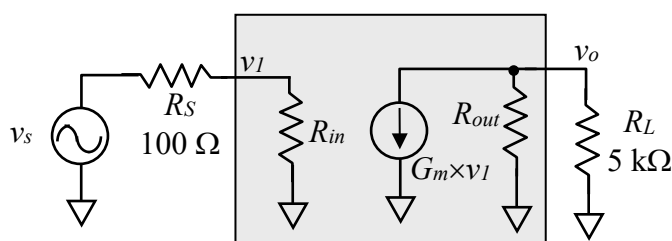(e) Determine the gain v_o/v_s of the amplifier using the 2-port network parameters derived in part (d).

$$A_V = \frac{v_o}{v_s} = \left(\frac{R_{in}}{R_S + R_{in}} \right) \times (-G_m) \times (R_{out} // R_L) = \frac{1.67 \text{ k}}{0.1 \text{ k} + 1.67 \text{ k}} \times (-40 \text{ m}) \times \frac{100 \text{ k} \times 5 \text{ k}}{100 \text{ k} + 5 \text{ k}} = -180$$

- Q4. Consider the amplifier shown in Fig. Q4. The transistor M_1 has $K_p = 500 \mu\text{A}/\text{V}^2$, $V_{THP} = -0.5 \text{ V}$ and $\lambda_p = 0.01 \text{ V}^{-1}$.

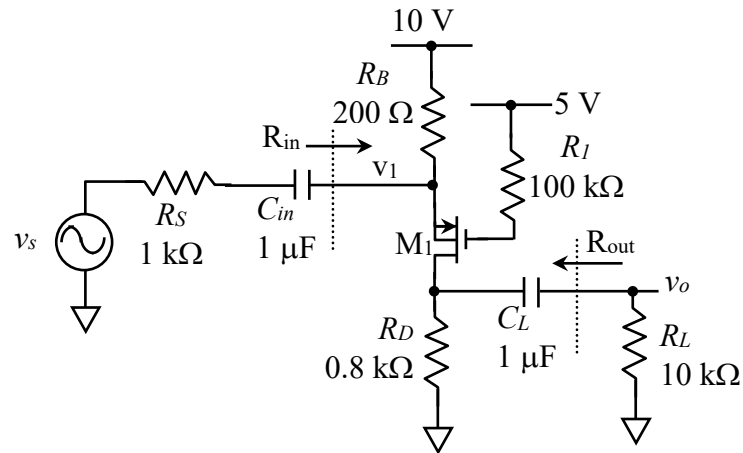


Fig. Q4

- What is the amplifier configuration?
- Determine the DC drain current of M_1 , $I_{D,M1}$ and verify the assumption used.
[Ans: $I_{D,M1} = 5.65 \text{ mA}$]
- What is the R_{in} for this amplifier?
[Ans: $R_{in} \approx 120 \Omega$]
- What is the R_{out} for this amplifier?
[Ans: $R_{out} \approx 0.8 \text{ k} \Omega$]
- Use the concept of two-port network and the important results derived in the lecture notes, determine the voltage gain of this amplifier.
[Ans: gain ≈ 0.27]

Q4. Solution:

MOSFET M_1 is of the p-channel type.

- (a) This amplifier configuration is **Common Gate (CG)**. Note that gate is effectively shorted to ground in AC operation as there is no current flowing through R_I ($i_g = 0$)
- (b) Determine DC drain current of M_1 , $I_{D,M1}$.

Assume M_1 is operating in saturation region -

$$V_G = 5 \text{ V (No Gate current } \Rightarrow V_G = 5 \text{ V)}$$

$$I_{D,M1} = K_p (|V_{GS}| - |V_{THP}|)^2 = K_p (V_S - 5 - 0.5)^2 = \frac{10 - V_S}{R_B} \text{ [Square law and Ohm's law]}$$

$$\Rightarrow 0.1V_S^2 - 0.1V_S - 6.975 = 0$$

$$V_S = \frac{0.1 \pm \sqrt{0.01 + 2.79}}{0.2} = 8.87 \text{ V or } -7.87 \text{ V}$$

$$V_S \text{ cannot be negative } \Rightarrow V_S = 8.87 \text{ V and } I_{D,M1} = 5.65 \text{ mA}$$

Note: In the above calculation of DC drain current, $I_{D,M1}$, we can assume negligible Channel Length Modulation Effect as λ_p is small [See Tutorial 3, Q4(c)].

$$|V_{DS}| = |10 - I_{D,M1}R_B - I_{D,M1}R_D| = |10 - 5.65\text{m} \times 0.2\text{k} - 5.65\text{m} \times 0.8\text{k}| = 4.35 \text{ V}$$


$$|V_{GS}| = |10 - I_{D,M1}R_B - 5| = |10 - 5.65\text{m} \times 0.2\text{k} - 5| = 3.87 \text{ V}$$

Check whether the assumption of saturation operation is correct:

$$|V_{DSsat}| = |V_{GS}| - |V_{THP}| = 3.87 - 0.5 = 3.37 \text{ V}$$

$$\Rightarrow |V_{DS}| > |V_{DSsat}|, \text{ hence } M_1 \text{ is in Saturation.}$$

(c)

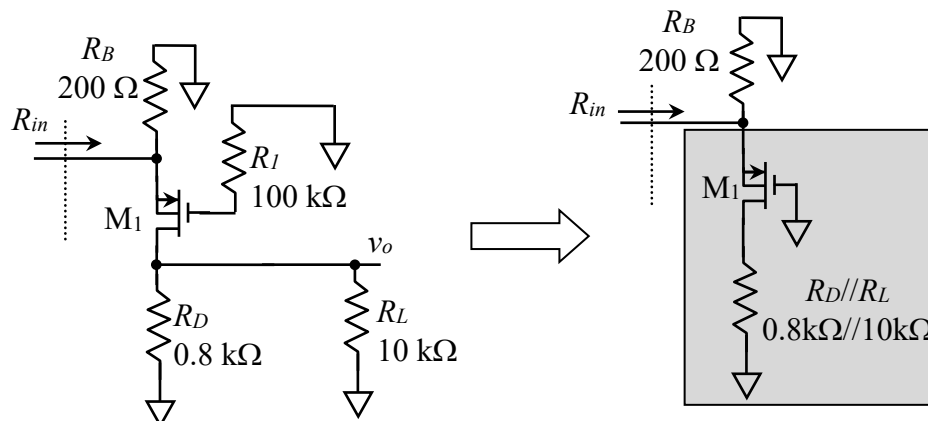


$$g_{m,M1} = 2\sqrt{K_P |I_{D,M1}|} = 2\sqrt{0.5\text{m} \times 5.65\text{m}} = 3.36\text{mA/V}$$

$$r_{o,M1} = \frac{1}{\lambda I_{D,M1}} = \frac{1}{0.01 \times 5.65\text{m}} = 17.7\text{k}\Omega$$

With the help of Table 2, Configuration D -

$$R_{in} = R_B // \left\{ \frac{1}{g_{m,M1}} \frac{r_{o,M1} + R_D // R_L}{r_{o,M1}} \right\} = 200 // 297 = 120\ \Omega$$


(d)

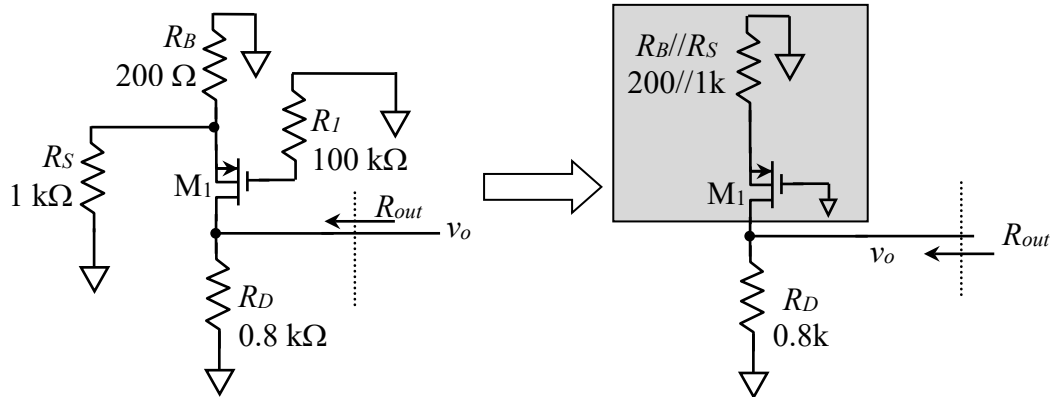

With the help of Table 2, Configuration B -

$$R_{out} = R_D // r_{o,M1} \{1 + g_{m,M1} (R_B // R_S)\} \approx 0.8\text{k}\Omega$$

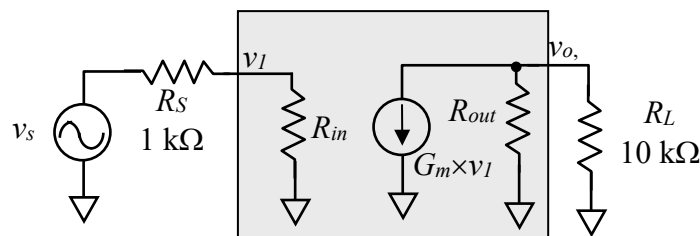(e) Common gate amplifier, $G_m = -g_{m,M1} = -3.36\text{mA/V}$ (Table 4, configuration B)



$$v_1 = \frac{R_{in}}{R_{in} + R_S} v_s = 0.107 v_s$$

$$v_o = -G_m v_1 (R_{out} // R_L) = 3.36\text{m} \times (0.8\text{k} // 10\text{k}) v_1 \approx 2.49 v_1 = 0.27 v_s$$

$$\frac{v_o}{v_s} = 0.27$$

- Q5. In the amplifier circuit shown in Fig. Q5, the BJT Q_1 has $\beta = 100$ and $V_A = 100$ V. The MOSFETs, M_1 and M_2 , are identical with $V_{TH} = -1.0$ V, $K_p = 2$ mA/V² and they do not experience Channel Length Modulation effect. The temperature is 300 K.

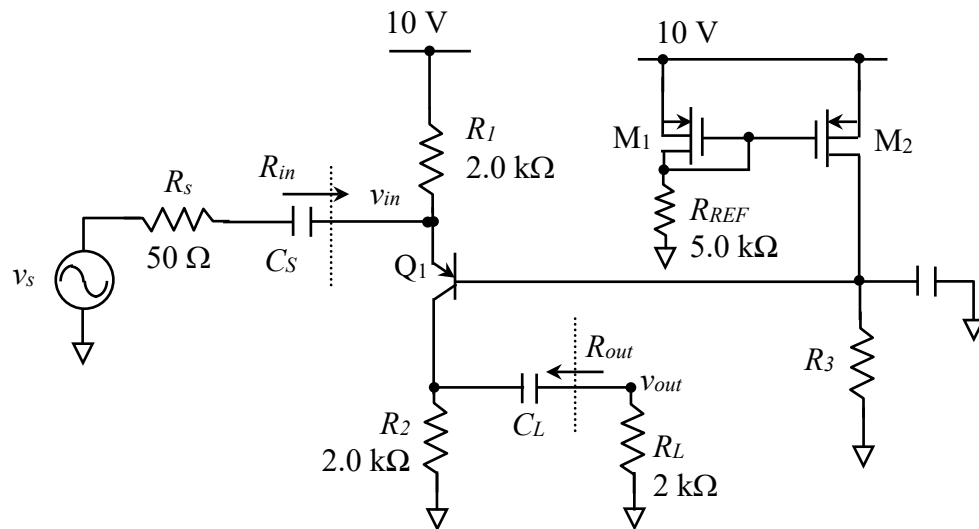


Fig. Q5

The BJT Q_1 operates in the forward active mode and its collector current, $I_{C,Q1} = 1.6$ mA. Ignore the Early effect of the BJT when performing DC analysis.

- Determine the drain current of the MOSFET M_2 , $I_{D,M2}$. (6 marks)
- Determine R_3 that will give rise to the desired $I_{C,Q1}$. (4 marks)
- Determine the values of the 2-port network equivalent parameters of the amplifier: G_m (or A_v), R_{in} and R_{out} . (8 marks)
- Determine the gain (v_{out}/v_s) of the amplifier. (2 marks)

Q5. Solution:

M₁ and M₂ are identical p-MOSFETs and they form a current mirror -

- $V_{THP} = -1.0 \text{ V}$
- $K_p = 2 \text{ mA/V}^2$
- $\lambda_p = 0$ (no Channel Length Modulation effect)

BJT is of the pnp type, $\beta = 100$, $V_A = 100 \text{ V}$

(a)

M₁ and M₂ form a current mirror $\Rightarrow I_{D,M2} = I_{D,M1}$.

(1 mark)

$$\begin{aligned}
 I_{D,M1} &= k_p (V_{SG,M1} - [V_{THP}])^2 \\
 I_{D,M1} &= k_p (10 - I_{D,M1} \times R_{REF} - [V_{THP}])^2 \\
 I_{D,M1} &= 2\text{m} \times (10 - I_{D,M1} \times 5.0\text{k} - 1.0)^2 \rightarrow 500I_{D,M1} = (9 - 5.0\text{k}I_{D,M1})^2 \\
 0 &= 81 - 90.5\text{k}I_{D,M1} + 25.0\text{M}I_{D,M1}^2 \\
 I_{D,M1} &= \frac{90.5\text{k} \pm \sqrt{90.25\text{M}}}{50.0\text{M}} = \frac{90.5\text{k} \pm 9.5\text{k}}{50.0\text{M}} \\
 I_{D,M1} &= \frac{81\text{k}}{50.0\text{M}} \text{ A or } \frac{100\text{k}}{50.0\text{M}} \text{ A} \\
 I_{D,M1} &= 1.62 \text{ mA or } 2.0 \text{ mA}
 \end{aligned}$$

(4 marks)


$$I_{D,M2} = I_{D,M1} = 1.62 \text{ mA}$$

$I_{D,M1} = 2.0 \text{ mA}$ is not valid, as corresponding $V_{SG,M1} = 10 - I_{D,M1} \times R_{REF} = 0.0 \text{ V} < [V_{THP}] = 1.0 \text{ V}$, i.e., no channel.

(1 mark)

(b)

The dc equivalent circuit –

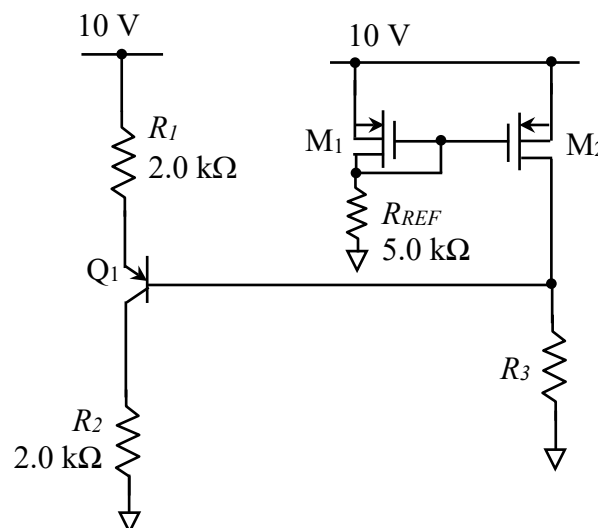

- BJT operates in forward active mode $\Rightarrow V_{EB,Q1} \approx 0.7 \text{ V}$
- $I_{C,Q1} = 1.6 \text{ mA}$ (Given) $\Rightarrow I_{B,Q1} = I_{C,Q1}/\beta = 0.016 \text{ mA}$

By KVL,

$$\begin{aligned}
 10 &= I_{E,Q1}R_1 + V_{EB,Q1} + (I_{B,Q1} + I_{D,M2})R_3 \\
 &= 1.01 \times 1.6\text{m} \times 2.0\text{k} + 0.7 + (0.016\text{m} + 1.62\text{m})R_3 \\
 \therefore R_3 &= \mathbf{3.709\text{ k}\Omega} \text{ (or } = \mathbf{3.729\text{ k}\Omega}, \text{ assuming } I_{E,Q1} \approx I_{C,Q1})
 \end{aligned}$$


(4 marks)

(c)

- $g_{m,Q1} = I_{C,Q1}/V_T = 1.6\text{m}/0.025 = 64\text{ mA/V}$
- $r_{\pi,Q1} = \beta_{Q1}/g_{m,Q1} = 100/64\text{m} = 1.563\text{ k}\Omega$
- $r_{o,Q1} = V_{A,Q1}/I_{C,Q1} = 100/1.6\text{m} = 62.5\text{ k}\Omega$

(3 marks)

The AC equivalent circuit –

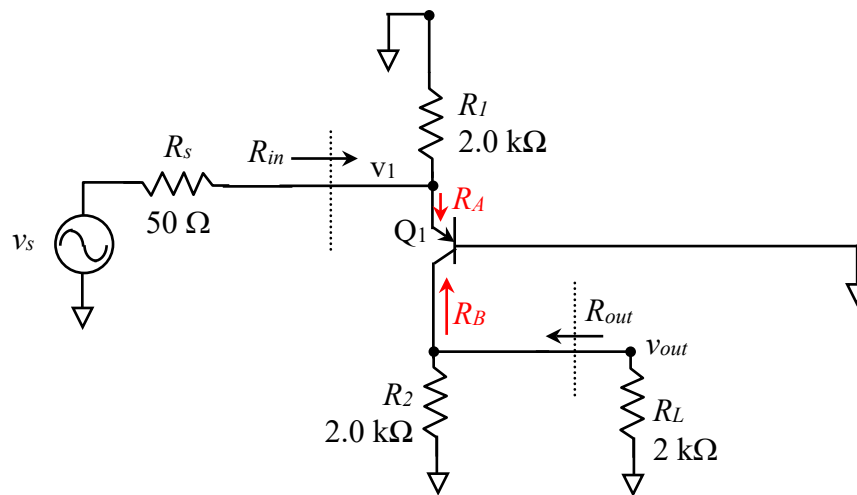

$$G_m = -g_{m,Q1} = \mathbf{-64\text{ mA/V}}$$

(1 mark)

$$R_{in} = R_1 // R_A$$

With the help of Table 1, Configuration D -

$$\begin{aligned}
 R_A &= \left[\frac{1}{g_{m,Q1}} \times \frac{r_{o,Q1} + (R_2 // R_L)}{r_{o,Q1} + (R_2 // R_L)/\beta_{Q1}} \right] = 15.9\text{ }\Omega \left(\text{or } \approx \frac{1}{g_{m,Q1}} = 15.60\text{ }\Omega \right) \\
 \therefore R_{in} &= R_1 // R_A \approx \mathbf{15.77\text{ }\Omega}
 \end{aligned}$$

(2 marks)

$$R_{out} = R_2 // R_B$$

With the help of Table 1, Configuration B

$$R_B = r_{o,Q1} \{1 + g_{m,Q1} [r_{\pi,Q1} // (R_1 // R_S)]\} = 251.71 \text{ k}\Omega$$

$$\therefore R_{out} = R_2 // R_B = \mathbf{1.984 \text{ k}\Omega}$$

(2 marks)

(d)

$$v_{out}/v_s = \frac{R_{in}}{R_s + R_{in}} \times (-G_m) \times (R_{out} // R_L) = \frac{15.77}{50 + 15.77} \times (64\text{m}) \times \frac{1.984\text{k} \times 2\text{k}}{1.984\text{k} + 2\text{k}} = 15.28$$

(2 marks)

- Q6. For the amplifier circuit shown in Fig. Q6, the MOS Transistor M_1 has the following parameters: $K_n = 1 \text{ mA V}^{-2}$, and $V_{THN} = 1 \text{ V}$. MOS transistors M_2 and M_3 are identical and have the following parameters: $K_p = 1 \text{ mA V}^{-2}$, and $V_{THP} = -1 \text{ V}$.


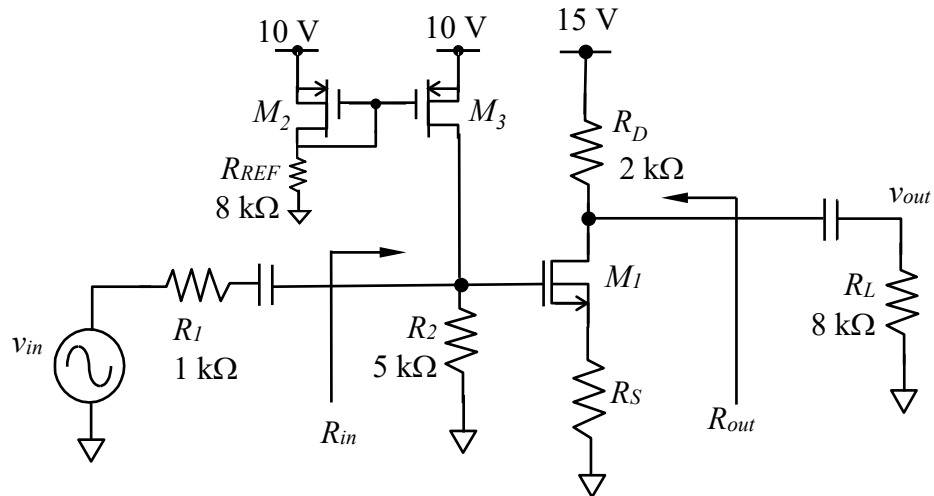


Fig. Q6

- Perform the DC analysis of the amplifier circuit shown in Fig. Q6, and show that the DC gate voltage of M_1 is 5 V. You need to explain briefly your answer.
- Calculate the value of R_S such that the drain current of M_1 is 4 mA. Verify that the M_1 is operating in the saturation region.
[Ans: $R_S = 0.5 \text{ k}\Omega$]
- Calculate the parameters, g_m and r_o , of the small-signal model of the transistor M_1 .
[Ans: $g_{m,M1} = 4 \text{ mA V}^{-1}$, and $r_{o,M1} = \infty$]
- What is the configuration of this amplifier?
- Calculate the values of R_{in} , and R_{out} .
[Ans: $R_{in} = 5 \text{ k}\Omega$ and $R_{out} = 2 \text{ k}\Omega$]
- Estimate the voltage gain, $A_v (= v_{out} / v_{in})$.
[Ans: $A_v = -1.78$]

Q6. Solution:

(a)

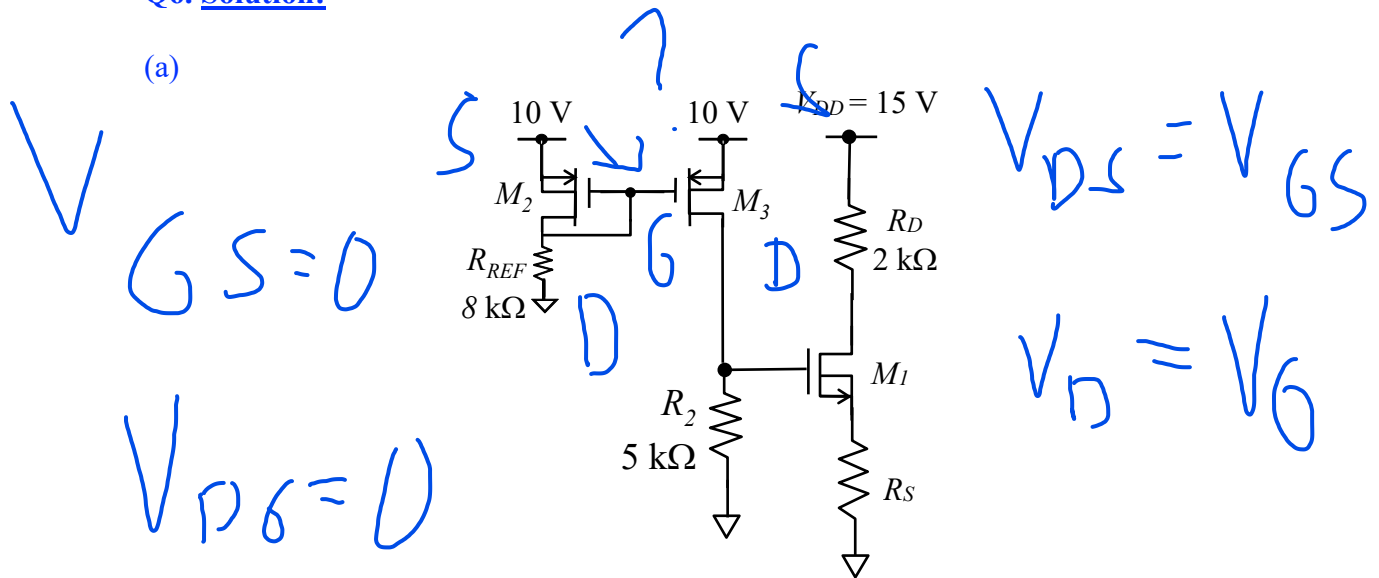

Equivalent circuit for DC analysis.

The two p-MOSFETs, M_2 and M_3 , form a current mirror current source. $I_{D,M2} = I_{D,M3}$.

Gate and drain of M_2 shorted together, $V_{G,M2} = V_{D,M2} \Rightarrow M_2$ is in saturation.

$$I_{D,M2} = K_{p,M2} (|V_{GS,M2}| - |V_{THP,M2}|)^2 = 1\text{m}([10 - V_{G,M2}] - 1)^2$$

$$I_{D,M2} = 1 \times (9 - I_{D,M2} R_{REF})^2 = (9 - 8I_{D,M2})^2 \quad (\text{Note: } I_{D,M2} \text{ in mA})$$

$$I_{D,M2} = 1 \text{ mA or } \frac{81}{64} \text{ mA}$$

$$I_{D,M2} = \mathbf{1 \text{ mA}} \quad (I_{D,M2} = \frac{81}{64} \text{ mA not valid, as } V_{G,M2} = I_{D,M2} R_{REF} = 10.125 \text{ V} > V_{S,M2} = 10 \text{ V} \Rightarrow \text{no channel})$$

$$\text{As } I_{G,M1} = 0, \quad V_{G,M1} = I_{D,M3} \times R_2 = 1\text{m} \times 5\text{k} = \mathbf{5 \text{ V}}.$$

(b) Assume n-MOSFET M_1 is operating in saturation region -

$$I_{D,M1} = K_{n,M1} (V_{GS,M1} - V_{THN,M1})^2$$

$$4\text{m} = 1\text{m}([V_{G,M1} - V_{S,M1}] - V_{THN,M1})^2 = 1\text{m}(5 - 4R_S - 1)^2 = 1\text{m}(4 - 4R_S)^2$$

$$\therefore R_S = 0.5 \text{ k}\Omega \text{ or } 1.5 \text{ k}\Omega$$

$$\mathbf{R_S = 0.5 \text{ k}\Omega} \quad (R_S = 1.5 \text{ k}\Omega \text{ not valid, as } V_{S,M1} = I_{D,M1} \times R_S = 6 \text{ V} > V_{G,M1} = 5 \text{ V} \Rightarrow \text{no channel})$$

$$V_{G,M1} = 5 \text{ V}, V_{S,M1} = I_{D,M1} \times R_S = 2 \text{ V}, \text{ and}$$

$$V_{D,M1} = V_{DD} - I_{D,M1} R_D = 15 - 4 \times 2 = 7 \text{ V}$$

M_1 is in saturation operation as,


- $V_{GS,M1} = 5 - 2 = 3 \text{ V} > V_{TH,M1} = 1 \text{ V}$, and
- $V_{DS,M1} = 7 - 2 = 5 \text{ V} > (V_{GS,M1} - V_{TH,M1}) = 2 \text{ V}$.

$$(c) \quad g_{m,M1} = 2\sqrt{K_n I_D} = 2\sqrt{1\text{m} \times 4\text{m}} = 4 \text{ mA V}^{-1}$$

$$r_{o,M1} = \frac{1}{\lambda_n I_D} = \frac{1}{0 \times 4\text{m}} = \infty$$

(d) The configuration of this amplifier is CS with degeneration.

(e)

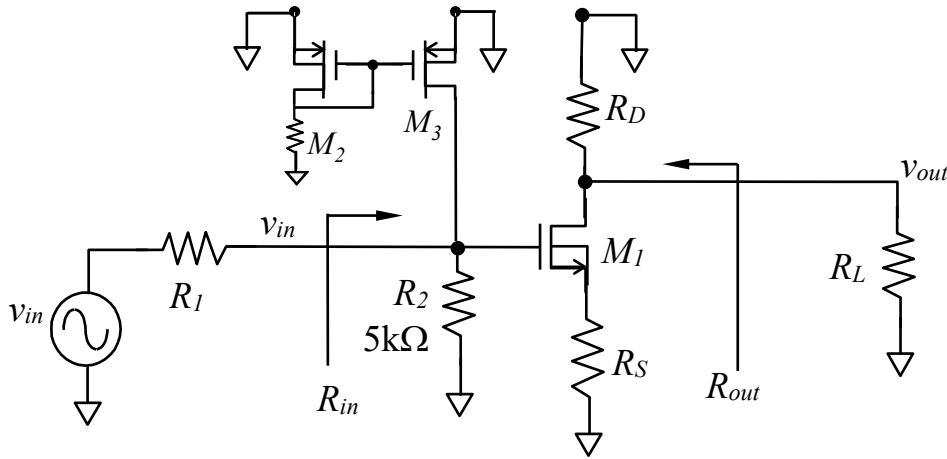

Equivalent circuit for ac analysis.

$$r_{o,M2} = r_{o,M3} = \infty \quad (\lambda_p = 0)$$

With the help of Table 2, Configuration A: $R_{in} = R_2 // r_{o,M3} // \infty \approx R_2 = 5 \text{ k}\Omega$

With the help of Table 2, Configuration B:

$$R_{out} = R_D // \{r_{o,M1} [1 + g_{m,M1} R_S]\} = 2\text{k} // \infty = 2 \text{ k}\Omega$$


(f) With the help of Table 4, configuration D –

$$A_v = \frac{v_{out}}{v_{in}} = \frac{R_{in}}{R_1 + R_{in}} \times (-G_m) \times (R_{out} // R_L) = -\frac{R_{in}}{R_1 + R_{in}} \left\{ \frac{g_{m,M1}}{1 + g_{m,M1} R_S} \right\} (R_{out} // R_L)$$

$$\approx -\frac{5\text{k}}{1\text{k} + 5\text{k}} \times \frac{4\text{m}}{1 + 4\text{m} \times 0.5\text{k}} \times (2\text{k} // 8\text{k}) = -1.78$$

Q7. Assume that the AC small-signal parameters of the BJT are $g_{m,Qi}$, $r_{\pi,Qi}$ and $r_{o,Qi}$, where $i = 1, 2$; and the AC small-signal parameters of the MOSFET are $g_{m,Mj}$, $g_{mb,Mj}$, $r_{i,Mj}$ and $r_{o,Mj}$, where $j = 1, 2$. Write down the expressions for the small-signal AC equivalent resistance (R_x) of the following configurations. V_{DD} and V_{BB} are DC voltage sources. I is a DC current source.

(a)

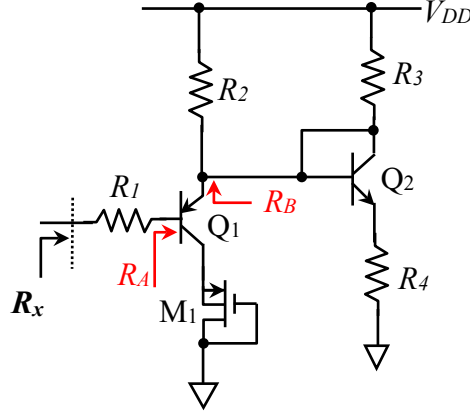
**Solution:**

$$R_x = R_1 + R_A$$

- $R_A = r_{\pi,Q1} + (1 + \beta_{Q1}) R_B$ (With the Help of Table 1, Configuration A)
- $R_B = \left[R_2 // R_3 // \left(\frac{1}{g_{m,Q2}} + R_4 \right) \right]$ (With the Help of Table 1, Configuration E)

$$\begin{aligned} R_x &= R_1 + R_A = R_1 + r_{\pi,Q1} + (1 + \beta_{Q1}) \left[R_2 // R_3 // \left(\frac{1}{g_{m,Q2}} + R_4 \right) \right] \\ &= R_1 + r_{\pi,Q1} \left\{ 1 + g_{m,Q1} \left[R_2 // R_3 // \left(\frac{1}{g_{m,Q2}} + R_4 \right) \right] \right\} \end{aligned}$$

(b)

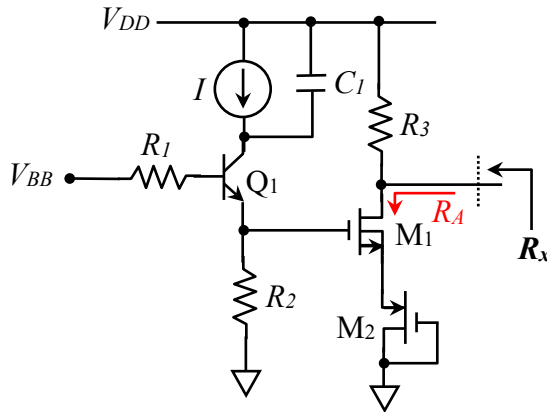**Solution:** $R_x = R_3 // R_A$

- $R_A = r_{o,M1} \left[1 + g_{m,M1} \left(\frac{1}{g_{m,M2}} \right) \right]$ (With the help of Table 1, Configuration B and Table 2, Configuration E)

$$R_x = R_3 // R_A = R_3 // \left\{ r_{o,M1} \left[1 + g_{m,M1} \left(\frac{1}{g_{m,M2}} \right) \right] \right\}$$

- Q8. A single-stage amplifier circuit is shown in Fig. Q8, where all the MOSFETs have identical Conductance Parameter of 0.5 mA/V^2 and Channel Length Modulation Factor of 0.01 V^{-1} . The Threshold Voltage of MOSFETs M_2 and M_3 are the same at -1 V , while that of MOSFET M_1 is -1.5 V with a body voltage of $V_B = 10 \text{ V}$.

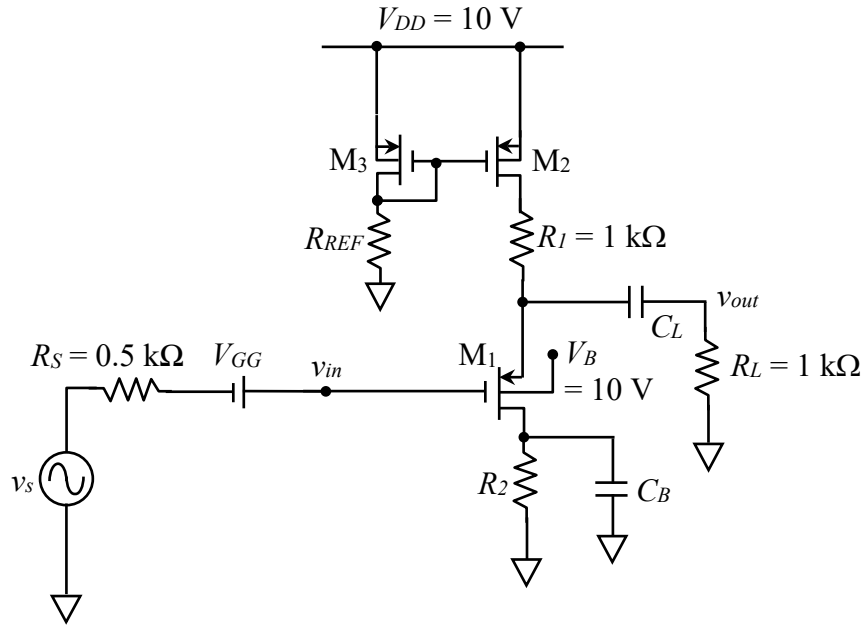


Fig. Q8

The amplifier circuit is designed to have a DC drain current of 1 mA for MOSFET M_1 .

- (a) Ignore Channel Length Modulation effect in the DC analysis, determine R_{REF} . You need to provide brief explanation to your calculation.

[Ans: $R_{REF} = 7.59 \text{ k}\Omega$]

- (b) Identify the configuration of the amplifier circuit.

- (c) Estimate the small-signal parameters of MOSFET M_1 : $g_{m,M1}$, $r_{o,M1}$ and $g_{mb,M1}$.

[Ans: $g_{m,M1} = 21.41 \text{ mA/V}$, $r_{o,M1} = 100 \text{ k}\Omega$, $g_{mb,M1} = -0.35 \text{ mA/V}$]

- (d) Estimate the two-port network parameters of the amplifier circuit: R_{in} , and R_{out} .

[Ans: $R_{out} = \infty$, $R_{out} = 565 \text{ }\Omega$]

- (e) Estimate the voltage gain v_{out}/v_s of the amplifier.

[Ans: $v_{out}/v_{in} \approx 0.51$]

- (f) For the amplifier circuit to operate properly, what is the constraint on the value of R_2 ?

[Ans: $R_2 < 6.18 \text{ k}\Omega$]

Q8. Solution:

All MOSFETs are of the p-channel type with $K_p = 0.5 \text{ mA/V}^2$, $\lambda_p = 0.01 \text{ V}^{-1}$.
 MOSFETs M_2 and M_3 have Threshold voltage, $V_{THP} = -1 \text{ V}$,
 MOSFET M_1 has Threshold voltage, $V_{THP1} = -1.5 \text{ V}$ (at $V_B = 10 \text{ V}$)
 $I_{D,M1} = 1 \text{ mA}$

- (a) *Ignore Channel Length Modulation effect in the DC analysis*, determine R_{REF} .

$$I_{D,M1} = 1 \text{ mA} = I_{S,M1} = I_{D,M2} = I_{D,M3}$$

($I_{D,M2} = I_{D,M3}$, as M_2 and M_3 form a **current mirror current source**)

Perform DC analysis –

M_3 in **saturation operation** (as **gate and drain** are **shorted together**) -

$$I_{D,M3} = K_p [|V_{GS,M3}| - |V_{THP}|]^2 = K_p [(V_{DD} - I_{D,M3} R_{REF}) - |V_{THP}|]^2$$

$$1\text{m} = 0.5\text{m}[(10 - 1\text{m} \times R_{REF}) - 1]^2$$

$$\pm\sqrt{1/0.5} = 9 - 1\text{m} \times R_{REF}$$

$$R_{REF} = 10.41 \text{ or } 7.59 \text{ k}\Omega$$

$R_{REF} = 7.59 \text{ k}\Omega$ ($R_{REF} = 10.41 \text{ k}\Omega$ is invalid, as $|V_{GS,M3}| = V_{DD} - I_{D,M3} R_{REF} = 10 - 1\text{m} \times 10.41\text{k} = -0.41 \text{ V} < |V_{THP}| = 1 \text{ V} \Rightarrow$ no channel)

OR,

$$I_{D,M3} = K_p [|V_{GS,M3}| - |V_{THP}|]^2$$

$$1\text{m} = 0.5\text{m}[V_{SG,M3} - 1]^2$$

$$\pm\sqrt{1/0.5} = V_{SG,M3} - 1$$

$$V_{SG,M3} = 2.41 \text{ or } -0.41 \text{ V}$$

$V_{SG,M3} = 2.41 \text{ V}$ ($V_{SG,M3} = -0.41 \text{ V} < |V_{THP}| = 1 \text{ V} \Rightarrow$ no channel)

$$R_{REF} = \frac{(V_{DD} - V_{SG,M3})}{I_{REF}} = \mathbf{7.59 \text{ k}\Omega}$$


- (b) Identify the configuration of the amplifier circuit.

Common Drain amplifier.

(c) Determine the small-signal parameters of MOSFET M₁: $g_{m,M1}$, $r_{o,M1}$ and $g_{mb,M1}$.

- $g_{m,M1} = 2\sqrt{K_p I_D} = 2\sqrt{0.5\text{m} \times 1\text{m}} = 1.41 \text{ mA/V}$
- $r_{o,M1} = \frac{1}{\lambda_p I_D} = \frac{1}{0.01 \times 1\text{m}} = 100 \text{ k}\Omega$
- $g_{mb,M1} = -g_{m,M1}/4 = -0.35 \text{ mA/V}$ (Body and source **not** shorted together)

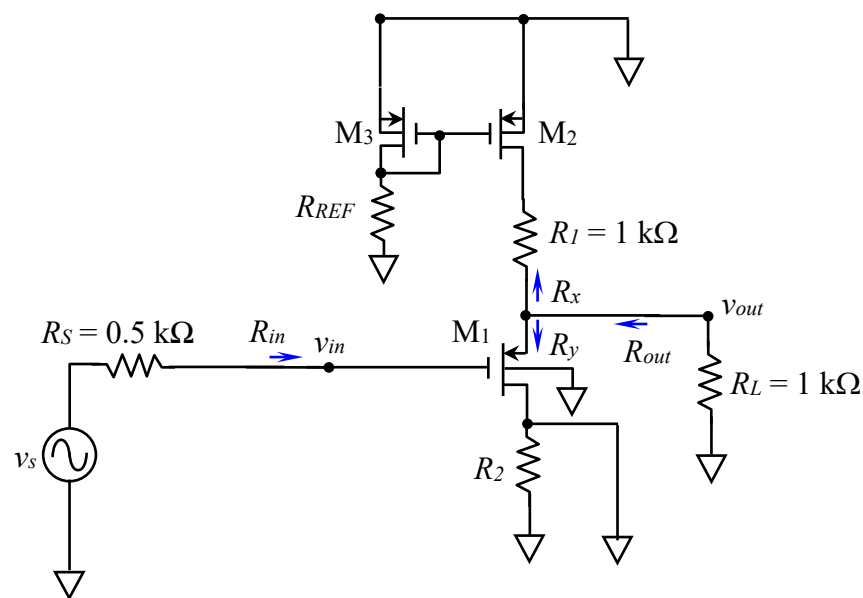(d) Estimate the two-port network parameters of the amplifier circuit: R_{in} , and R_{out} .



Equivalent circuit for small-signal ac analysis

With the help of Table 2, Configuration A: $R_{in} = \infty$

$$R_{out} = R_x // R_y$$

- R_x is the equivalent resistance looking into the drain of M₂ in series with R_1 . With the help of Table 2, Configuration B: $R_x = r_{o,M2} + R_1 = 101 \text{ k}\Omega$
- R_y is the equivalent resistance looking into the source of M₁. With the help of Table 2, Configuration C: $R_y = \frac{1}{g_{m,M1} - g_{mb,M1}} = \frac{1}{1.41\text{m} + 0.35\text{m}} = 568.2 \text{ }\Omega$

$$\text{So, } R_{out} = R_x // R_y = 565 \text{ }\Omega$$

- (e) Estimate the voltage gain v_{out}/v_s of the amplifier.

With the help of Table 4, Configuration C –

$$\frac{v_{out}}{v_s} = \frac{v_{out}}{v_{in}} = \left\{ \frac{g_{m,M1}(R_x//R_L)}{1+(g_{m,M1}-g_{mb,M1})(R_x//R_L)} \right\} \approx \frac{1.41\text{m} \times (101\text{k}/1\text{k})}{1+(1.41\text{m}+0.35\text{m}) \times (101\text{k}/1\text{k})} \approx 0.51$$

- (f) For the amplifier circuit to operate properly, what is the constraint on the value of R_2 ?

For the amplifier circuit to operate properly, both M_1 and M_2 must operate in **saturation**, meaning

- $|V_{DS,M1}| = V_{SD,M1} > (|V_{GS,M1}| - |V_{THP1}|)$, and
- $|V_{DS,M2}| = V_{SD,M2} > (|V_{GS,M2}| - |V_{THP}|)$

$$|V_{GS,M2}| = |V_{GS,M3}| = V_{SG,M3} = V_{DD} - I_{D,M3} \times R_{REF} = 10 - 1\text{m} \times 7.59\text{k} = 2.41\text{ V}$$

$$I_{D,M1} = K_p [|V_{GS,M1}| - |V_{THP1}|]^2$$

$$1\text{m} = 0.5\text{m} [|V_{GS,M1}| - 1.5]^2$$

$$\pm\sqrt{1/0.5} = [|V_{GS,M1}| - 1.5]$$

$$|V_{GS,M1}| = 2.91 \text{ or } 0.086\text{ V}$$

$$|V_{GS,M1}| = 2.91\text{ V} \text{ (} 0.086\text{ V} < |V_{THP1}| \text{ not valid)}$$

By KVL,

$$V_{SD,M1} + V_{SD,M2} = V_{DD} - I_{D,M1}(R_1 + R_2)$$

$$(V_{SD,M1} + V_{SD,M2}) > [(|V_{GS,M1}| - |V_{THP1}|) + (|V_{GS,M2}| - |V_{THP}|)]$$

$$V_{DD} - I_{D,M1}(R_1 + R_2) > (2.91 - 1.5) + (2.41 - 1)$$

$$10 - 1\text{m} \times (1\text{k} + R_2) > (2.91 - 1.5) + (2.41 - 1)$$

$$\therefore R_2 < 6.18\text{ k}\Omega$$